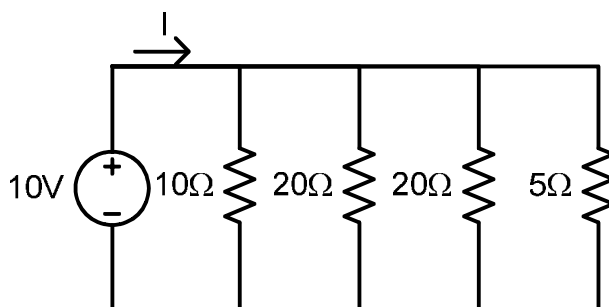


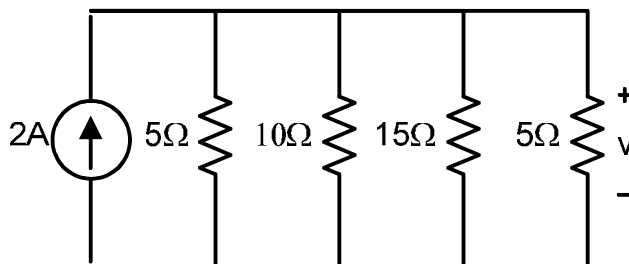
ECSE 200: Fundamentals of Electrical Engineering
Assignment 1
Winter 2006

Question 1


a) For the given circuit, calculate the value of the current I




b) For the given circuit, calculate the value of the voltage v

**Question 2**

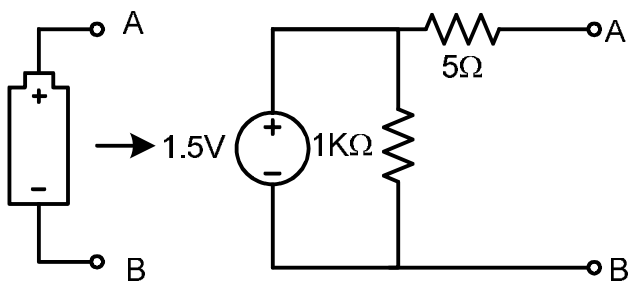
a) If a 1.5V DC battery is modeled as a 1.5V ideal source, with parallel and series resistances as shown in the diagram, calculate the value of the open-circuit voltage v_{ab}



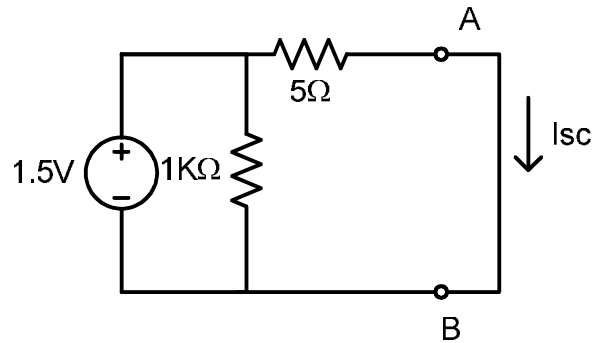b) If we short circuit terminals A and B, calculate the value of the short circuit current I_{sc}




c) If a $10\text{K}\Omega$ resistor, R , is connected between terminals A and B as shown, what is the power supplied to R ? What is the total power consumed in the circuit including the internal power dissipated inside the battery?

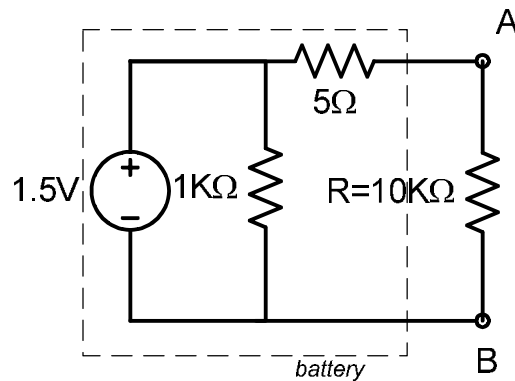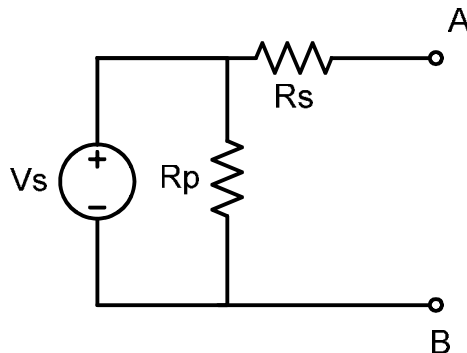

Question 3


A non-ideal source (Battery) is modeled using the circuit below where A & B are the terminals of the battery. In order to determine the model parameters V_s , R_s and R_p , the following tests were performed:

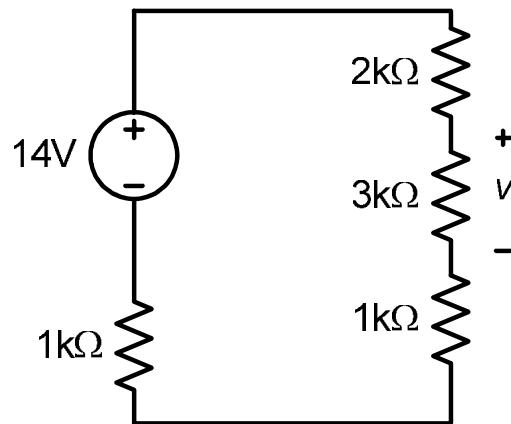- 1) The open circuit voltage was measured to be $v_{ab} = 9\text{V}$
 - 2) The short circuit current was measured to be $I_{sc} = 0.5\text{A}$
 - 3) The internal open-circuit power dissipation was measured to be $P_{int} = 0.1\text{ mW}$
- Determine the values of V_s , R_s and R_p .

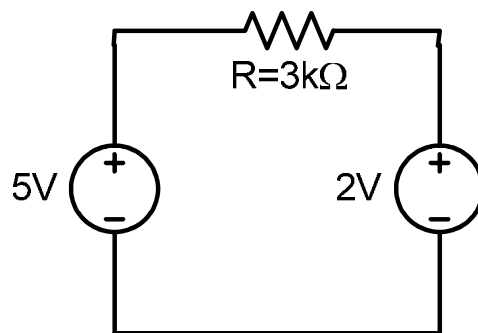


Question 4

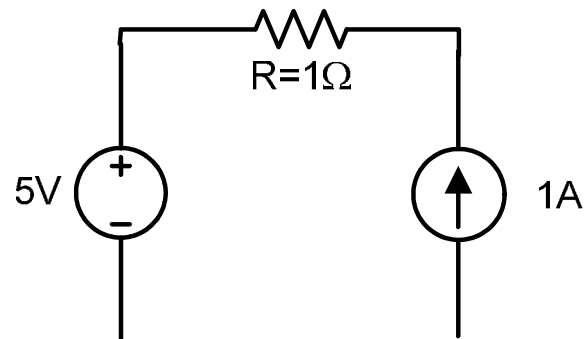
For the given circuit, calculate the value of the voltage 'v'

**Question 5**

For the given circuit, calculate the power consumed/supplied by each element


**Question 6**

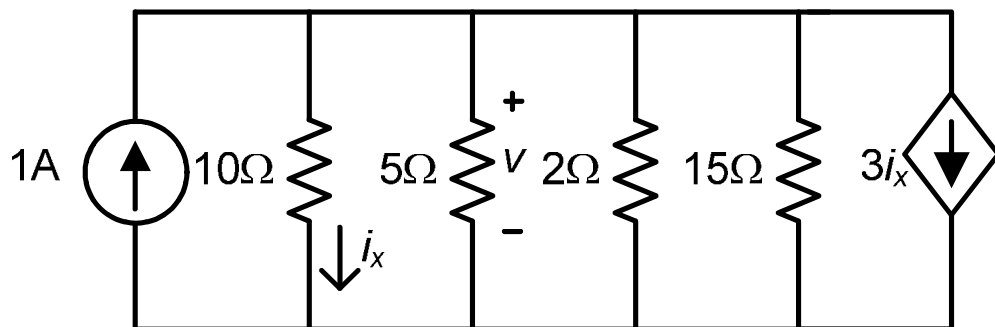For the given circuit, calculate the power consumed/supplied by each element

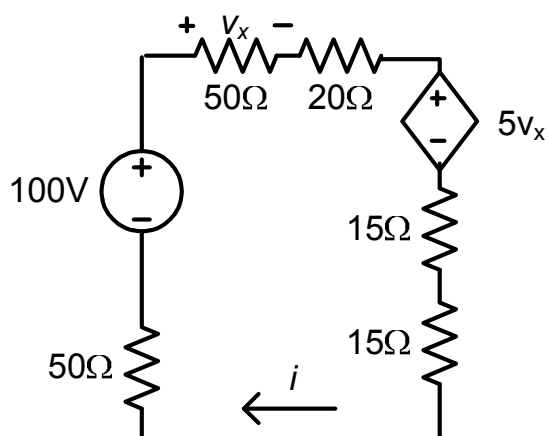


Question 7

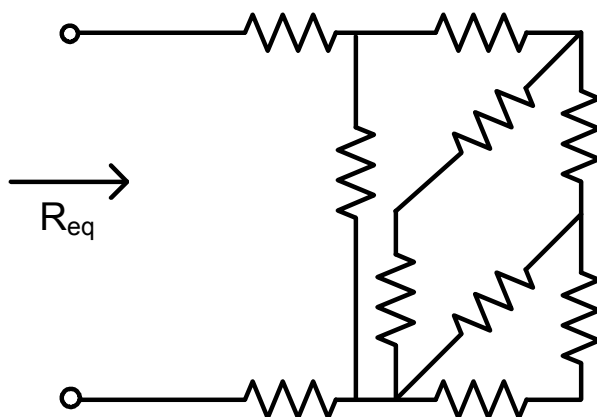
For the circuit shown, calculate the value of the voltage ' v ' as defined

**Question 8**

For the circuit shown, calculate the value of the current ' i ' as defined.


**Question 9**

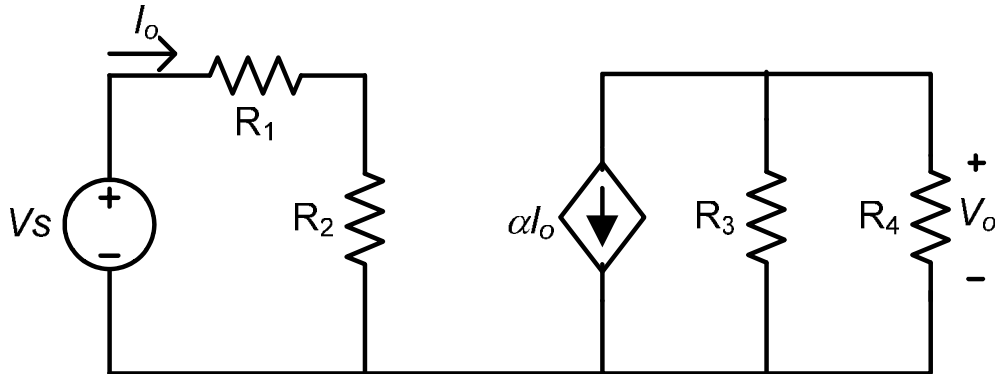For the circuit shown below, find the value of the equivalent resistance, R_{eq} . All resistors are 1Ω .

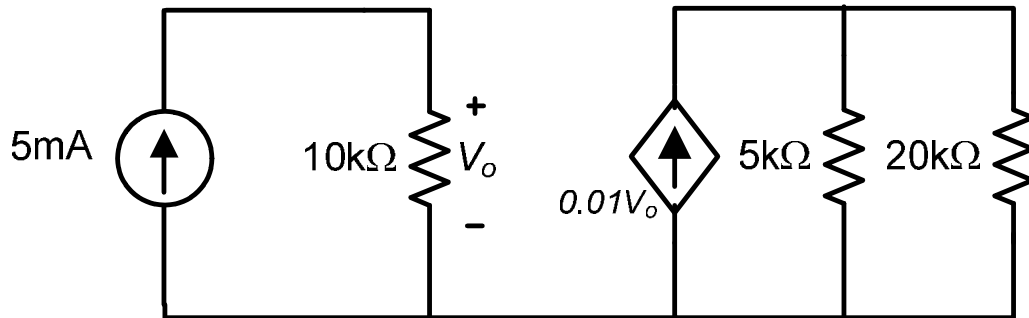


Question 10


For the circuit shown below, find V_o/V_s in terms of α , R_1 , R_2 , R_3 , and R_4 . If $R_1 = R_2 = R_3 = R_4$, what value of α will produce $|V_o/V_s| = 10$?

**Question 11**

For the network shown below, find the current, voltage, and power associated with the 20-k Ω resistor.

**Question 12**

Obtain the value of ' v ' and ' i ' in the following circuit

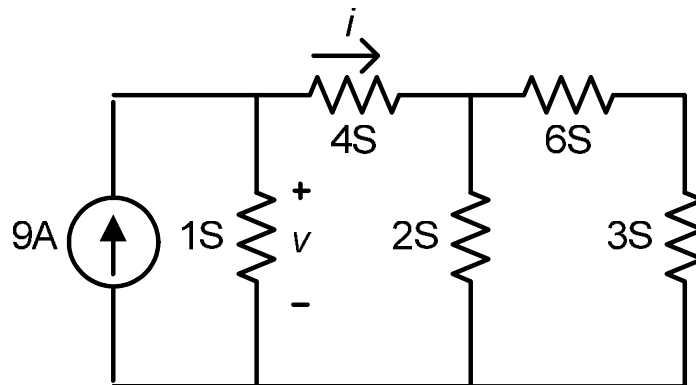

Question 13

For the circuit shown below,

- Find the equivalent resistance R_{AB} seen by the source to the right of terminals A and B as shown in the following circuit.
- Calculate the value of the voltage ' v '.

