

ECSE 200: Fundamentals of Electrical Engineering


Assignment 4 (part 2)

Winter 2006

Question 1

Consider the linear circuit provided below. Assume that the circuit is unconditionally stable and that the ideal op-amp model is valid. Answer each of the following:


- Provide a clear and concise definition for the ideal op-amp model. What limitation is assumed about the operation of this model with regard to the open loop gain A ?
- Find the value of V_s that makes the current source output power equal to 0.
- Find the value of V_s that makes the current labeled I_B equal to 40mA.

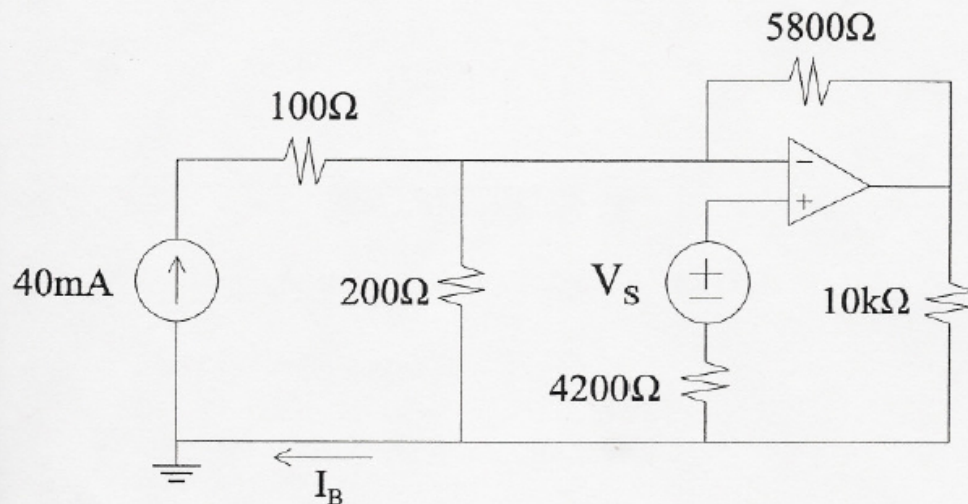

Question 2

Consider the linear circuit below. Assume that the circuit is unconditionally stable; the ideal op-amp model is valid; and $R_L = 12\text{k}\Omega$. Answer each of the following questions:


- Find the power supplied by each of the three voltage sources (3 values).
- Find the power supplied to the circuit through the output of the op-amp.
- Find the total charge that flows through the op-amp output in one hour (give the amount and sign of the charge, and the direction of the flow).

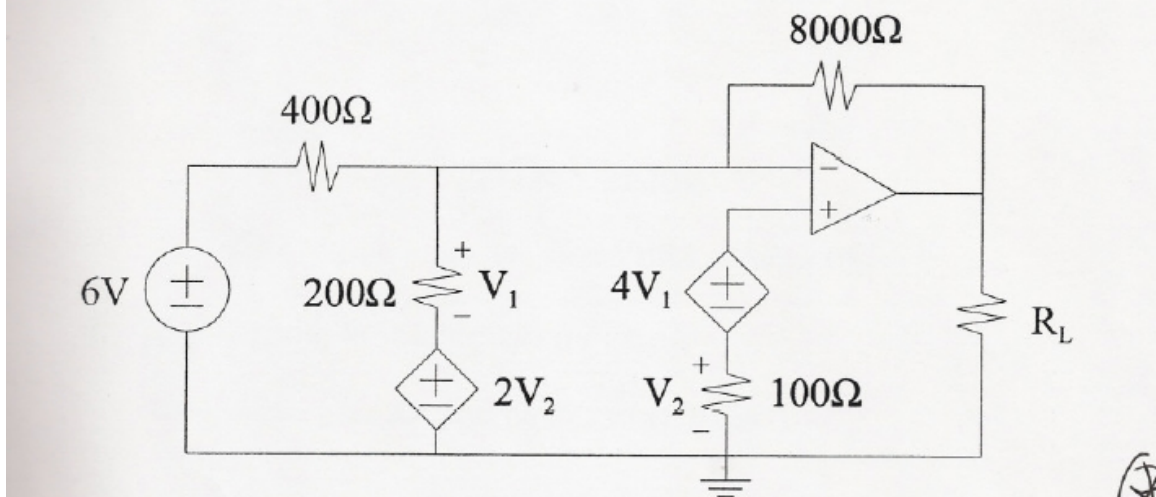

Question 3


Consider the linear circuit below. Assume that the circuit is unconditionally stable, and that the ideal op-amp model is valid. Answer each of the following three questions:

- Find the value of the feedback branch current, labeled I_F in the circuit diagram.
- Find the power supplied by each of the two voltage sources (2 values).
- Find the value of the power absorbed by the $81\text{k}\Omega$ resistor.

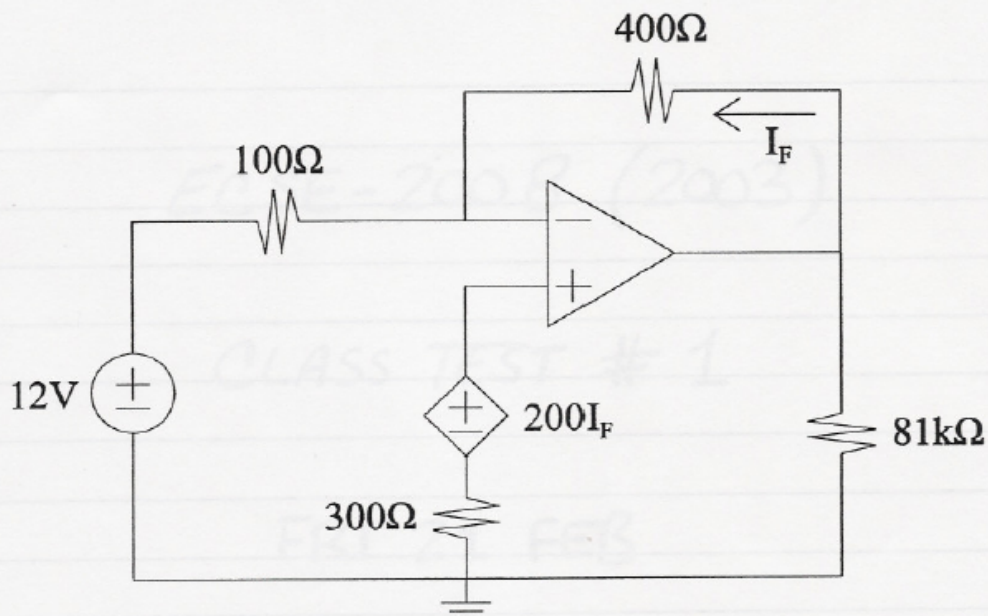

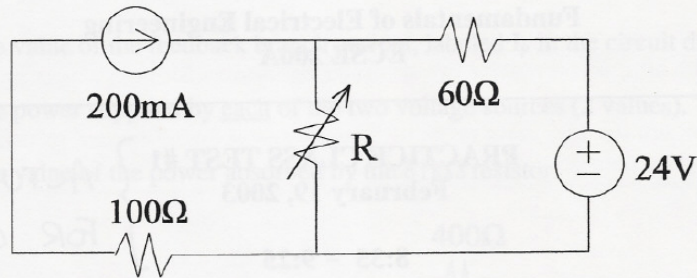Question 4

Consider the linear circuit provided below and answer each of the following questions.




- Calculate the value of the heat dissipated by the variable resistor "R", if $R = 60\Omega$.
- Calculate the power supplied by each of the two sources (2 values), for $R = 60\Omega$.
- Calculate the value of the variable resistor R that would cause the power absorbed by the 60Ω resistor to be exactly zero. Briefly explain your solution approach.

Question 5

Answer each of the following: (The circuit illustrated below applies to parts b and c)

- State (clearly & concisely!) the definition for the power absorbed by a two-terminal, lumped-parameter, circuit element. (You may use diagrams as well as words...)
- Find the individual values for the powers absorbed by each element in the circuit below (3 values), and then show that the total power is conserved for this circuit.
- State how the amount of power absorbed by the resistor would change (increase / decrease / no change) if the independent voltage source is replaced by a practical battery with an open-circuit voltage of 12V. Also, briefly explain why.

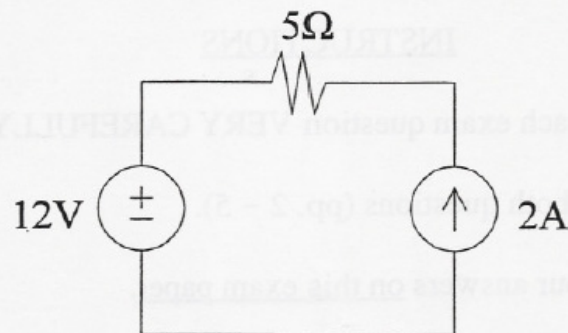

Question 6

Consider the linear networks provided below; answer each of the following questions:

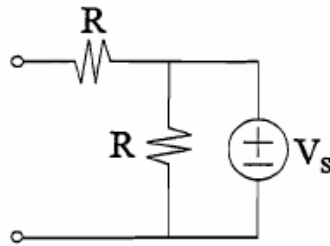


Fig. 1. See (b).


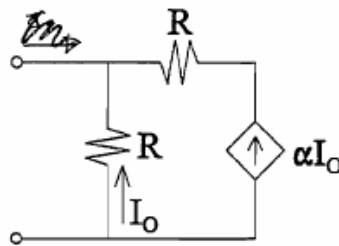


Fig. 2. See (c).

- Clearly and concisely state the operational definition of Ohm's Law.
- Clearly demonstrate whether the network shown in Fig. 1 is ohmic or non-ohmic. Determine an expression for the equivalent resistance of the network if it is ohmic.
- Clearly demonstrate whether the network shown in Fig. 2 is ohmic or non-ohmic. Determine an expression for the equivalent resistance of the network if it is ohmic.

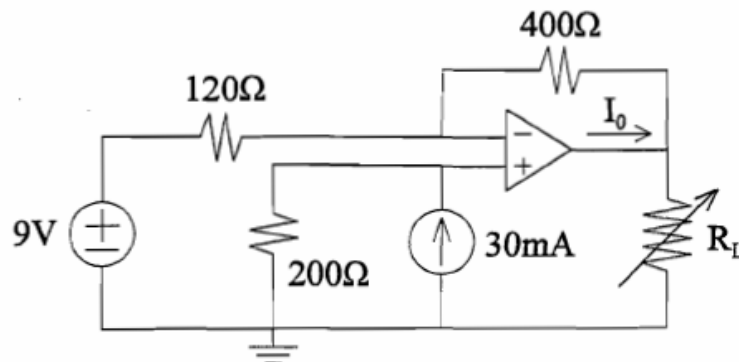Question 7

Consider the circuit provided below and answer each of the following questions:
(Assume that the ideal op-amp model is valid for each part.)



- Find the power_s absorbed by each of the three fixed resistances, if $R_L = 520\Omega$.
- Find the op-amp output current labelled I_o if $R_L = 160\Omega$.
- Assume that the op-amp supplies are fused to shutdown if the total op-amp output power demand exceeds 300mW. Find the smallest value of R_L that can be used in this circuit without causing the op-amp power supplies to shutdown. Finally, find the power absorbed by this minimal load resistance.