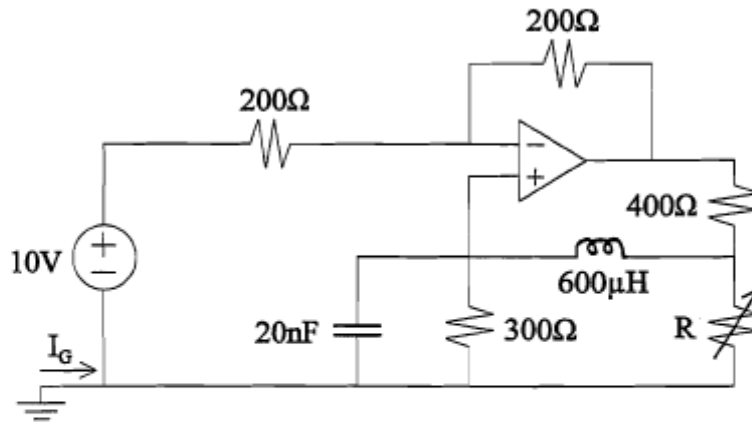


ECSE 200: Fundamentals of Electrical Engineering
Assignment 7
 Winter 2006

Question 1


Consider the linear circuit shown below. Assume that the op-amp is ideal, and that the circuit is stable and operating in D.C. steady-state. Answer the following questions:



- Calculate the power supplied to the circuit by the independent source if $R = 600\Omega$.
- Find the value (non-negative) of the variable resistance R that yields $I_G = 250\text{mA}$.
- Find the two non-negative values of R that would yield the highest and the lowest stored energy levels for the passive elements of the circuit. Also, find the values of these two steady-state stored energy levels, and briefly explain how they would be affected (increase / decrease / no change) if the $600\mu\text{H}$ inductor was non-ideal.

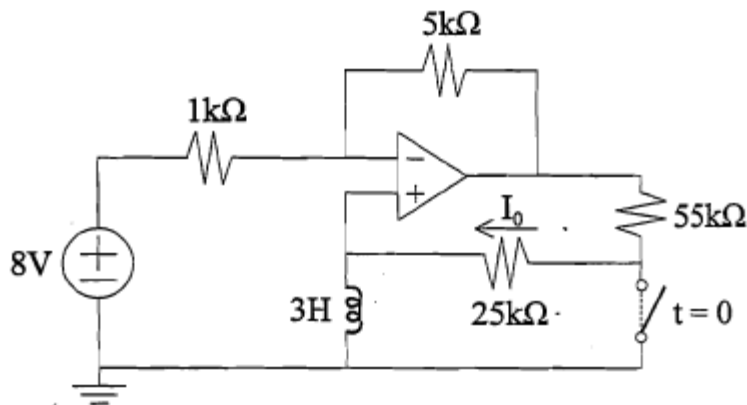Question 2


Assume the ideal op-amp circuit below is stable, and answer the following questions: (The switch is open for all $t < 0$, then closes at $t = 0$, and remains closed for all $t > 0$.)



- Find the value of the energy that is stored by the inductor at time $t = 0^-$.
- Determine the current labeled I_0 , as a function of time, for all time $t > 0$.

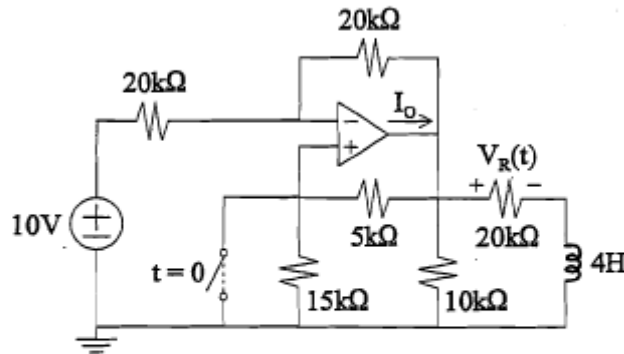Question 3


Assume the ideal op-amp circuit below is stable, and answer the following questions:
(The switch is open for all $t < 0$, then closes at $t = 0$, and remains closed for all $t > 0$.)



- Determine the resistor voltage labeled $V_R(t)$ for all time $t > 0$.
- Determine the op-amp output current labeled I_O for all time $t > 0$.
- Explain qualitatively how and why the individual voltage and current results found in parts (a) and (b) would change (or not change) if the inductor was non-ideal.

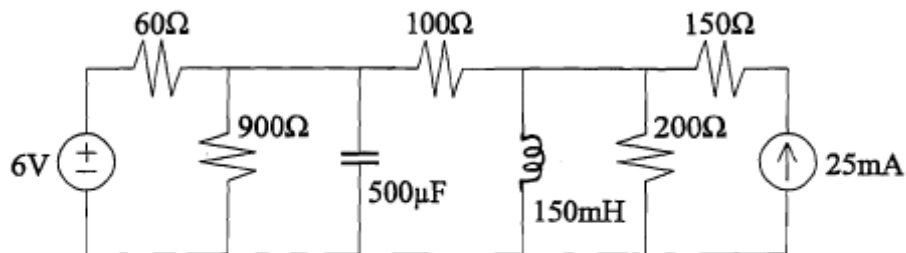Question 4


Consider the circuit provided below. Assume that all the elements are linear and ideal, and that the circuit is operating in DC steady-state. Answer the questions listed below:



- Calculate the powers supplied by the two sources (two values).
- Determine which resistor dissipates the most heat per second, and find the value of the electrical energy absorbed by that resistor in one second.
- Determine which resistor dissipates the least heat per second, and find the value of the electrical energy absorbed by that resistor in one second.
- Calculate the energies stored by the capacitor and the inductor (two values).

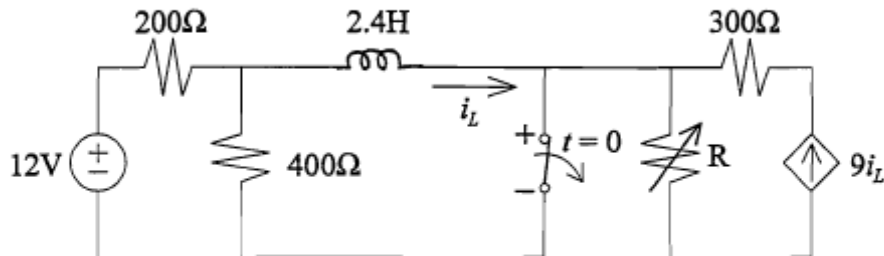Question 5


Consider the switched R-L circuit provided below. The switch is set to remain closed until time $t = 0$, at which time it opens and stays open. Assume all the circuit elements are ideal, and answer the questions listed below.



- Find the voltage across the open-circuited switch for all time $t > 0$, if $R = 50\Omega$. Assume that the circuit is operating in *dc* steady state just prior to time $t = 0$.
- Find the value of R which minimizes the energy stored by the inductor as $t \rightarrow \infty$.
- Find the value of R which maximizes the energy stored by the inductor as $t \rightarrow \infty$.

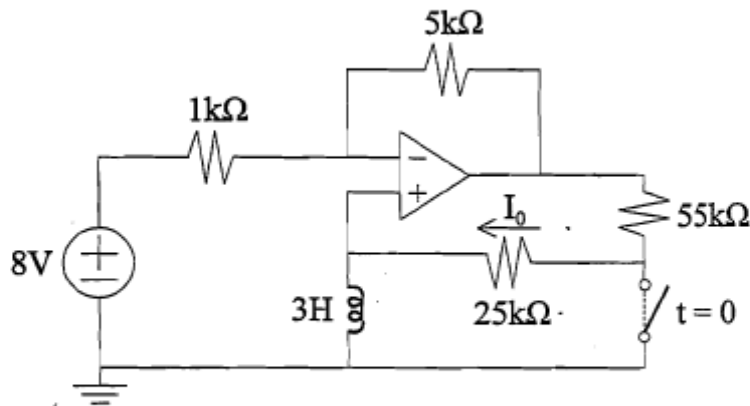Question 6


Assume the ideal op-amp circuit below is stable, and answer the following questions: (The switch is open for all $t < 0$, then closes at $t = 0$, and remains closed for all $t > 0$.)



- Find the value of the energy that is stored by the inductor at time $t = 0^-$.
- Determine the current labeled I_0 , as a function of time, for all time $t > 0$.

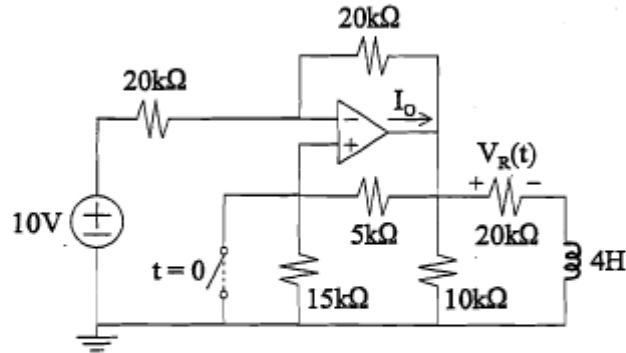Question 7


Assume the ideal op-amp circuit below is stable, and answer the following questions:
(The switch is open for all $t < 0$, then closes at $t = 0$, and remains closed for all $t > 0$.)



- Determine the resistor voltage labeled $V_R(t)$ for all time $t > 0$.
- Determine the op-amp output current labeled I_o for all time $t > 0$.
- Explain qualitatively how and why the individual voltage and current results found in parts (a) and (b) would change (or not change) if the inductor was non-ideal.

Question 8

For the following circuit, calculate the value of $i_L(t)$ for $t > 0$

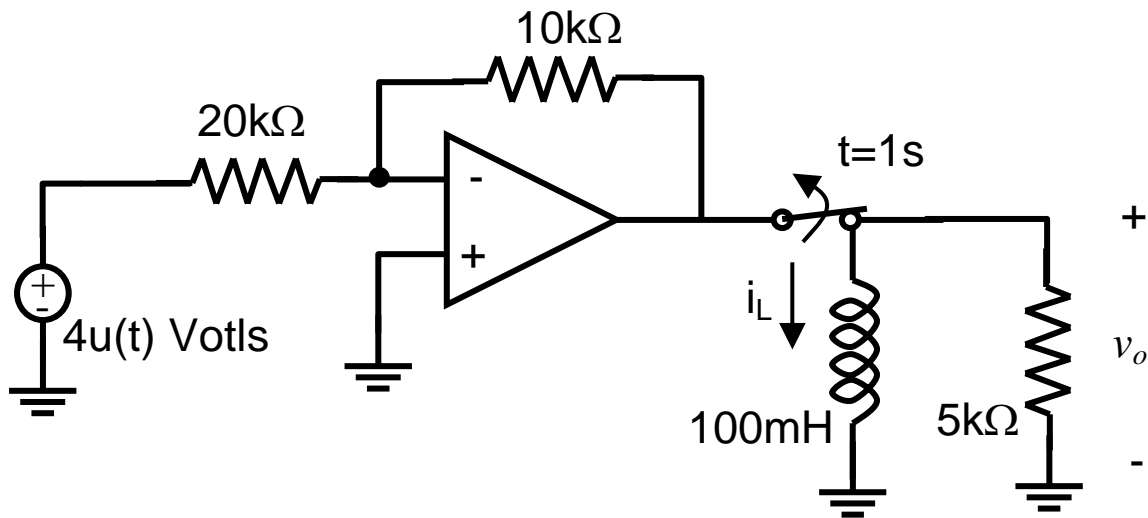

Question 9

QUESTION 2: (6MARKS)

Assume the circuit in Figure Q2.1 is in steady state at $t < 0$. At $t = 20\text{ms}$, the current in the inductor is measured to be $i_L = 1.22\text{A}$.

- Calculate the time constant of the circuit.
- Calculate the current i_L in the 50Ω resistor at $t = 40\text{ms}$.


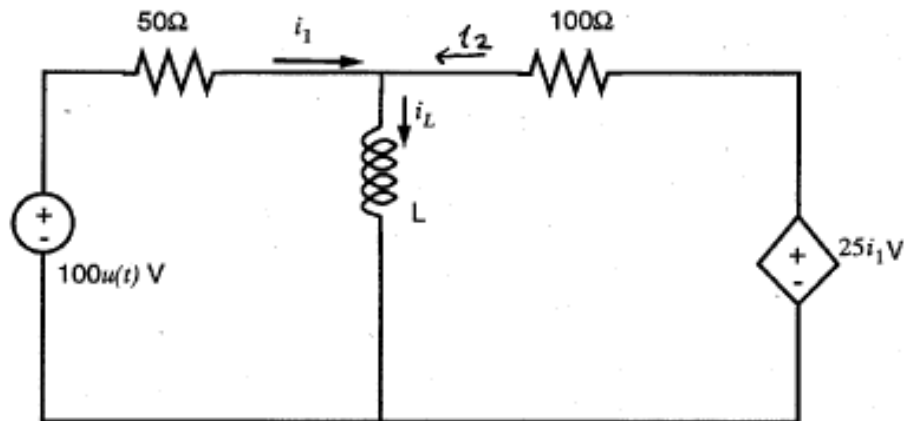


Figure Q2.1

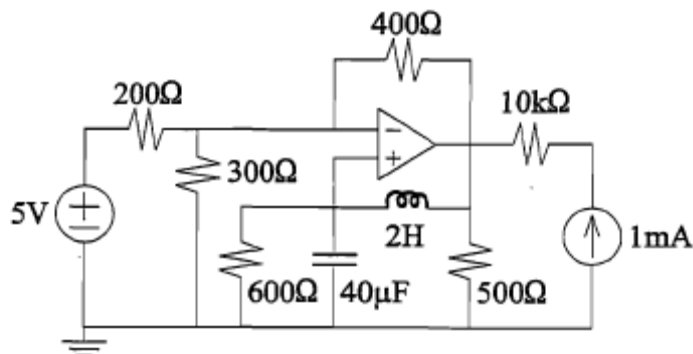Question 10

Consider the circuit provided below. Assume that all the elements are linear and ideal, and that the circuit is in stable DC steady-state operation. Answer the questions below:




- Calculate the powers supplied by the two sources (two values).
- Determine which resistor dissipates the most heat per second, and find the value of the electrical energy absorbed by that resistor in one second.
- Determine which resistor dissipates the least heat per second, and find the value of the electrical energy absorbed by that resistor in one second.
- Calculate the energies stored by the capacitor and the inductor (two values).


Question 11

Consider the circuit given below. Calculate the value of R that yields maximum power transfer to the two-terminal network connected at the right-hand-side of terminals AA' if the entire circuit is operating in DC steady-state. Also, find the steady-state energies stored by the capacitor and the inductor, for this optimal value of R .

Note: The parameter " R " appears in the definition of three different circuit resistors.

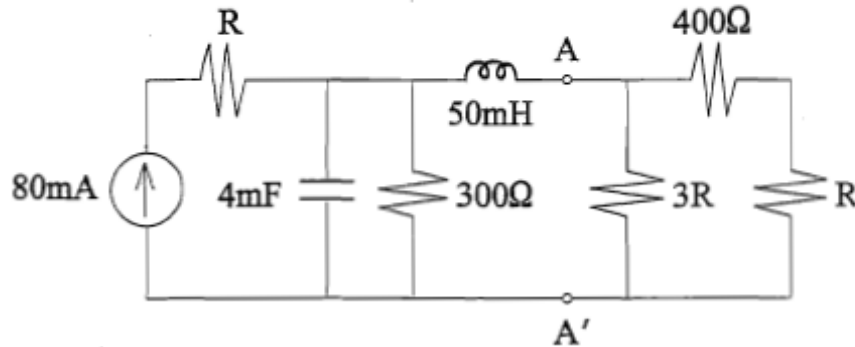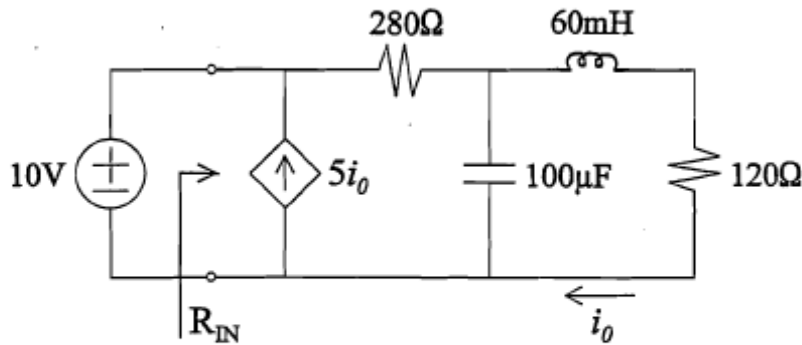**Question 12**

Assume that the circuit shown below is operating under *d.c. steady-state* conditions for the purpose of answering the following questions.



- Calculate the steady-state power supplied by the current source.
- Calculate the steady-state input resistance seen by the voltage source.
- Calculate the steady-state energies stored by the capacitor and the inductor.