

Assignment 4(part 1) solutions

Question 1

$$\text{KCL @ } V_0: (6 - V_0) / 150 - V_0 / 600 + 0.02 = 0$$

$$\Rightarrow V_0 = 7.2 \text{ V}$$

$$P_{6V} = 6 I_V = 6 [(6 - V_0) / 150] = -48 \text{ mW (supplied!)}$$

$$P_{20\text{mA}} = 0.02 V_I = 0.02 (V_0 + 2) = 184 \text{ mW (supplied!)}$$

Question 2

Negligible open-circuit losses mean that the battery can be accurately modeled by an independent voltage source (ideal emf source) of value V_{OC} , connected in series with a single internal resistance R_{INT} . Therefore, the object is to find the values of V_{OC} and R_{INT} , based on current measurements.

The exact short-circuit current of the battery, say I_{SC} , may be measured by connecting the ideal ammeter across the terminals of the battery, which provides: $V_{OC} = I_{SC} R_{INT}$.

The exact $10\text{k}\Omega$ load current for the battery, say I_L , can be measured by connecting the battery, resistor and ammeter into a single series loop. This setup provides the relation: $V_{OC} = I_L (10,000 + R_{INT})$.

Combining these two V_{OC} relations yields the expression: $I_{SC} R_{INT} = I_L (10,000 + R_{INT})$, from which it is evident that the "measured" value of $R_{INT} = 10,000 I_L / (I_{SC} - I_L)$.

Finally, substituting this result for R_{INT} in either of the two V_{OC} relations provided above yields an expression for the exact value of V_{OC} , e.g., $V_{OC} = 10,000 I_{SC} I_L / (I_{SC} - I_L)$.


Question 3

$$(a) \quad I_s = 0.01V_0; \quad V_s = -300(0.01V_0) - V_0 = -4V_0; \\ \Rightarrow V_s = -400 I_s \Rightarrow V_s \propto I_s \Rightarrow \text{Ohmic device.}$$

$$(b) \quad R_{EQ} = V_s / I_s = -400 \, \Omega$$

$$(c) \quad P_{\text{Supplied}} = I_s (-V_s) = (0.01V_0)(4V_0) = 0.04 V_0^2; \\ \text{KCL: } (V_0 - 5) / 100 + V_0 / 200 - 0.01V_0 = 0; \\ \Rightarrow V_0 = 10V; \Rightarrow P_{\text{Supplied}} = 4W$$

Question 4

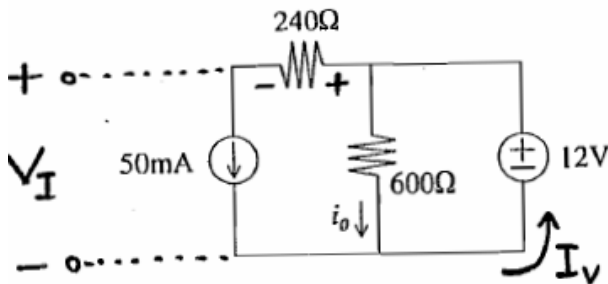

$$i. (a) \quad \text{KVL: } V_I = 12 - 0.05 \times 240 = 0; \\ \Rightarrow P_I = 0.05 V_I = 0W$$

$$\text{KCL: } I_v = 0.05 + 12 / 600 = 70mA \\ \Rightarrow P_v = 12 I_v = 840mW$$

(b) Model: ideal ammeter in series with 30Ω .


Connection: meter in series with 600Ω .

$$\Rightarrow i_0 = 12 / (600 + 30) \approx 19mA$$

(c) KVL $\Rightarrow P_I = 0W$; (same as before)

$$\text{KCL: } I_v \approx 0.05 + 0.019 = 69mA \\ \Rightarrow P_v \approx 12 I_v = 828mW$$

Question 5

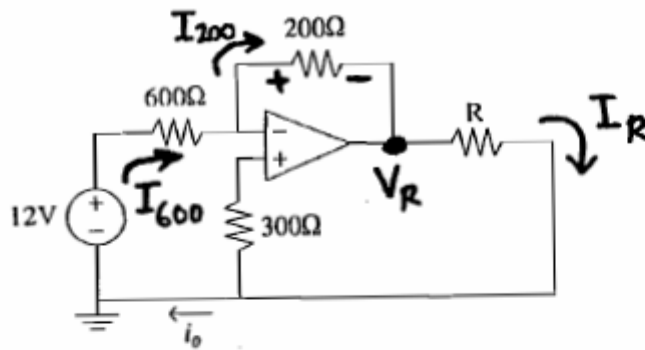


(a) $i_0 = I_R = V_R / 4000$; $V_R = -200 I_{200}$;
 $I_{200} = I_{600} = 12 / 600 = 20\text{mA} \Rightarrow i_0 = -1\text{mA}$

(b) $P_{\text{heat}} = 600 (I_{600})^2 + 200 (I_{200})^2 + (V_R)^2 / R$;
 $P_{\text{heat}} = 0.32 + 16 / R$; $P_{12V} = 12 I_{600} = 0.24\text{W}$
 $\Rightarrow$ Solve $P_{12V} = 0.5 P_{\text{heat}}$ for R
 $0.24 = 0.16 + 8 / R \Rightarrow R = 100\ \Omega$

Question 6

(Extra space for solution to #5)

CIRCUIT MODEL: (BATTERY + BULB)

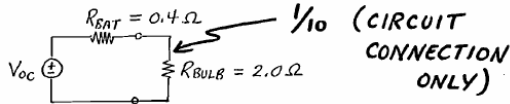

NB. BATTERY MODEL SHUNT RESISTOR IS NOT USED BECAUSE % BATTERY LOSSES ARE NEGLIGIBLE

1. OHMIC BULB RATED AT 72W FOR 12V (d.c.).

$$\Rightarrow R_{BULB} = \frac{V^2}{P} = \frac{144}{72} = 2.0 \Omega \quad \frac{2}{10}$$

2. $I_{BULB}(0+) = 5A \Rightarrow R_{BAT}$.

$$V_{BULB} = (5)(2) = 10V;$$

$$\Rightarrow V_{R_{BAT}} = V_{OC} - V_{BULB} = 12 - 10 = 2V;$$

(AT TIME 0+)

$$\Rightarrow R_{BAT} = \frac{V_{R_{BAT}}(0+)}{I_{BAT}(0+)} = \frac{2}{5} = 0.4 \Omega \quad \frac{2}{10}$$

(CON'D)

PROBLEM ANALYSIS/SOLUTION:

$$V_{BULB}(t > 0) = \frac{2}{2.4} V_{OC}(t > 0) \quad \dots \text{ASSUMES?}$$

$$\Rightarrow V_{OC} = 12V \rightarrow V_{BULB} = 10V (\geq 6V)$$

$$V_{OC} = 9V \rightarrow V_{BULB} = 7.5V (\geq 6V)$$

$$V_{OC} = 6V \rightarrow V_{BULB} = 5V (< 6V!)$$

$\Rightarrow$ BULB FAILS WHEN V_{OC} SWITCHES FROM 9V DOWN TO 6V.

$\frac{2}{5}$ $\Rightarrow$ 54 kJ REMAIN IN BATTERY AT TIME OF BULB FAILURE (AS PER V_{OC} PLOT). $(\frac{2}{10})$

TIME TO DISSIPATE $144 - 54 = 90 \text{ kJ}$:

$$\text{FIRST } 72 \text{ kJ AT } 12V \Rightarrow \frac{144}{2.4} = 60W \Rightarrow 20 \text{ MINS}$$

$$+ \text{ NEXT } 18 \text{ kJ AT } 9V \Rightarrow \frac{81}{2.4} = 33.75W \Rightarrow 8 \text{ MINS } 53 \text{ SEC}$$

$\frac{2}{5}$ $\Rightarrow$ TOTAL TIME TO FAILURE = 28 MINS 53 SEC $(\frac{2}{10})$

TOTAL ENERGY DISSIPATED BY BULB:

BY POWER DIVISION BETWEEN R_{BAT} AND R_{BULB} , THE FRACTION OF 90 kJ DISSIPATED BY R_{BULB} IS

$$\frac{1}{5} \times 90 \text{ kJ} = 18 \text{ kJ} \quad \frac{2}{10}$$

Question 7

(a) KCL @ V_0 : (ASSUME LOWER NODE AS GROUND)

$$2 - \frac{V_o}{200} - 3 I_o = 0 \quad ; \quad V_o = 1000 I_o$$

$$\Rightarrow V_0 = 250V \text{ AND } I_0 = 250mA //$$

(b) MEASURE V_o USING $R_m = 3000\Omega$:

$$2 - \frac{V_M}{3000} - \frac{V_M}{200} - 3I'_0 = 0 ; \quad V_M = 1000 I'_0$$

$$\Rightarrow V_m = 240V_{//} \quad (R_m = 26\Omega \Rightarrow V_m \approx 43V)$$

MEASURE I_0 USING $R_m = 26\Omega$:

$$2 - \frac{V_0'}{200} - 3I_m = 0 \quad ; \quad V_0' = (1000 + 26) I_m$$

$$\Rightarrow I_M = 246 \text{ mA} // (R_M = 3000 \Omega \Rightarrow I_M \approx 87 \text{ mA})$$

(3)

(c) SINCE I_0 INDEPENDENT OF VALUE OF 300Ω , AND V_0 INDEPENDENT OF VALUE OF 600Ω RESISTANCE, MEASURE I_{300} AND V_{600} (USING EITHER R_m !).

THEN: $I_m = \frac{1}{2} I_{300}$ ($= I_0$ ACTUAL), AND

$$V_M = \frac{1}{3} V_{600} (= V_0 \text{ ACTUAL}) //$$

Question 8

$$(a) \text{ KCL @ } -V_A: \frac{4+V_A}{1000} + \frac{V_A}{5000} + \frac{V_A-V_0}{2500} = 0$$

$$\Rightarrow 8V_A - 2V_O = -20$$

$$\text{KCL @ } -V_0: \quad \frac{V_0 - V_A}{2500} + \frac{\alpha V_A + V_0}{1000} + \frac{V_0}{5000} = 0$$

$$\Rightarrow (2-5\alpha)V_A = 8V_0$$

ELIMINATE V_o : $V_A = -16/(6+\alpha)$

For $\alpha \rightarrow \infty$: $V_A \rightarrow 0$; $V_o = 4V_A + 10 \rightarrow 10V$;

$$V_o/V_s = 10/4 = 2.5 //$$

$$(b) P_{\diamond}^{sup} = (\alpha V_A) I$$

$$\begin{aligned} \text{FOR } V_A = 0: I &= -(I_S + I_0) \\ &= -\left(\frac{4}{1000} + \frac{10}{5000}\right) = -6 \text{ mA} ; \end{aligned}$$

$$\begin{aligned} \text{BY KVL: } \alpha V_A &= -V_0 + 1000 I = -16 \text{ V} ; \\ (V_A \rightarrow 0) \end{aligned}$$

$$\Rightarrow P_{\diamond}^{sup} = (-16)(-0.006) = +96 \text{ mW} //$$





$$(c) P_{R_A} = V_A^2 / R_A \quad \text{WHERE } V_A = -16 / (6 + \alpha) ;$$

$$P_{R_A} = 200 \mu\text{W} \Rightarrow V_A = \pm 1 \text{ V} \dots (R_A = 5 \text{ k}\Omega)$$

$$\begin{aligned} \Rightarrow \text{CHOOSE } \alpha &= 70 \text{ OR } \alpha = -22 // \\ (\text{BOTH WILL PROVIDE } 200 \mu\text{W}) \end{aligned}$$

Question 9

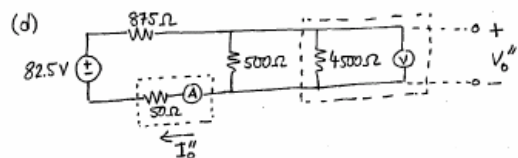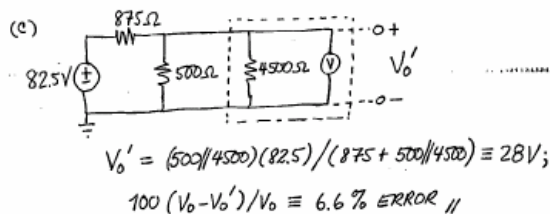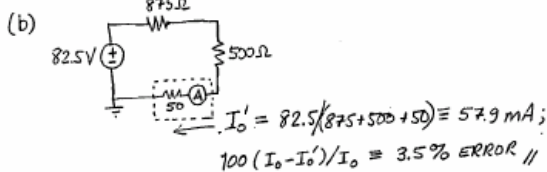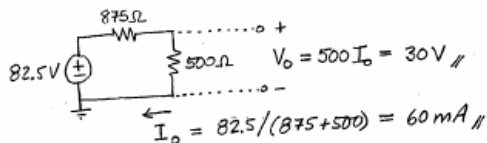(a) REDUCE CIRCUIT: (e.g. SOURCE TRANSFORMATIONS)



$$I_0'' = 82.5 / (875 + 500 // 4500 + 5) = 60 \text{ mA} ;$$

(ZERO ERROR!!) //


$$V_0'' = \frac{(500 // 4500)(82.5)}{875 + 500 // 4500 + 5} = 27 \text{ V} ; (10 \% \text{ ERROR})$$

NOTE: I_0'' ERROR REDUCED FROM I_0' LEVEL (TO ZERO!)

BECAUSE VOLT METER LOADING EFFECT IS EXACTLY CANCELLED BY AMMETER LOADING EFFECT. V_0'' ERROR INCREASED FROM V_0' LEVEL BECAUSE AMMETER LOADING EFFECT ADDS TO THAT OF VOLT METER (TO FURTHER DECREASE VOLTAGE DIVISION FOR 500Ω).


Question 10

1. REDUCE CIRCUIT USING SOURCE TRANSFORMATIONS :
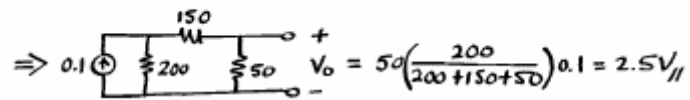
$$\Rightarrow 0.1 \text{ A} \parallel 200 \Omega \xrightarrow{150 \Omega} \text{V}_o = 50 \left(\frac{200}{200 + 150 + 50} \right) 0.1 = 2.5 \text{ V}_{//}$$


FOR VOLTMETER :

$$50 \rightarrow 50 \parallel 5500 \approx 49.55 \Omega$$
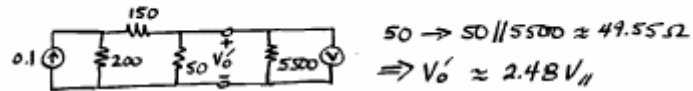
$$\Rightarrow V_o' \approx 2.48 \text{ V}_{//}$$


Question 11

$$V_+ = V_- = V_o / 2 ; V_o = 40 \text{ V} ; I_o = 140 \text{ mA}_{//}$$

$$P_{\text{TOTAL}} = P_{150} + P_{300} + 2P_{200} + P_{1000} + P_{10V} \approx 8.27 \text{ W}_{//}$$

$$\text{SOLVE } P_{150} + P_{300} + 2P_{200} + P_R = 10 P_{10V} \text{ FOR } R ;$$

$$\Rightarrow R = \frac{40^2}{(2/3)} = 2400 \Omega_{//}$$