


Assignment 5 Solutions

Question 1

- (a) Find R_{Th} seen by R , for $R' = 50\Omega$; set $R = R_{Th}$.

$$\begin{aligned} R_{Th} &= R' + (100 + 300) \parallel (V_{OC} / I_{SC}) \\ &= 50 + 400 \parallel 400 = 250\Omega \end{aligned}$$

- (b)

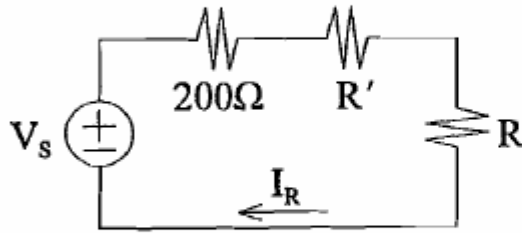

$$\begin{aligned} P_R &= (I_R)^2 R \\ \max(I_R) &\Rightarrow \max(P_R) \\ R' = 0 &\Rightarrow \max(I_R) \\ (R' \text{ non-negative!}) \end{aligned}$$

- (c) $P_R = (I_R)^2 R$ where $I_R = V_s / (200 + R' + R)$

$$\therefore R' = 0 \Rightarrow \max(P_R) \quad \forall \text{ non-negative } R$$

$$\therefore \text{Set } R' = 0 \text{ and } R = R_{Th} = 200 + R' = 200\Omega$$

Question 2

- (a) Max. heating \Rightarrow max. power \Rightarrow set $R = R_{Th}$

(Using "generalized KCL" - see class notes...)

$$-(V_{OC} + 2I')/4 + 8 + I' = 0; \quad I' = -V_{OC}/2$$

$$\Rightarrow V_{OC} = 16V \quad (V_{OC} \text{ circuit ?!})$$

$$-(V_2 + 2I'')/4 + 8 + I'' - V_2/6 = 0;$$

$$I'' = -V_2/2 \Rightarrow V_2 = 12V;$$

$$\Rightarrow I_{SC} = 2A \quad (I_{SC} \text{ circuit ?...})$$

$$\text{Therefore, set } R = R_{Th} = V_{OC} / I_{SC} = 8\Omega$$

$$(b) P_R = \frac{1}{2} (V_{OC})^2 / (R + R_{Th}) = \frac{1}{2} (16)^2 / 16 = 8W$$

Question 3

MODIFY INPUT CIRCUIT (THEV. EQ.) TO SIMPLIFY:

$$V_{OC} = (0.03)250 = 7.5V ; R_{Th} = 500\Omega //$$

(a) SOLVE $R = R_{Th}$ (SEEN AT TERMINALS OF "R").

$$I = 7.5/500 = 15mA ; V_o = -(0.015)600 = -9V ;$$

$$\Rightarrow V_{oc} = V_o = -9V ; I_{sc} = V_o/450 = -20mA ;$$

$$\Rightarrow R_{Th} = V_{oc}/I_{sc} = 450\Omega // \text{ (SET } R = 450\Omega // \text{)}$$

(b) P_{30mA} SUPPLIED = $P_{100} + P_{250} + P_{250}$ ABSORBED ;

$$\Rightarrow P_{OP-AMP} = I^2 600 + V_o^2/(900) = 225mW //$$

Question 4

Set $R = R_{Th}$ for circuit connected to R: ($R_{Th} = V_{oc}/I_{sc}$)

$$\Rightarrow \text{open-circuit R} \Rightarrow I_o = -4I_o \Rightarrow I_o = 0 \Rightarrow V_{oc} = 20V$$

$$\Rightarrow \text{short-circuit R} \Rightarrow I_{sc} = 5I_o \text{ and KCL} \Rightarrow V_o = 4V$$

$$\Rightarrow I_{sc} = 200mA \text{ and } R_{Th} = 100\Omega \Rightarrow \text{set } R = 100\Omega.$$

$$\text{Also: } P_R = \frac{1}{2} P_{20V} = \frac{1}{2} (20)^2 / (100 + 100) = 1W.$$


Solve $20I_o = (20 - 400I_o)(4I_o)$ for I_o , to find $P_o = P_\phi$:

$$\Rightarrow I_o = 37.5mA \rightarrow I_R = 5I_o = 187.5mA$$

$$\Rightarrow V_{oc} = I_R(R_{Th} + R) \rightarrow R = V_{oc}/I_R - R_{Th} = 6\frac{2}{3}\Omega.$$

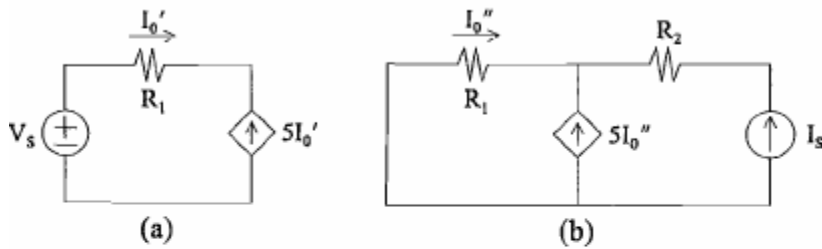Question 5

Answer: (Two independent sources \Rightarrow two circuits.)



Also: Briefly outline the steps you would take to solve for the power supplied by the voltage source using the superposition circuit solutions for the current " I_0 ".

Solve for I_0' using circuit (a).

Solve for I_0'' using circuit (b).

Calculate $P_{\text{Supplied}} = V_s (I_0' + I_0'')$.

Question 6

Optimal $R_{\text{BULB}} = R_{\text{Th}} = V_{\text{OC}} / I_{\text{SC}} = 12 / 3\frac{1}{3} = 3.6 \, \Omega$;

$\Rightarrow P_{\text{BULB}} = 0.5 (V_{\text{OC}})^2 / (R_{\text{BULB}} + R_{\text{Th}}) = 10\text{W}$.

Non-zero $R_{\text{WIRE}} \Rightarrow R_{\text{LOAD}} = R_{\text{BULB}} + R_{\text{WIRE}} \neq R_{\text{Th}}$;


\Rightarrow Unmatched load $\Rightarrow P_{\text{OUT}}$ decrease.

Require $R_{\text{EQ}} = 3.6 \, \Omega$; but, $R_{60\text{W}} = (12)^2 / 60 = 2.4 \, \Omega$;

\Rightarrow Use three 60W bulbs: one in series with two in parallel.

Note: $2.4 \, \Omega + 2.4 \, \Omega \parallel 2.4 \, \Omega = 3.6 \, \Omega$.

Question 7

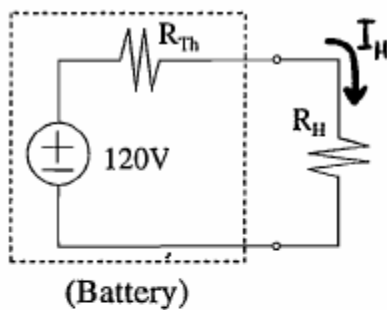

$$R_{Th} = V_{OC} / I_{SC}$$

$$= 120V / 15A = \mathbf{8\Omega}$$

Set $R_H = R_{Th}$ for P_{MAX}

$$\Rightarrow \text{Use } 8\Omega / 2\Omega m^{-1} = \mathbf{4m \parallel}$$

(b) $P_H = (V_H)^2 / R_H = (120V / 2)^2 / 8\Omega = \mathbf{450 W \parallel}$


(c) $I_H = V_H / R_H = (120V / 2) / 8\Omega = \mathbf{7.5A}$

\Rightarrow 2.5A limit means I_H must divide **3** ways...


Minimum cost \Rightarrow **3** equal length parallel wires...

$$\Rightarrow 3 \times 24\Omega \Rightarrow 72\Omega / 2\Omega m^{-1} = \mathbf{36 m \parallel}$$

Question 8

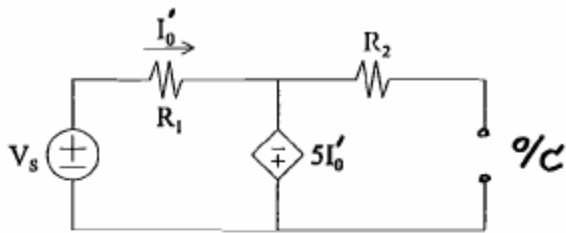

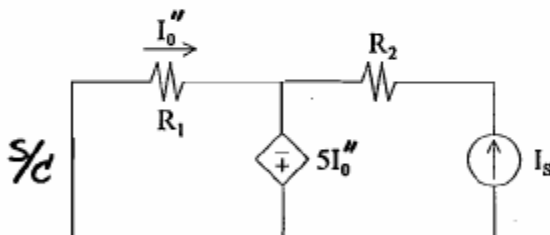Solve for I_0' , current due to V_s alone.




Solve for I_0'' , current due to I_s alone.

Total current: $I_0 = I_0' + I_0''$

Question 11

Find the Thevenin Equivalent Circuit, maximum power will be delivered if $R = R_{th}$.


1) V_{oc}

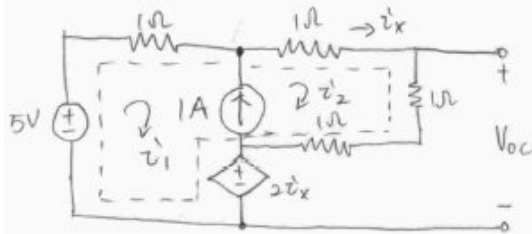

$$\begin{aligned} \text{Supermesh: } 5 - v_1 - 3v_2 - 2v_x &= 0 \\ v_2 - v_1 &= 1 \\ v_2 &= v_x \end{aligned} \quad \left. \vphantom{\begin{aligned} 5 - v_1 - 3v_2 - 2v_x &= 0 \\ v_2 - v_1 &= 1 \\ v_2 &= v_x \end{aligned}} \right\} \Rightarrow \begin{aligned} v_1 &= 0 \\ v_2 &= 1 \text{ A} \end{aligned}$$

$$V_{oc} = 2v_2 + 2v_x = 4 \text{ V}$$

2) i_{sc}

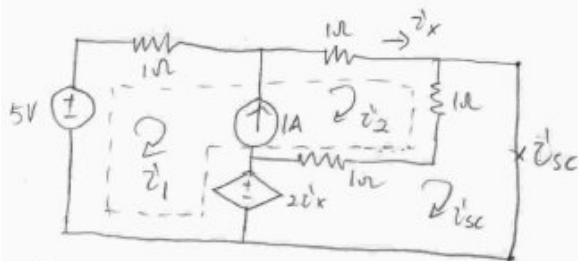

$$\begin{aligned} \text{Supermesh: } 5 - v_1 - 3v_2 - 2v_x + 2v_{sc} &= 0 \\ \text{mesh 3: } 2v_{sc} - 2v_x - 2v_2 &= 0 \\ v_2 - v_1 &= 1 \end{aligned} \quad \left. \vphantom{\begin{aligned} 5 - v_1 - 3v_2 - 2v_x + 2v_{sc} &= 0 \\ 2v_{sc} - 2v_x - 2v_2 &= 0 \\ v_2 - v_1 &= 1 \end{aligned}} \right\} \Rightarrow \begin{aligned} v_1 &= 2 \text{ A} \\ v_2 &= 3 \text{ A} \\ v_{sc} &= 6 \text{ A} \end{aligned}$$

3) R_{th}

$$R_{th} = \frac{V_{oc}}{i_{sc}} = \frac{4 \text{ V}}{6 \text{ A}} = \frac{2}{3} \Omega$$


Hence, $R = R_{th} = \frac{2}{3} \Omega$

$$P = \left(\frac{V_{oc}}{2} \right)^2 \cdot \frac{1}{R} = 6 \text{ W}$$

Question 12

First find the Thevenin equivalent of the bridge circuit, simplify the circuit, then find v_o .

1) V_{oc}

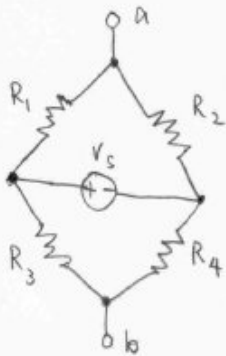


$$V_{oc} = V_{ab} = V_a - V_b$$

By voltage division:

$$V_a = \frac{R_2}{R_1 + R_2} V_s, \quad V_b = \frac{R_4}{R_3 + R_4} V_s$$


$$V_{oc} = \left(\frac{R_2}{R_1 + R_2} - \frac{R_4}{R_3 + R_4} \right) V_s$$

2) R_{th}

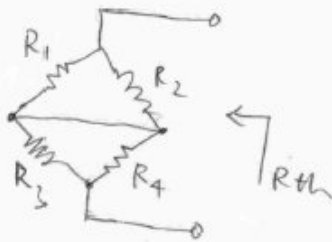

$$\begin{aligned} R_{th} &= R_1 \parallel R_2 + R_3 \parallel R_4 \\ &= \frac{R_1 R_2}{R_1 + R_2} + \frac{R_3 R_4}{R_3 + R_4} \end{aligned}$$

3) simplified circuit

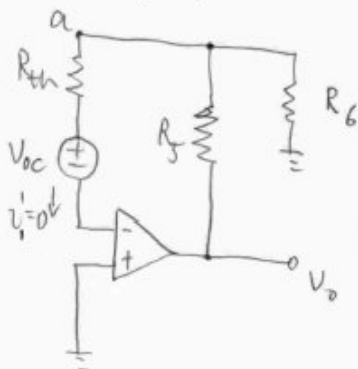

$$V_a = V_{oc} + R_{th} i_1 \quad \left. \begin{aligned} i_1 &= 0 \\ V_a &= V_{oc} \end{aligned} \right\} \Rightarrow V_a = V_{oc}$$


At node 'a' using KCL:

$$i_1 + \frac{V_a - V_o}{R_5} + \frac{V_a}{R_6} = 0$$


$$\frac{V_{oc} - V_o}{R_5} + \frac{V_{oc}}{R_6} = 0$$

$$V_o = \left(1 + \frac{R_5}{R_6} \right) V_{oc} = \left(1 + \frac{R_5}{R_6} \right) \left(\frac{R_2}{R_1 + R_2} - \frac{R_4}{R_3 + R_4} \right) V_s \quad //$$

Question 13

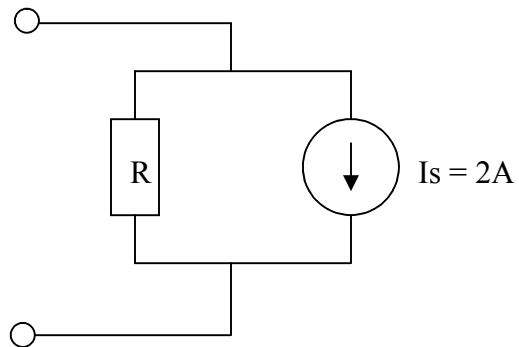

Question 14

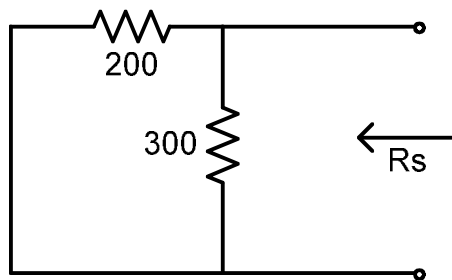


$$R_s = 200 \parallel 300 = (200 \cdot 300) / 500 = 120$$

$$20 \parallel R = 20;$$

$$R \rightarrow \infty$$

Question 15

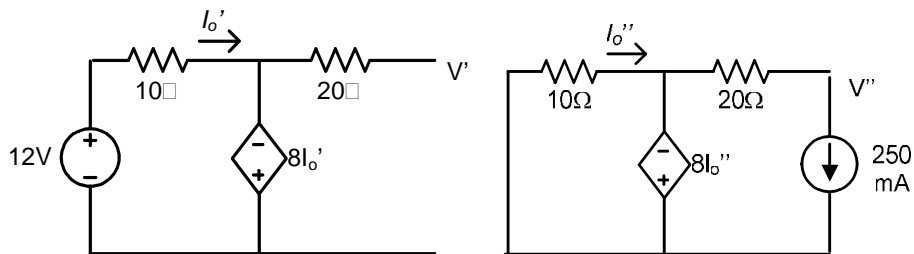

$$10I_o' - 8I_o' - 12 = 0$$

$$2I_o' = 12$$

$$I_o' = 6 \rightarrow V' = -48V$$

$$\text{KVL: } -8I_o'' + 10I_o'' = 0 \rightarrow I_o'' = 0; V'' = -0.25 \cdot 20 = -5V$$

$$\text{Therefore, } P = I(V' + V'') = 0.25 \cdot (-48 - 5) = -13.25W \text{ (Supplied), Watts is Joules/second.}$$