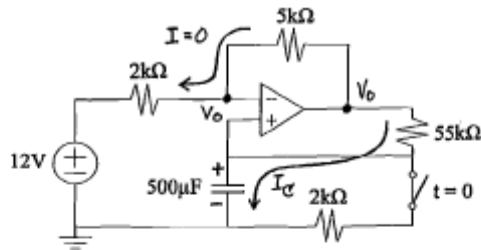


## Assignment 6 Solutions

### Question 1




- (a) Find the net charge stored on the upper plate of the capacitor at time  $t = 0^-$ .  
 (b) Find the exponential time constant of the circuit for time  $t > 0$ .

a) Circuit is in DC steady-state operation at  $t = 0^-$  ;

$$\begin{aligned} \Rightarrow I_c &= 0 \Rightarrow I_{55k\Omega} = 0 \quad (\text{Switch open!}) \\ \Rightarrow V_+ &= V_- = V_o = V_c \Rightarrow I_{5k\Omega} = I_{12V} = 0 \\ \Rightarrow V_c(0^-) &= 12V ; Q^{UP} = C V_c(0^-) = +6mC \end{aligned}$$

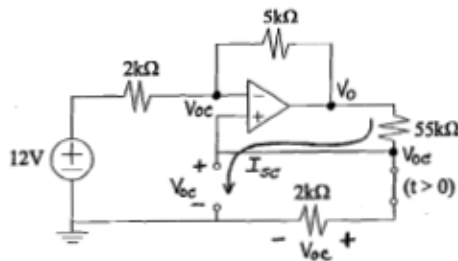b)  $T_c = R_{Th} C$  ;  $R_{Th} = V_{oc} / I_{sc}$  ( $t > 0$  circuit!)

$\Rightarrow$  Find  $V_{oc}$  and  $I_{sc}$  (w.r.t.  $C$  ; switch closed)



Find  $V_{oc}$  :

$$\begin{aligned} \text{KCL @ } V_- : (12 - V_{oc}) / 2000 &= (V_{oc} - V_o) / 5000 \\ \Rightarrow 7 V_{oc} - 2 V_o &= 60 ; \end{aligned}$$

$$\begin{aligned} \text{KCL @ } V_+ : (V_o - V_{oc}) / 55000 &= V_{oc} / 2000 \\ \Rightarrow 2 V_o &= 57 V_{oc} ; \end{aligned}$$

Therefore:  $V_{oc} = -6 / 5 \text{ V}$

Find  $I_{sc}$  :

$$I_{sc} = V_o / 55000 ; V_o = -(12 / 2000) (5000) = -30V$$

Find  $R_{Th}$  :  $R_{Th} = V_{oc} / I_{sc} = 2200\Omega$

Find  $T_c$  :  $T_c = R_{Th} C = (2200)(0.0005) = 1.1s$

### Question 2

$$(a) V_o(t) = V_o(\infty) + [V_o(0) - V_o(\infty)] e^{-t/R_{Th}C} : t > 0 ;$$

$$= 0 + 5 e^{-500t/R_{Th}} : t > 0 .$$

$\Rightarrow R_{Th}$  REQUIRED... (SEEN AT TERMINALS OF "C")

⊗ DRIVE  $t > 0$  CIRCUIT WITH  $-1V$  SOURCE ;

$$\Rightarrow R_{Th} = R_{IN} = 1/I_o = [4(\frac{1}{5} + \frac{1}{20})]^{-1} = 1\Omega //$$

$$\Rightarrow V_o(t) = 5 e^{-500t} V : t > 0 //$$

$$(b) P_{ABS} = (0.75 I_o)(-V_o) \text{ WHERE } I_o = -V_o \text{ (SHOW!)}$$

$$\Rightarrow P_{ABS} = 0.75 I_o^2 = 0.75 V_o^2 = 18.75 e^{-1000t} W : t > 0 //$$

### Question 3

Yes, the op-amp output current  $I_o$  must vary with time.  
The  $t > 0$  capacitor charging current varies with time,  
however, the source current does not. Therefore, KCL  
at the op-amp output requires  $I_o$  must vary with time.

$$V_c(t) = V_c(\infty) + [V_c(0\pm) - V_c(\infty)] e^{-t/T_c} : t > 0$$

$$V_c(0\pm) = 0 ; V_c(\infty) = V_o = -(0.005)(1200) = -6V ;$$

$$R_{Th} = V_{OC} / I_{SC} = 30k\Omega ; \{ V_{OC} = V_o ; I_{SC} = V_o / 30k\Omega \}$$

$$T_c = R_{Th} C = (30k\Omega)(800nF) = 24ms ;$$

$$\Rightarrow V_c(t) = -6 + 6 e^{-t/0.024} V : t > 0.$$

$$P_{5mA} = 0.005V_1 = (0.005)[(800)(0.005)] = 20mW : t > 0$$

### Question 4

$$\text{Switch closed: } T_c = (20k\Omega)(800\mu F) = 16s ;$$

$$5T_c \rightarrow 10T_c = 1\text{min } 20s \rightarrow 2\text{min } 40s.$$

$$V_c(t_0) = 6V \rightarrow V_s(t_0^+) = (20k\Omega \parallel 5k\Omega)(3mA) = 12V ;$$

$$\text{O/C } 800\mu F \rightarrow V_s(t \rightarrow \infty) = (5k\Omega)(3mA) = 15V ;$$

$$\text{Switch open} \rightarrow T_c = (20k\Omega + 5k\Omega)(800\mu F) = 20s ;$$

$$\Rightarrow V_s(t) = c_1 + c_2 e^{-(t-t_0)/T_c} = 15 - 3 e^{-0.05(t-t_0)} V : t > t_0.$$

$$V_c(t \rightarrow \infty) = 0 \rightarrow \min W_c ; \text{ Set } (3mA)R = 6V \rightarrow R = 2k\Omega$$

$$V_c(t \rightarrow \infty) \rightarrow \infty \rightarrow \max W_c ; \text{ Set } (3mA)R \rightarrow \infty \rightarrow R \rightarrow \infty$$

### Question 5

$$t < 0 \text{ (charging)} \quad T_C = R_{Th} C = (20k\Omega)(5\mu F) = 0.1 s$$

→ Circuit in steady-state at  $t = 0^-$ , because switch at position "a" for  $2s = 20 T_C //$  ( $> 5-10 T_C$  's)

$$V_C(0^-) \cong (4mA)(20k\Omega) = 80V \quad \Rightarrow V_C(0^+) \cong 80V$$

$$V_C(t \rightarrow \infty) = 120V ; T_C(t > 0) = (25k\Omega)(5\mu F) = 0.125 s$$

$$\Rightarrow V_C(t) \cong 120 - 40e^{-8t} V : t > 0 //$$

$$Q_C(t) = C V_C(t) : (t = 0^+ \rightarrow V_{MIN} ; t \rightarrow \infty \rightarrow V_{MAX})$$

$$Q_{MIN} = C V_{MIN} \cong (5\mu F)(80V) = 400 \mu C$$

$$Q_{MAX} = C V_{MAX} = (5\mu F)(120V) = 600 \mu C //$$

### Question 6

$$(c) \text{ Suppose } Q_{MAX}(d) = C(d) V_{MAX}(d) \cong C_0 V_0 :$$

$$\Rightarrow Q_{MAX}(a) \cong (3C_0/2)(2V_0/3) = C_0 V_0$$

$$\Rightarrow Q_{MAX}(b) \cong (5C_0/4)(2V_0/3) = \frac{5}{6} C_0 V_0$$

↘ But, what is  $V_{MAX}(c)$ ? (How can we calculate it?)

$$\text{For "series" interpretation, } Q(3\epsilon_0) = Q(2\epsilon_0) \text{ ???}$$

$$\Rightarrow C(3\epsilon_0) V(3\epsilon_0) = C(2\epsilon_0) V(2\epsilon_0) ;$$

$$\Rightarrow V(2\epsilon_0) = 1.5 V(3\epsilon_0) \Rightarrow V_{MAX}(c) = \frac{5}{6} V_0 \text{ ???}$$

$$\Rightarrow Q_{MAX}(c) \cong (6C_0/5)(5V_0/6) = C_0 V_0$$

$$\Rightarrow Q_{MAX}(a) \cong Q_{MAX}(c) \cong Q_{MAX}(d) > Q_{MAX}(b) //$$

$$(a) C(d) = C_0 : C(a) \cong \frac{3}{2} C_0$$


$$C(b) \cong C_0/2 + (3C_0/2)/2 = \frac{5}{4} C_0$$

$$C(c) \cong [1/(2C_0) + 1/(3C_0)]^{-1} = \frac{6}{5} C_0$$

$$\Rightarrow C(d) < C(c) < C(b) < C(a) //$$

$$(b) \text{ Smallest charging circuit } T_C \Rightarrow \text{shortest charge time ;}$$
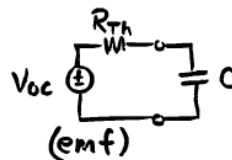
$$T_C = [R_{Th}(\text{source})] C \Rightarrow \text{SMALLEST } C = C(d)$$




OR, WHATEVER YOU INDICATED IN YOUR ANSWER TO (a)...

### Question 7

Trigger OFF:  $V_T = V_C + V_{1\Omega}$ ; Trigger ON:  $I_T = I_C + 3/9$ ;  
 $V_T(0^+) = \overbrace{V_C(0^+)}^0 + \overbrace{V_{1\Omega}(0^+)}^{0.3V} = 0.3V < 2V \Rightarrow$  Trigger OFF;  
 Trigger turns "ON" when  $V_C + V_{1\Omega} = 2V$ , i.e. when  $V_{9\Omega} = \underline{1V}$   
 Therefore, after closing the switch (trigger OFF) the capacitor charges up until  $I_C$  drops to  $\underline{1/9A}$ ; then the trigger turns ON and the capacitor discharges through the bulb ( $1\Omega$  resistor) until  $I_C$  reduces to  $0.4 - \underline{0.33} = \underline{0.07}$ ; then the trigger turns OFF and the capacitor begins to recharge. Any light when trigger OFF?

Trigger OFF:  $\max(P_{\text{Bulb}}) = [V_{\text{Bulb}}(0^+)]^2 = 90\text{mW} \Rightarrow$  no light.

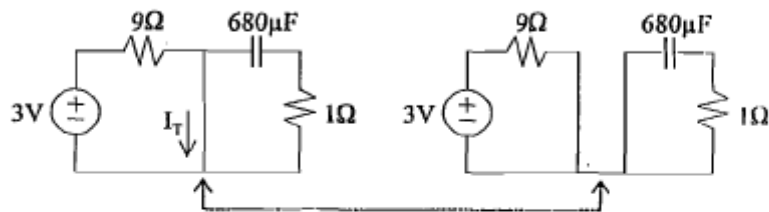Trigger ON:  $\max(P_{\text{Bulb}}) = [V_{\text{Bulb}}(\text{ON}^+)]^2 = [V_C(\text{ON}^+)]^2$ .



KVL & voltage divider  $\Rightarrow [V_C(\text{ON}^+)] = 3 - \underline{(9+1)(1/9)} \approx \underline{1.89V}$


$\Rightarrow \max(P_{\text{Bulb}}) = [V_C(\text{ON}^+)]^2 \approx \underline{3.57W}$  ( $\Rightarrow$  light output)

Light output continues until  $V_{\text{Bulb}}$  drops to  $0.4V$  ( $I_{\text{Bulb}} = 0.4A$ );

$\Rightarrow$  Light output stops before trigger turns OFF.  
 (because  $3V$  source contributes  $1/3A$  to  $I_T$ )

$\Rightarrow$  Bulb flash energy  $= 0.5 C [(1.89)^2 - (0.4)^2] \approx \underline{1.16mJ}$   
 (energy discharged by capacitor during bulb flash) (?!)

### Question 8

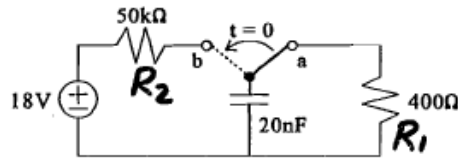

NB.  $T_c(0^-) = R_1 C = 8 \mu s$   
 $\Rightarrow V_c(0^-) = 0$


$Q_{\max} = Q(\infty) = C V(\infty)$   
 $= 20 \times 10^{-9} (18) = 360 \text{ nC} //$

$Q = 0.99 Q_{\max}$  AT  $t \sim 4.6 T_c(0^+)$   
 (SOLVING  $0.01 = e^{-t/T_c} \Rightarrow 4.6 T_c$ )

$T_c(0^+) = R_2 C = 1 \text{ ms} \Rightarrow t = 4.6 \text{ ms}$

### Question 9



(a)  $t = 0^-$  CIRCUIT:

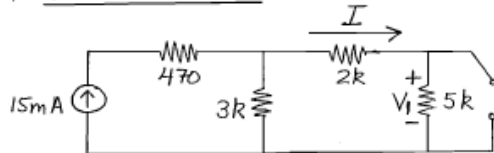

$I = \frac{3000}{2000 + 5000 + 3000} \times 0.015 = 4.5 \text{ mA}$

$V_1(0^-) = 5000 I = 22.5 \text{ V} //$


(b)  $t = 0^+$  CIRCUIT:

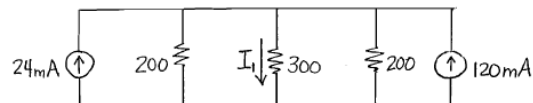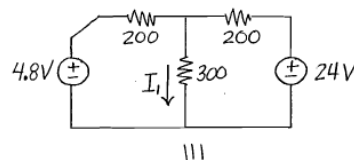

$I_1(0^+) = \frac{200 \parallel 200}{300 + 200 \parallel 200} (0.024 + 0.120)$


$I_1(0^+) = 36 \text{ mA} //$

(c)  $t \rightarrow \infty$  CIRCUIT:

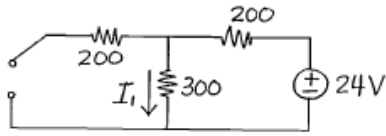

$$I_1(\infty) = \frac{24}{200+300} = 48 \text{ mA} //$$

(d)  $t > 0$  CIRCUIT:

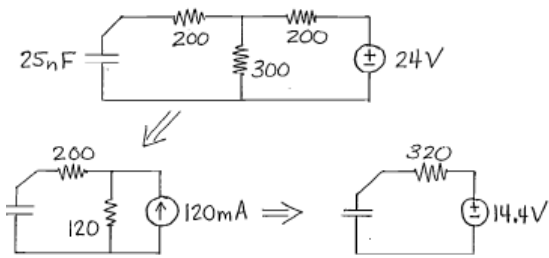

HENCE,  $T_c(0^+) = R_{Th} C$

$$= 320 (25 \times 10^{-9})$$

$$= 8 \mu s //$$

(e) (BASED ON  $t > 0$  CIRCUIT...)

$$V_2(t) = 300 I_1(t) : t > 0$$

$$I_1(t) = I_1(\infty) + [I_1(0^+) - I_1(\infty)] e^{-t/T_c}$$

$$= 0.048 + (-0.012) e^{-125000t}$$

$$\Rightarrow V_2(t) = 14.4 - 3.6 e^{-125000t} \text{ V} : t > 0 //$$

### Question 10

Will be posted on Monday

### Question 11

Will be posted on Monday