

ECSE 210 WINTER 2007

FINAL EXAM SOL.

① (a)  $f = 60 \text{ Hz}$

$\therefore \omega = 2\pi f \text{ rad/sec}$

To find  $Z_L$  for max.

power transfer, we



need to find impedance seen by the load  $Z_L$ . So

take  $Z_L$  out and find out Thevenin ckt. seen

from terminals A & B.

Find  $V_{oc}$ :

Apply KVL around mesh  $\underline{I}_1$

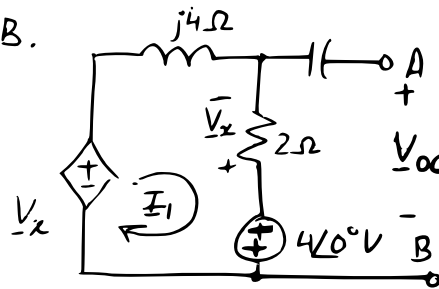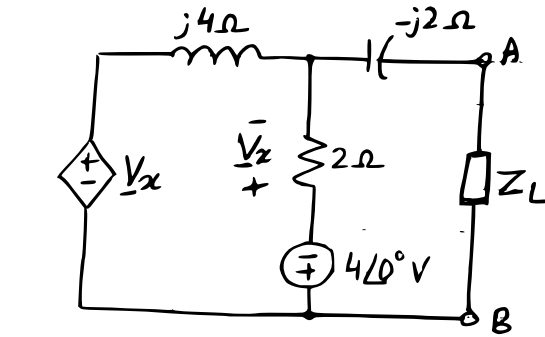

$$j4\underline{I}_1 + 2\underline{I}_1 - 4\angle 0 - \underline{V}_x = 0$$

$$j4\underline{I}_1 + 2\underline{I}_1 - 4\angle 0 - \underbrace{2(-\underline{I}_1)}_{\underline{V}_x} = 0$$

$$\underline{I}_1 (j4 + 2 + 2) = 4\angle 0 \Rightarrow \underline{I}_1 = \frac{4\angle 0}{4+j4} = \frac{4\angle 0}{4\sqrt{2}\angle 45^\circ}$$


$$\underline{I}_1 = \frac{1}{\sqrt{2}} \angle -45^\circ \text{ A}$$

$$\therefore \underline{V}_{oc} = 2\underline{I}_1 - 4\angle 0 = \sqrt{2}\angle -45^\circ - 4\angle 0 = 1-j1-4$$

$$\underline{V}_{oc} = -3-j1 = 3.162 \angle -161.565^\circ \text{ V} \quad \text{--- ①}$$

Find  $\underline{I}_{sc}$

Apply KVL around mesh #1:

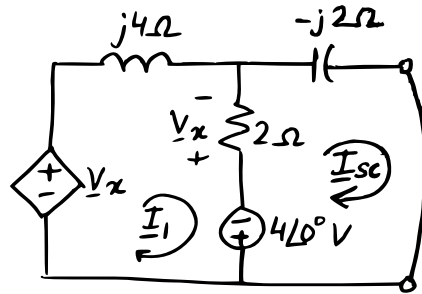

$$j4\underline{I}_1 + 2(\underline{I}_1 - \underline{I}_{sc}) - 4\angle 0^\circ - \underline{V}_x = 0$$

$$j4\underline{I}_1 + 2\underline{I}_1 - 2\underline{I}_{sc} - 4\angle 0^\circ - \underbrace{2(\underline{I}_{sc} - \underline{I}_1)}_{\underline{V}_x} = 0$$

$$\underline{I}_1 (j4 + 2 + 2) + \underline{I}_{sc} (-2 - 2) = 4\angle 0^\circ$$

$$\underline{I}_1 (4 + j4) - 4\underline{I}_{sc} = 4$$

$$\underline{I}_1 (1 + j1) - \underline{I}_{sc} = 1 \quad \text{--- (2)}$$

Apply KVL around mesh:  $\underline{I}_{sc}$ :

$$-j2\underline{I}_{sc} + 4\angle 0^\circ + (\underline{I}_{sc} - \underline{I}_1) 2 = 0$$

$$-j2\underline{I}_{sc} + 4\angle 0^\circ + 2\underline{I}_{sc} - 2\underline{I}_1 = 0$$

$$-2\underline{I}_1 + \underline{I}_{sc} (2 - j2) = -4$$

$$-\underline{I}_1 + \underline{I}_{sc} (1 - j1) = -2 \quad \text{--- (3)}$$

From (3):

$$\underline{I}_1 = \underline{I}_{sc} (1 - j1) + 2$$

∴ (2) becomes

$$(\underline{I}_{sc} (1 - j1) + 2)(1 + j1) - \underline{I}_{sc} = 1$$

$$\underline{I}_{sc} ((1 - j1)(1 + j1) - 1) = 1 - 2(1 + j1)$$

$$I_{sc} = \frac{-1-j2}{1} = -(1+j2) \text{ A} = 2.236 \angle -116.57^\circ \quad \text{--- (4)}$$

Using (2) & (4),  $Z_{TH} = \frac{V_{oc}}{I_{sc}}$

$$= \frac{3.162 \angle -161.57^\circ}{2.236 \angle -116.57^\circ} = \sqrt{2} \angle -45^\circ = 1-j1 \Omega$$

∴ For max. power transfer  $Z_L = Z_{TH}^* = 1+j1 \Omega$   
 $= \sqrt{2} \angle 45^\circ \Omega$

(b) Max. power transferred to the load:

$$P_{Lmax} = \frac{1}{2} |I_L|^2 R_L = \frac{1}{2} \left| \frac{V_{oc}}{Z_{TH} + Z_L} \right|^2 R_L$$

$$= \frac{1}{2} \left| \frac{3.162 \angle -161.57^\circ}{1+j1} \right|^2 \times R_L = \frac{1}{2} \left( \frac{3.162}{2} \right)^2$$

$$P_{Lmax} = 1.25 \text{ W}$$

(c):  $Z_L = 1+j1 \leftarrow$  inductive impedance = ~~inductive~~


$$R_L = 1 \Omega \quad jX_L = j1 \Omega \Rightarrow L\omega = 1 \Rightarrow L = \frac{1}{\omega} = 2.65 \text{ mH}$$

$$\therefore Z_L = R_L + jX_L = R_L + jL\omega$$

$$R_L = 1 \Omega$$

$$L = 2.65 \text{ mH}$$

(2)(a)

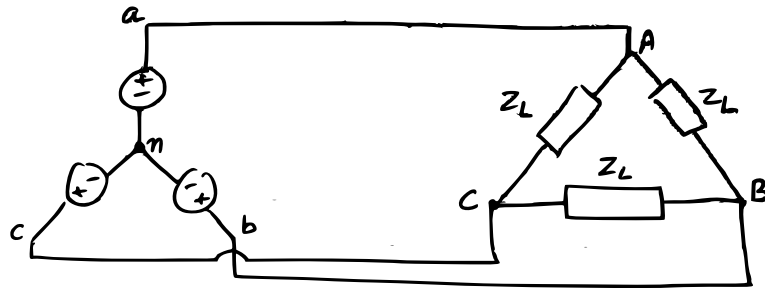

$$V_L = 208 \text{ V rms.}$$

$$P_T = 1200 \text{ W} \quad \text{pf} = 20^\circ \text{ lagging} = \cos(-20^\circ) = 0.94$$

$$P_L (\text{power consumed per load phase}) = \frac{1200}{3} = 400 \text{ W}$$

$$\text{Now, } P_L = V_\Delta I_\Delta \cos \theta$$

$$\therefore 400 = 208 I_\Delta \times 0.94$$

$$I_\Delta = 2.05 \text{ A rms}$$

↙ current in each load phase

$$\therefore \text{mag. of line current } I_L = \sqrt{3} I_\Delta = \boxed{3.55 \text{ A rms}}$$

$$|Z_L| = \frac{V_L}{I_\Delta} = \frac{208}{2.05} = 101.46 \Omega$$

$$\text{Since } \theta = +20^\circ, \Rightarrow R_L = 101.46 \cos(+20^\circ) = 95.34 \Omega$$
$$jX_L = j101.46 \sin(+20^\circ) = +j32.61 \Omega$$

$$\text{OR } \boxed{Z_L = 101.46 \angle 20^\circ \Omega}$$

② (b)  $V_L = 34,500 \text{ V rms}$ ,  $f = 60 \text{ Hz}$

Balanced 3-ph load power consumption  $|S_T| = 24 \times 10^6 \text{ VA}$   
at  $0.78 \text{ pf lag}$

So load angle:  $\cos^{-1} 0.78 = 38.74^\circ$

$$\therefore \underline{S}_T = 24 \times 10^6 \angle 38.74^\circ = 18.72 \times 10^6 + j 15.02 \times 10^6 \text{ VA}$$

$$= P_T + j Q_T$$

Desired new pf =  $0.94 \text{ lead}$ .  $\therefore \theta_{\text{new}}$  (load angle after pf correction) =  $-\cos^{-1} 0.94 = -19.95^\circ$

With pf correction, real power consumption remains the same and new caps consume additional vars.

$$\therefore |\underline{S}_{\text{new}}| \cos \theta_{\text{new}} = 18.72 \times 10^6 \text{ W}$$

$$\therefore |\underline{S}_{\text{new}}| = \frac{18.72 \times 10^6}{0.94} = 19.91 \times 10^6 \text{ VA}$$

$$\therefore \underline{S}_{\text{new}} = 19.91 \times 10^6 \angle -19.95^\circ \text{ VA}$$

$$\therefore j Q_{\text{new}} = j 19.91 \times \sin(-19.95^\circ) \times 10^6$$

$$= -j 6.79 \times 10^6 \text{ vars}$$

$$\Rightarrow j Q_T + j Q_{\text{cap}} = -j 6.79 \times 10^6 \Rightarrow j Q_{\text{cap}} = -j 21.81 \times 10^6 \text{ VAR}$$

For each cap:  $-j \left( \frac{V_L}{\sqrt{3}} \right)^2 C \omega = -j \frac{21.81 \times 10^6}{3}$

$$C = \frac{21.81 \times 10^6 \times 3}{3 \times 34500^2 \times 2\pi \times 60} = \boxed{48.6 \mu\text{F}}$$

③


$P_L = 20 \text{ kW}$ ,  $0.8$  pf lagging.  $\Rightarrow \omega = 2\pi f = 377 \text{ rad/s}$

$$\underline{V}_L = 220 \angle 0^\circ \text{ V rms}$$

$$f = 60 \text{ Hz}$$

$$\underline{Z}_e = 0.09 + j0.3 \Omega$$
$$= 0.313 \angle 73.3^\circ \Omega$$
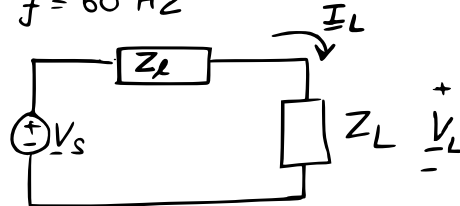
$$\theta_L = \cos^{-1} 0.8 = 36.87^\circ$$



$$P_L = V_L I_L \cos \theta_L$$

$$\therefore I_L = \frac{P_L}{V_L \cos \theta_L} = \frac{20000}{220 \times 0.8} = 113.64 \text{ A rms}$$

$$\propto \underline{I}_L = 113.64 \angle -36.87^\circ \text{ A rms}$$

So, line impedance drop  $\underline{V}_e = \underline{I}_L \underline{Z}_e = 113.64 \angle -36.87^\circ \times 0.313 \angle 73.3^\circ$

$$\underline{V}_e = 35.59 \angle 36.43^\circ = 28.64 + j21.14 \text{ V rms}$$

$$\therefore \underline{V}_s = \underline{V}_L + \underline{V}_e = 220 + j0 + 28.64 + j21.14$$
$$= 248.64 + j21.14 = 249.54 \angle 4.86^\circ \text{ V rms}$$

$$\Rightarrow v_s(t) = 249.54 \cos(377t + 4.86^\circ) \text{ V rms. Ans.}$$

(b) pf seen by the source:  $\cos(4.86 - -36.87^\circ)$   
 $= \cos(41.73) = 0.746$  lagging  
Ans

4(a) Apply KCL at the inverting node:

$$\frac{V_i - 0}{R_1 + \frac{1}{Cs}} = \frac{0 - V_o}{R_2}$$

$$\Rightarrow H(s) = \frac{V_o}{V_i} = \frac{-R_2}{R_1 + \frac{1}{Cs}} = -\frac{s \frac{R_2}{R_1}}{s + \frac{1}{R_1 C}}$$

$\therefore$  one zero at  $s = 0$

one pole at  $s = \frac{1}{-R_1 C}$

From the given Bode plot, we know the pole is

$$\text{at } \omega = 500 \text{ rad/s} \quad \therefore 500 = \left| \frac{1}{-R_1 C} \right|$$

$$\therefore R_1 = \frac{1}{500 \times 3 \times 10^{-6}} = \boxed{666.67 \Omega}$$

Now, note that as  $\omega \rightarrow \infty$ ;  $20 \log_{10} |H(j\omega)| = 34 \text{ dB}$

$$\text{or } |H(j\omega)| \Big|_{\omega \rightarrow \infty} = 50.119$$


$$\text{Also } H(j\omega) = \frac{-j\omega R_2/R_1}{j\omega + \frac{1}{R_1 C}} \quad \therefore |H(j\omega)| = \frac{\omega R_2/R_1}{\sqrt{\omega^2 + \frac{1}{R_1^2 C^2}}}$$

$$|H(j\omega)| = \frac{R_2}{R_1} \frac{1}{\sqrt{1 + \frac{1}{R_1^2 C^2 \omega^2}}} \Rightarrow |H(j\omega)| \Big|_{\omega \rightarrow \infty} = \frac{R_2}{R_1}$$

since as  $\omega \rightarrow \infty$ ;  $\frac{1}{R_1^2 C^2 \omega^2} \rightarrow 0$

$$\therefore \frac{R_2}{R_1} = 50.119. \quad \text{With } R_1 = 666.67 \Omega, \quad \boxed{R_2 = 33.4 \text{ k}\Omega}$$

(b)

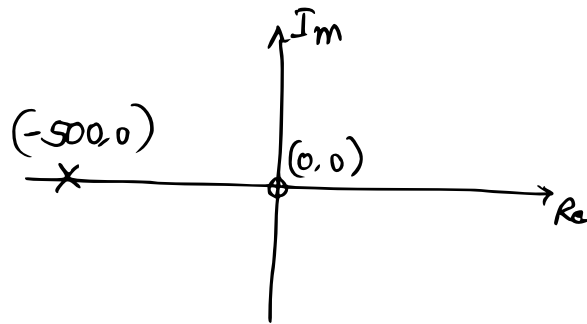

one zero at  $(0,0)$   
one pole at  $\frac{1}{-R_1C} = (-500,0)$


(c) Real part of the pole is  $< 0$ .  $\therefore$  the ckt. is stable.



5 (a) For  $0 < t < 0.02$  sec, the ckt. is

Apply KCL at A:

$$\frac{v-24}{R_1} = -C \frac{dv}{dt}$$

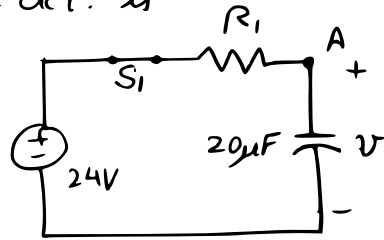

$$-\frac{v}{R_1} + \frac{24}{R_1} = C \frac{dv}{dt}, \text{ or } \frac{dv}{dt} + \frac{1}{RC} v = \frac{24}{R_1 C}$$

Natural sol.  $v_n = K_1 e^{st}$ ; charac. eq  $s + \frac{1}{RC} = 0$

$$\therefore v_n = K_1 e^{-\frac{1}{RC}t}$$

Forced sol.  $v_f = A$ . Putting this into the ode gives

$$0 + \frac{A}{RC} = \frac{24}{RC} \Rightarrow A = 24$$

$$\therefore v = v_n + v_f = K_1 e^{-\frac{1}{RC}t} + 24$$

$$v(0) = 0 = K_1 + 24 \Rightarrow K_1 = -24$$

$$\therefore v = 24 \left( 1 - e^{-\frac{1}{RC}t} \right) \text{ V}$$

Now,  $t = 0.02$  sec,  $v = 16$  V,  $R_1 = ?$

$$16 = 24 \left( 1 - e^{-\frac{0.02}{R_1 C}} \right)$$

$$24 e^{-\frac{0.02}{R_1 C}} = 8 \Rightarrow e^{-\frac{0.02}{R_1 C}} = \frac{1}{3} \Rightarrow \frac{-0.02}{R_1 C} = \ln \frac{1}{3}$$

$$\Rightarrow R_1 C = \frac{-0.02}{\ln \frac{1}{3}} = 0.0182 \text{ s}$$

$$\Rightarrow R_1 = \frac{-0.02}{20 \times 10^{-6} \times \ln \frac{1}{3}} = \boxed{910.24 \Omega}$$


(b) We are adding  $R_2$  to the ckt, hence the time constant will get smaller. To maintain 16V for  $t > 0.02$  basically means that the ckt. is in steady state wrt the new time constant. In this situation, cap. is open ckt., and using voltage divider:

$$\frac{24}{R_1 + R_2} R_2 = 16 \Rightarrow R_2 = R_1 \times 2 = 1820.48 \Omega$$

⑥ (a) Given the mag. resp. of a parallel RLC ckt.

$$Z(s) = \left( \frac{1}{R} + \frac{1}{Ls} + Cs \right)^{-1}$$
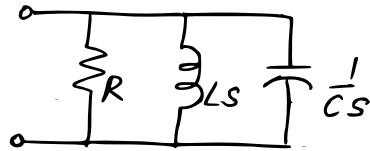
$$= \frac{1}{Cs + \frac{1}{R} + \frac{1}{Ls}}$$



$$Z(j\omega) = \frac{1}{jC\omega + \frac{1}{R} + \frac{1}{jL\omega}} = \frac{\frac{1}{R} - j\left(C\omega - \frac{1}{L\omega}\right)}{\frac{1}{R^2} + \left(C\omega - \frac{1}{L\omega}\right)^2}$$

(a) At resonance,  $\omega_r$ ,  $C\omega_r = \frac{1}{L\omega_r}$

$$\text{and } Z(j\omega_r) = R$$

From the given graph, at resonance, gain  $|Z(j\omega)| = R$   
 $= 3998.9 \Omega$

$$(b) \quad Q = \frac{\omega_r}{\omega_2 - \omega_1} = \frac{2.2491}{2.3322 - 2.172} = 14.04$$

$$(c) \quad \omega_0 \text{ (resonant freq)} = 2249.1 \text{ Hz (where the peak occurs in the gain plot)}$$

$$= (2\pi) 2249.1 \text{ rad/sec}$$

$$= 14131.5 \text{ rad/sec}$$

$$(d) \quad Z(s) = \left( \frac{1}{R} + \frac{1}{Ls} + Cs \right)^{-1} = \dots = \frac{s/C}{s^2 + \frac{s}{RC} + \frac{1}{LC}}$$

$$Z(j\omega) = \frac{j\omega/C}{\frac{1}{LC} - \omega^2 + j\omega \frac{1}{RC}}$$

$$(e) \quad \text{From (a) } R = 3998.9 \Omega$$

$$\text{Also, } \omega_0 = \frac{1}{\sqrt{LC}} = 14131.5$$

Note that in this case:

Quality factor is also defined as

$$Q = R \sqrt{\frac{C}{L}} = 14.04 \text{ (from (b))}$$

$$\therefore \sqrt{\frac{C}{L}} = \frac{14.04}{3998.9} \Rightarrow \frac{C}{L} = 12.33 \times 10^{-6} \quad \text{(e1)}$$

$$\text{Since } \frac{1}{\sqrt{LC}} = 14131.5 \Rightarrow \frac{1}{LC} = 0.1997 \times 10^9 \quad \text{(e2)}$$

Solving equations (e1) and (e2),

$$L = 20.15 \text{ mH}$$

$$C = 0.2485 \mu\text{F}$$