

--	--

--	--

FAMILY NAME
(PRINT)

FIRST NAME
(PRINT)

SECTION

STUDENT I.D.

Circuit Analysis
ECSE 210

Examiner: Prof. M. D. Levine

Co-Examiner: Prof. R. Khazaka

Signature: *Martin Levine*

Signature: *R. Khazaka*

Date: Tuesday, April 11, 2006

Time: 2:00 PM

INSTRUCTIONS

- Use either a pen or HB pencil.
- The total number of points in this examination is 35, which will be pro-rated to 70% of the final grade.
- This is a closed book examination.
- Make sure that your solutions are written on the *consecutive* pages provided. Four extra pages may be found at the end.
- You are permitted regular and translation dictionaries.
- Faculty standard calculator permitted only.
- This examination paper must be returned.

EVALUATION
OF EXAM
PAPER

Question #	1	2	3	4	5	6
weight	5	6	8	6	5	4
SCORE						

Total Score

--

[6 marks]

1. The circuit below, containing a two-port with a hybrid parameter matrix H within it, was designed to have a transfer function given by:


$$\frac{V_o(s)}{V_{in}(s)} = \frac{2s - 10}{s^2 + 27s + 2}$$

(a) Sketch the h-parameter equivalent model for the two-port.

(2 marks)

(b) Determine whether the circuit in the figure satisfies the above transfer function. Show the details of your analysis.

(4 marks)

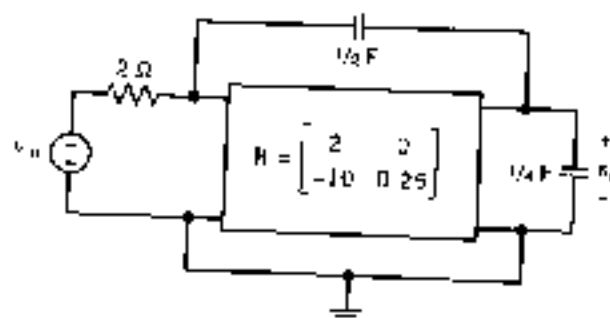


Write the final answer on page 6.

[5 marks]

2. Consider the circuit shown below.

(a) Determine the type of filter that the circuit represents. Explain your reasoning. (3 marks)

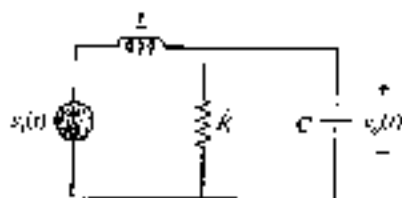
(b) Calculate the corner or cutoff frequency when $R=2k\Omega$, $L=2H$ and $C=2\mu F$. (3 marks)



Write the final answer on page 10.

[8 marks]

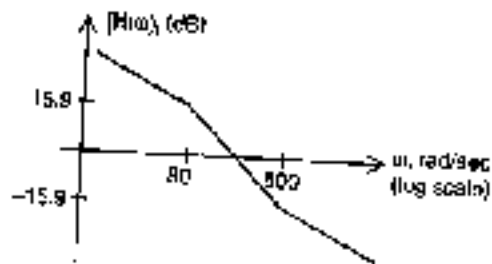3. Determine the transfer function $H(s)$ for the amplitude Bode plot shown below.



Write the final answer on page 14.

[6 marks]


4. The figure below shows a balanced Y-to- Δ three-phase circuit. The phase voltages of the Y-connected source are $V_a=110\angle 0^\circ$ V rms, $V_b=110\angle -120^\circ$ V rms, and $V_c=110\angle +120^\circ$ V rms. The line impedances are each $Z_L=10+j5 \Omega$. The impedances of the Δ -connected load are each $Z_A=75+j225 \Omega$.

(a) Determine the phase currents in the Δ -connected load.

(5 marks)

(b) Determine the total average power delivered to the load.

(1 mark)

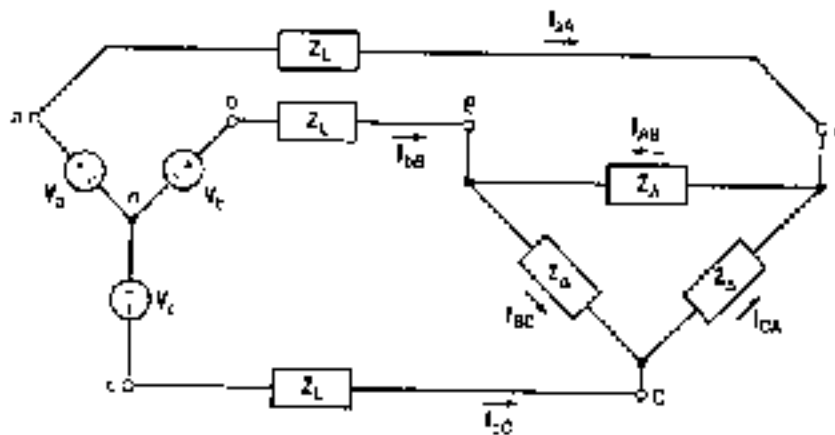

Write the final answer on page 18.

[5 marks]

5. The input to the circuit shown below is the voltage of the current source,

no trace


$$v_s(t) = 7.28 \cos(4t + 77^\circ) \text{ V}$$

The output is the voltage across the inductor,

$$v_o(t) = 4.254 \cos(4t + 311^\circ) \text{ V}$$

Determine the following:

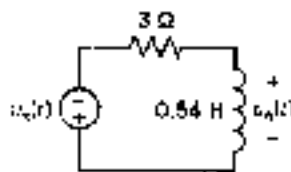- (a) The average power supplied by the voltage source (2 marks)
- (b) The average power received by the resistor (1 mark)
- (c) The average power received by the inductor (1 mark)
- (d) The power factor of the impedance of the series connection of the resistor and inductor (1 mark)



Write the final answer on page 22.

[4 marks]


6. Consider the circuit shown below. The input to the circuit is the voltage source, $v_s(t)$, and the output is the voltage across the $4\ \Omega$ resistor. When the input is $v_s(t) = 8.93 \cos(2t + 54^\circ)$ V, the corresponding output is $v_o(t) = 3.83 \cos(2t + 83^\circ)$ V.

(a) Determine the voltage, $v_o(t)$, across the $9\ \Omega$ resistor.

(2 marks)

(b) Determine the value of the capacitance C .

(2 marks)

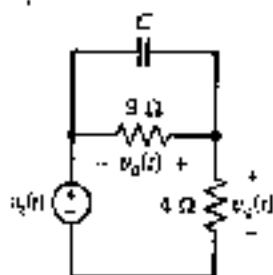

Write the final answer on page 26.