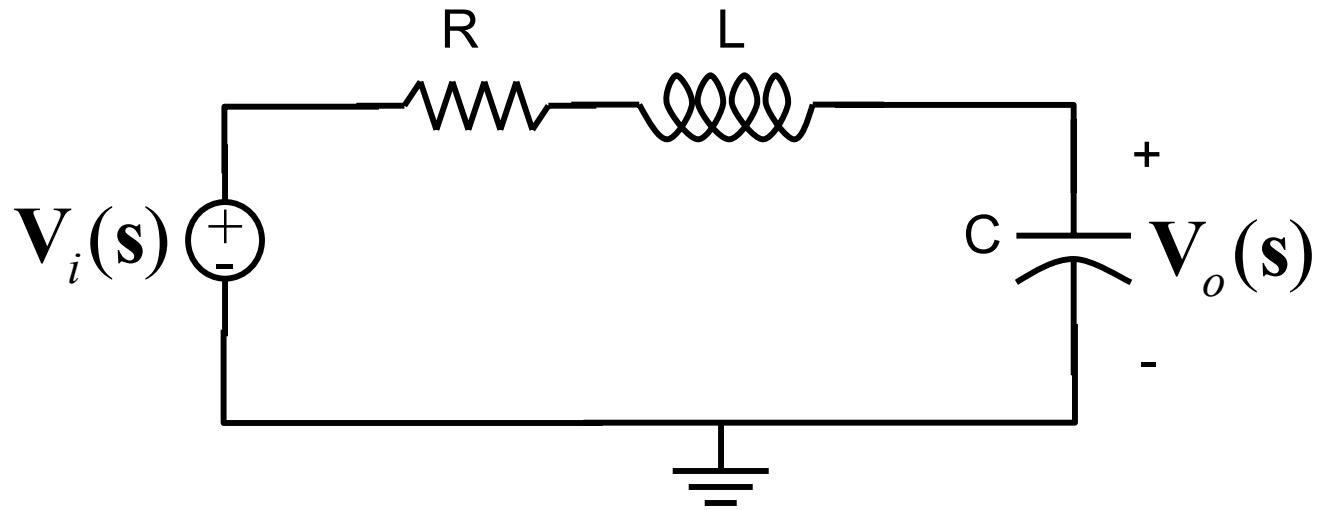


ECSE 210: Circuit Analysis

Lecture #26:

Resonant Circuits

Poles and Circuit Dynamics



$$V_o(s) = \frac{1/sC}{R + sL + 1/sC} V_i(s) = \frac{1}{LCs^2 + RCs + 1} V_i(s)$$

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{1/LC}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

Poles and Circuit Dynamics

$$\mathbf{H}(s) = \frac{\mathbf{V}_o(s)}{\mathbf{V}_i(s)} = \frac{1/LC}{s^2 + \frac{R}{L}s + \frac{1}{LC}} = \frac{\omega_o^2}{s^2 + 2\zeta\omega_o s + \omega_o^2}$$

$$\omega_o = \sqrt{\frac{1}{LC}}$$

$$\zeta = \frac{R/L}{2\omega_o}$$

so that

$$\zeta = \frac{R/L}{2\omega_o} = \frac{R}{L} \frac{1}{2} \sqrt{LC} = \frac{R}{2} \sqrt{\frac{C}{L}}$$

Poles and Circuit Dynamics

$$\mathbf{H(s)} = \frac{\mathbf{V}_o(\mathbf{s})}{\mathbf{V}_i(\mathbf{s})} = \frac{\omega_o^2}{\mathbf{s}^2 + 2\zeta\omega_o\mathbf{s} + \omega_o^2}$$

If $\zeta < 1 \rightarrow p_{1,2} = -\zeta\omega_o \pm j\omega_o\sqrt{1-\zeta^2} = -\alpha \pm j\omega_d$

$$\omega_d = \omega_o\sqrt{1-\zeta^2}$$

For $\zeta < \frac{1}{\sqrt{2}} \rightarrow$ **the amplitude peaks at** $\omega_r = \omega_o\sqrt{1-2\zeta^2}$

$\rightarrow \omega_o$ is the undamped natural frequency (from the circuit).


$\rightarrow \omega_d$ is the damped natural frequency.

$\rightarrow \omega_r$ is the resonant frequency.

Poles and Frequency Response

$$\omega_r = 70.7 \text{ rad./sec.}$$

$$\zeta = 0.5 < 0.707$$

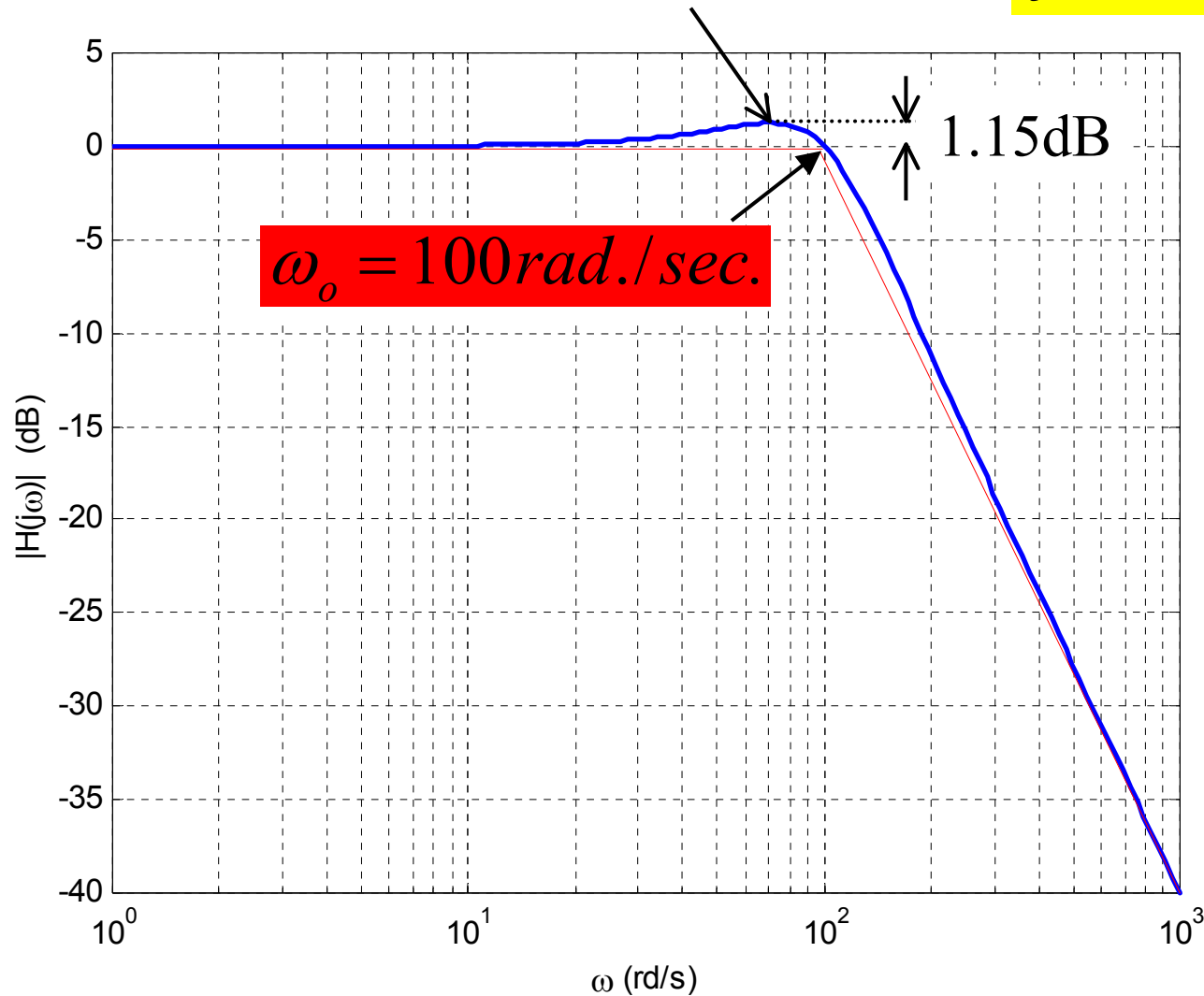

Poles and Natural Response

$$\mathbf{H}(s) = \frac{\mathbf{V}_o(s)}{\mathbf{V}_i(s)} = \frac{\omega_o^2}{s^2 + 2\zeta\omega_o s + \omega_o^2}$$

$$\zeta < 1 \quad \longrightarrow \quad p_{1,2} = -\zeta\omega_o \pm j\omega_o\sqrt{1-\zeta^2} = -\alpha \pm j\omega_d$$

$$\omega_d = \omega_o\sqrt{1-\zeta^2}$$

Natural response:

$$v_n(t) = A_n e^{-\alpha t} \cos(\omega_d t + \phi)$$


↙ Damped natural frequency

Poles and Natural Response


$$\mathbf{H(s)} = \frac{\mathbf{V}_o(\mathbf{s})}{\mathbf{V}_i(\mathbf{s})} = \frac{1/LC}{s^2 + \frac{R}{L}s + \frac{1}{LC}} = \frac{\omega_o^2}{s^2 + 2\zeta\omega_o s + \omega_o^2}$$

$$p_{1,2} = -\zeta\omega_o \pm j\omega_o\sqrt{1-\zeta^2} = -\alpha \pm j\omega_d$$

complex poles

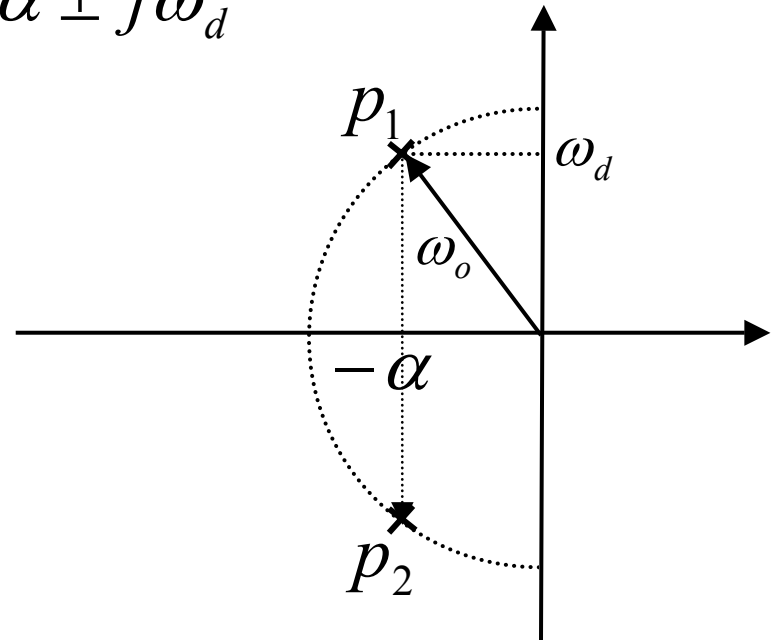

Series Resonant Circuit

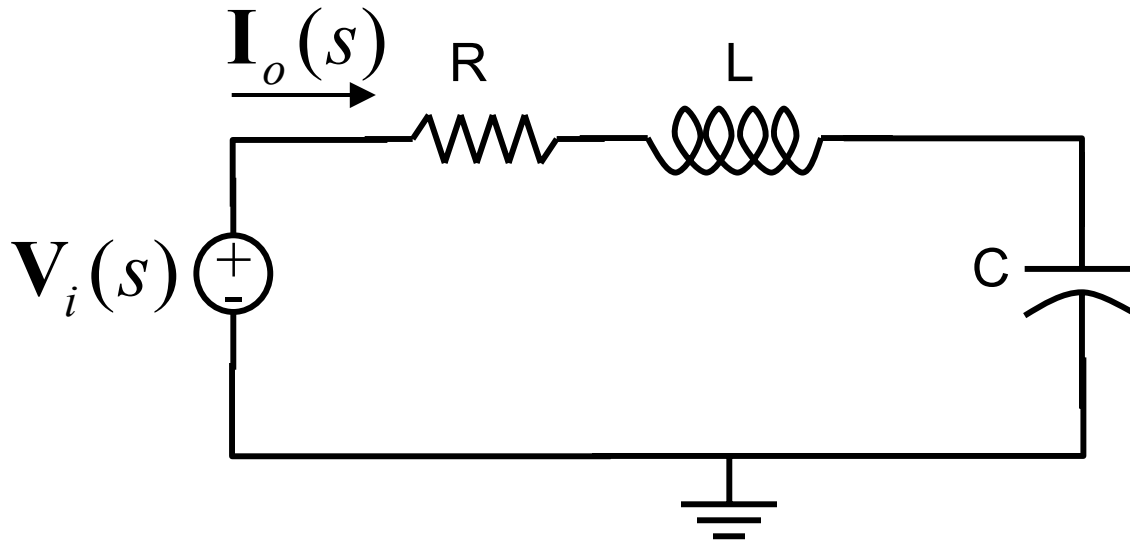

$$\mathbf{H}(s) = \frac{\mathbf{I}_o(s)}{\mathbf{V}_i(s)} = \mathbf{Y}(s) = \frac{1}{R + sL + \frac{1}{sC}} = \frac{\frac{1}{L}s}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

Note that $D(s)$ is second order $\rightarrow = \frac{N(s)}{s^2 + 2\zeta\omega_0 s + \omega_0^2}$

Resonant Circuits

$$\mathbf{H}(s) = \frac{N(s)}{s^2 + 2\zeta\omega_o s + \omega_o^2} = \frac{\frac{1}{L}s}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$\omega_o = \sqrt{\frac{1}{LC}} \quad \zeta = \frac{R}{2} \sqrt{\frac{C}{L}}$$

Remember : $\omega_r = \omega_o \sqrt{1 - 2\zeta^2}$.

$$p_{1,2} = -\zeta\omega_o \pm j\omega_o \sqrt{1 - \zeta^2}$$

How does the numerator affect the response $I_o(s)$ for a given input $V_i(s)$?

What is the resonant frequency, ω_r ?

Resonant Circuits


ω_r , the resonant frequency, is defined as the frequency at which $|H(j\omega)|$ is a maximum (or minimum).

$$\mathbf{H}(s) = \frac{\mathbf{I}_o(s)}{\mathbf{V}_i(s)} = \mathbf{Y}(s) = \frac{N(s)}{R + sL + \frac{1}{sC}} = \frac{N(j\omega)}{R + j\left(\omega L - \frac{1}{\omega C}\right)}$$

Maximum occurs when:

$$\omega L - \frac{1}{\omega C} = 0$$
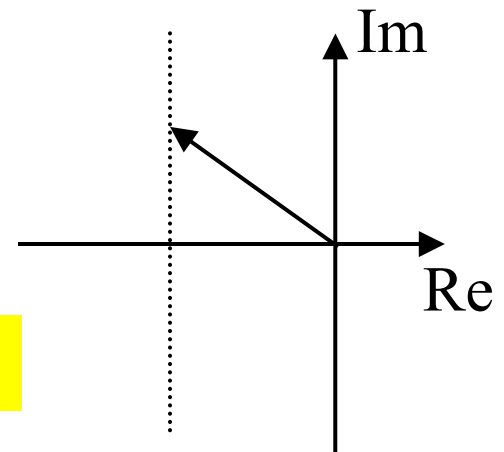
$$\omega_r = \sqrt{\frac{1}{LC}} \rightarrow \text{Same as } \omega_o \text{ in this case.}$$



Resonant Circuits

It is often difficult to find the exact frequency at which the maximum response occurs for a given circuit. There are two common approximations that work reasonably well for lightly damped circuits:

- The frequency at which the impedance $Z(s)=Y^{-1}(s)$ is real is taken to be the resonant frequency.
- The undamped natural frequency ω_o is taken to be the resonant frequency.

Recall: Quality Factor

The quality factor of a circuit is defined in terms of energy:

$$Q = 2\pi \frac{\text{total energy stored}}{\text{energy dissipated per cycle}}$$

The resonant Q is the Q at the resonant frequency.

$$Q_o = 2\pi \frac{\textit{maximum total energy stored}}{\text{energy dissipated per cycle}}$$

For the series resonant circuit:

$$Q_o = \frac{\omega_o L}{R} = \frac{1}{\omega_o RC} = \frac{1}{R} \sqrt{\frac{L}{C}}$$


Bandwidth

$$R = 2\Omega$$

$$C = 5\mu F$$

$$L = 2mH$$

Linear Frequency Scale Plot

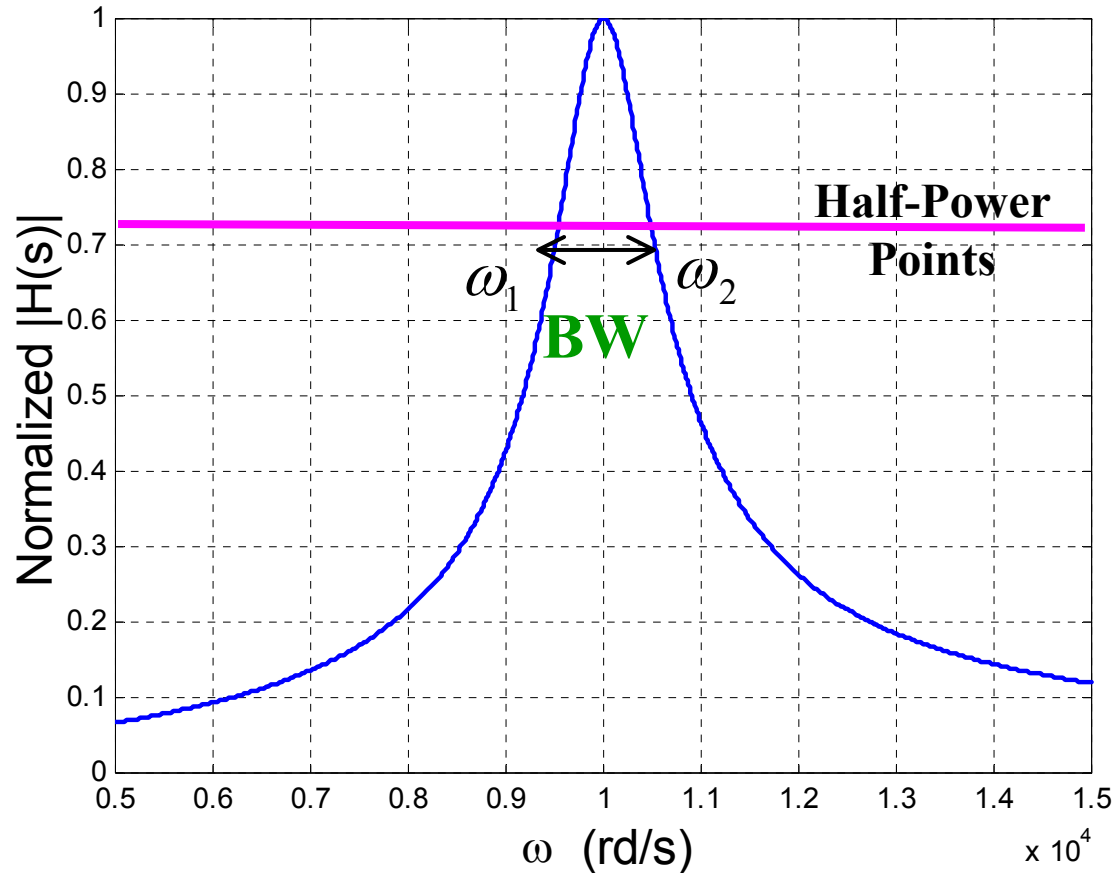

$$\frac{|H(j\omega_r)|}{\sqrt{2}}$$

$$BW = \omega_2 - \omega_1$$

Quality Factor and Bandwidth

$$\mathbf{H}(j\omega) = \frac{\mathbf{I}_o(\mathbf{s})}{\mathbf{V}_i(\mathbf{s})} = \mathbf{Y}(\mathbf{s}) = \frac{N(\mathbf{s})}{R + \mathbf{s}L + \frac{1}{\mathbf{s}C}} = \frac{N(j\omega)}{R + j\left(\omega L - \frac{1}{\omega C}\right)}$$

$$\mathbf{H}(j\omega_r) = \frac{N(j\omega)}{R}$$

$$Q_o = \frac{\omega_o L}{R} = \frac{1}{\omega_o RC} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$\frac{\mathbf{H}(j\omega)}{\mathbf{H}(j\omega_r)} = \frac{1}{1 + j\left(\omega \frac{L}{R} - \frac{1}{\omega RC}\right)} = \frac{1}{1 + jQ_o\left(\frac{\omega}{\omega_o} - \frac{\omega_o}{\omega}\right)}$$

Quality Factor and Bandwidth

$$\frac{|\mathbf{H}(j\omega)|}{|\mathbf{H}(j\omega_r)|} = \frac{1}{\sqrt{1 + Q_o^2 \left(\frac{\omega}{\omega_o} - \frac{\omega_o}{\omega} \right)^2}} = \frac{1}{\sqrt{2}}$$

$$Q_o^2 \left(\frac{\omega}{\omega_o} - \frac{\omega_o}{\omega} \right)^2 = 1 \quad \longrightarrow \quad Q_o \left(\frac{\omega}{\omega_o} - \frac{\omega_o}{\omega} \right) = \pm 1$$

$$\omega = \pm \frac{\omega_o}{2Q_o} \pm \omega_o \sqrt{\left(\frac{1}{2Q_o} \right)^2 + 1}$$

Quality Factor and Bandwidth

Taking only positive roots:

$$\omega_1 = \omega_o \left[\frac{-1}{2Q_o} + \sqrt{\left(\frac{1}{2Q_o}\right)^2 + 1} \right]$$

$$\omega_2 = \omega_o \left[\frac{+1}{2Q_o} + \sqrt{\left(\frac{1}{2Q_o}\right)^2 + 1} \right]$$

$$BW = \omega_2 - \omega_1 = \frac{\omega_o}{Q_o}$$

Quality Factor and Bandwidth


It can also be shown that: $\omega_1\omega_2 = (\omega_o)^2$

- The resonant frequency is the geometric mean of the two half power frequencies.
- The bandwidth is referred to as half-power or 3dB bandwidth.
- For a series RLC circuit, Q is inversely proportional to the bandwidth.

$$Q_o = \frac{\omega_o}{BW} = \frac{\omega_o L}{R} = \frac{1}{\omega_o RC} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

- A high Q series RLC circuit has a small resistance and a small bandwidth (circuit is very *selective*).


Example

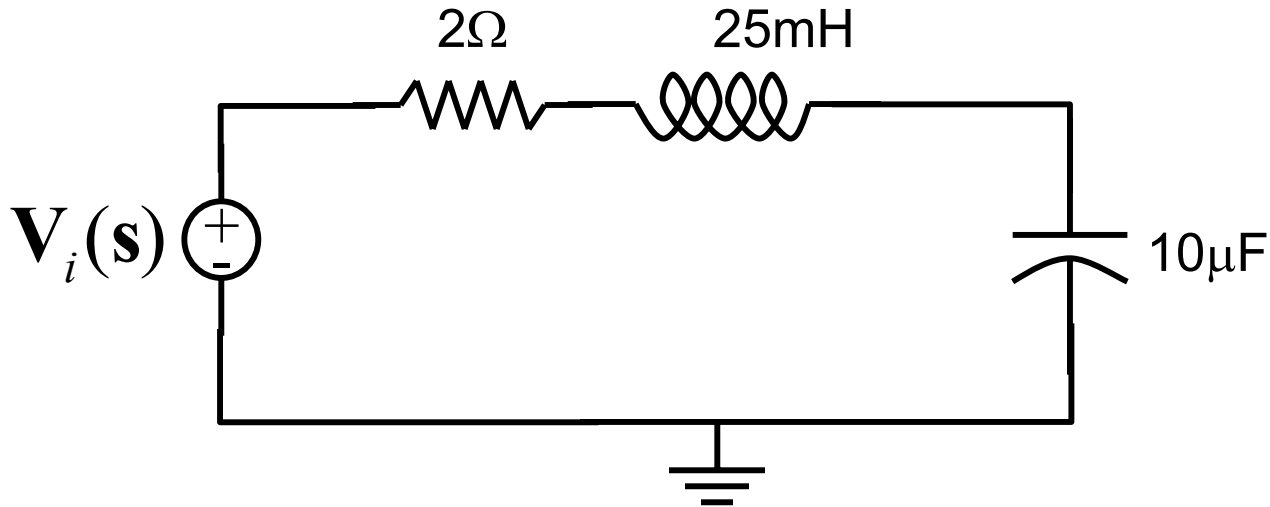

Resonant frequency $\omega_o = \sqrt{\frac{1}{LC}} = 2000 \text{ rad./sec.}$

$$Q_o = \frac{\omega_o L}{R} = 25 \quad BW = \omega_1 - \omega_2 = \frac{\omega_o}{Q_o} = 80 \text{ rad./sec.}$$

Example

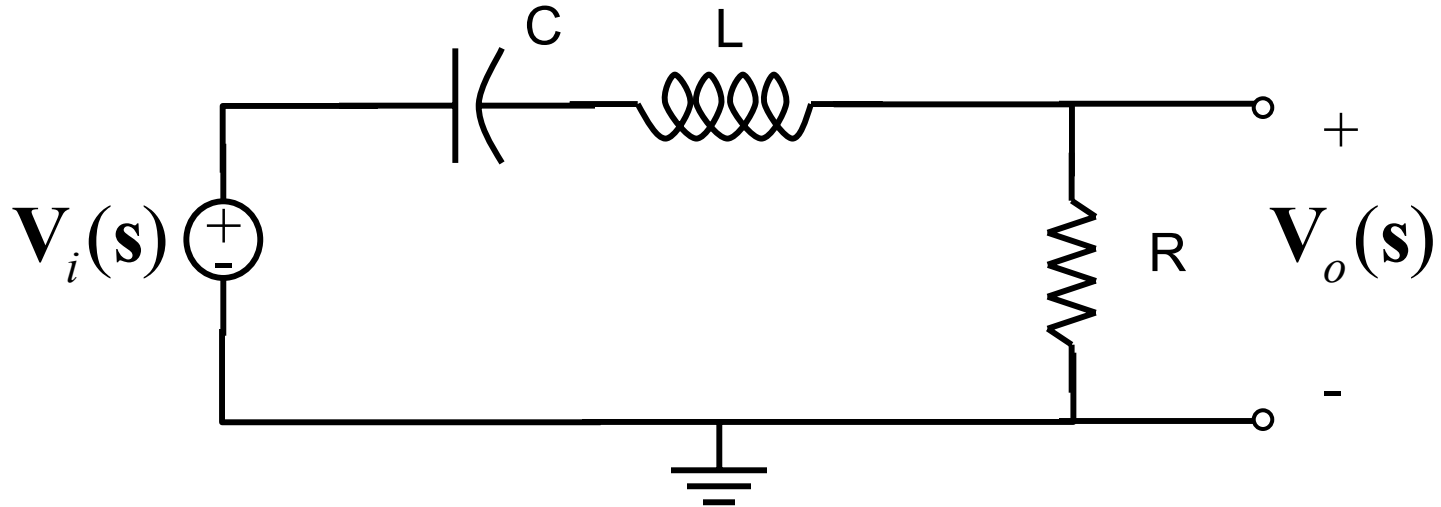

Find R , L and C such that the above circuit operates as a *band-pass* filter with a center frequency of 1000 rad./sec. and bandwidth of 100 rad./sec.

Example

$$\omega_o = \sqrt{\frac{1}{LC}} = 1000 \text{ rad./sec.} \quad \longrightarrow \quad LC = 10^{-6}$$

$$BW = \frac{\omega_o}{Q_o} = 100 \quad \longrightarrow \quad Q_o = \frac{\omega_o}{100} = 10$$

$$Q_o = \frac{\omega_o L}{R} \quad \longrightarrow \quad \frac{L}{R} = 10^{-2}$$

→ Two equations and three unknowns. Therefore we have multiple solutions.

Example

→ For example, choose:

$$C = 1\mu F$$

→ $L = \frac{10^{-6}}{C} = 1H$

→ $R = \frac{L}{10^{-2}} = 100\Omega$

→ The above is one set of parameters that satisfy the design requirements. We can find others.