

ECSE 210: Circuit Analysis

Lecture #28:

Passive Filter Networks



Passive Filter Networks

Filters are designed to *pass* signals in a given frequency range and *reject* or *attenuate* signals outside that range.


- “**Pass**” frequency range is called “passband”.
- “**Reject**” frequency range is called the “rejection band”
- There are four common passive filter types:
 1. **Low-pass**: designed to pass low frequencies and reject high frequencies.
 2. **High-pass**: designed to pass high frequencies and reject low frequencies.
 3. **Band-pass**: designed to pass frequencies within a specific band and reject all others.
 4. **Band-reject**: designed to reject frequencies within a specific band and reject all others.

Low-Pass Filter

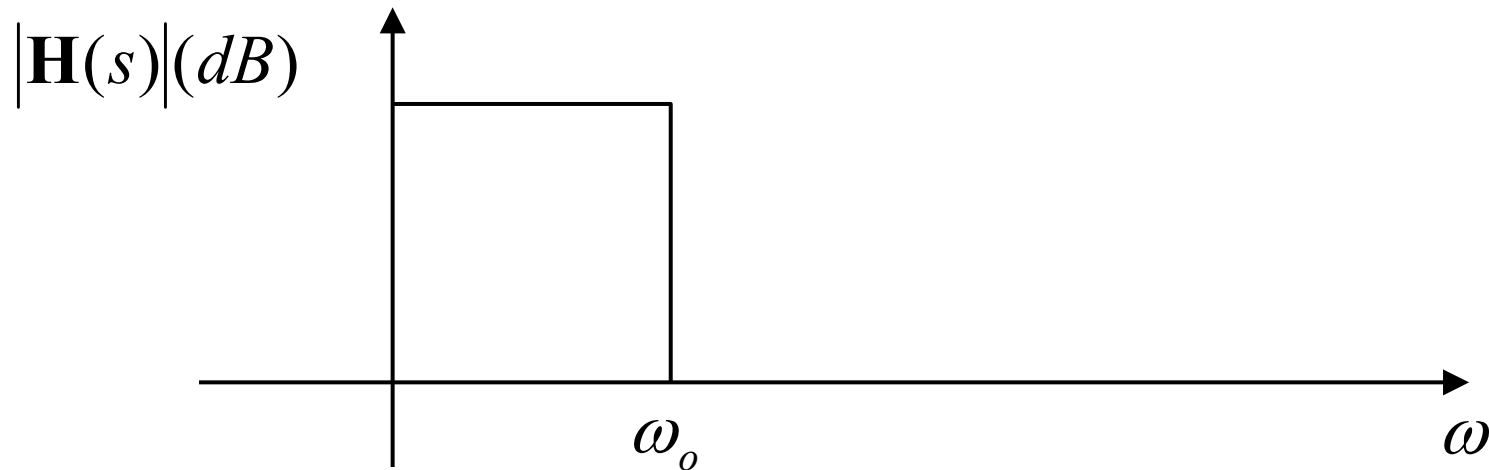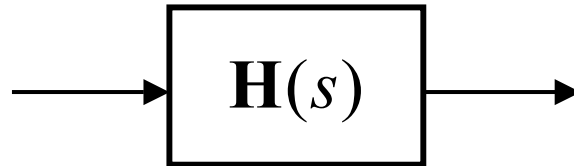Ideal response: Pass all frequencies up to a cut-off ω_o , but reject all frequencies above it.



Low Pass Filter Example

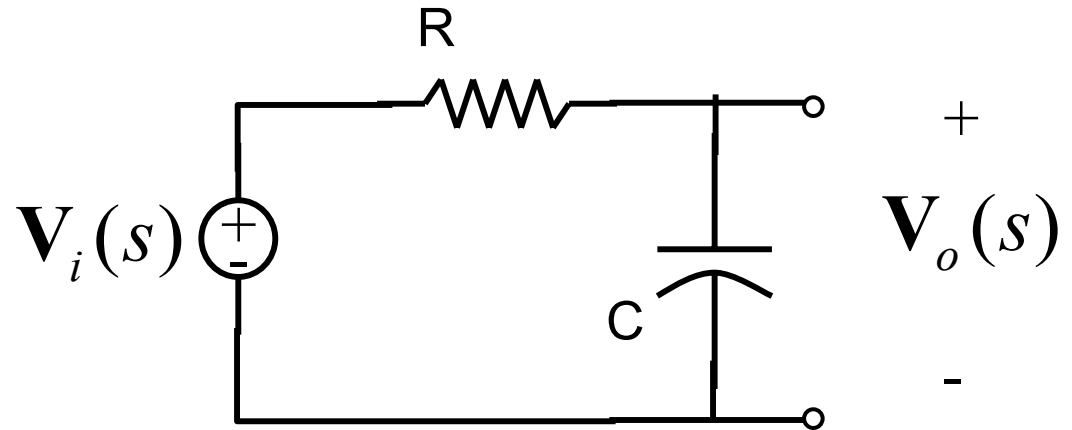

$$\mathbf{H}(s) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{1/sC}{R + 1/sC} = \frac{1}{1 + sRC} = \frac{\omega_o}{s + \omega_o}$$


$$\omega_o = \frac{1}{RC}$$

Circuit has a single real pole: $p = -\omega_o$

→ **First order filter.**


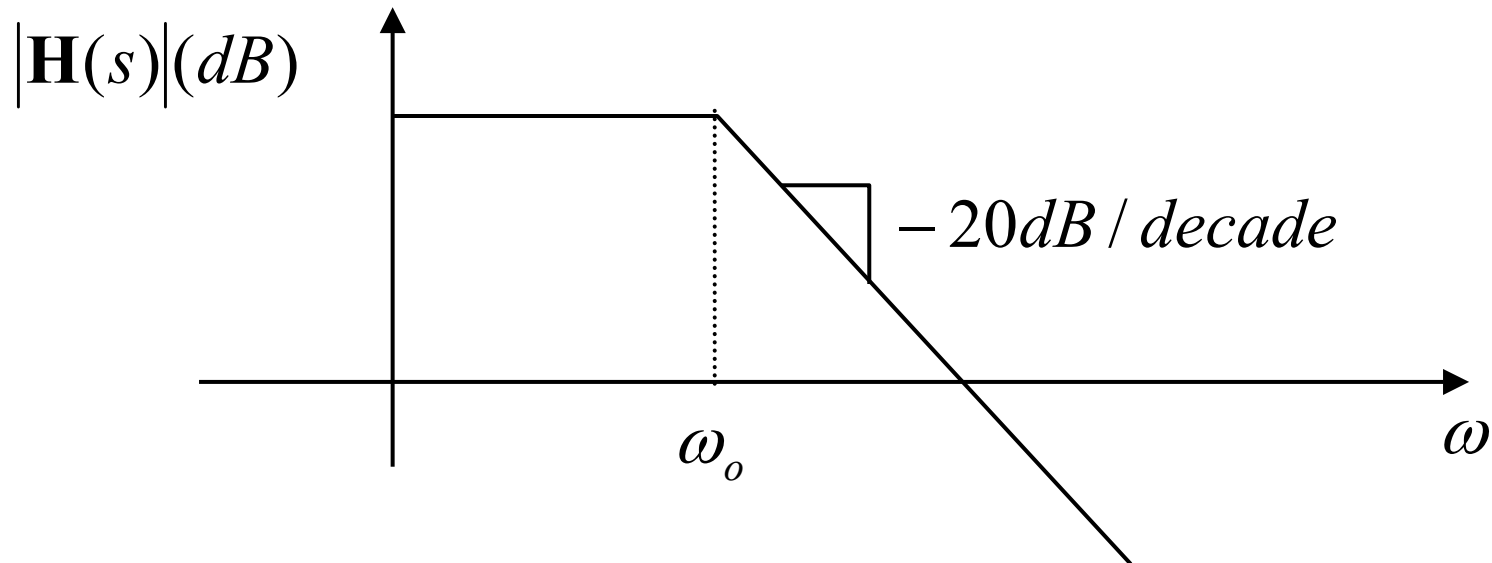
Example Low-Pass Filter

→ First order filter: $\mathbf{H}(s) = \frac{\omega_o}{s + \omega_o}$




High-Pass Filter

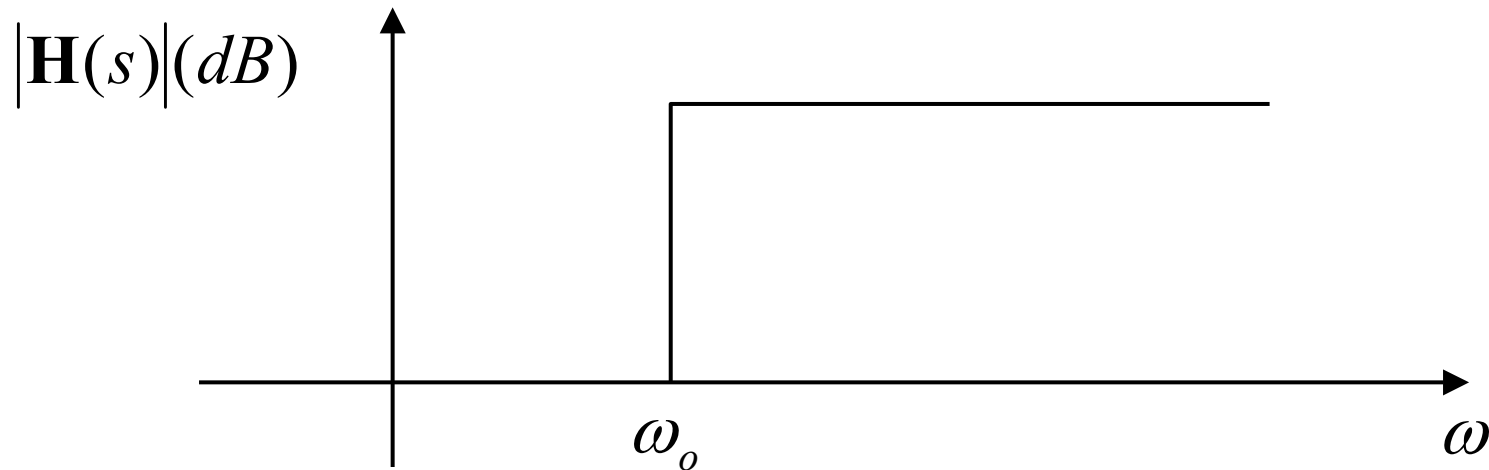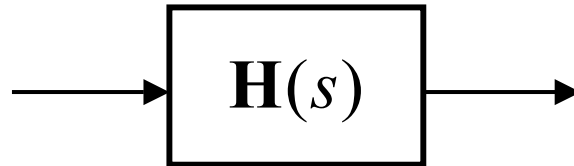Ideal response: Pass all frequencies above a cut-off ω_o , but reject all frequencies below it.



High-Pass Filter Example

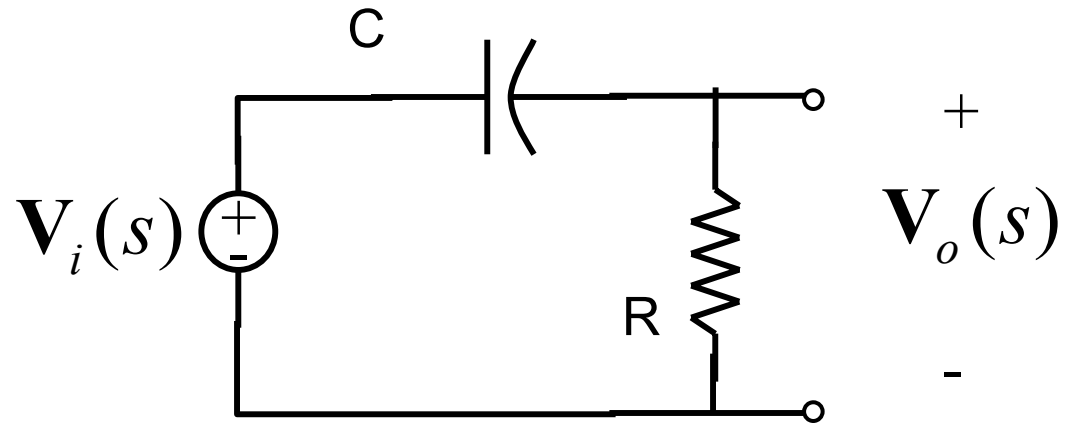

$$\mathbf{H}(s) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{R}{R + \frac{1}{sC}} = \frac{sRC}{1 + sRC} = \frac{s}{s + \omega_o} \quad \omega_o = \frac{1}{RC}$$


Circuit has a single real pole $p = -\omega_o$
and a single zero at the origin

→ **First order filter.**

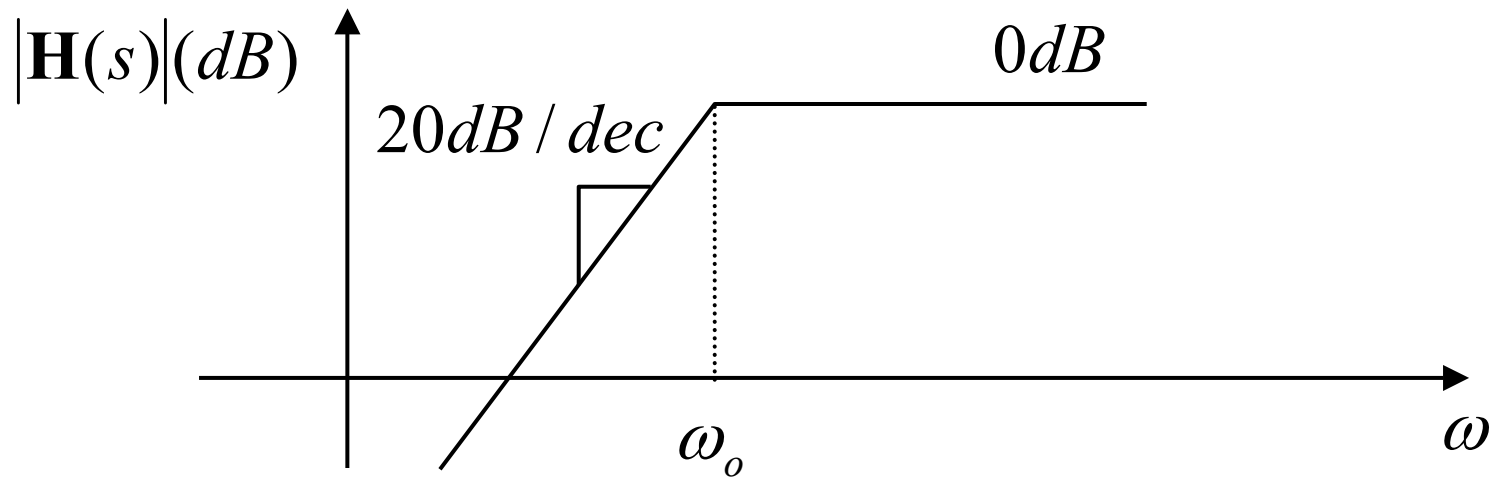Example Low-Pass Filter



→ First order filter.

$$\mathbf{H}(s) = \frac{s}{s + \omega_o}$$




Band-Pass Filter

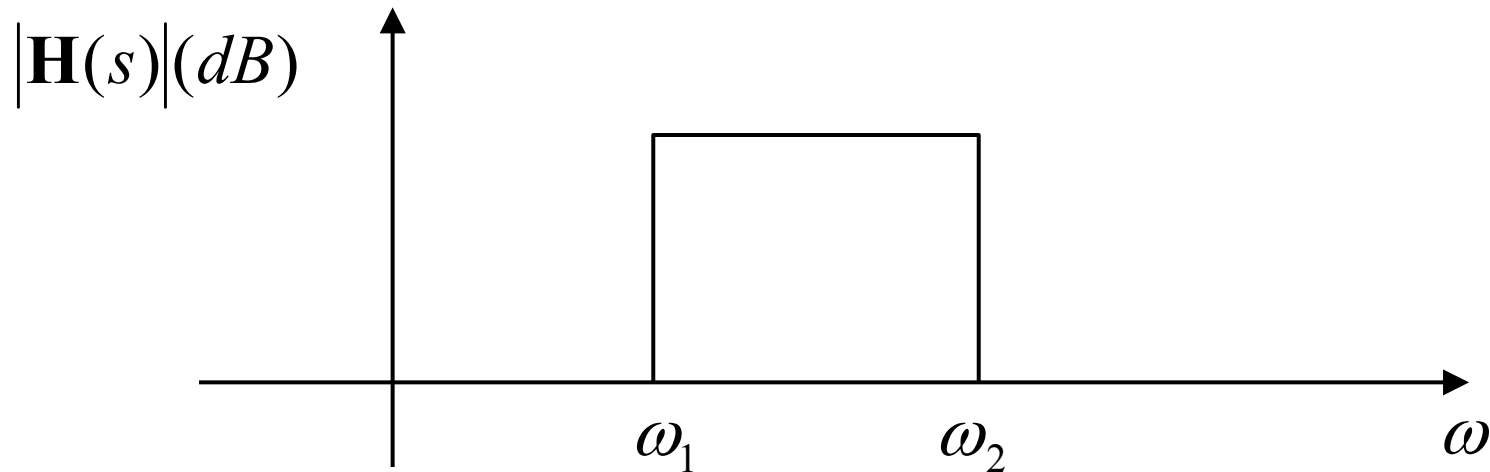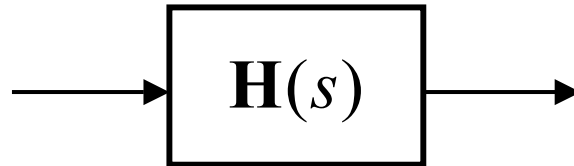Ideal response: Pass all frequencies within a specific band (frequency range), but reject all other frequencies.



Band-Pass Filter Example

Series Resonant circuit

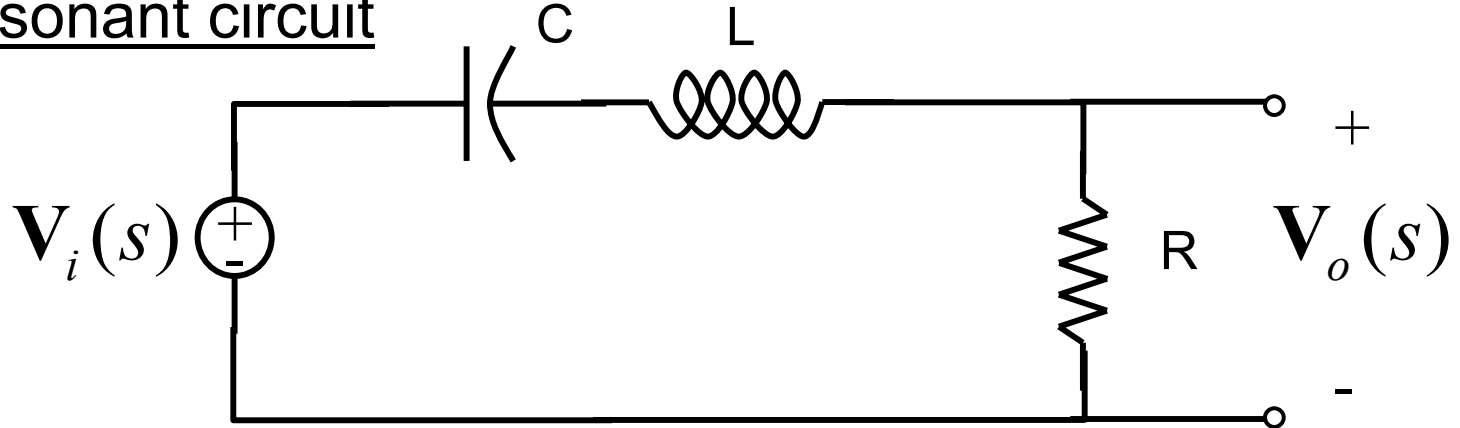

$$\mathbf{H}(s) = \frac{V_o}{V_i} = \frac{R}{R + sL + \frac{1}{sC}} = \frac{sRC}{1 + RCs + LCs^2} = \frac{j\omega RC}{1 - \omega^2 LC + j\omega RC}$$

$$|\mathbf{H}(s)| = \frac{\omega RC}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}}$$

Band-Pass Filter Example

$$|\mathbf{H}(s)| = \frac{\omega RC}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}}$$

$$\omega \rightarrow 0 \quad \longrightarrow \quad |\mathbf{H}(s)| \rightarrow 0$$

$$\omega \rightarrow \infty \quad \longrightarrow \quad |\mathbf{H}(s)| \rightarrow 0$$

Response is Maximum at resonant frequency $\omega_o = \frac{1}{\sqrt{LC}}$

The pass-band is between the two half-power frequencies.

Band-Pass Filter Example

Half-power frequencies:

$$|\mathbf{H}(s)| = \frac{\omega RC}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}} = \frac{1}{\sqrt{2}}$$

$$\frac{(\omega RC)^2}{(1 - \omega^2 LC)^2 + (\omega RC)^2} = \frac{1}{2} \quad \Rightarrow \quad 2(\omega RC)^2 = (1 - \omega^2 LC)^2 + (\omega RC)^2$$

$$\Rightarrow (1 - \omega^2 LC)^2 = (\omega RC)^2 \quad \Rightarrow \quad 1 - \omega^2 LC = \pm \omega RC$$

Band-Pass Filter Example

Half-power frequencies:

$$1 - \omega^2 LC = \pm \omega RC \quad \longrightarrow \quad \omega^2 \pm \frac{R}{L} \omega - \omega_o^2 = 0$$

Solving for two positive roots results in half-power or cut-off frequencies:



$$\omega_1 = \frac{-\left(\frac{R}{L}\right) + \sqrt{\left(\frac{R}{L}\right)^2 + 4\omega_o^2}}{2}$$

$$\omega_2 = \frac{+\left(\frac{R}{L}\right) + \sqrt{\left(\frac{R}{L}\right)^2 + 4\omega_o^2}}{2}$$


$$BW = \omega_2 - \omega_1 = \frac{R}{L}$$

Band-Reject Filter

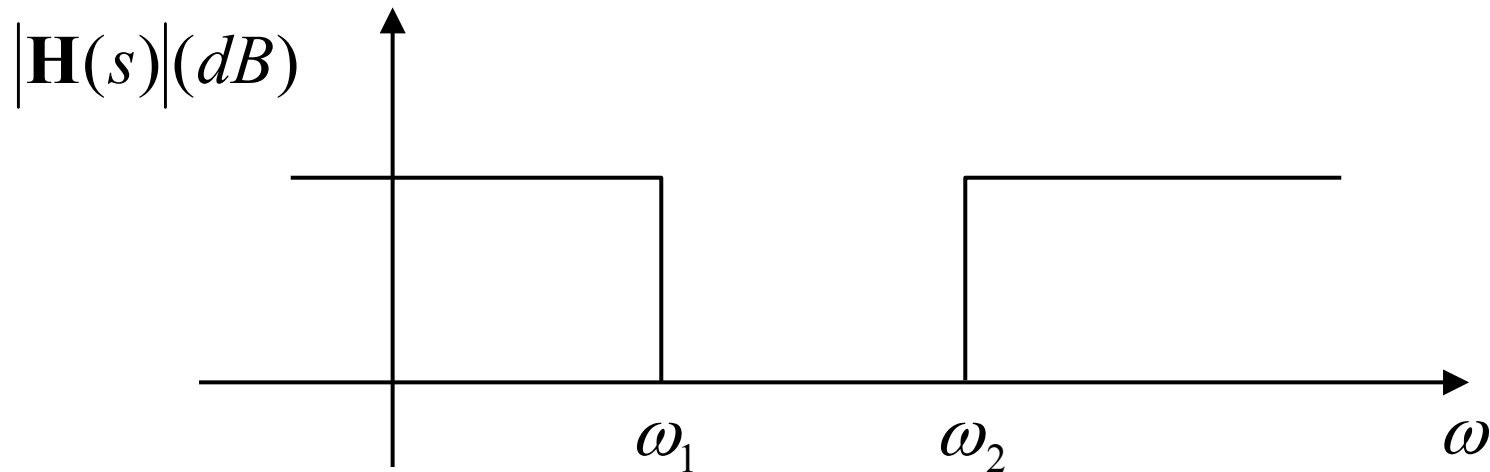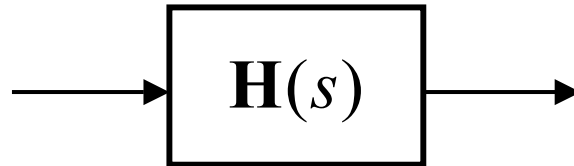Ideal response: Rejects all frequencies within a specific band (frequency range), but passes all other frequencies.



Band-Reject Filter Example

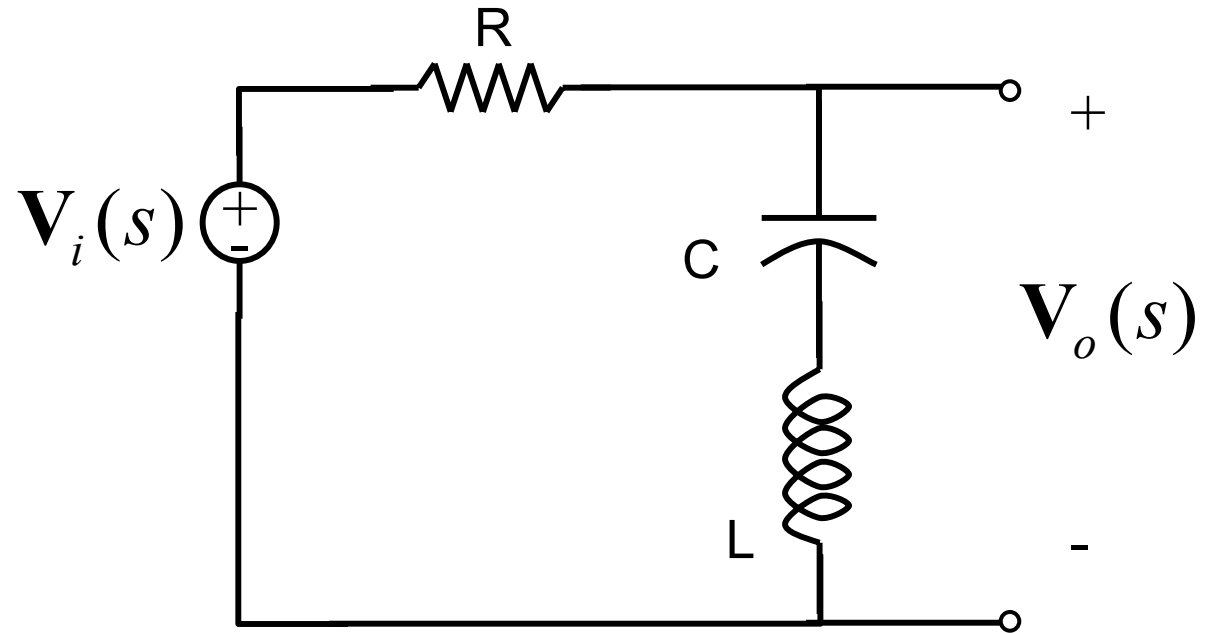

$$\mathbf{H}(s) = \frac{V_o}{V_i} = \frac{sL + \frac{1}{sC}}{R + sL + \frac{1}{sC}} = \frac{s^2LC + 1}{1 + RCs + LCs^2} = \frac{1 - \omega^2LC}{1 - \omega^2LC + j\omega RC}$$

$$|\mathbf{H}(s)| = \frac{1 - \omega^2LC}{\sqrt{(1 - \omega^2LC)^2 + (\omega RC)^2}}$$

Band-Reject Filter Example

$$|\mathbf{H}(s)| = \frac{|1 - \omega^2 LC|}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}}$$

$$\omega \rightarrow 0 \quad \Rightarrow \quad |\mathbf{H}(s)| \rightarrow 1$$

$$\omega \rightarrow \infty \quad \Rightarrow \quad |\mathbf{H}(s)| \rightarrow 1$$

$$\text{At } \omega_o = \frac{1}{\sqrt{LC}} \quad \Rightarrow \quad |\mathbf{H}(s)| = 0$$

Center frequency = resonant frequency

The rejection band is between the two half-power frequencies.

Band-Pass Filter Example

Half-power frequencies:

$$|\mathbf{H}(s)| = \frac{|1 - \omega^2 LC|}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}} = \frac{1}{\sqrt{2}}$$

$$\Rightarrow 2(1 - \omega^2 LC)^2 = (1 - \omega^2 LC)^2 + (\omega RC)^2$$

$$\Rightarrow 1 - \omega^2 LC = \pm \omega RC \quad \Rightarrow \quad \omega^2 \pm \frac{R}{L} \omega - \omega_o^2 = 0$$

Band-Reject Filter Example

Half-power frequencies:

$$\omega^2 \pm \frac{R}{L}\omega - \omega_o^2 = 0$$


Solving for two positive roots results in half-power or cut-off frequencies:

$$\omega_1 = \frac{-\left(\frac{R}{L}\right) + \sqrt{\left(\frac{R}{L}\right)^2 + 4\omega_o^2}}{2}$$

$$\omega_2 = \frac{+\left(\frac{R}{L}\right) + \sqrt{\left(\frac{R}{L}\right)^2 + 4\omega_o^2}}{2}$$

$$BW = \omega_2 - \omega_1 = \frac{R}{L}$$

LOADING

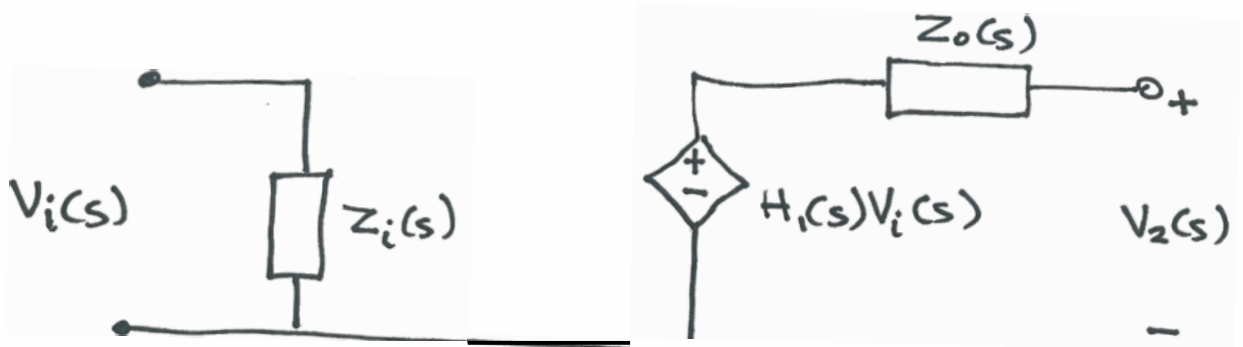


A Model of the first filter stage.

- No current in the output impedance

- $$V_2(s) = H_1(s) V_i(s)$$

↑
TRANSFER
FUNCTION

LOADING FOR A CASCADE

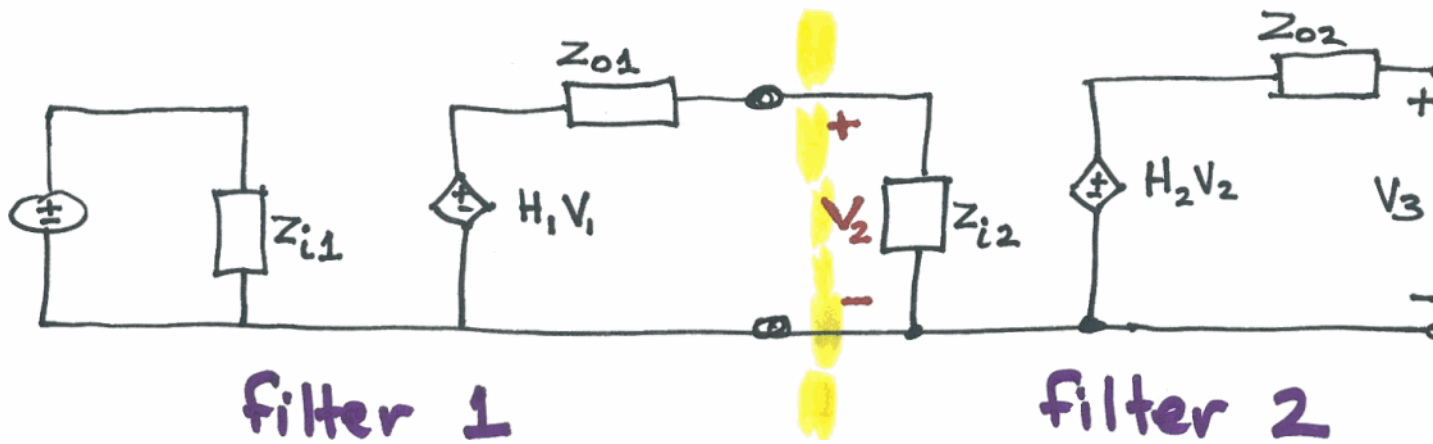

- $V_3 = H_2 V_2$
- $V_2 = \frac{Z_{i2}}{Z_{o1} + Z_{i2}} H_1 V_1$ voltage divider
- Connecting second stage to first stage has changed the output V_2 of the first stage.
- The second stage is loading the first stage.
- Now $V_3 = H_2 \frac{Z_{i2}}{Z_{o1} + Z_{i2}} H_1 V_1$
- or $H = \frac{V_3}{V_1} = H_2 \frac{Z_{i2}}{Z_{o1} + Z_{i2}} H_1$
- $H = H_1 H_2$ if
 - ① $Z_{i2} = \infty$ (very large)
 - or ② $Z_{o1} = 0$ (very small)

➔ MINIMAL LOADING