


ECSE 210: Circuit Analysis

Lecture #30:

Two-Port Networks

Two-Port Impedance Parameters

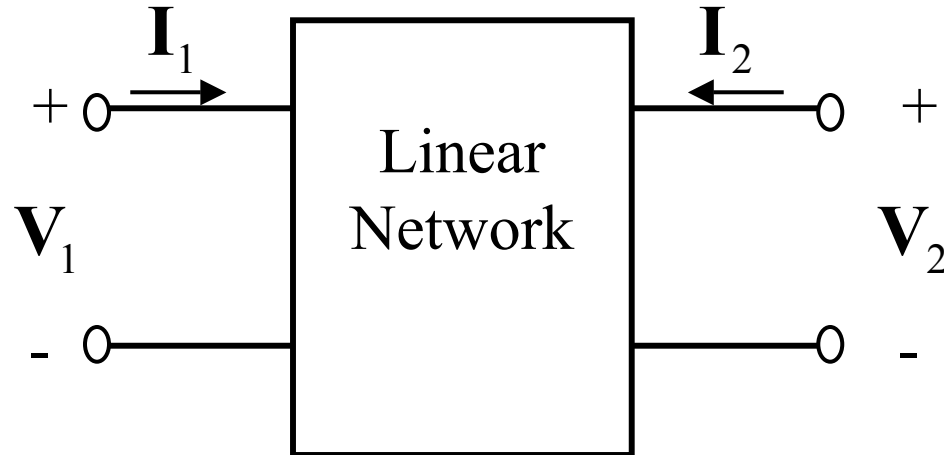→ Commonly referred to as the *Z-parameters*.



→ Note the voltage polarities, and current directions.

→ Using the principle of superposition we get:

$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$

Z-Parameters

$$\begin{aligned} \mathbf{V}_1 &= z_{11}\mathbf{I}_1 + z_{12}\mathbf{I}_2 \\ \mathbf{V}_2 &= z_{21}\mathbf{I}_1 + z_{22}\mathbf{I}_2 \end{aligned} \quad \longrightarrow \quad \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix}$$

- Two equations describe two-port operation.
- z_{ij} are **complex** constants of proportionality with units of Ohms (Ω).
- Once z_{11} , z_{12} , z_{21} , z_{22} are known, the input/output operation of the two-port network is **completely** defined.
- z_{ij} are the **impedance parameters** or Z-parameters.
- The Z-parameter matrix is:

$$\mathbf{Z} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix}$$

Z-Parameters

$$\begin{aligned} \mathbf{V}_1 &= z_{11}\mathbf{I}_1 + z_{12}\mathbf{I}_2 \\ \mathbf{V}_2 &= z_{21}\mathbf{I}_1 + z_{22}\mathbf{I}_2 \end{aligned} \quad \rightarrow \quad \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix}$$


$$\mathbf{I}_2 = 0 \quad \rightarrow \quad \mathbf{V}_1 = z_{11}\mathbf{I}_1 \quad \rightarrow \quad z_{11} = \left. \frac{\mathbf{V}_1}{\mathbf{I}_1} \right|_{\mathbf{I}_2=0}$$

$$\mathbf{I}_2 = 0 \quad \rightarrow \quad \mathbf{V}_2 = z_{21}\mathbf{I}_1 \quad \rightarrow \quad z_{21} = \left. \frac{\mathbf{V}_2}{\mathbf{I}_1} \right|_{\mathbf{I}_2=0}$$

$$\mathbf{I}_1 = 0 \quad \rightarrow \quad \mathbf{V}_1 = z_{12}\mathbf{I}_2 \quad \rightarrow \quad z_{12} = \left. \frac{\mathbf{V}_1}{\mathbf{I}_2} \right|_{\mathbf{I}_1=0}$$

$$\mathbf{I}_1 = 0 \quad \rightarrow \quad \mathbf{V}_2 = z_{22}\mathbf{I}_2 \quad \rightarrow \quad z_{22} = \left. \frac{\mathbf{V}_2}{\mathbf{I}_2} \right|_{\mathbf{I}_1=0}$$

Z-Parameters vs. Y-Parameters

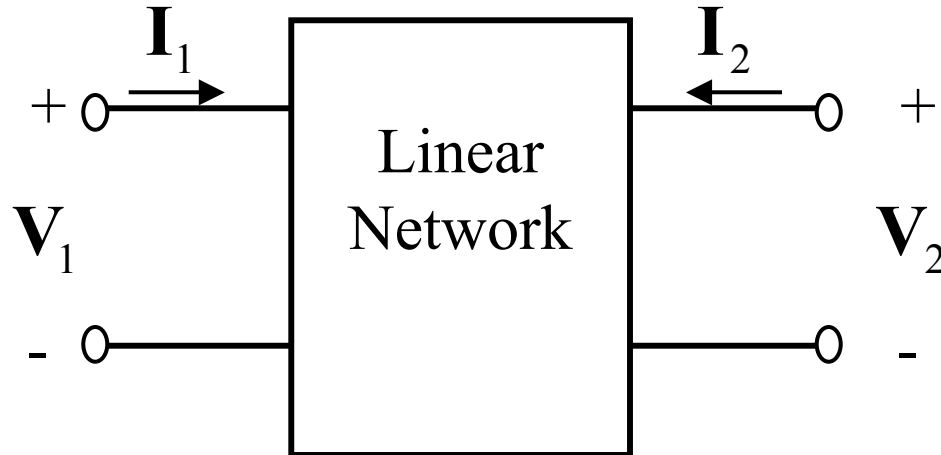

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$


$$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}^{-1}$$

$$\mathbf{Z} = \mathbf{Y}^{-1}$$

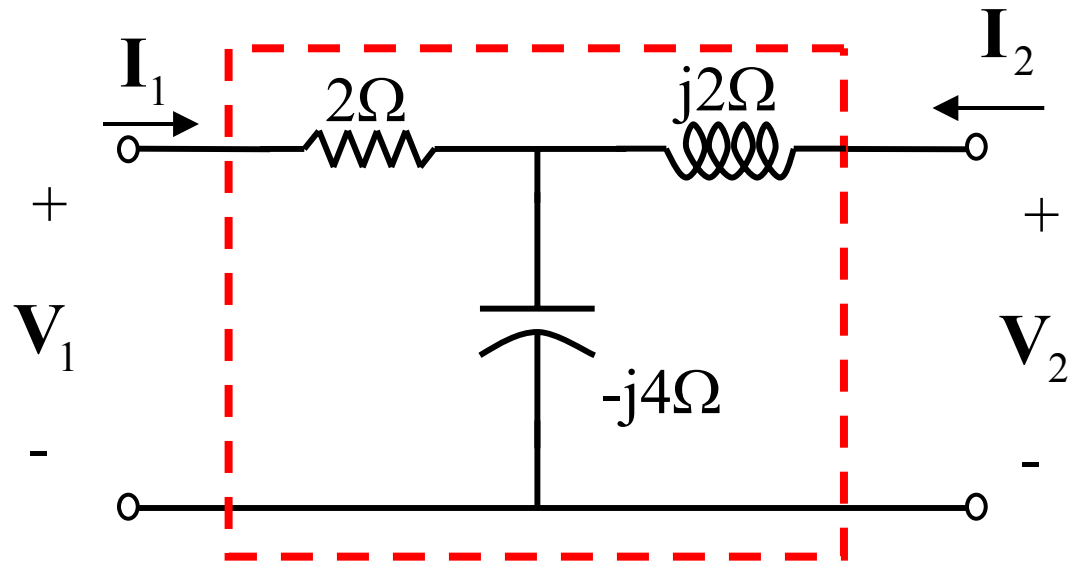Example

→ Z-parameters can be found “experimentally”.


$$\begin{aligned} \mathbf{V}_1 &= z_{11}\mathbf{I}_1 + z_{12}\mathbf{I}_2 \\ \mathbf{V}_2 &= z_{21}\mathbf{I}_1 + z_{22}\mathbf{I}_2 \end{aligned} \quad \longrightarrow \quad \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix}$$



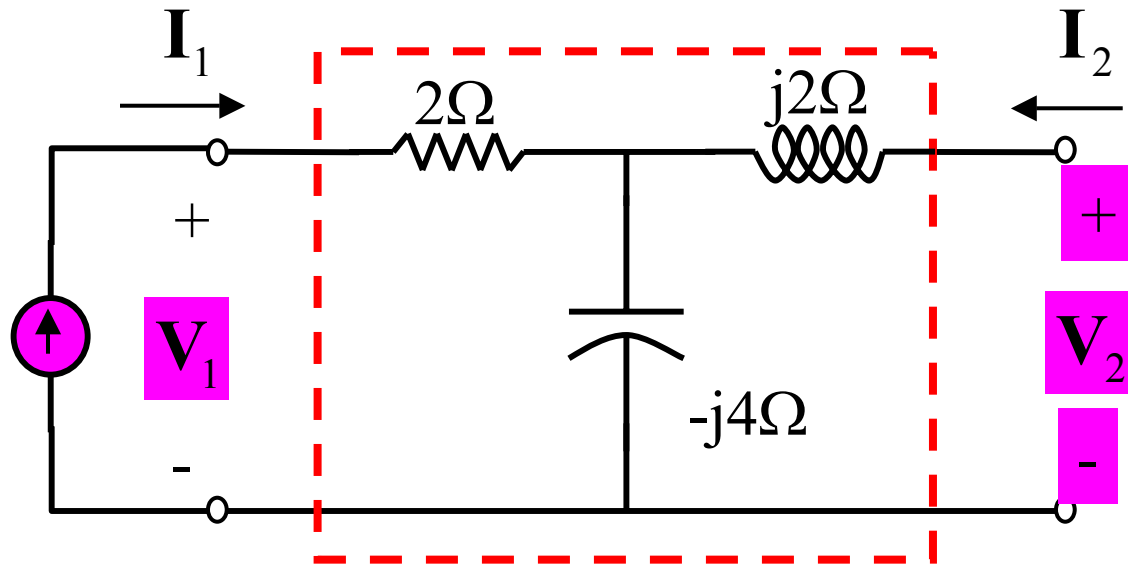Example

→ Open circuit port 2:


$$\begin{aligned} \mathbf{V}_1 &= z_{11}\mathbf{I}_1 + z_{12}\mathbf{I}_2 \\ \mathbf{V}_2 &= z_{21}\mathbf{I}_1 + z_{22}\mathbf{I}_2 \end{aligned} \quad \Rightarrow \quad \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix}$$



$$\mathbf{V}_1 = z_{11}\mathbf{I}_1$$

$$\mathbf{V}_2 = z_{21}\mathbf{I}_1$$

Example

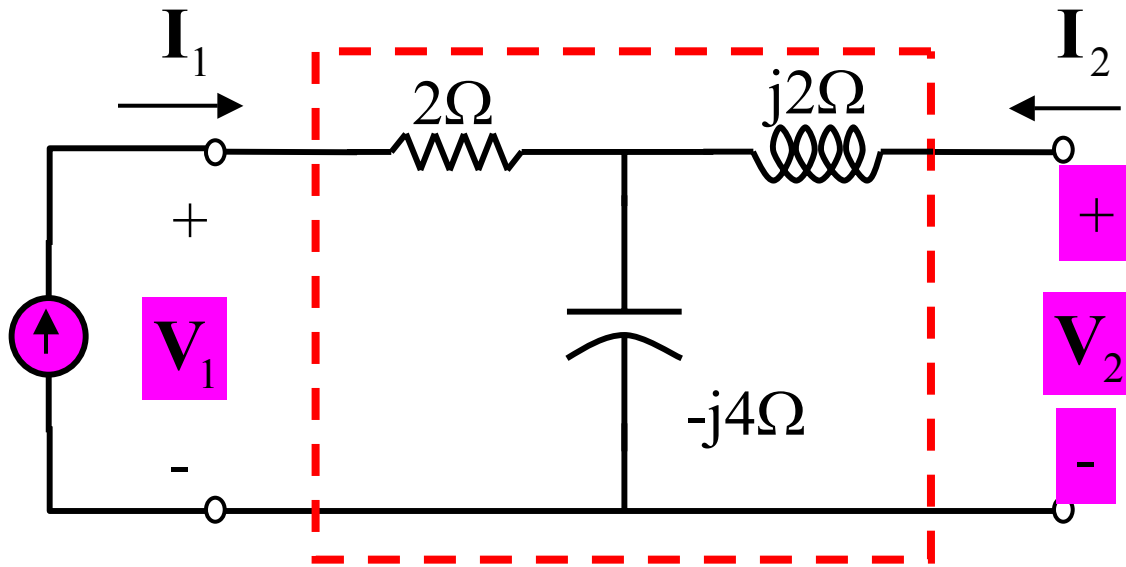

$$V_1 = (2 - 4j)I_1$$


$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = 2 - 4j\Omega$$

$$V_2 = \frac{-4j}{2 - 4j} V_1 = \frac{-4j}{2 - 4j} (2 - 4j)I_1$$

$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = -4j\Omega$$

Example

→ Open circuit port 1:

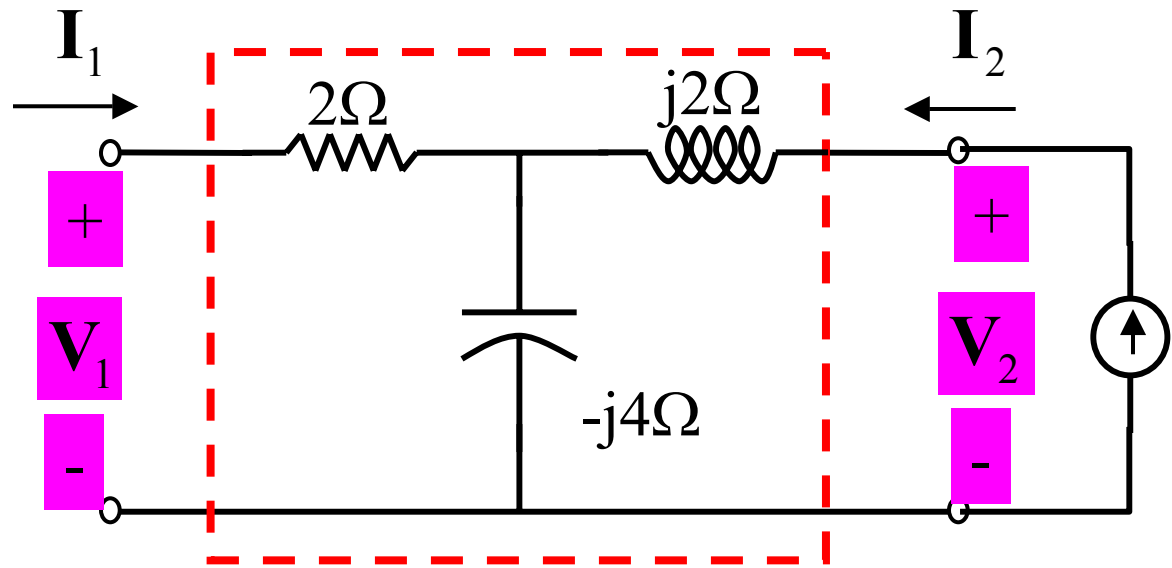


$$\mathbf{V}_2 = (2j - 4j)\mathbf{I}_2 = -2j\mathbf{I}_2 \quad \mathbf{V}_1 = \frac{-4j}{2j - 4j} \mathbf{V}_2 = \frac{-4j}{-2j} (-2j)\mathbf{I}_2$$

$$z_{22} = \left. \frac{\mathbf{V}_2}{\mathbf{I}_2} \right|_{\mathbf{I}_1=0} = -2j\Omega$$


$$z_{12} = \left. \frac{\mathbf{V}_1}{\mathbf{I}_2} \right|_{\mathbf{I}_1=0} = -4j\Omega$$

Example

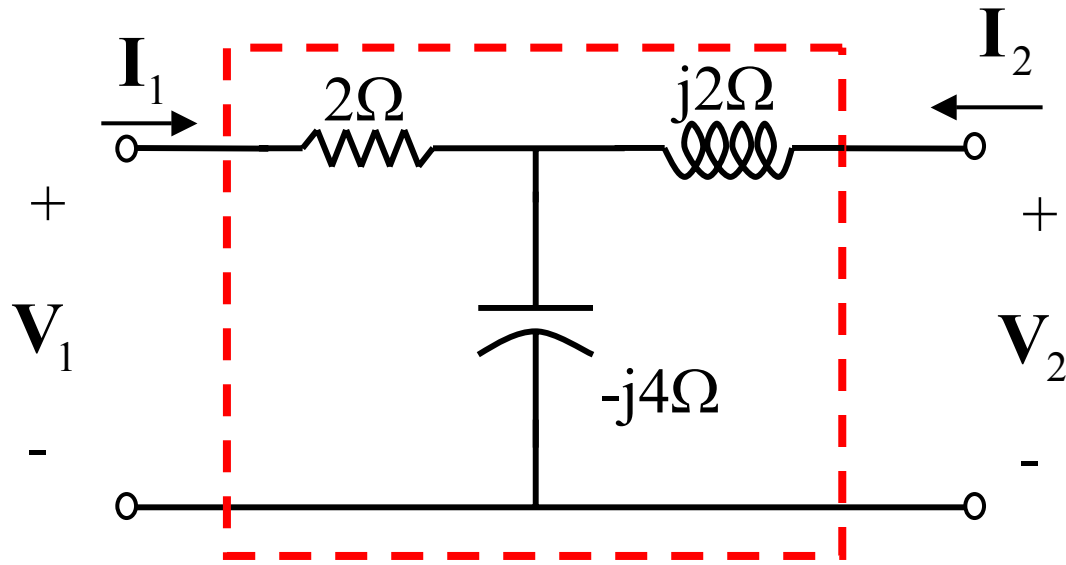

$$\mathbf{V}_1 = (2 - 4j)\mathbf{I}_1 - 4j\mathbf{I}_2$$

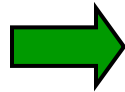
$$\mathbf{V}_2 = -4j\mathbf{I}_1 - 2j\mathbf{I}_2$$



$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} 2 - 4j & -4j \\ -4j & -2j \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix}$$

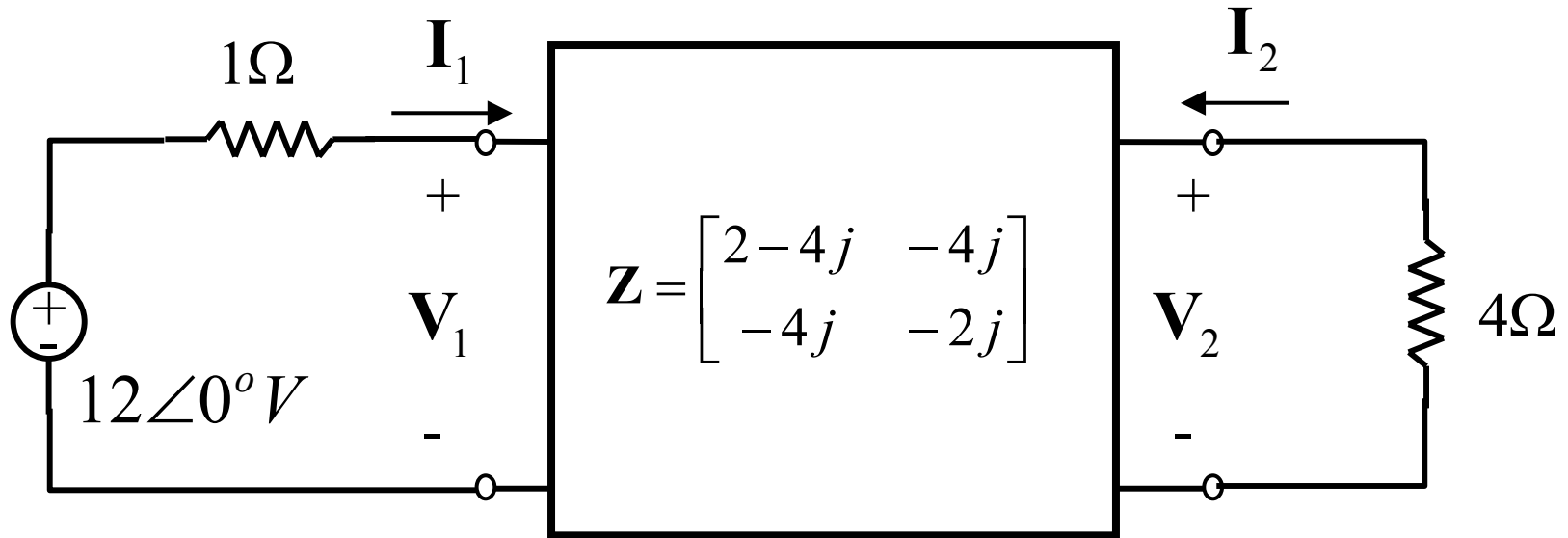Example 2

Find the current through the 4Ω resistor.



$$\left. \begin{aligned} V_1 &= 12\angle 0 - (1\Omega)I_1 \\ V_2 &= -(4\Omega)I_2 \end{aligned} \right\}$$

Boundary conditions
due to terminations.

Example 2

Z-parameter equations:

$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} 2 - 4j & -4j \\ -4j & -2j \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} \quad \Rightarrow \quad \begin{aligned} \mathbf{V}_1 &= (2 - 4j)\mathbf{I}_1 - 4j\mathbf{I}_2 \\ \mathbf{V}_2 &= -4j\mathbf{I}_1 - 2j\mathbf{I}_2 \end{aligned}$$


Boundary conditions:

$$\mathbf{V}_1 = 12\angle 0^\circ - (1\Omega)\mathbf{I}_1 \quad \mathbf{V}_2 = -(4\Omega)\mathbf{I}_2 \quad (\text{Eliminates } \mathbf{V}_1 \text{ and } \mathbf{V}_2)$$

$$\Rightarrow \begin{cases} (3 - 4j)\mathbf{I}_1 - 4j\mathbf{I}_2 = 12\angle 0^\circ \\ -4j\mathbf{I}_1 + (4 - 2j)\mathbf{I}_2 = 0 \end{cases} \quad \Rightarrow \quad \mathbf{I}_2 = 1.61\angle 137.7^\circ \text{ A}$$


Example 3

Find the impedance (Z) parameters of the circuit below:

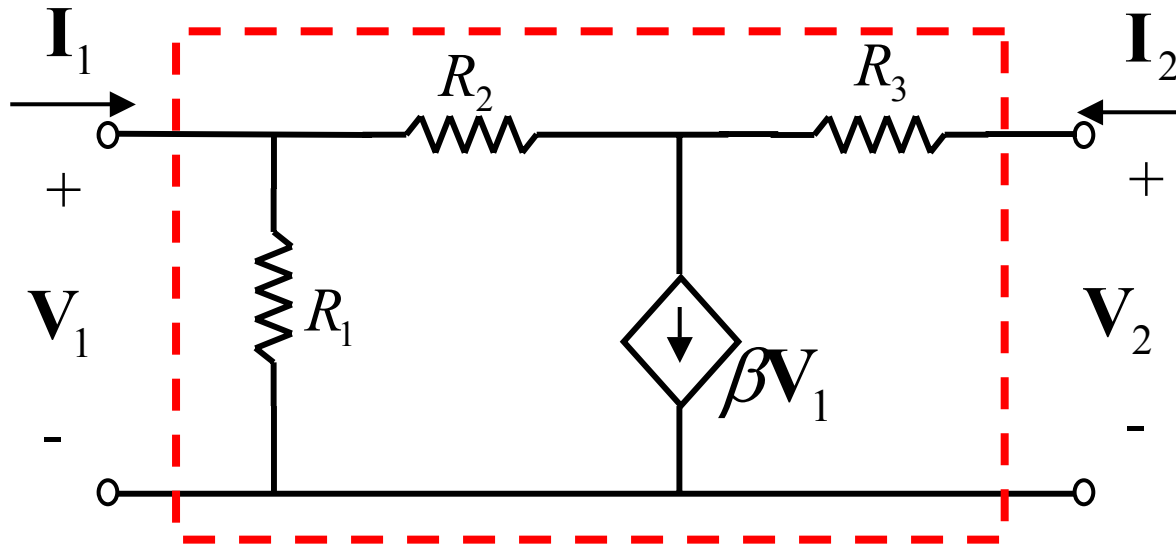

Example 3

Open-circuit port 2:

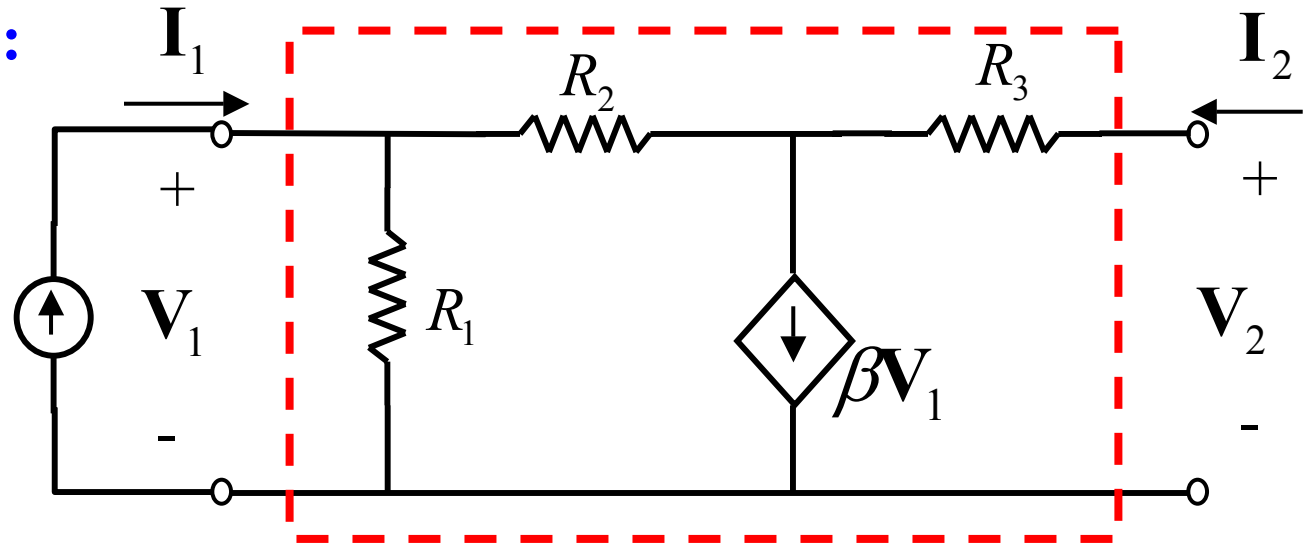


$$\mathbf{I}_1 = \frac{\mathbf{V}_1}{R_1} + \beta \mathbf{V}_1 \quad \rightarrow \quad z_{11} = \left. \frac{\mathbf{V}_1}{\mathbf{I}_1} \right|_{\mathbf{I}_2=0} = \frac{R_1}{1 + \beta R_1} \Omega \quad \textcircled{1}$$

$$\mathbf{V}_2 = \mathbf{V}_1 - R_2 (\beta \mathbf{V}_1) = (1 - \beta R_2) \frac{R_1}{1 + \beta R_1} \mathbf{I}_1$$

$$z_{21} = \left. \frac{\mathbf{V}_2}{\mathbf{I}_1} \right|_{\mathbf{I}_2=0} = \frac{R_1 (1 - \beta R_2)}{1 + \beta R_1} \Omega \quad \textcircled{2}$$

Example 3

Open-circuit port 1:

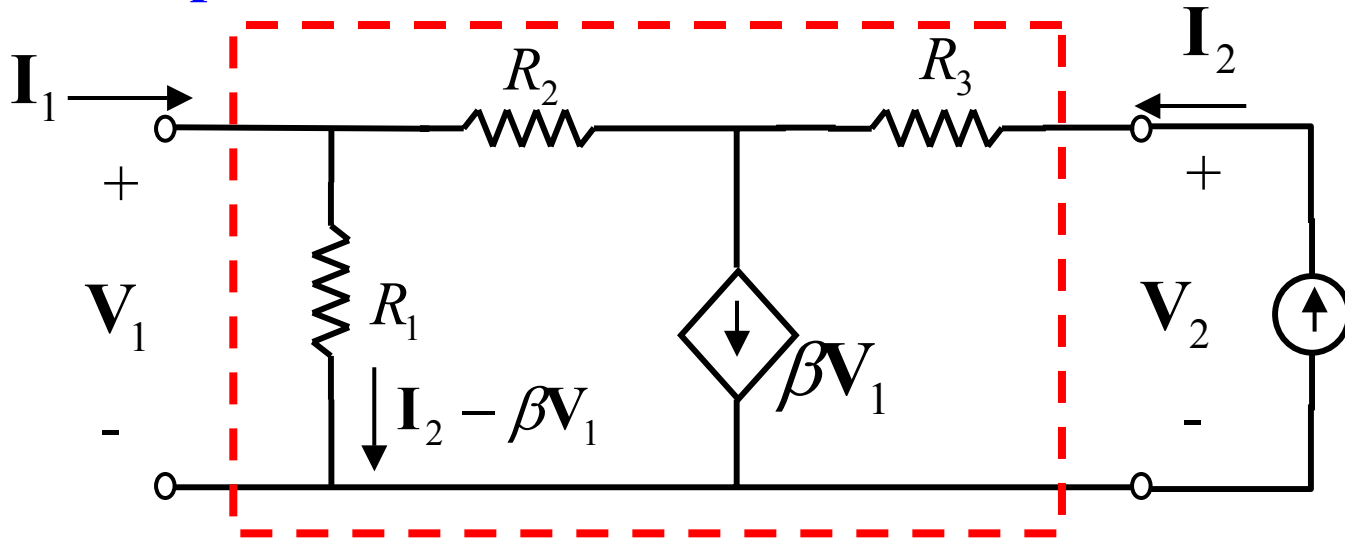


$$V_2 = R_3 I_2 + (R_1 + R_2)(I_2 - \beta V_1) = (R_1 + R_2 + R_3)I_2 - (R_1 + R_2)\beta V_1$$

$$V_2 = (R_1 + R_2 + R_3)I_2 - (R_1 + R_2)\beta \frac{R_1}{R_1 + R_2} (V_2 - I_2 R_3)$$

$$V_2(1 + \beta R_1) = (R_1 + R_2 + R_3 + \beta R_1 R_3)I_2$$

Example 3

Open-circuit port 1 (cont'd):

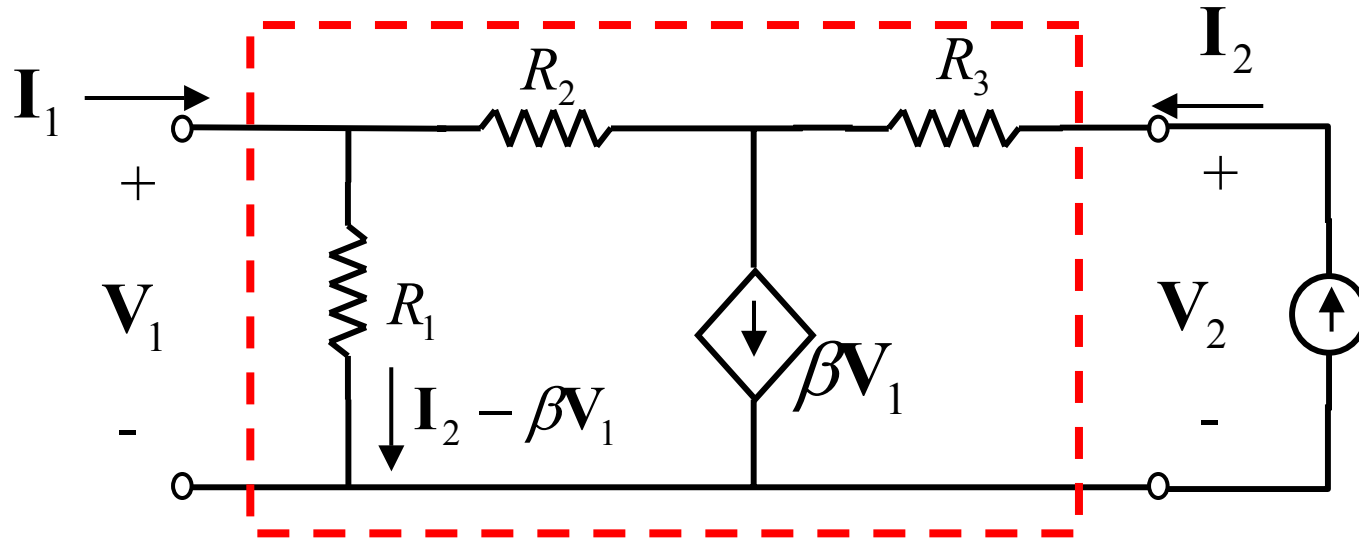


$$V_2(1 + \beta R_1) = (R_1 + R_2 + R_3 + \beta R_1 R_3)I_2$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = \frac{(R_1 + R_2 + R_3 + \beta R_1 R_3)}{(1 + \beta R_1)} \quad \text{③}$$

Example 3

Open-circuit port 1:

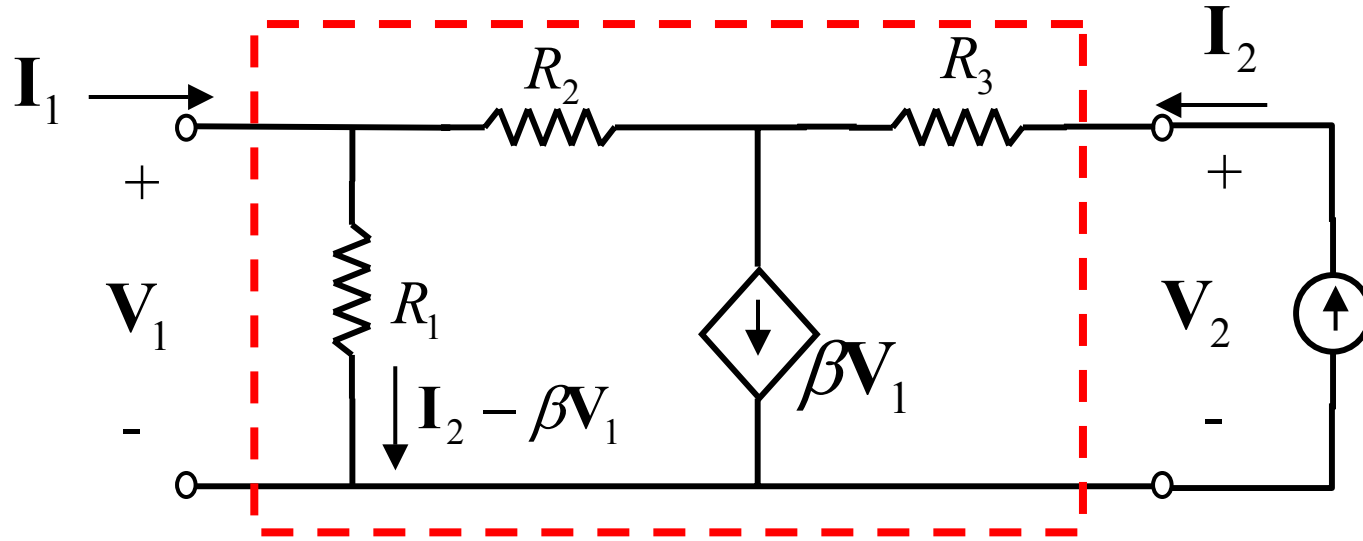


$$V_1 = R_1 (I_2 - \beta V_1)$$

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = \frac{R_1}{1 + \beta R_1} \Omega \quad \textcircled{4}$$

Two-Port Hybrid Parameters

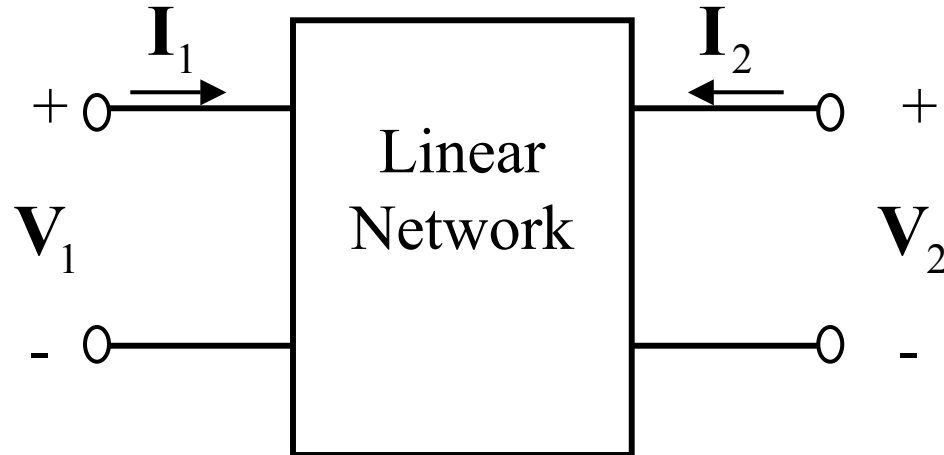→ Commonly referred to as the *H-parameters*.



→ Note the voltage polarities and current directions.

→ Using the principle of superposition we get:

$$\rightarrow V_1 = h_{11}I_1 + h_{12}V_2$$

$$\rightarrow I_2 = h_{21}I_1 + h_{22}V_2$$

H-Parameters

$$\begin{aligned} \mathbf{V}_1 &= h_{11}\mathbf{I}_1 + h_{12}\mathbf{V}_2 \\ \mathbf{I}_2 &= h_{21}\mathbf{I}_1 + h_{22}\mathbf{V}_2 \end{aligned} \quad \longrightarrow \quad \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{V}_2 \end{bmatrix}$$

- **Two equations describe two-port operation.**
- h_{ij} are complex constants of proportionality with units of Ohms (Ω), Siemens (S) or no units.
- Common in transistor models.
- Once h_{11} , h_{12} , h_{21} , h_{22} are known, the input/output operation of the two-port network is **completely** defined.
- h_{ij} are the hybrid parameters or H-parameters.
- The H-parameter matrix is:

$$\mathbf{H} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix}$$

H-Parameters

$$\begin{aligned} \mathbf{V}_1 &= h_{11}\mathbf{I}_1 + h_{12}\mathbf{V}_2 \\ \mathbf{I}_2 &= h_{21}\mathbf{I}_1 + h_{22}\mathbf{V}_2 \end{aligned} \quad \rightarrow \quad \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{V}_2 \end{bmatrix}$$


$$\mathbf{V}_2 = 0 \quad \rightarrow \quad \mathbf{V}_1 = h_{11}\mathbf{I}_1 \quad \rightarrow \quad h_{11} = \left. \frac{\mathbf{V}_1}{\mathbf{I}_1} \right|_{\mathbf{V}_2=0}$$

$$\mathbf{V}_2 = 0 \quad \rightarrow \quad \mathbf{I}_2 = h_{21}\mathbf{I}_1 \quad \rightarrow \quad h_{21} = \left. \frac{\mathbf{I}_2}{\mathbf{I}_1} \right|_{\mathbf{V}_2=0}$$

$$\mathbf{I}_1 = 0 \quad \rightarrow \quad \mathbf{V}_1 = h_{12}\mathbf{V}_2 \quad \rightarrow \quad h_{12} = \left. \frac{\mathbf{V}_1}{\mathbf{V}_2} \right|_{\mathbf{I}_1=0}$$

$$\mathbf{I}_1 = 0 \quad \rightarrow \quad \mathbf{I}_2 = h_{22}\mathbf{V}_2 \quad \rightarrow \quad h_{22} = \left. \frac{\mathbf{I}_2}{\mathbf{V}_2} \right|_{\mathbf{I}_1=0}$$

Inverse Hybrid Parameters

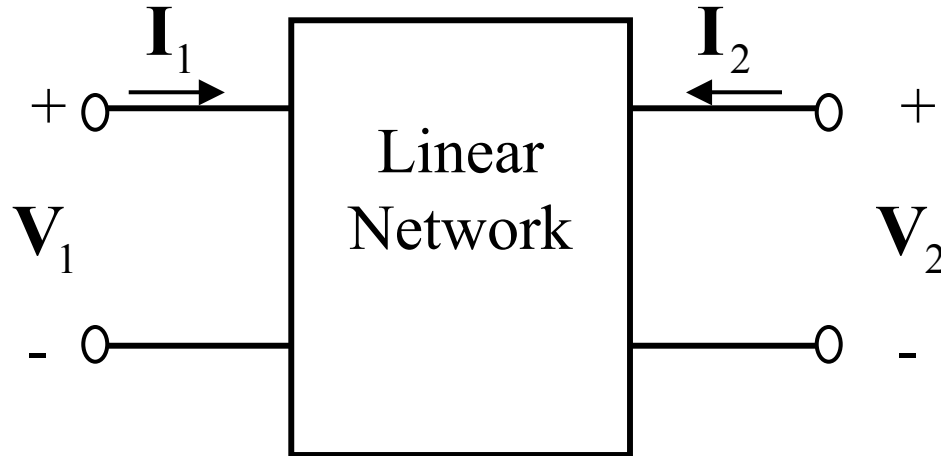

$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{V}_2 \end{bmatrix}$$

$$\begin{bmatrix} \mathbf{I}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_2 \end{bmatrix}$$

$$\begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix}^{-1}$$

$$\mathbf{G} = \mathbf{H}^{-1}$$

Hybrid/Inverse Hybrid Parameters


→ How to find Hybrid/Inverse Hybrid parameters.

→ Given hybrid parameters, calculate the inverse hybrid parameters by taking the inverse of the matrix and vice versa.

or

→ Calculate parameters directly using open/short circuit tests.

Example

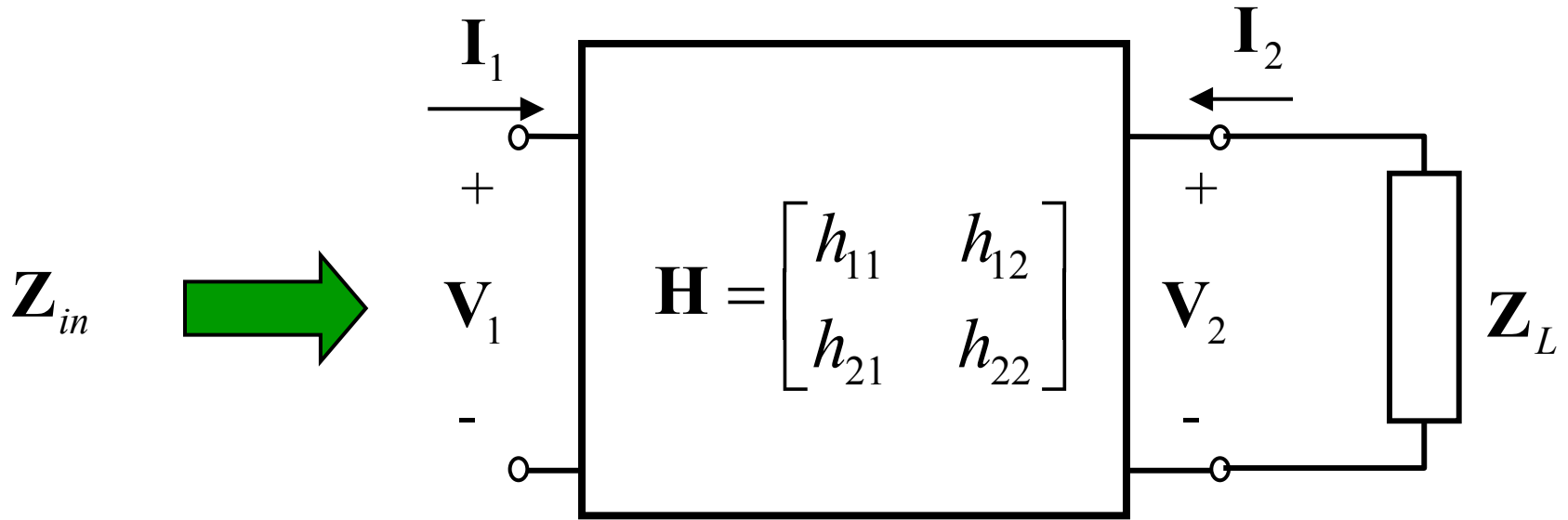

Calculate the input impedance

$$Z_{in} = \frac{V_1}{I_1}$$

Example

$$\left. \begin{aligned} \mathbf{V}_1 &= h_{11}\mathbf{I}_1 + h_{12}\mathbf{V}_2 \\ \mathbf{I}_2 &= h_{21}\mathbf{I}_1 + h_{22}\mathbf{V}_2 \end{aligned} \right\} \text{Hybrid parameters equations}$$


$$\mathbf{V}_2 = -\mathbf{I}_2\mathbf{Z}_L \quad \text{Terminal condition}$$

$$\left\{ \begin{aligned} \mathbf{V}_1 &= h_{11}\mathbf{I}_1 - h_{12}(\mathbf{I}_2\mathbf{Z}_L) \\ \mathbf{I}_2 &= h_{21}\mathbf{I}_1 - h_{22}(\mathbf{I}_2\mathbf{Z}_L) \end{aligned} \right.$$

$$\longrightarrow \mathbf{Z}_{in} = h_{11} - \frac{h_{12}h_{21}\mathbf{Z}_L}{1 + h_{22}\mathbf{Z}_L}$$

Two-Port Transmission Parameters

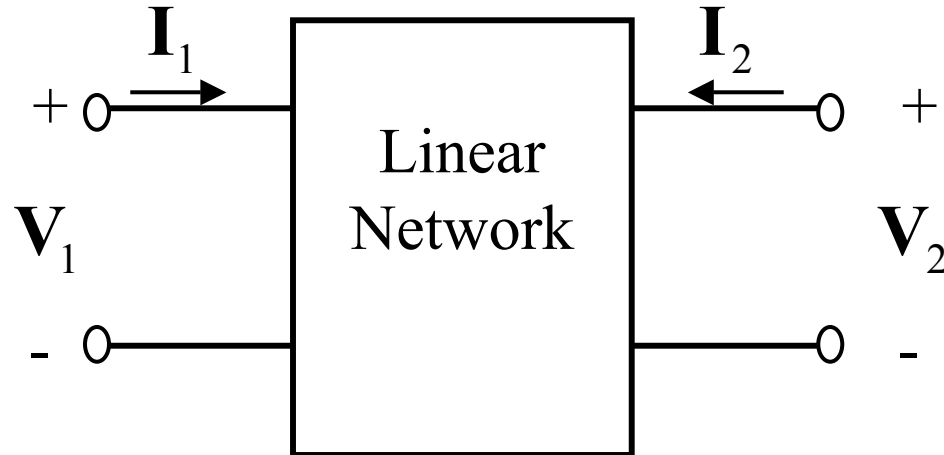→ Commonly referred to as the *ABCD-parameters*.



→ Note the voltage polarities and current directions.

→ Using the principle of superposition we get:

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

ABCD- Parameters

$$\begin{aligned} \mathbf{V}_1 &= A\mathbf{V}_2 - B\mathbf{I}_2 \\ \mathbf{I}_1 &= C\mathbf{V}_2 - D\mathbf{I}_2 \end{aligned} \quad \rightarrow \quad \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} \mathbf{V}_2 \\ -\mathbf{I}_2 \end{bmatrix}$$

- Two equations describe two-port operation.
- A , B , C and D are **complex** constants of proportionality with units of Ohms (Ω), Siemens (S), or no units.
- Common in transmission line models.
- Once A , B , C and D are known, the input/output operation of the two-port network is **completely** defined.
- The transmission parameter matrix is:

$$T = \begin{bmatrix} t_{11} & t_{12} \\ t_{21} & t_{22} \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix}$$