

ECSE 210: Circuit Analysis

Lecture #10:

- Second Order Circuits Conclusion**
- Sinusoids**
- Circuits with Sinusoidal Forcing Functions**

RLC Circuits: Final Remarks

1. RLC circuit analysis leads to second order ODEs.
2. RLC circuit response is determined by the roots of the characteristic equation of the governing ODE:

$$s^2 + 2\alpha s + \omega_o^2 = 0$$

where: α is the exponential damping coefficient and ω_o is the undamped resonant frequency


3. *Real and unequal roots* ($\alpha > \omega_o$) \rightarrow overdamped;
Complex & unequal roots ($\alpha < \omega_o$) \rightarrow underdamped;
Real and equal roots ($\alpha = \omega_o$) \rightarrow critically damped.
 4. The general response/solution of even very simple RLC circuits can be very difficult to determine in the time domain.
- \rightarrow Use *transform* methods which simplify the analysis.

Sinusoids

The sinusoidal forcing function is a very important electric circuit excitation:

1. It is the dominant waveform in the electric power industry.
 2. All periodic electrical signals can be represented by a sum of sinusoids (Fourier analysis).
- We will study the steady-state forced response of circuits sourced by sinusoidal driving functions.
(ac steady-state analysis)

Sinusoids

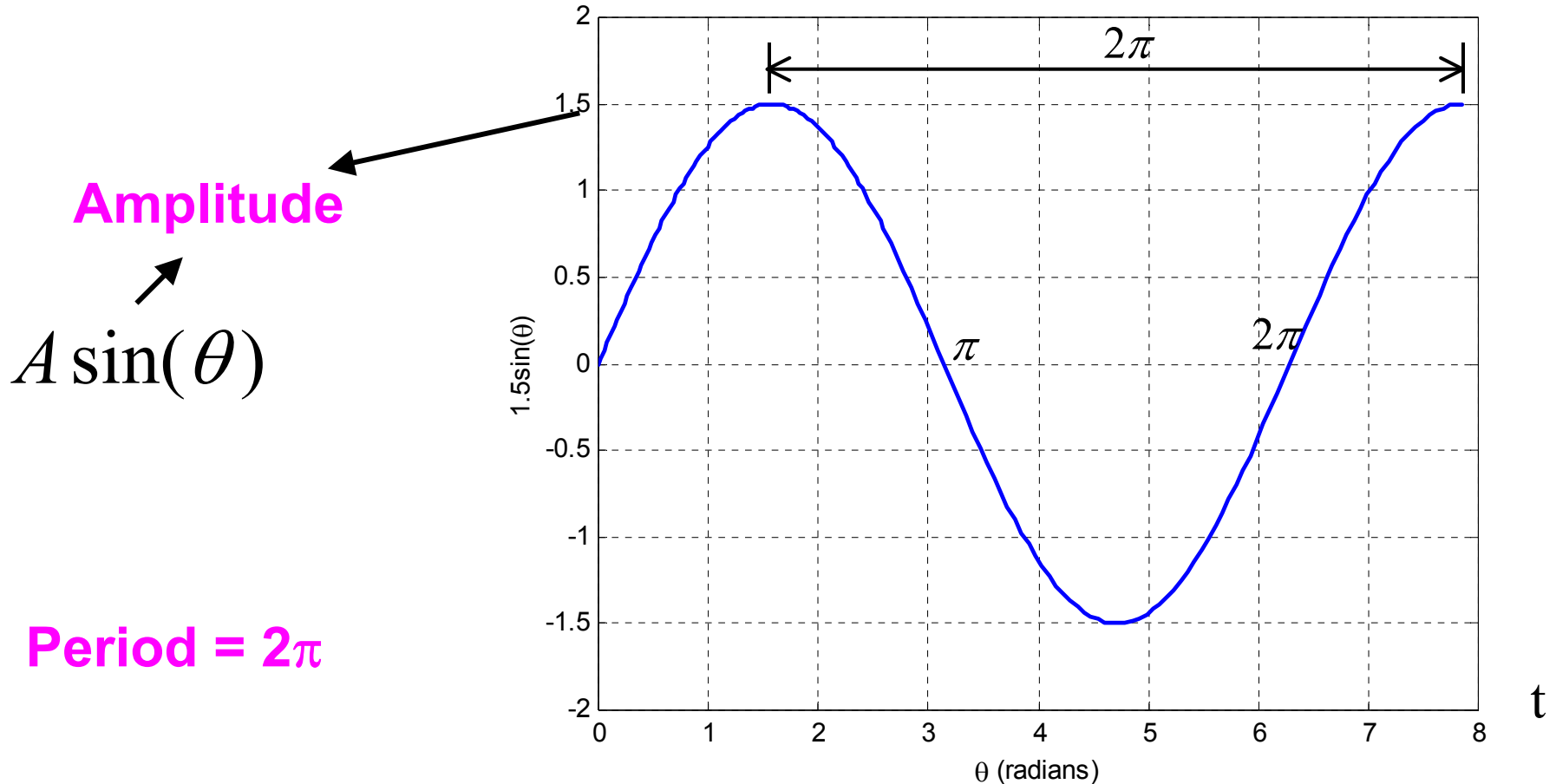

$$A \sin(\theta) = A \sin(\theta + 2\pi)$$

$$A \sin(\theta) = A \sin(\theta + 2k\pi) \quad k \text{ is an integer}$$


Sinusoids $\theta \rightarrow \omega t$

Amplitude \uparrow

$$x(t) = A \sin(\omega t)$$

$$\omega = 4\pi \text{ rd/s}$$

\downarrow
Angular frequency

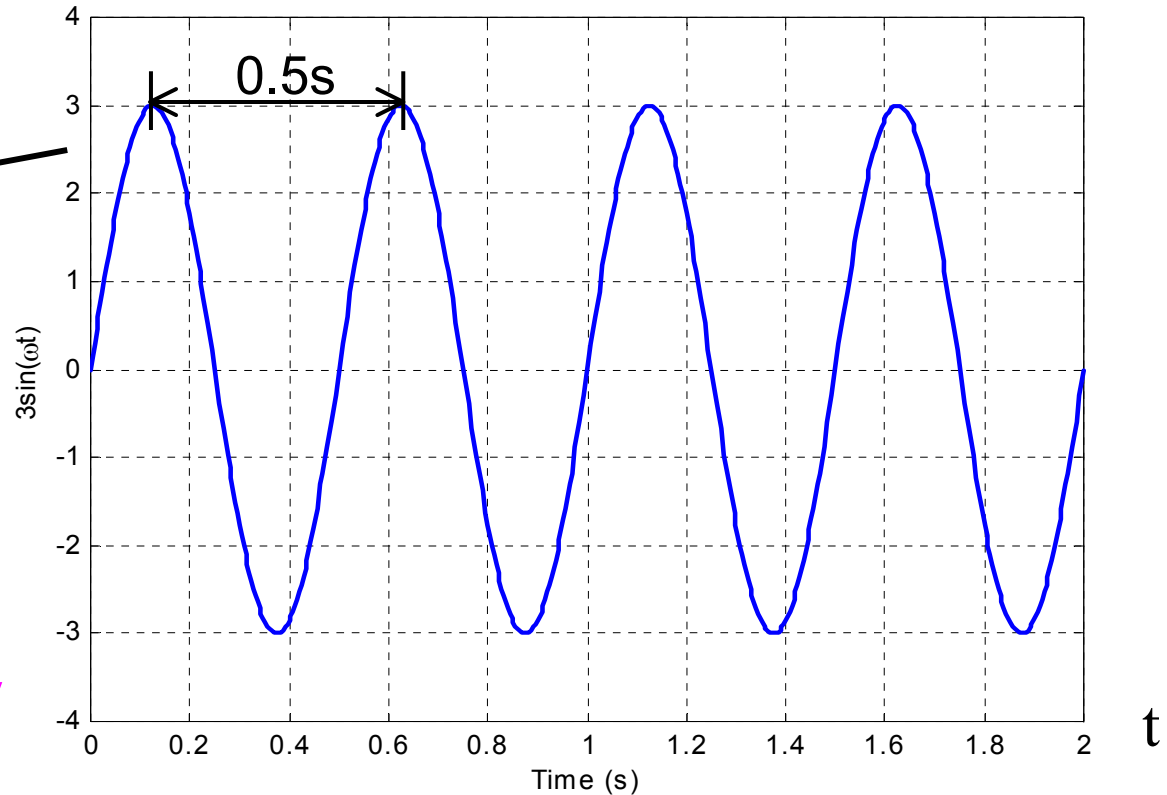

Period T of a sine wave: $x(t) = x(t + T)$

$$A \sin(\omega t) = A \sin(\omega(t + T)) = A \sin(\omega t + \omega T)$$

$$\omega T = 2\pi \quad \longrightarrow \quad T = \frac{2\pi}{\omega}$$

Sinusoids

- Period of $x(\theta) = \sin(\theta)$ is 2π radians
- Period of $x(t) = \sin(\omega t)$ is $T = \frac{2\pi}{\omega}$ seconds
 - **One cycle takes T seconds.**
 - How many cycles per second?

$$f = \frac{1}{T} \quad \text{Hertz (Hz) or cycles/second}$$

Note: For frequency f in Hertz (Hz), period T in seconds (s) and angular frequency ω in radians/second (rd/s) we have:

$$T = \frac{2\pi}{\omega} \quad f = \frac{1}{T} \quad \omega = 2\pi f$$


Generalized Sinusoids

Amplitude

$$x(t) = A \sin(\omega t + \theta)$$

Angular frequency

Phase angle

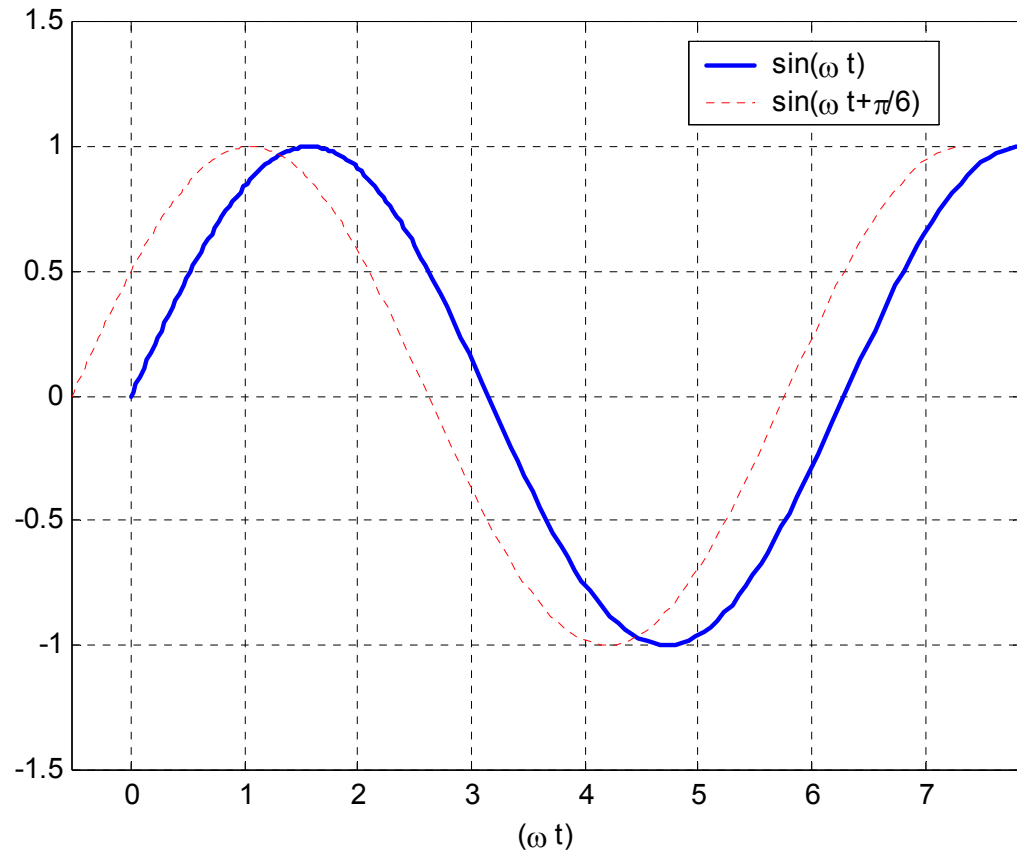

Convention

$A \sin(\omega t)$ **lags** wave $A \sin(\omega t + \theta)$ by θ radians

Phase Angle

By convention:

$$x_1(t) = A_1 \sin(\omega t + \theta_1)$$

$$x_2(t) = A_2 \sin(\omega t + \theta_2)$$

x_1 **leads** x_2 by $\theta_1 - \theta_2$ radians, or
 x_2 **lags** x_1 by $\theta_1 - \theta_2$ radians

Also: $\theta_1 = \theta_2 \rightarrow x_1$ and x_2 are “in phase”
 $\theta_1 \neq \theta_2 \rightarrow x_1$ and x_2 are “out of phase”

- We can only compare phase angles if x_1 and x_2 have the same angular frequency ω .
- The phase angle is often expressed in degrees.
- When comparing phase angles, express both functions as either sine or cosine with positive amplitude.

Trigonometric Identities (Confirm!)

$$\cos(\omega t) = \sin(\omega t + 90^\circ) = -\cos(\omega t \pm 180^\circ)$$

$$\sin(\omega t) = \cos(\omega t - 90^\circ) = -\sin(\omega t \pm 180^\circ)$$

$$\sin(\alpha + \beta) = \sin(\alpha) \cos(\beta) + \cos(\alpha) \sin(\beta)$$

$$\sin(\alpha - \beta) = \sin(\alpha) \cos(\beta) - \cos(\alpha) \sin(\beta)$$

$$\cos(\alpha + \beta) = \cos(\alpha) \cos(\beta) - \sin(\alpha) \sin(\beta)$$

$$\cos(\alpha - \beta) = \cos(\alpha) \cos(\beta) + \sin(\alpha) \sin(\beta)$$

Sum of Sine and Cosine

Since $\sin(\alpha + \beta) = \sin(\alpha) \cos(\beta) + \cos(\alpha) \sin(\beta)$

Then $x(t) = A \sin(\omega t + \theta)$

$$= \underbrace{A \cos(\theta)}_{B_1} \sin(\omega t) + \underbrace{A \sin(\theta)}_{B_2} \cos(\omega t)$$

$$= B_1 \sin(\omega t) + B_2 \cos(\omega t)$$

$$B_1^2 + B_2^2 = A^2 (\cos^2(\theta) + \sin^2(\theta)) = A^2 \quad \Rightarrow \quad A = \sqrt{B_1^2 + B_2^2}$$

$$\frac{B_2}{B_1} = \frac{\sin(\theta)}{\cos(\theta)} = \tan(\theta) \quad \Rightarrow \quad \theta = \tan^{-1}\left(\frac{B_2}{B_1}\right)$$

Example

$$\left. \begin{aligned} v_1(t) &= 12 \sin(377t + 60^\circ) \\ v_2(t) &= -6 \cos(377t + 30^\circ) \end{aligned} \right\} \text{Find frequency and phase angles}$$

Choose to express both as sine with positive amplitude

$$v_1(t) = 12 \sin(377t + 60^\circ)$$

$$\begin{aligned} v_2(t) &= -6 \cos(377t + 30^\circ) = 6 \cos(377t + 210^\circ) \\ &= 6 \sin(377t + 300^\circ) \end{aligned}$$

Phase difference is $60 - 300 = -240^\circ$

→ v_1 leads v_2 by 120° (Why?)

$$\text{Also: } f = \frac{\omega}{2\pi} = \frac{377}{2\pi} = 60 \text{ Hz}$$

Sinusoidal Forcing Function

Recall the form of the *natural* response of a linear *second order circuit*:

$$x_n(t) = C_1 e^{\lambda_1 t} + C_2 e^{\lambda_2 t} \quad \rightarrow \text{Overdamped}$$

$$x_n(t) = C_1 e^{-\alpha t} + C_2 t e^{-\alpha t} \quad \rightarrow \text{Critically damped}$$

$$x_n(t) = e^{-\alpha t} [B_1 \cos \omega_d t + B_2 \sin \omega_d t] \quad \rightarrow \text{Underdamped}$$

At $t \rightarrow \infty$ the *natural response* goes to zero and we are left with the forced response.

Sinusoidal Forcing Function

Recall the form of the *forced* response of a linear second order circuit:

For a sinusoidal forcing function $\sin(\omega t)$ the forced response has the form:

$$A \sin(\omega t) + B \cos(\omega t)$$

- Therefore, in the steady-state (after all transients have died out):

A linear *second order* circuit with a sinusoidal input will have sinusoidal branch voltages and currents at the same frequency as the input.

Sinusoidal Forcing Function

We can generalize the above conclusion for **any linear** circuit:

In the steady-state (after all transients have died out):

A linear circuit with a sinusoidal input will have sinusoidal branch voltages and currents at the same frequency as the input.

For example, a circuit in an input of the form:

$$A \sin(\omega t + \theta)$$

will have an output (a solution) in the steady state in the form:

$$B \sin(\omega t + \phi) \quad \text{Need to determine two parameters.}$$

Example

KVL


$$L \frac{di}{dt} + Ri = V_m \cos(\omega t)$$

Assume steady-state (ss):

$$i(t) = A \cos(\omega t + \phi)$$

$$i(t) = A \cos(\phi) \cos(\omega t) - A \sin(\phi) \sin(\omega t)$$
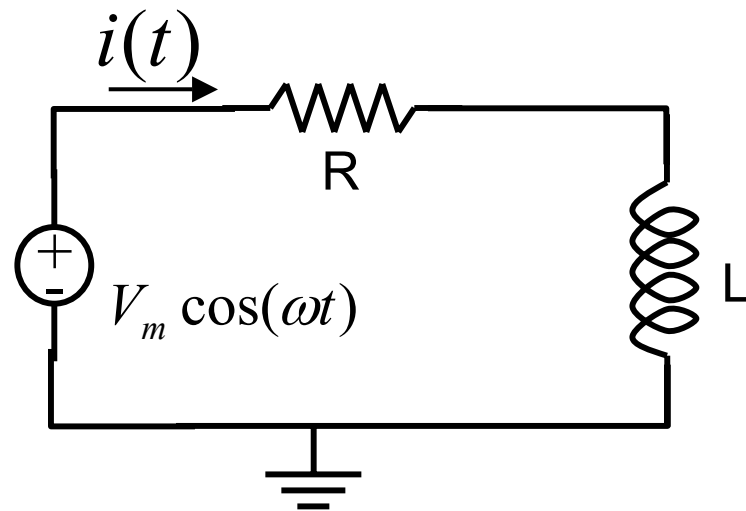
$$i(t) = A_1 \cos(\omega t) + A_2 \sin(\omega t) \longrightarrow \text{Substitute into ODE}$$



$$L \frac{d}{dt} (A_1 \cos(\omega t) + A_2 \sin(\omega t)) + R (A_1 \cos(\omega t) + A_2 \sin(\omega t)) = V_m \cos(\omega t)$$

Example

$$L \frac{d}{dt} (A_1 \cos(\omega t) + A_2 \sin(\omega t)) + R(A_1 \cos(\omega t) + A_2 \sin(\omega t)) = V_m \cos(\omega t)$$

$$-L\omega A_1 \sin(\omega t) + L\omega A_2 \cos(\omega t) + RA_1 \cos(\omega t) + RA_2 \sin(\omega t) = V_m \cos(\omega t)$$

$$\begin{cases} -L\omega A_1 + RA_2 = 0 \\ L\omega A_2 + RA_1 = V_m \end{cases}$$



$$A_1 = \frac{RV_m}{R^2 + \omega^2 L^2}$$

$$A_2 = \frac{\omega L V_m}{R^2 + \omega^2 L^2}$$

$$i(t) = \frac{RV_m}{R^2 + \omega^2 L^2} \cos(\omega t) + \frac{\omega L V_m}{R^2 + \omega^2 L^2} \sin(\omega t)$$

Example

$$i(t) = \frac{RV_m}{R^2 + \omega^2 L^2} \cos(\omega t) + \frac{\omega L V_m}{R^2 + \omega^2 L^2} \sin(\omega t)$$

$$i(t) = A \cos(\omega t + \phi)$$

Convert to simpler form

$$i(t) = A \cos(\phi) \cos(\omega t) - A \sin(\phi) \sin(\omega t) \quad \text{Compare to above}$$

$$\tan(\phi) = \frac{A \sin(\phi)}{A \cos(\phi)} = -\frac{\omega L}{R} \quad \rightarrow \quad \phi = -\tan^{-1}\left(\frac{\omega L}{R}\right)$$

$$A^2 = \frac{R^2 V_m^2}{(R^2 + \omega^2 L^2)^2} + \frac{(\omega L)^2 V_m^2}{(R^2 + \omega^2 L^2)^2} = \frac{V_m^2}{R^2 + \omega^2 L^2}$$

$$A = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}}$$