


ECSE 210: Circuit Analysis

Lecture #14:

AC Steady State Analysis

Steady State Power Analysis

Sources With Different Frequencies



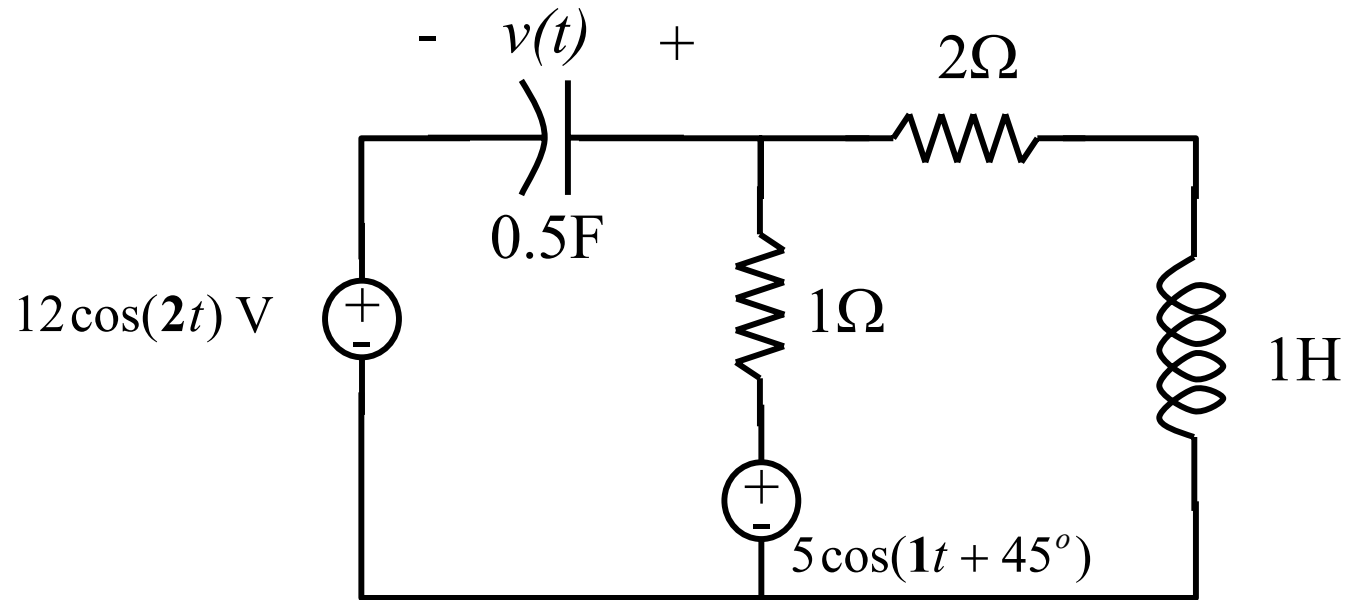


→ Two sources at different frequencies.

→ We must use superposition.


(Only meaningful in the time domain!)

Sources With Different Frequencies

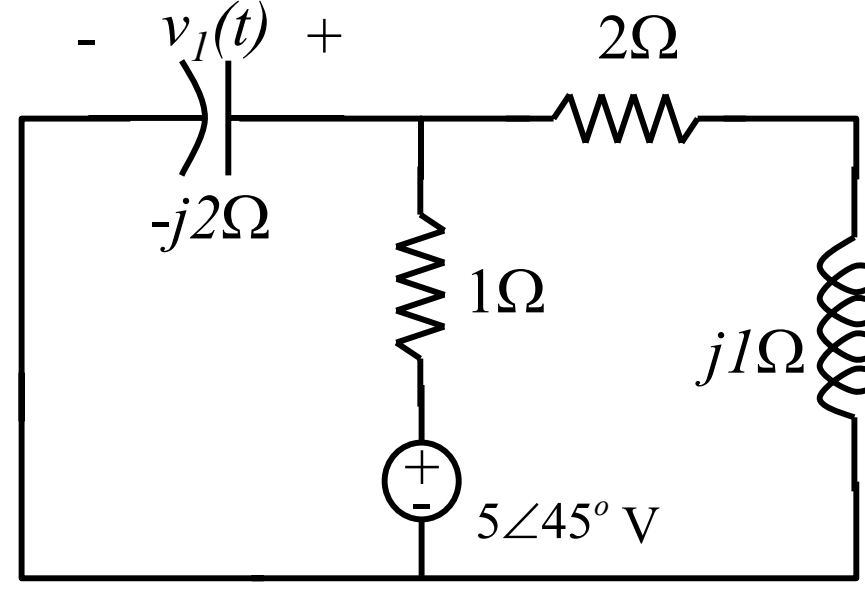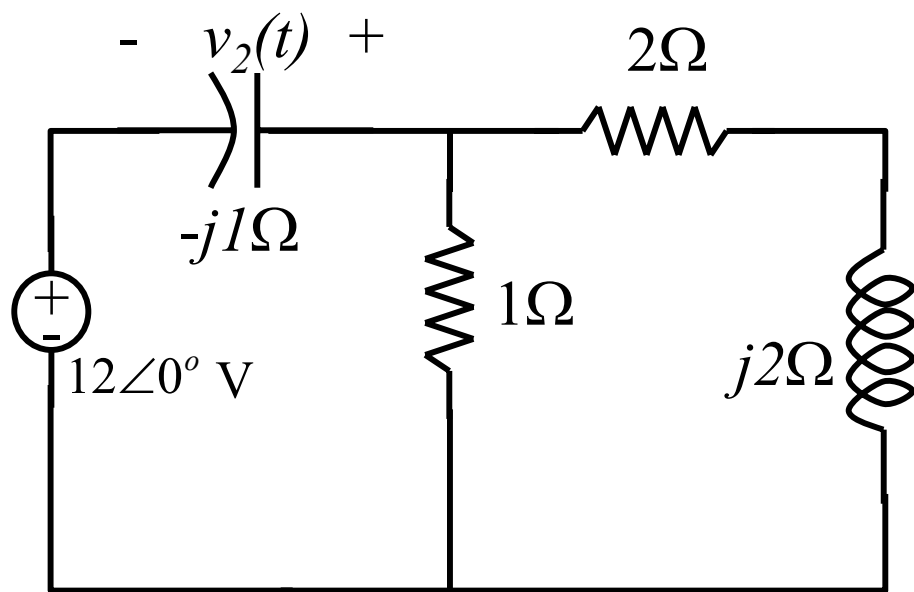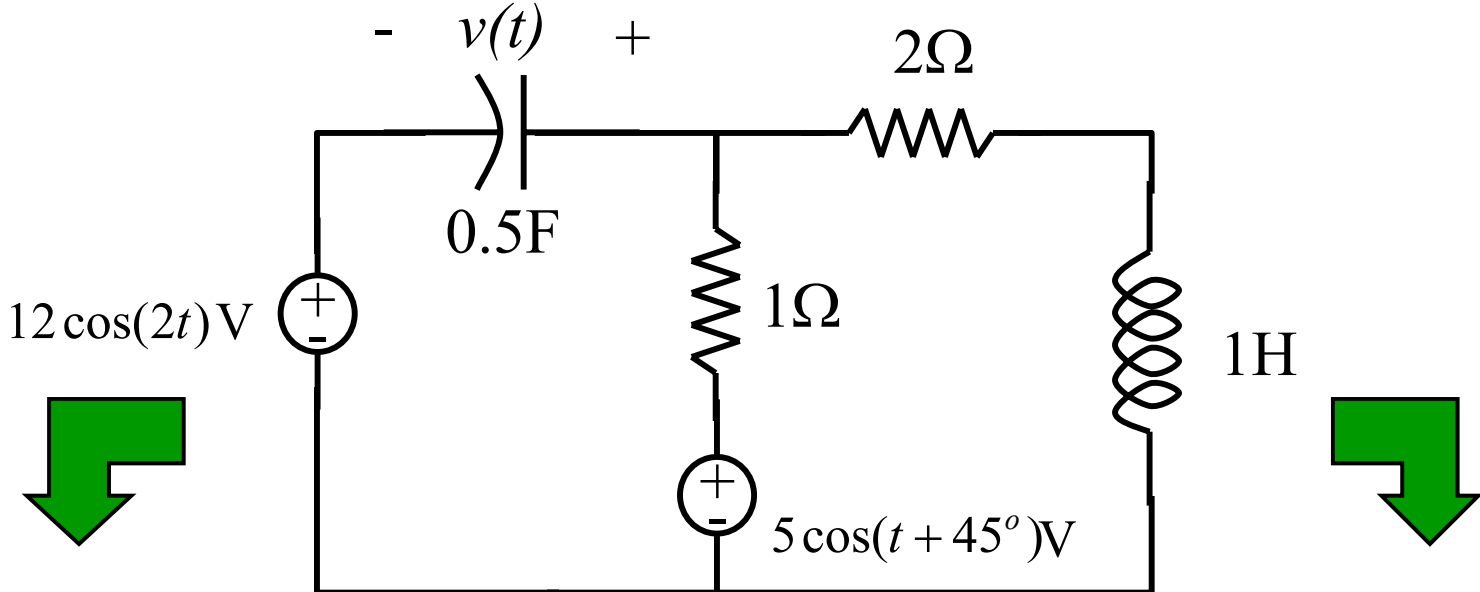

Sources With Different Frequencies
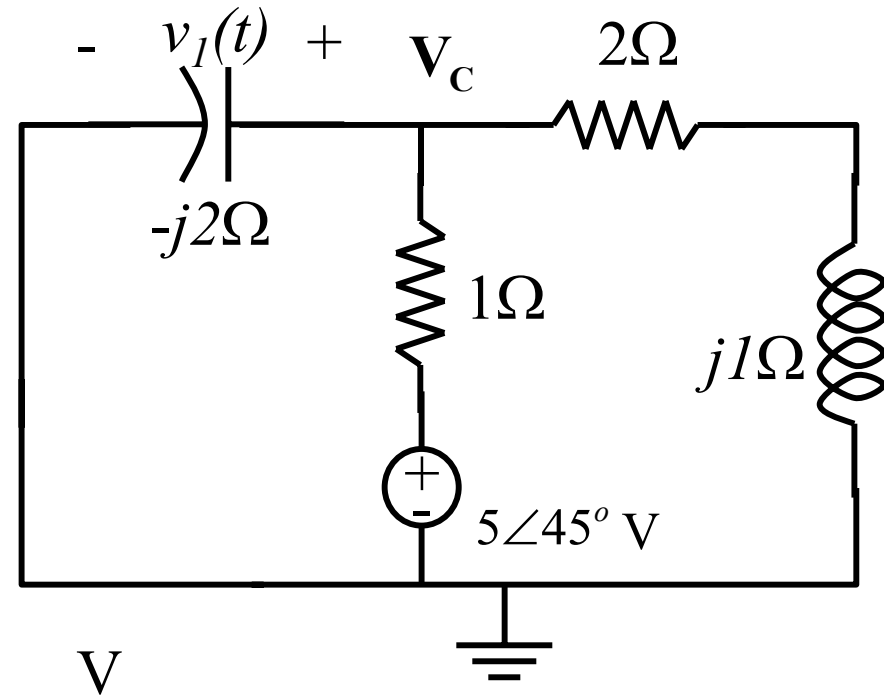
$$\mathbf{V}_C = \frac{(-j2\Omega) \parallel (2\Omega + j1\Omega)}{1\Omega + (-j2\Omega) \parallel (2\Omega + j1\Omega)} (5\angle 45^\circ)$$




$$\mathbf{V}_C = (0.7\angle -12.09^\circ)(5\angle 45^\circ) = 3.5\angle 32.9^\circ$$

$$v_1(t) = 3.5 \cos(t + 32.9^\circ) \text{ V}$$

Sources With Different Frequencies
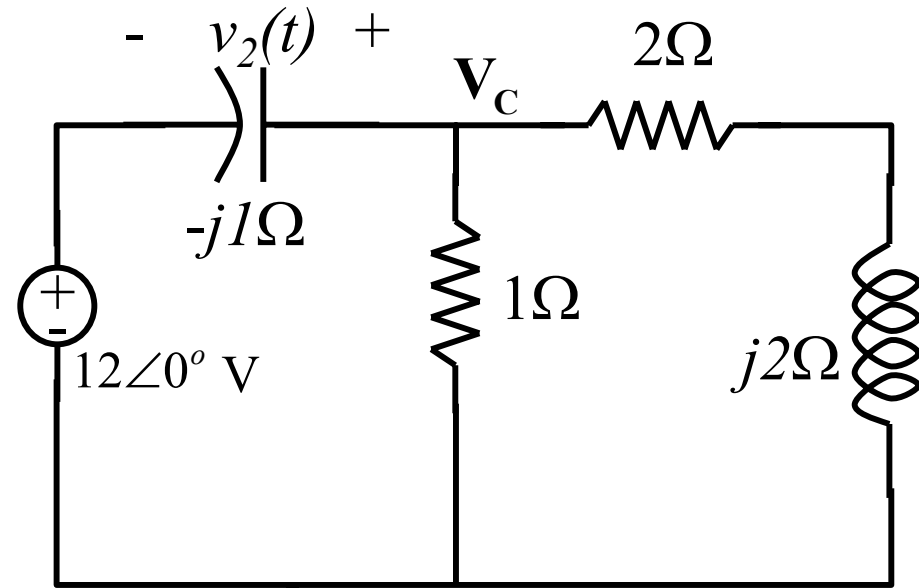
$$V_C = \frac{(2\Omega + j2\Omega) \parallel (1\Omega)}{(2\Omega + j2\Omega) \parallel (1\Omega) - j1\Omega} (12\angle 0^\circ)$$



$$V_C = (0.686\angle 59.04^\circ)(12\angle 0^\circ) = 8.23\angle 59.04^\circ \text{ V}$$

$$V_2 = (8.23\angle 59.04^\circ) - (12\angle 0^\circ) = 10.5\angle 138^\circ \text{ V}$$

$$v_2(t) = 10.5 \cos(2t + 138^\circ) \text{ V}$$

Sources With Different Frequencies

$$v_1(t) = 3.5 \cos(t + 32.9^\circ) \quad \text{V}$$

$$v_2(t) = 10.5 \cos(2t + 138^\circ) \quad \text{V}$$

$$v(t) = v_1(t) + v_2(t) = 3.5 \cos(t + 32.9^\circ) + 10.5 \cos(2t + 138^\circ)$$


→ Note we can only add waveforms at different frequencies in the time domain. We **CANNOT** add their phasors. Each phasor is defined at a specific frequency and phasors with different frequencies cannot be added.

Instantaneous Power

Passive Sign Convention:

→ Power **supplied** to circuit/circuit element:

$$p(t) = i(t)v(t)$$

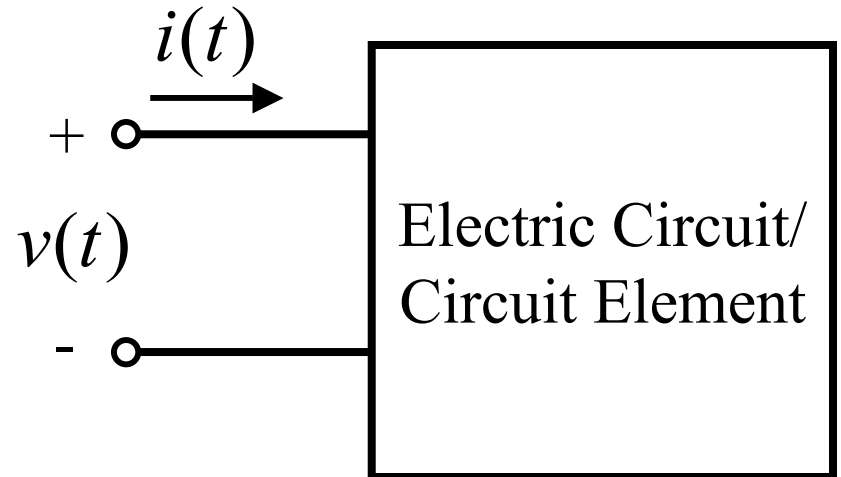


→ In the case of sinusoidal excitation in the steady state:

$$v(t) = V_m \cos(\omega t + \theta_V) \quad i(t) = I_m \cos(\omega t + \theta_I)$$

$$p(t) = I_m V_m \cos(\omega t + \theta_V) \cos(\omega t + \theta_I)$$

→ Recall: $\cos(\alpha) \cos(\beta) = \frac{1}{2} [\cos(\alpha + \beta) + \cos(\alpha - \beta)]$

Instantaneous Power


$$p(t) = I_m V_m \cos(\omega t + \theta_V) \cos(\omega t + \theta_I)$$
$$p(t) = \underbrace{\frac{I_m V_m}{2} \cos(\theta_V - \theta_I)}_{\text{Constant}} + \underbrace{\frac{I_m V_m}{2} \cos(2\omega t + \theta_V + \theta_I)}_{\text{Periodic in time}}$$

1. For circuits with time varying inputs (e.g., sinusoidal input) the **instantaneous** power is a function of time denoted as $p(t)$.
2. For circuits with sinusoidal inputs in the **steady state**, $p(t)$ has a constant component and a periodic component.

Example 1

$$v(t) = 10 \cos(10^4 t) \text{ V}$$


$$\mathbf{V} = 10 \angle 0^\circ \text{ V} \quad 10 \cos(10^4 t) \text{ V}$$

$$\begin{aligned} Z &= 50 \Omega + j\omega L \Omega = 50 + j120 \Omega \\ &= 130 \angle 67.4^\circ \Omega \end{aligned}$$


$$\mathbf{I} = \frac{\mathbf{V}}{Z} = \frac{10 \angle 0^\circ}{130 \angle 67.4^\circ} = 76.9 \angle -67.4^\circ$$

$$i(t) = 76.9 \cos(10^4 t - 67.4^\circ) \text{ mA}$$

$$\begin{aligned} p(t) &= \left[76.9 \cos(10^4 t - 67.4^\circ) \right] \left[10 \cos(10^4 t) \right] \\ &= \frac{769}{2} \cos(67.4^\circ) + \frac{769}{2} \cos(2 \times 10^4 t - 67.4^\circ) \text{ mW} \end{aligned}$$

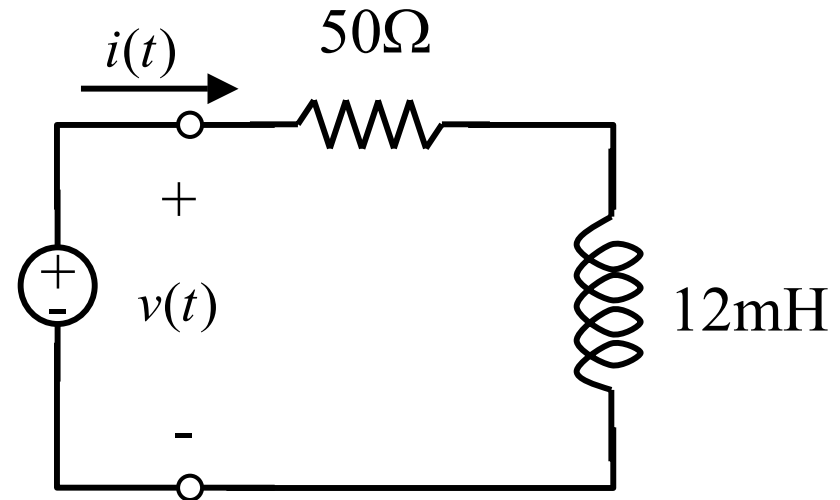

Example 1

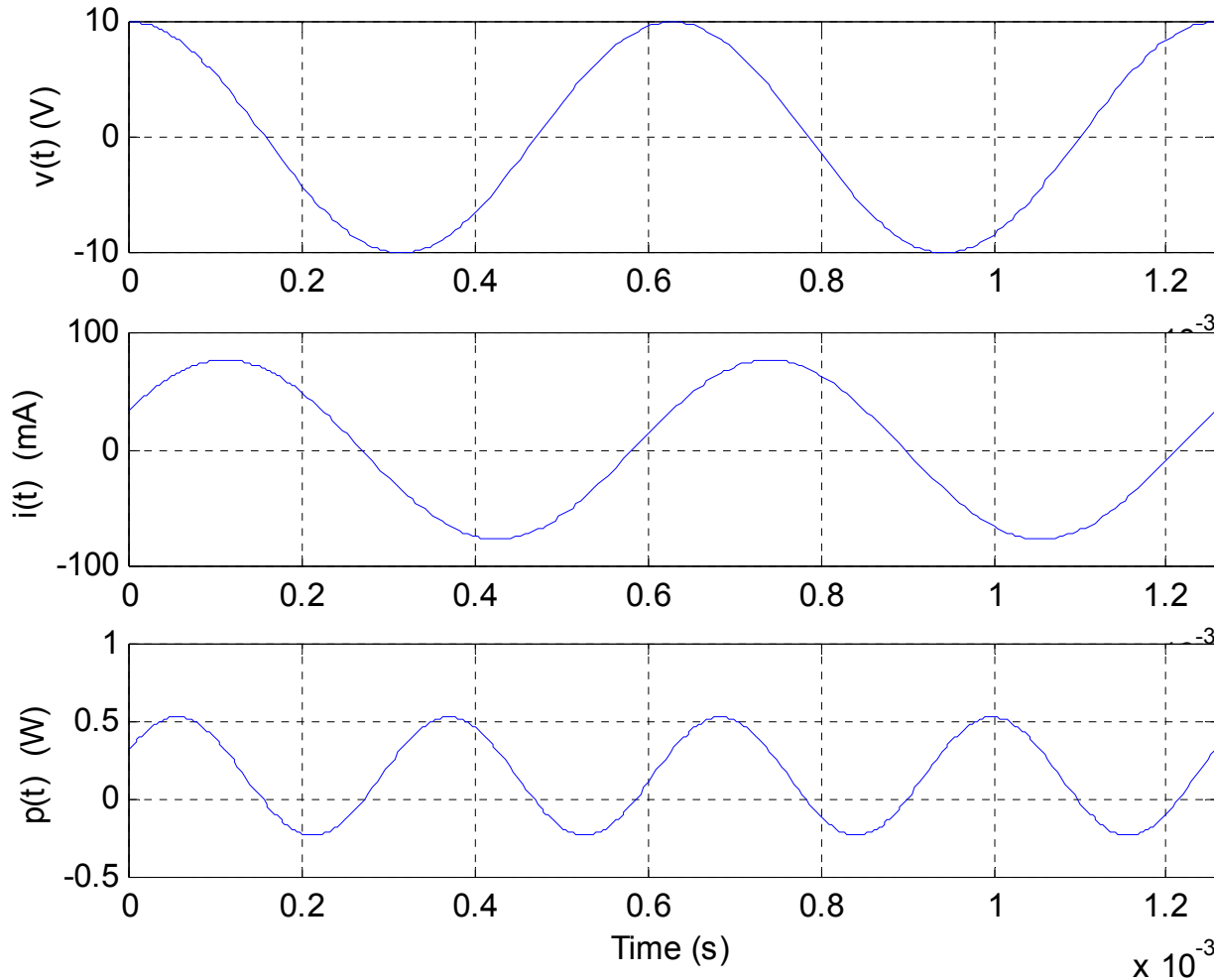

$$p(t) = 0.15 + 0.38 \cos(2 \times 10^4 t - 67.4^\circ) \quad \text{W}$$

Average Power

- In the case of periodic excitation in the steady-state, the **instantaneous power** $p(t)$ is a periodic function of time.
 - The average value of $p(t)$ over one period (the **average power**) is a useful indicator of how much power is absorbed/supplied.
 - The *average power* is NOT a function of time for a periodic excitation!
- For a general periodic function $x(t)$, such that $x(t+T)=x(t)$ the average value X is given by

$$X_{ave} = \frac{1}{T} \int_{t_0}^{t_0+T} x(\tau) d\tau$$

Average Power

→ In the case of Example 1:

$$p(t) = 0.15 + 0.38 \cos(2 \times 10^4 t - 67.4^\circ)$$

$$P_{avg} = \frac{1}{T} \int_0^T p(\tau) d\tau = \underbrace{\frac{1}{T} \int_0^T 0.15 d\tau}_{0.15} + \underbrace{\frac{1}{T} \int_0^T 0.38 \cos(2 \times 10^4 \tau - 67.4^\circ) d\tau}_{\text{zero}}$$

$$P_{avg} = 0.15 \text{ W}$$

Average Power

→ General case

$$p(t) = \underbrace{\frac{I_m V_m}{2} \cos(\theta_V - \theta_I)}_{\text{constant}} + \frac{I_m V_m}{2} \cos(2\omega t + \theta_V + \theta_I)$$

constant

$$P_{avg} = \frac{1}{T} \int_0^T \frac{I_m V_m}{2} \cos(\theta_V - \theta_I) d\tau + \underbrace{\frac{1}{T} \int_0^T \frac{I_m V_m}{2} \cos(2\omega\tau + \theta_V + \theta_I) d\tau}_{\text{zero}}$$

zero

$$P_{avg} = \frac{I_m V_m}{2} \cos(\theta_V - \theta_I)$$

Average Power Consumed by a General Load


$$\mathbf{Z} = Z \angle \theta_Z$$

$$P_{avg} = \frac{I_m V_m}{2} \cos(\theta_V - \theta_I) \quad V_m \angle \theta_V \text{ V}$$

$$V_m \angle \theta_V = (I_m \angle \theta_I)(Z \angle \theta_Z) = I_m Z \angle (\theta_I + \theta_Z)$$

$$V_m = I_m Z \quad \theta_V = \theta_I + \theta_Z$$
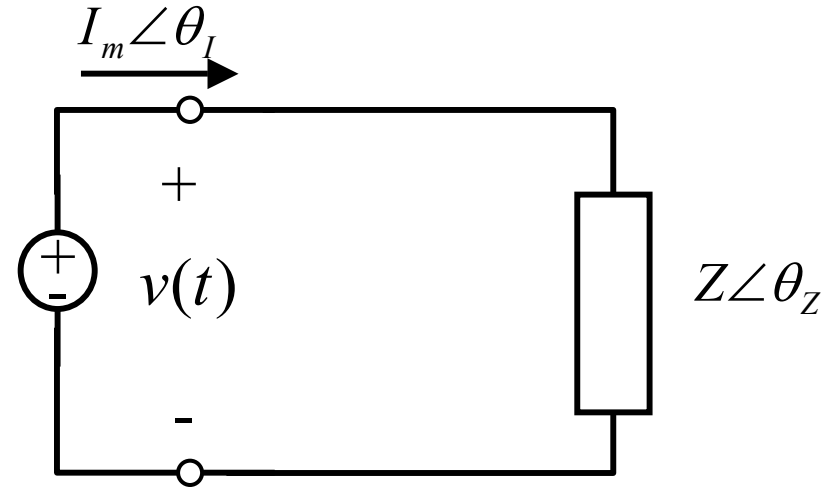
$$I_m = \frac{V_m}{Z} \quad \theta_I = \theta_V - \theta_Z$$



→ Substitute into power equation:

$$P_{avg} = \frac{1}{2} I_m^2 Z \cos(\theta_Z)$$



and

$$P_{avg} = \frac{1}{2} \frac{V_m^2}{Z} \cos(\theta_Z)$$




Average Power in a Resistor

For ac

If $Z = R$
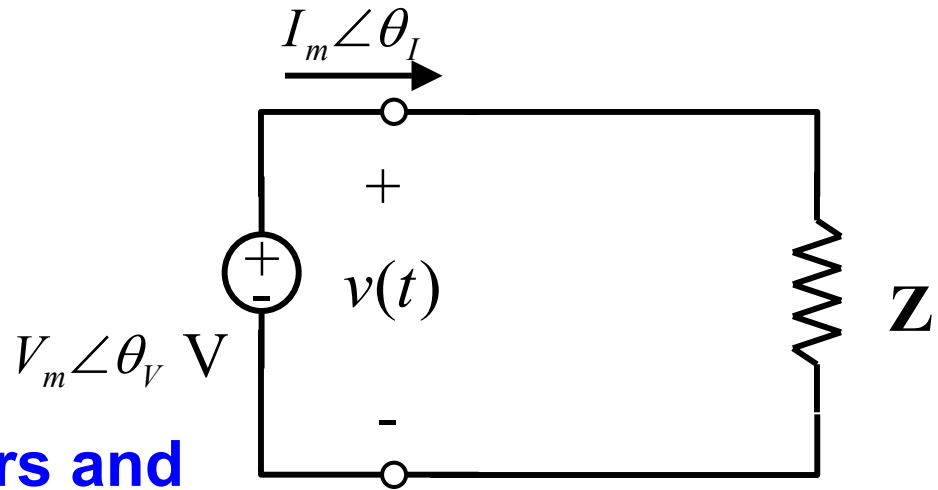
$$P_{avg} = \frac{1}{2} I_m^2 R \cos(0) = \frac{1}{2} I_m^2 R$$



Note that by using phasors and impedances we are implicitly assuming sinusoidal signals.

→ In the case of dc, the average power in a resistor is:

$$P_{dc} = i_{dc}^2 R$$

→ What is the **dc current** that produces the same average power as ac case?

$$\frac{I_m}{\sqrt{2}}$$

Root Mean Square

We define the **Effective** or **Root Mean Square (RMS)** value of a sinusoidal voltage or current waveform as the amplitude divided by the square root of 2:

$$I_{rms} = \frac{I_m}{\sqrt{2}} \qquad V_{rms} = \frac{V_m}{\sqrt{2}}$$

In this case, the average power in a general impedance is given by:

$$P_{avg} = \frac{I_m V_m}{2} \cos(\theta_V - \theta_I) = I_{rms} V_{rms} \cos(\theta_V - \theta_I)$$

$$P_{avg} = I_{rms}^2 Z \cos(\theta_Z)$$

$$P_{avg} = \frac{V_{rms}^2}{Z} \cos(\theta_Z)$$

RMS Value of a Periodic Waveform


1. We looked at the RMS or effective value of sinusoidal wave forms.
2. This is a useful way of comparing average power due to general periodic waveforms.

→ Consider the instantaneous power in a resistor:


$$p(t) = i^2(t)R$$

→ The average power is:
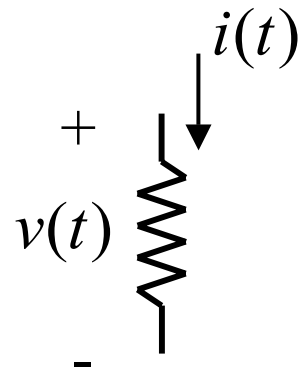
$$P_{avg} = \frac{1}{T} \int_0^T p(\tau) d\tau = \frac{1}{T} \int_0^T i^2(\tau) R d\tau$$



RMS Value of a Periodic Waveform
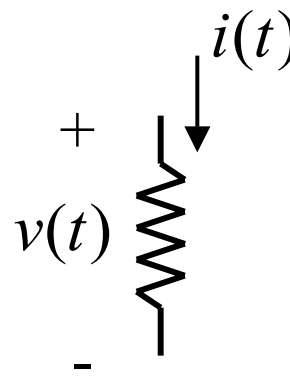
$$P_{avg} = \frac{1}{T} \int_0^T i^2(\tau) R d\tau = R \left[\frac{1}{T} \int_0^T i^2(\tau) d\tau \right] = RI_{rms}^2$$


The diagram shows a resistor symbol with a zigzag line. To its left, the voltage is labeled $v(t)$ with a '+' sign at the top and a '-' sign at the bottom. To its right, the current is labeled $i(t)$ with a downward-pointing arrow.

The *effective* value of the periodic waveform $i(t)$ is the dc current that results in the **same average power**:

$$I_{rms} = \sqrt{\frac{1}{T} \int_0^T i^2(\tau) d\tau}$$

The above quantity is the *root* of the *mean* of the *square* of $i(t)$ also known as the **Root Mean Square (RMS)** or effective value.

RMS Value of a Sine Wave


$$i(t) = I_m \cos(\omega t + \theta_I) \qquad T = \frac{2\pi}{\omega}$$

$$I_{rms} = \sqrt{\frac{1}{T} \int_0^T i^2(\tau) d\tau} = \sqrt{\frac{\omega}{2\pi} \int_0^{\frac{2\pi}{\omega}} I_m^2 \cos^2(\omega\tau + \theta_I) d\tau}$$

$$\text{Recall: } \cos^2(\alpha) = \frac{1}{2} + \frac{1}{2} \cos(2\alpha)$$

$$I_{rms} = I_m \sqrt{\frac{\omega}{2\pi} \int_0^{\frac{2\pi}{\omega}} \left[\frac{1}{2} + \frac{1}{2} \cos(2\omega\tau + 2\theta_I) \right] d\tau} = \frac{I_m}{\sqrt{2}}$$

RMS Example

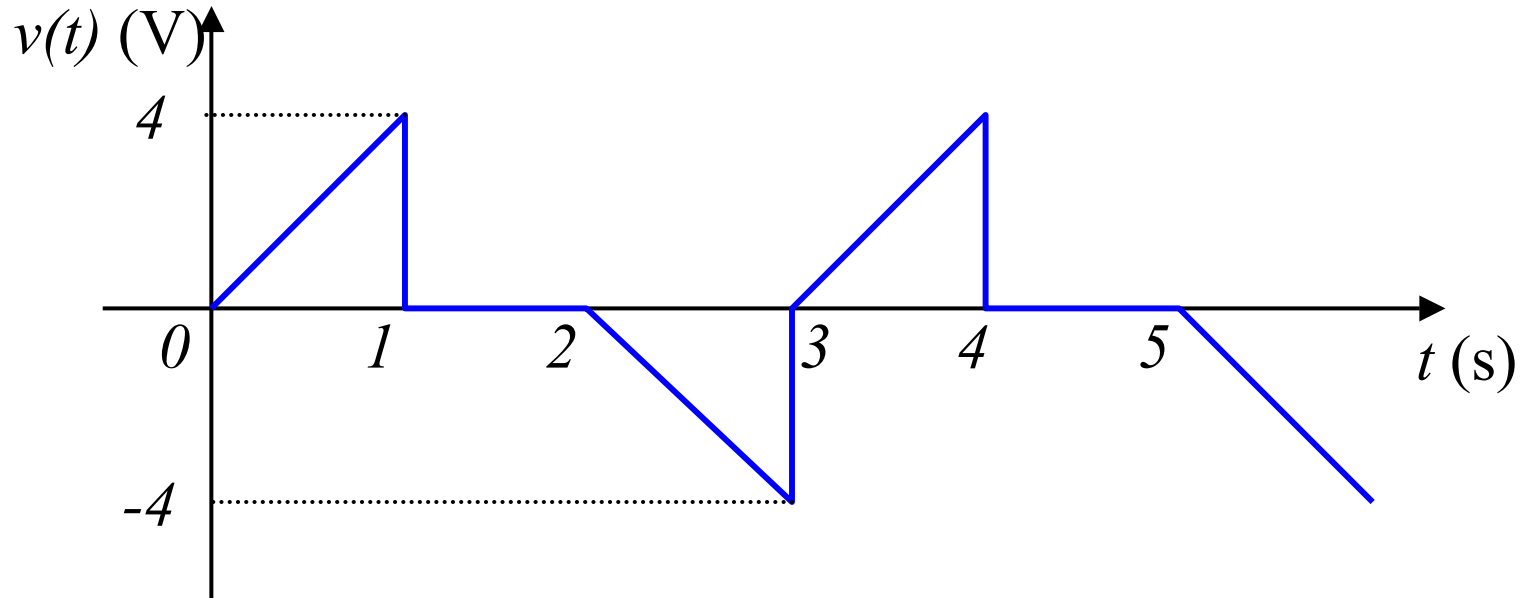

$$v(t) = \begin{cases} 4t \text{ V} & 0 < t \leq 1 \\ 0 \text{ V} & 1 < t \leq 2 \\ -4t+8 \text{ V} & 3 < t \leq 3 \end{cases}$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(\tau) d\tau}$$

RMS Example

Since

$$v(t) = \begin{cases} 4t \text{ V} & 0 < t \leq 1 \\ 0 \text{ V} & 1 < t \leq 2 \\ -4t + 8 \text{ V} & 2 < t \leq 3 \end{cases}$$

$$V_{rms} = \sqrt{\frac{1}{3} \left[\int_0^1 (4\tau)^2 d\tau + \int_1^2 (0)^2 d\tau + \int_2^3 (-4\tau + 8)^2 d\tau \right]}$$

$$V_{rms} = \sqrt{\frac{1}{3} \left[\frac{16t^3}{3} \Big|_0^1 + \left(64t - \frac{64t^2}{2} + \frac{16t^3}{3} \right) \Big|_2^3 \right]} = 1.89V$$

RMS Conclusion

- The RMS value of a periodic waveform is a **measure** to compare the *effectiveness* of sources in delivering power to a resistive load.
- The RMS or *effective* value of a waveform is the value of the *dc* waveform that supplies the same average power to a resistive load.
- In the case of sinusoidal waveforms, we have shown that the RMS value is given by:

$$i(t) = I_m \cos(\omega t + \theta_I)$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

RMS Phasor

$$\mathbf{V}_{\text{rms}} = \frac{V_m}{\sqrt{2}} \angle \theta_V$$

$$\mathbf{I}_{\text{rms}} = \frac{I_m}{\sqrt{2}} \angle \theta_I$$


$$V_m \angle \theta_V = (I_m \angle \theta_I)(Z \angle \theta_Z) = I_m Z \angle (\theta_I + \theta_Z)$$

$$V_{\text{rms}} \angle \theta_V = (I_{\text{rms}} \angle \theta_I)(Z \angle \theta_Z) = I_{\text{rms}} Z \angle (\theta_I + \theta_Z)$$


→ Note: The impedance is still the same!

→ Example: Find the RMS phasor of: $v(t) = 4 \cos(4t + 30^\circ)$
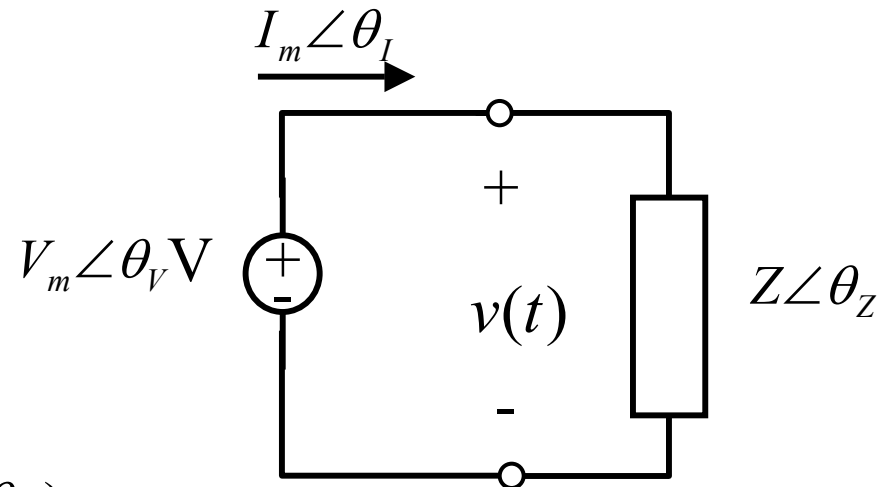
$$\mathbf{V}_{\text{rms}} = V_{\text{rms}} \angle \theta_v = \frac{4}{\sqrt{2}} \angle 30^\circ$$



AC Steady-State Power

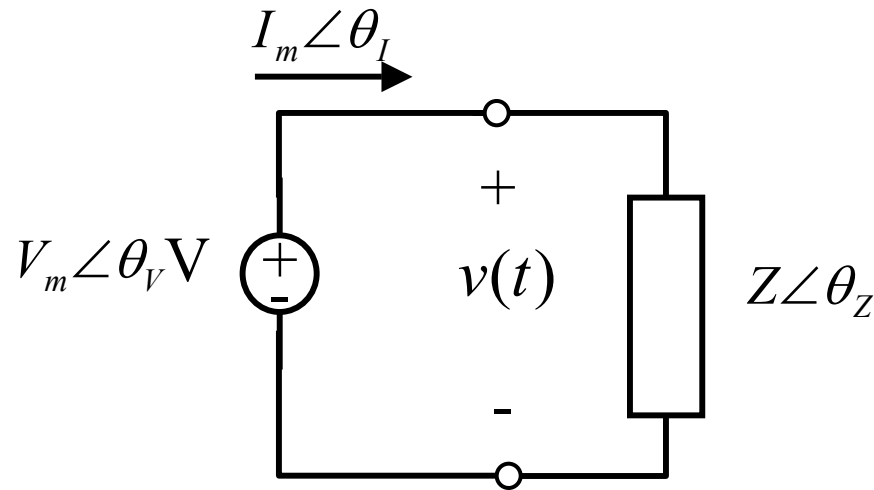

$$P_{avg} = \frac{I_m V_m}{2} \cos(\theta_V - \theta_I)$$

$$P_{avg} = \frac{1}{2} I_m^2 Z \cos(\theta_Z)$$

$$P_{avg} = \frac{1}{2} \frac{V_m^2}{Z} \cos(\theta_Z)$$

$$P_{avg} = I_{rms} V_{rms} \cos(\theta_V - \theta_I)$$

$$P_{avg} = I_{rms}^2 Z \cos(\theta_Z)$$

$$P_{avg} = \frac{V_{rms}^2}{Z} \cos(\theta_Z)$$