

ECSE 210: Circuit Analysis

Lecture #15:

Steady State Power Analysis

AC Steady-State Power

Recall:

$$V_{rms} \angle \theta_V = (I_{rms} \angle \theta_I)(Z \angle \theta_Z) = I_{rms} Z \angle (\theta_I + \theta_Z)$$

$$\theta_Z = \theta_V - \theta_I$$


$$P_{avg} = I_{rms} V_{rms} \cos(\theta_V - \theta_I)$$

$$P_{avg} = I_{rms} V_{rms} \cos(\theta_Z)$$

$$P_{avg} = I_{rms}^2 Z \cos(\theta_Z) \quad P_{avg} = \frac{V_{rms}^2}{Z} \underbrace{\cos(\theta_Z)}$$

power factor
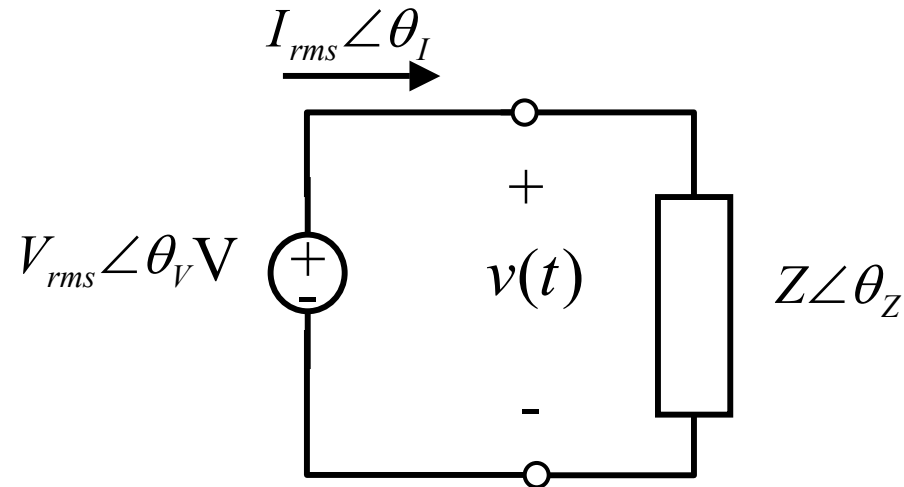
$$\text{power factor} = \cos(\theta_Z) = \cos(\theta_V - \theta_I)$$



Complex Power


$$\mathbf{V}_{\text{rms}} = V_{\text{rms}} \angle \theta_V \quad \mathbf{Z} = Z \angle \theta_Z$$

$$\mathbf{I}_{\text{rms}} = I_{\text{rms}} \angle \theta_I$$

$$\mathbf{I}_{\text{rms}}^* = I_{\text{rms}} \angle -\theta_I$$

Define complex power as:
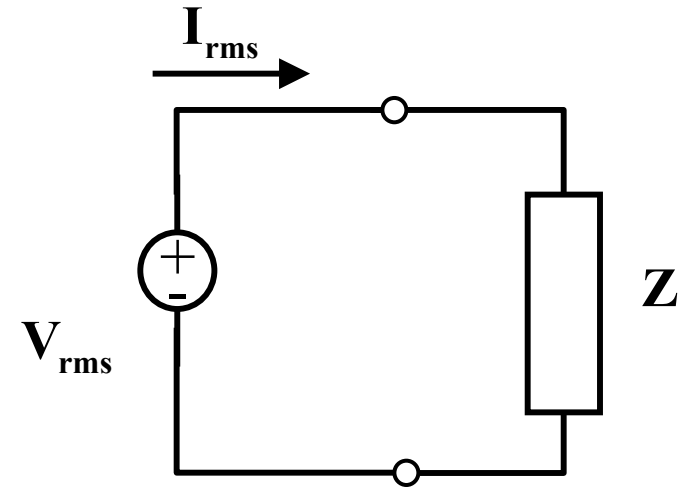
$$\mathbf{S} = \mathbf{V}_{\text{rms}} \mathbf{I}_{\text{rms}}^*$$



$$\begin{aligned} \mathbf{S} = \mathbf{V}_{\text{rms}} \mathbf{I}_{\text{rms}}^* &= V_{\text{rms}} I_{\text{rms}} \angle (\theta_V - \theta_I) = V_{\text{rms}} I_{\text{rms}} e^{j(\theta_V - \theta_I)} \\ &= \underbrace{V_{\text{rms}} I_{\text{rms}} \cos(\theta_V - \theta_I)}_{P_{\text{avg}}} + j V_{\text{rms}} I_{\text{rms}} \sin(\theta_V - \theta_I) \end{aligned}$$

P_{avg}

AC Steady-State Power


Complex power:

$$\mathbf{S} = \mathbf{V}_{\text{rms}} \mathbf{I}_{\text{rms}}^* \quad \longrightarrow \quad P_{\text{avg}} = \text{Re}[\mathbf{S}]$$

$$\mathbf{V}_{\text{rms}} = \mathbf{Z} \mathbf{I}_{\text{rms}}$$

$$\mathbf{S} = \mathbf{Z} \mathbf{I}_{\text{rms}} \mathbf{I}_{\text{rms}}^* = \mathbf{Z} |\mathbf{I}_{\text{rms}}|^2 = \mathbf{Z} I_{\text{rms}}^2$$
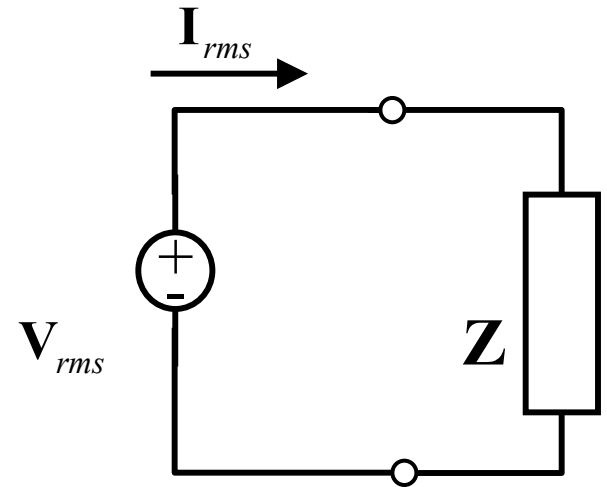
$$P_{\text{avg}} = \text{Re}[\mathbf{S}] = \text{Re}[\mathbf{Z}] I_{\text{rms}}^2 = I_{\text{rms}}^2 Z \cos(\theta_z)$$




Nomenclature/Conventions

$$\mathbf{S} = \mathbf{V}_{\text{rms}} \mathbf{I}_{\text{rms}}^* = V_{\text{rms}} I_{\text{rms}} \angle(\theta_V - \theta_I)$$

$$\theta_V - \theta_I = \theta_Z$$

$$\mathbf{S} = P + jQ$$

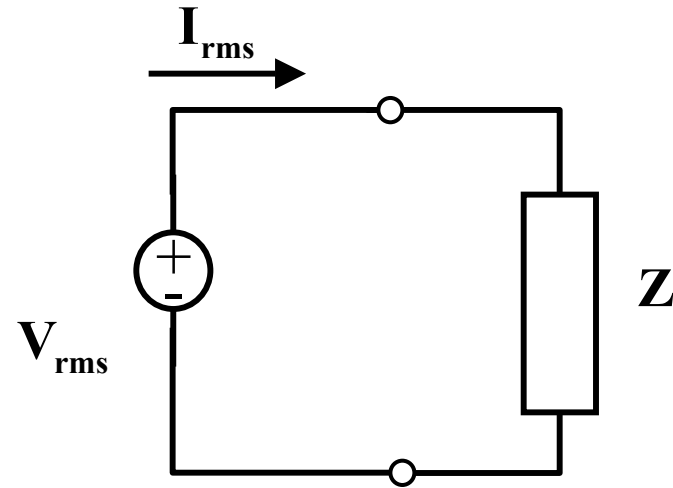

- \mathbf{S} is a complex number.
- The magnitude of \mathbf{S} is the *apparent power*.
(Units: volt-ampere VA or kVA)
- The angle of \mathbf{S} is the *power factor angle*.
- The real part of \mathbf{S} is the *average power*. (Units: watts)
- The imaginary part of \mathbf{S} is the *reactive power*.
(Units: volt-ampere reactive (VAR))

Example

$$\mathbf{V}_{rms} = \frac{10}{\sqrt{2}} \angle 0^\circ = 7.07 \angle 0^\circ \text{ V}$$

$$10 \cos(10^4 t) \text{ V}$$


$$\mathbf{Z} = 50 + j10^4(12 \times 10^{-3}) = 50 + j120 \Omega$$

$$\mathbf{I}_{rms} = \frac{\mathbf{V}_{rms}}{\mathbf{Z}}$$

$$\mathbf{I}_{rms} = \frac{7.07 \angle 0^\circ}{130 \angle 67.38^\circ} = 54.4 \angle -67.38^\circ \text{ mA}$$

$$\mathbf{S} = \mathbf{V}_{rms} \mathbf{I}_{rms}^* = (7.07 \angle 0^\circ \text{ V})(54.4 \angle 67.38^\circ \text{ mA}) = 0.385 \angle 67.38^\circ \text{ VA}$$
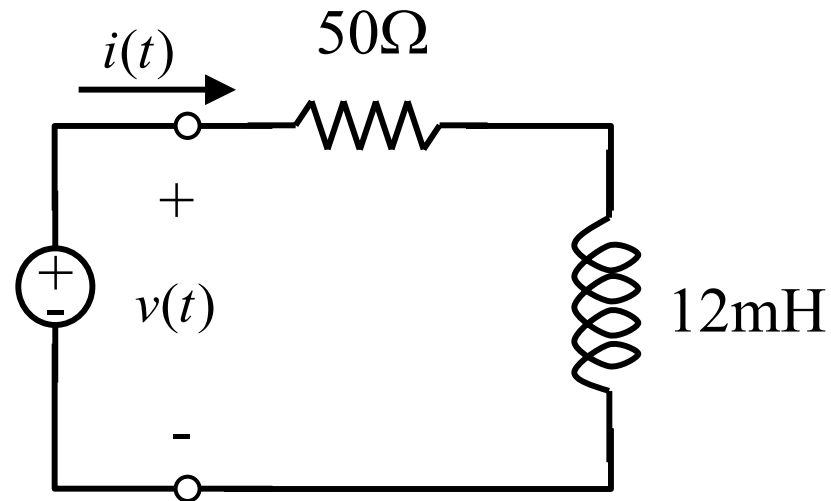
$$\mathbf{S} = \mathbf{V}_{rms} \mathbf{I}_{rms}^* = 0.385 \cos(67.38^\circ) + j0.385 \sin(67.38^\circ) = 0.15 + 0.36j$$



Example

$$\mathbf{S} = \mathbf{V}_{\text{rms}} \mathbf{I}_{\text{rms}}^* = 0.385 \angle 67.38^\circ = 0.15 + 0.36j$$

Apparent power

$$S = 0.385 \text{ VA}$$

Average power


$$P = 0.15 \text{ W}$$

Reactive power

$$Q = 0.36 \text{ VAR}$$

Power factor angle

$$= 67.38^\circ$$

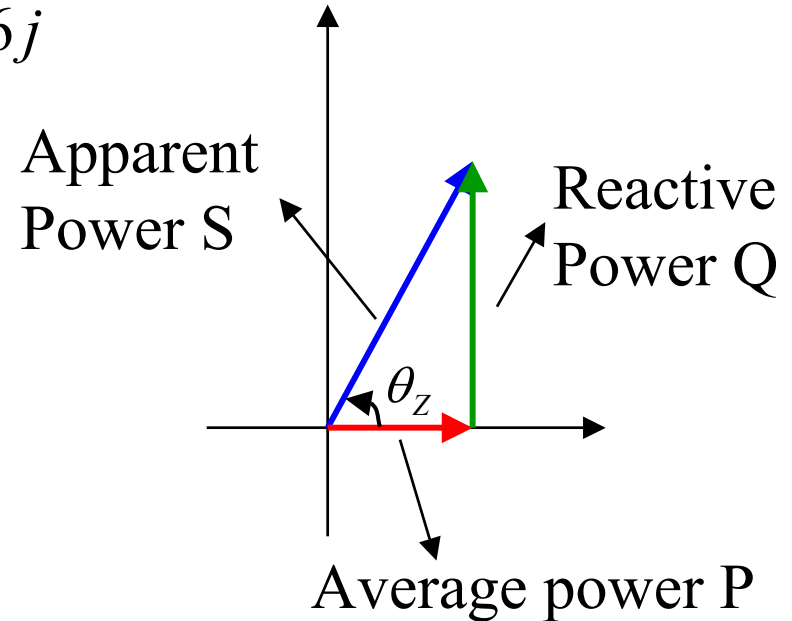


Power triangle

Power Factor

$$P_{avg} = I_{rms} V_{rms} \cos(\theta_V - \theta_I) = I_{rms} V_{rms} \cos(\theta_Z)$$

$$\text{power factor} = \frac{\text{Average power}}{\text{Apparent power}}$$
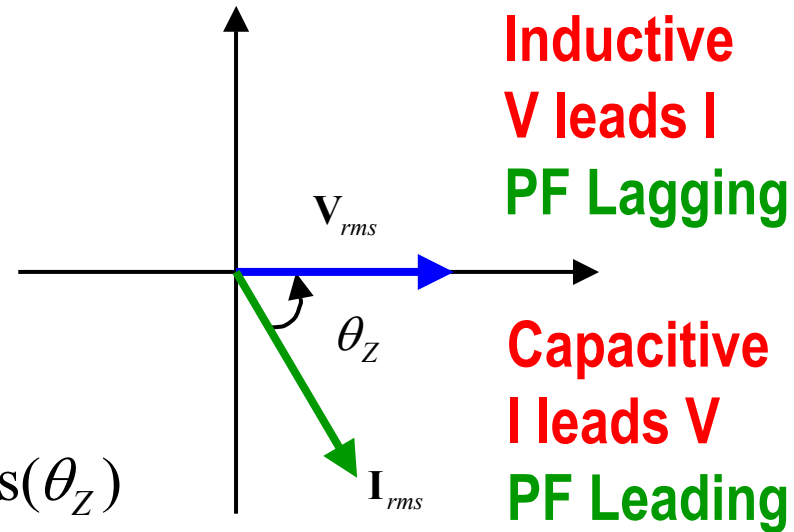
$$\text{power factor} = \frac{P_{avg}}{I_{rms} V_{rms}} = \cos(\theta_V - \theta_I) = \cos(\theta_Z)$$



- For an inductive load, the current lags the voltage and we have a **lagging power factor**.
- For a capacitive load the current leads the voltage and we have a **leading power factor**.
- **It is the current that lags and leads not the power factor!**
- For a purely resistive load the power factor is 1.
- For a purely reactive load the power factor is 0.

Power Factor

Case Study:

An industrial load consumes 50kW at a pf of 0.8 lagging, from a 220V (rms), 60Hz line.

What can we conclude?

→ Lagging pf → Current is lagging.

$$\rightarrow P_{avg} = I_{rms} V_{rms} \times pf = I_{rms} (220V)(0.8) = 50000W$$

$$\rightarrow I_{rms} = \frac{50000W}{(220V)(0.8)} = 284.1A$$

$$\rightarrow \cos(\theta_V - \theta_I) = 0.8 \quad \rightarrow \quad |\theta_V - \theta_I| = 36.9^\circ$$

Power Factor

Given: $V_{\text{rms}} = 220 \angle 0^\circ V$ and **lagging** current

→ $I_{\text{rms}} = 284.1 \angle -36.9^\circ A$ and $|\theta_V - \theta_I| = 36.9^\circ$


V leads I

→ The impedance of the load is:

$$Z_L = \frac{V_{\text{rms}}}{I_{\text{rms}}} = \frac{220}{284.1 \angle -36.9^\circ} = 0.774 \angle 36.9^\circ \Omega$$

**Inductive
Impedance**

Power Factor

$$\mathbf{V}_{\text{rms}} = 220 \angle 0^\circ V \quad \mathbf{I}_{\text{rms}} = 284.1 \angle -36.9^\circ A \quad P_{\text{avg}} = 50 \text{ kW}$$

→ **What is the problem with the situation above?**

→ How much current is required to supply the same power to a purely resistive load (pf=1) ?

$$P_{\text{avg}} = 50 \text{ kW} = V_{\text{rms}} I_{\text{rms}} = 220 I_{\text{rms}} \quad \rightarrow \quad I_{\text{rms}} = 227.3 A$$

→ **A resistive load requires much less current.**

→ This means less resistive losses (I^2R) in the transmission lines.

→ The large current in the reactive case (e.g., pf=0.8) results from the transfer of energy back and forth from the source to the load and vice versa.

Power Factor Correction

→ Suppose we wish to raise the power factor of the plant from 0.8 lagging to 0.95 lagging.

→ $Z = 0.774 \angle 36.9^\circ \Omega$

→ $Y = \frac{1}{Z} = 1.29 \angle -36.9^\circ S$

$Y = 1.03 - j0.775 S$


→ Existing pf:

$$pf = \cos(36.9^\circ) = 0.8$$

→ Desired pf:

$$pf = \cos(\theta_{new}^\circ) = 0.95$$

→ **Add parallel capacitor**

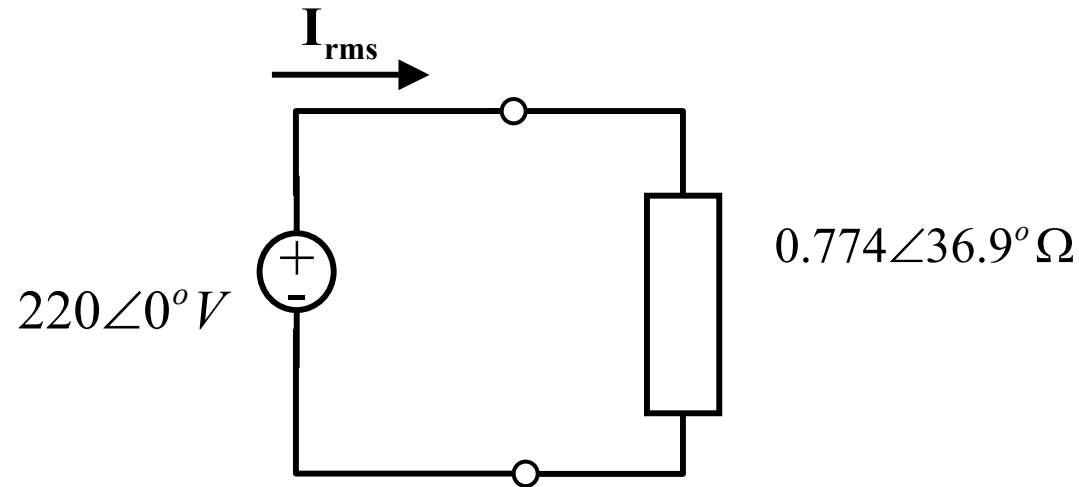

Power Factor Correction

$$Y_{new} = 1.03 + j(B_c - 0.775)$$



$$pf_{new} = \cos(\theta_{new}^{\circ}) = 0.95$$

$$\theta_{new}^{\circ} = -18.19^{\circ}$$

$$\tan(\theta_{new}^{\circ}) = \frac{B_c - 0.775}{1.03} = -0.323$$

$$B_c = 0.437S = \omega C = (2\pi \times 60)C$$


$$C = 1158\mu F$$

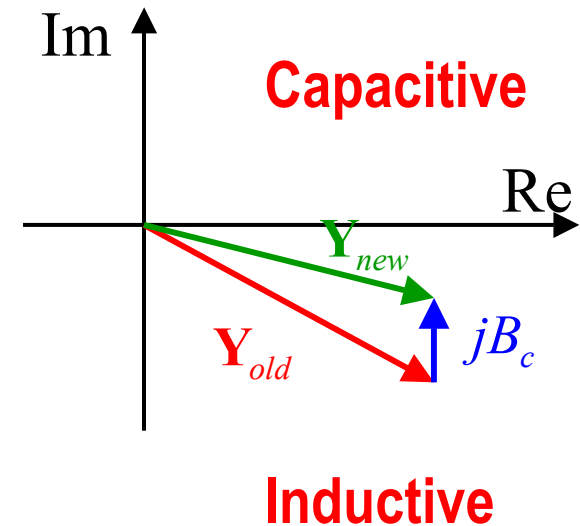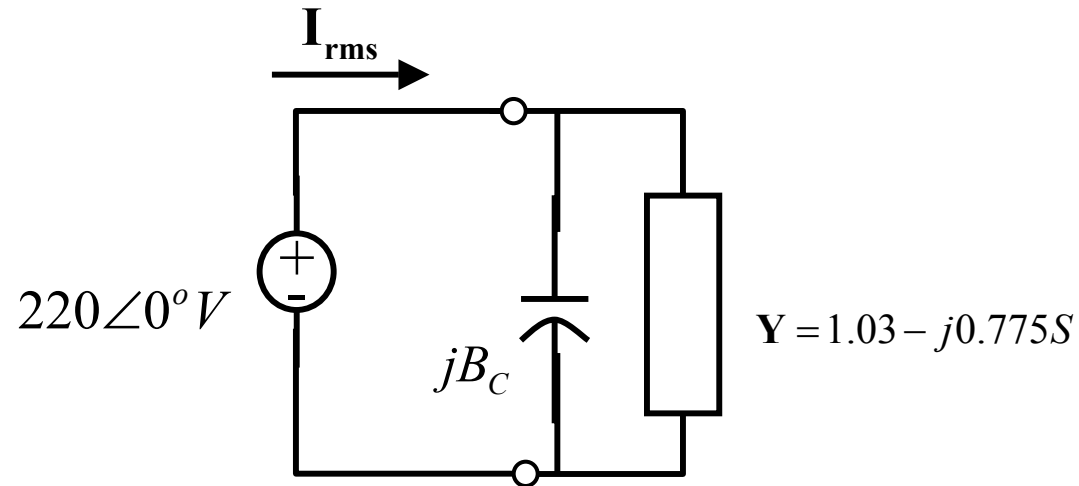

Maximum Average Power Transfer

Recall:

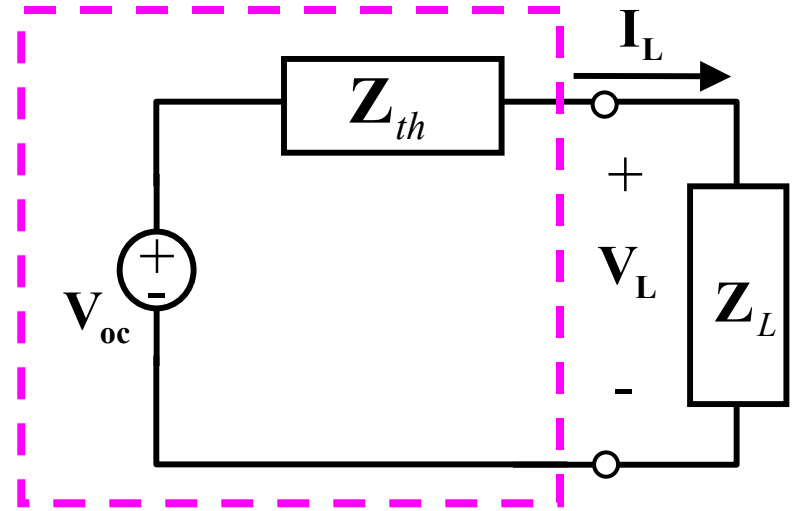For resistive circuits, maximum power transfer occurs when the load R_L is set to the **Thevenin equivalent resistance of the remainder of the circuit.**



- What is the relation between Z_{th} and Z_L which yields the *maximum average power transfer* to the load Z_L ?
- In the above circuit, V_{oc} is the RMS source voltage phasor, V_L is the RMS voltage phasor at the load, and I_L is the RMS current phasor.

Maximum Average Power Transfer


$$\mathbf{Z}_{th} = R_{th} + jX_{th} \quad \mathbf{Z}_L = R_L + jX_L$$

$$\mathbf{V}_{oc} = V_{oc} \angle \theta_{oc}$$

$$\mathbf{I}_L = \frac{\mathbf{V}_{oc}}{\mathbf{Z}_{th} + \mathbf{Z}_L}$$

$$\mathbf{V}_L = \frac{\mathbf{Z}_L}{\mathbf{Z}_{th} + \mathbf{Z}_L} \mathbf{V}_{oc}$$
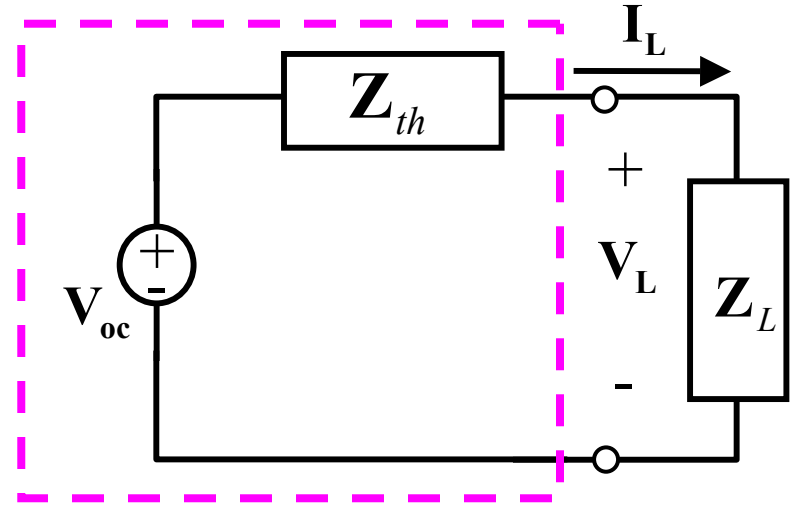
$$\mathbf{S} = \mathbf{V}_L \mathbf{I}_L^* = \frac{\mathbf{Z}_L}{(\mathbf{Z}_{th} + \mathbf{Z}_L)} \frac{1}{(\mathbf{Z}_{th} + \mathbf{Z}_L)^*} \mathbf{V}_{oc} \mathbf{V}_{oc}^*$$



Maximum Average Power Transfer

$$\mathbf{Z}_{th} = R_{th} + jX_{th} \quad \mathbf{Z}_L = R_L + jX_L \quad \mathbf{V}_{oc} = V_{oc} \angle \theta_{oc}$$

$$\mathbf{S} = \mathbf{V}_L \mathbf{I}_L^* = \frac{\mathbf{Z}_L}{(\mathbf{Z}_{th} + \mathbf{Z}_L)(\mathbf{Z}_{th} + \mathbf{Z}_L)^*} \mathbf{V}_{oc} \mathbf{V}_{oc}^*$$

$$\mathbf{V}_{oc} \mathbf{V}_{oc}^* = V_{oc}^2$$

$$\mathbf{Z}_{th} + \mathbf{Z}_L = R_{th} + R_L + j(X_{th} + X_L)$$

$$(\mathbf{Z}_{th} + \mathbf{Z}_L)(\mathbf{Z}_{th} + \mathbf{Z}_L)^* = (R_{th} + R_L)^2 + (X_{th} + X_L)^2$$

$$\mathbf{S} = \frac{R_L + jX_L}{(R_{th} + R_L)^2 + (X_{th} + X_L)^2} V_{oc}^2$$

$$P_{avg} = \text{Re}[\mathbf{S}] = \frac{R_L V_{oc}^2}{(R_{th} + R_L)^2 + (X_{th} + X_L)^2}$$

Maximum Average Power Transfer

$$P_{avg} = \text{Re}[\mathbf{S}] = \frac{R_L V_{oc}^2}{(R_{th} + R_L)^2 + (X_{th} + X_L)^2}$$

Maximize the power: $X_L = -X_{th}$

$$P_{avg} = \text{Re}[\mathbf{S}] = \frac{R_L V_{oc}^2}{(R_{th} + R_L)^2}$$


$$\frac{dP_{avg}}{dR_L} = \left(\frac{1}{(R_{th} + R_L)^2} - \frac{2R_L}{(R_{th} + R_L)^3} \right) V_{oc}^2 = \frac{R_{th} - R_L}{(R_{th} + R_L)^3} V_{oc}^2$$

Maximum power occurs at: $R_L = R_{th}$

$$\mathbf{Z}_L = R_{th} - jX_{th} = \mathbf{Z}_{th}^*$$

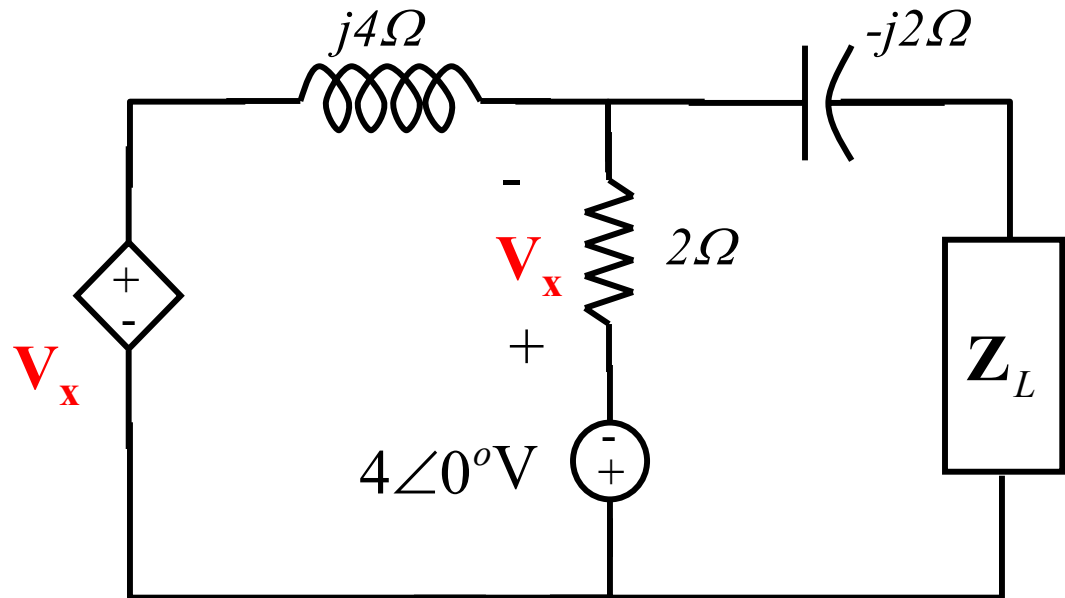Example

Find the value of Z_L for maximum average power transfer. Then find the average power delivered to Z_L .



→ First find the Thevenin equivalent of the circuit seen from the terminals of Z_L .

Example

→ Thevenin equivalent of the circuit seen from the terminals of Z_L .

KVL


$$-V_x + j4I_1 - V_x - \frac{4}{\sqrt{2}} = 0$$

Also: $V_x = -2I_1$

$$-2V_x - j2V_x = \frac{4}{\sqrt{2}}$$

$$V_x = 1\angle 135^\circ V$$
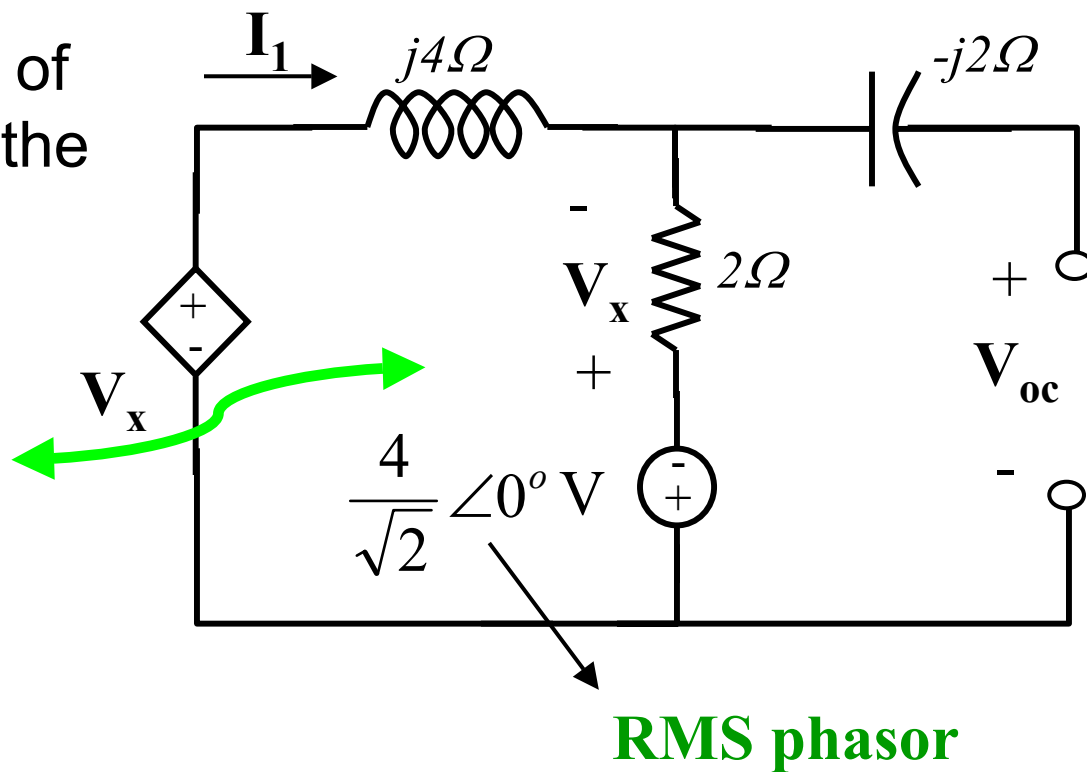
$$V_{oc} = -\left(1\angle 135^\circ + \frac{4}{\sqrt{2}}\right) = -2.24\angle 18.43^\circ V = \frac{-3-j}{\sqrt{2}} \text{ V rms}$$



Example

Find Thevenin impedance:


$$-\mathbf{V}_x + j4\mathbf{I}_1 + 2(\mathbf{I}_1 - \mathbf{I}_{sc}) - \frac{4}{\sqrt{2}} = 0$$

$$\frac{4}{\sqrt{2}} + 2(\mathbf{I}_{sc} - \mathbf{I}_1) - j2\mathbf{I}_{sc} = 0$$

$$\mathbf{V}_x = -2(\mathbf{I}_1 - \mathbf{I}_{sc})$$

$$\rightarrow \mathbf{I}_{sc} = -\frac{(1 + 2j)}{\sqrt{2}}$$
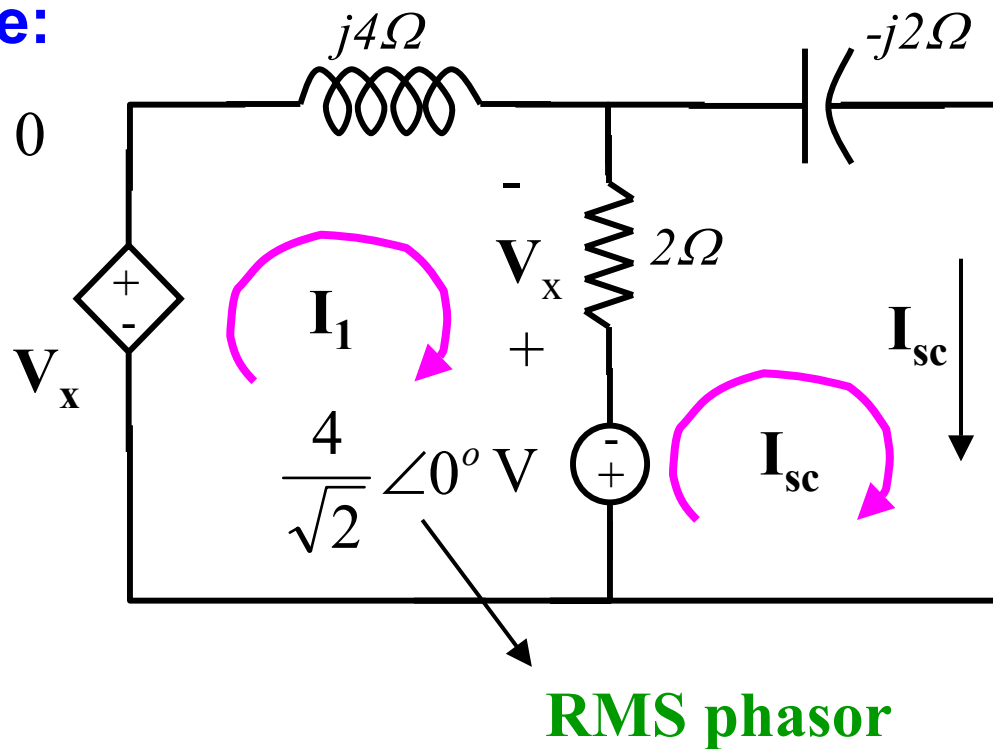
$$\mathbf{Z}_{th} = \frac{\mathbf{V}_{oc}}{\mathbf{I}_{sc}} = \frac{\frac{3 + j}{\sqrt{2}}}{\frac{(1 + 2j)}{\sqrt{2}}} = 1 - j\Omega$$



Example

$$\mathbf{V}_{oc} = -2.24 \angle 18.43^\circ \text{ V rms}$$

$$\mathbf{Z}_{th} = 1 - j = \sqrt{2} \angle -45^\circ \Omega$$


For maximum average power transfer:

$$\mathbf{Z}_L = \mathbf{Z}_{th}^* = 1 + j = \sqrt{2} \angle 45^\circ \Omega$$

$$\mathbf{I}_L = \frac{-2.24 \angle 18.43^\circ}{2} = -1.118 \angle 18.43^\circ \text{ A}$$

$$\mathbf{V}_L = \mathbf{I}_L \mathbf{Z}_L \quad \mathbf{S} = \mathbf{I}_L^* \mathbf{V}_L = \mathbf{I}_L \mathbf{I}_L^* \mathbf{Z}_L = (1.118)^2 (1 + j)$$
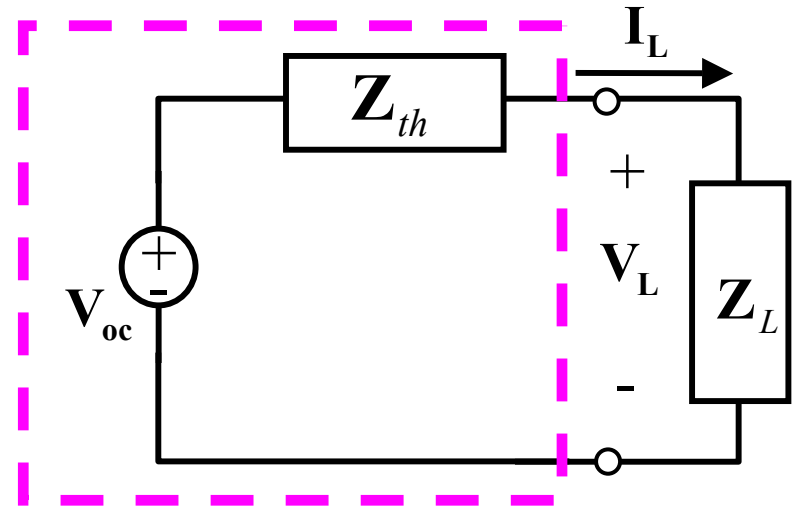
$$P_{avg} = \text{Re}[\mathbf{S}] = (1.118)^2 = 1.25 \text{ W}$$



Superposition and Power

Consider the following dc circuit:

We can use superposition to find v_1 .


☆ v_1 due to first source alone:

$$v_1' = \frac{2\Omega \parallel 2\Omega}{2\Omega \parallel 2\Omega + 2\Omega} 3 = 1V$$

🕒 v_1 due to second source alone:

$$v_1'' = \frac{2\Omega \parallel 2\Omega}{2\Omega \parallel 2\Omega + 2\Omega} 3 = 1V$$

Total voltage: $v_1 = v_1' + v_1'' = 2V$

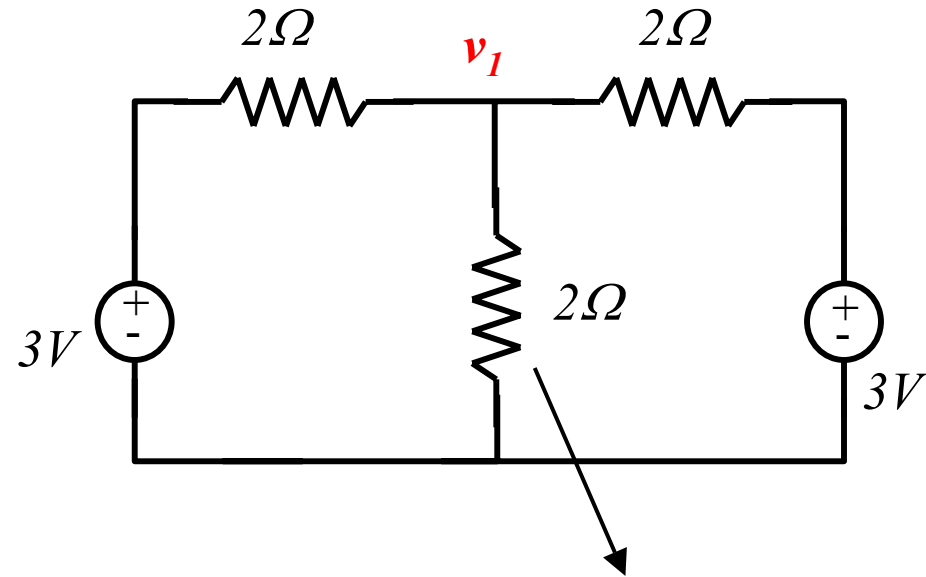

Calculate power dissipated in this resistor.

Power: $P = \frac{v_1^2}{R} = 2W$

Superposition and Power

Consider the same dc circuit again:

Try superposition directly on power.

Power due to first source alone

$$P_1 = \frac{(1)^2}{2} = 0.5W \quad V_I = 1$$

Power due to second source alone


$$P_2 = \frac{(1)^2}{2} = 0.5W \quad V_I = 1$$

Total power:

$$P = P_1 + P_2 = 1W$$



Wrong answer!!!

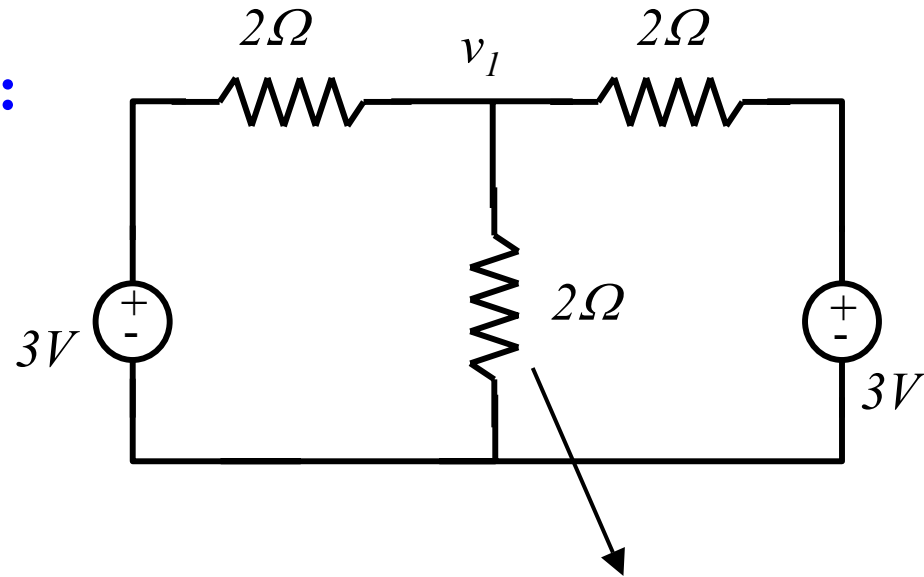

**Calculate power
dissipated in this resistor.**

Superposition and Power

1. In general we cannot apply the superposition principle directly to determine the power.
2. One can show that **power superposition** works for sources of **different frequencies**, but we will not worry about this here.
3. **Do not apply superposition directly to calculate the power!**