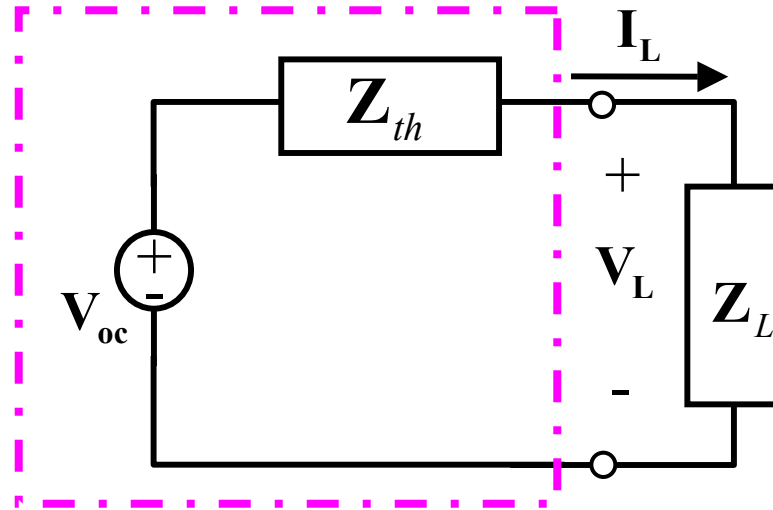


ECSE 210: Circuit Analysis

Lecture#16:



Steady State Power Analysis

Maximum Average Power Transfer




- The maximum power transfer from a source with a Thevenin impedance Z_{th} to a load Z_L occurs when Z_L is the **complex conjugate** of Z_{th} .
- In the above case, the source and load impedances are said to be matched.
- Is it possible to “correct” an impedance mismatch?

Example

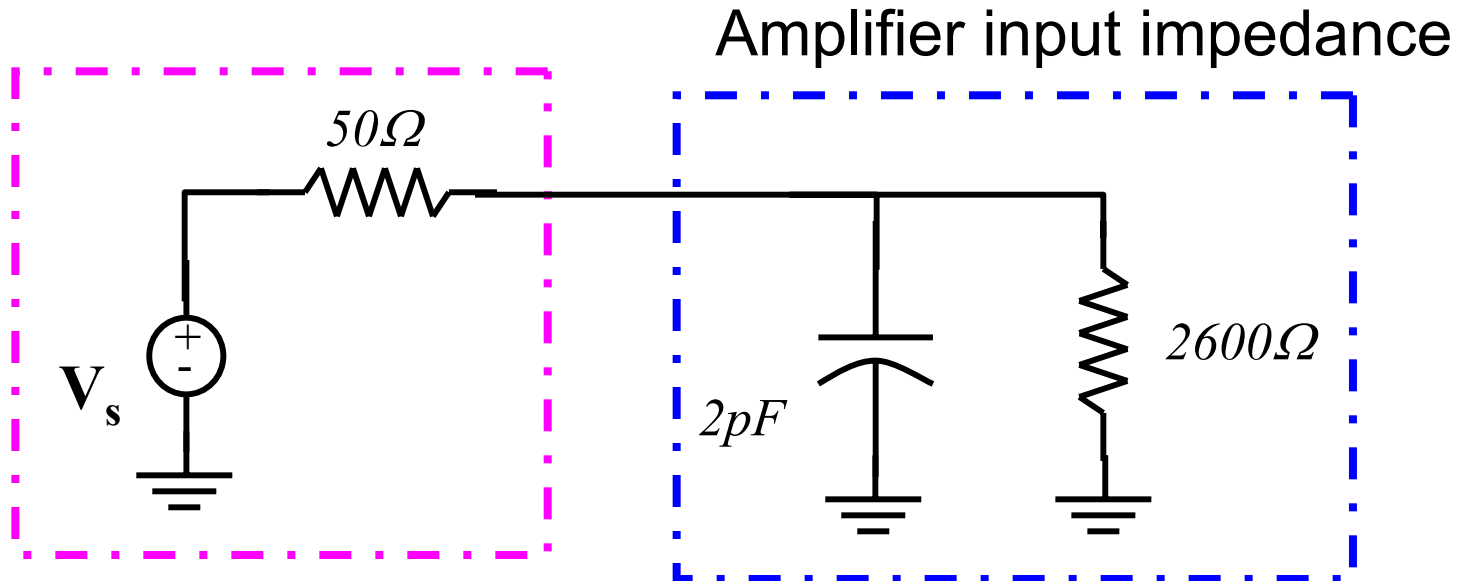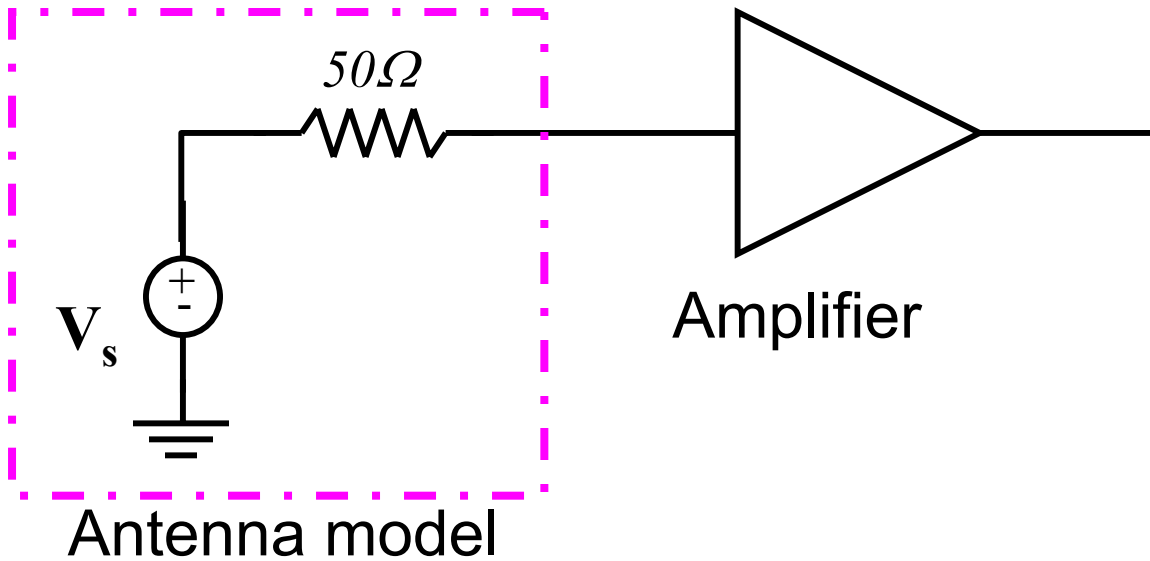

Example

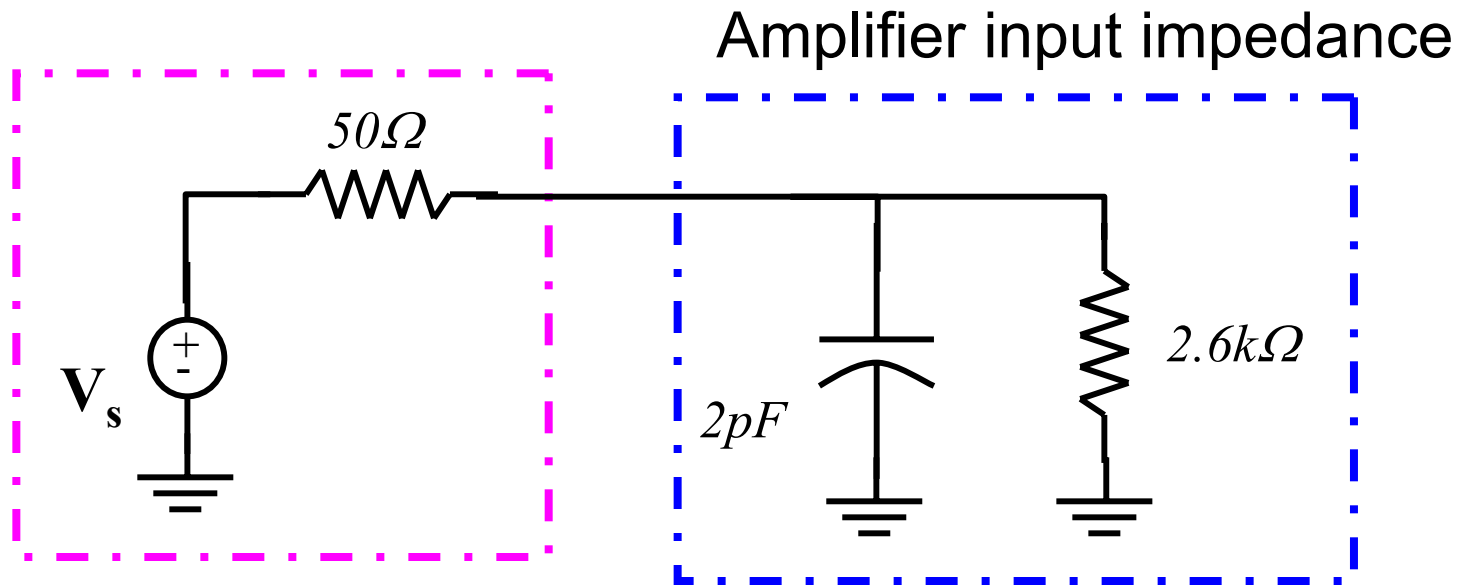


- If the circuit is operating at **$f = 1\text{ GHz}$** , what is the average power supplied to the amplifier?
- At 1 GHz, the input impedance of the amplifier is:

$$\mathbf{Z}_L = \left(\frac{1}{2600} + j(2\pi \times 1 \times 10^9 \times 2 \times 10^{-12}) \right)^{-1} = 2.43 - j79.5\Omega$$

capacitive load

$$\mathbf{Z}_L = 79.54 \angle -88.25^\circ \Omega$$

Example

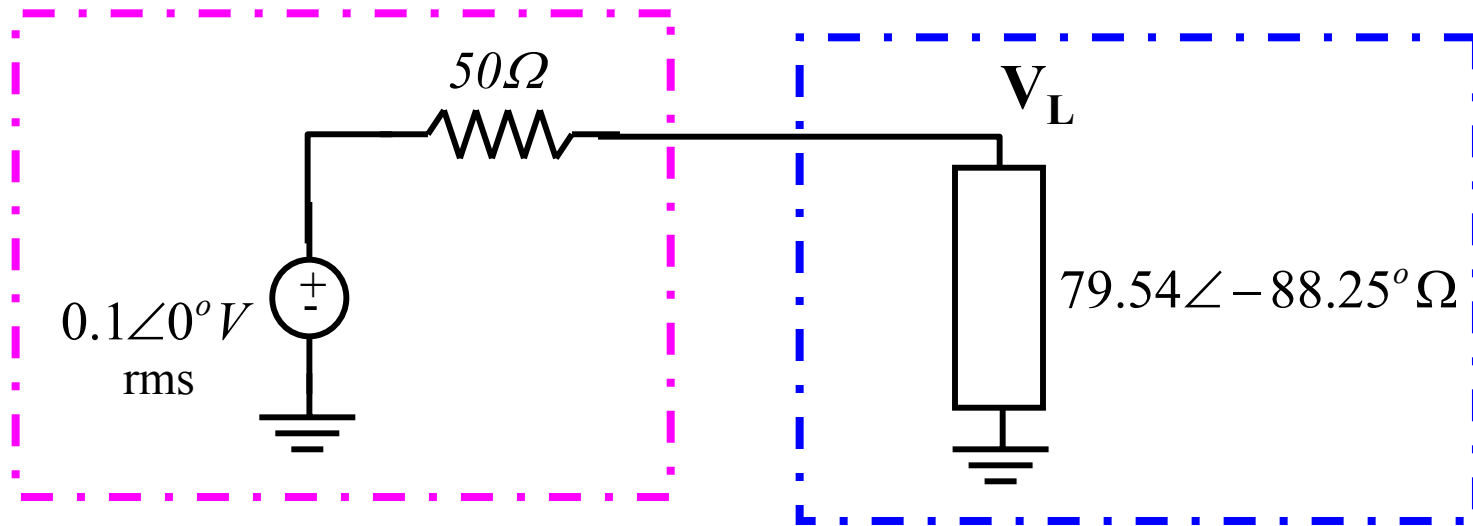


$$V_L = \frac{79.54\angle -88.25^\circ \Omega}{79.54\angle -88.25^\circ \Omega + 50\Omega} 0.1\angle 0^\circ = 83.52\angle -31.65^\circ mV$$

$$I_L = \frac{83.52\angle -31.65^\circ mV}{79.54\angle -88.25^\circ \Omega} = 1.05\angle 56.59^\circ mA$$

$$S = V_L I_L^* = (83.52\angle -31.65^\circ mV)(1.05\angle -56.59^\circ mA) = 87.7\angle -88.25^\circ \mu VA$$

$$P_{avg} = \text{Re}[S] = 2.68\mu W$$

Example

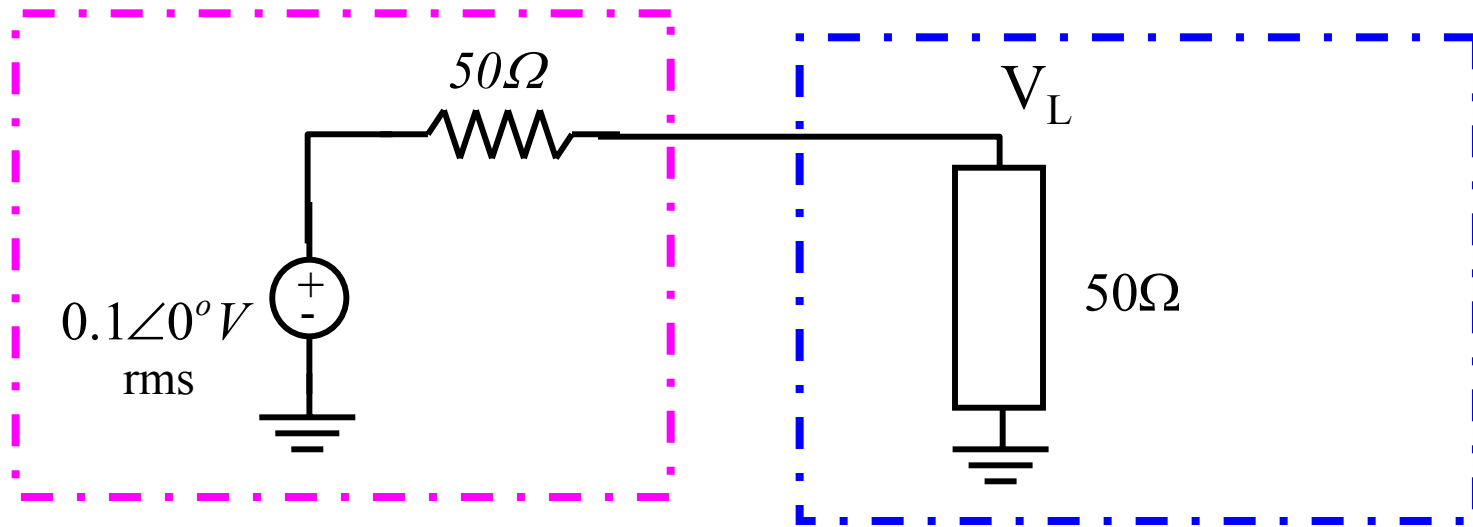

- What is the maximum power that the source can supply to the load?
- Maximum power is delivered when the impedances are matched (complex conjugates).


$$V_L = \frac{50}{50 + 50} 0.1\angle 0^\circ V = 0.05\angle 0^\circ V$$

$$I_L = \frac{0.05\angle 0^\circ V}{50} = 1\angle 0^\circ mA$$

$$S = (1\angle 0^\circ mA)(0.05\angle 0^\circ V) = 50 \times 10^{-6} \angle 0^\circ VA$$

$$P_{avg} = 50 \mu W$$

Impedance Matching

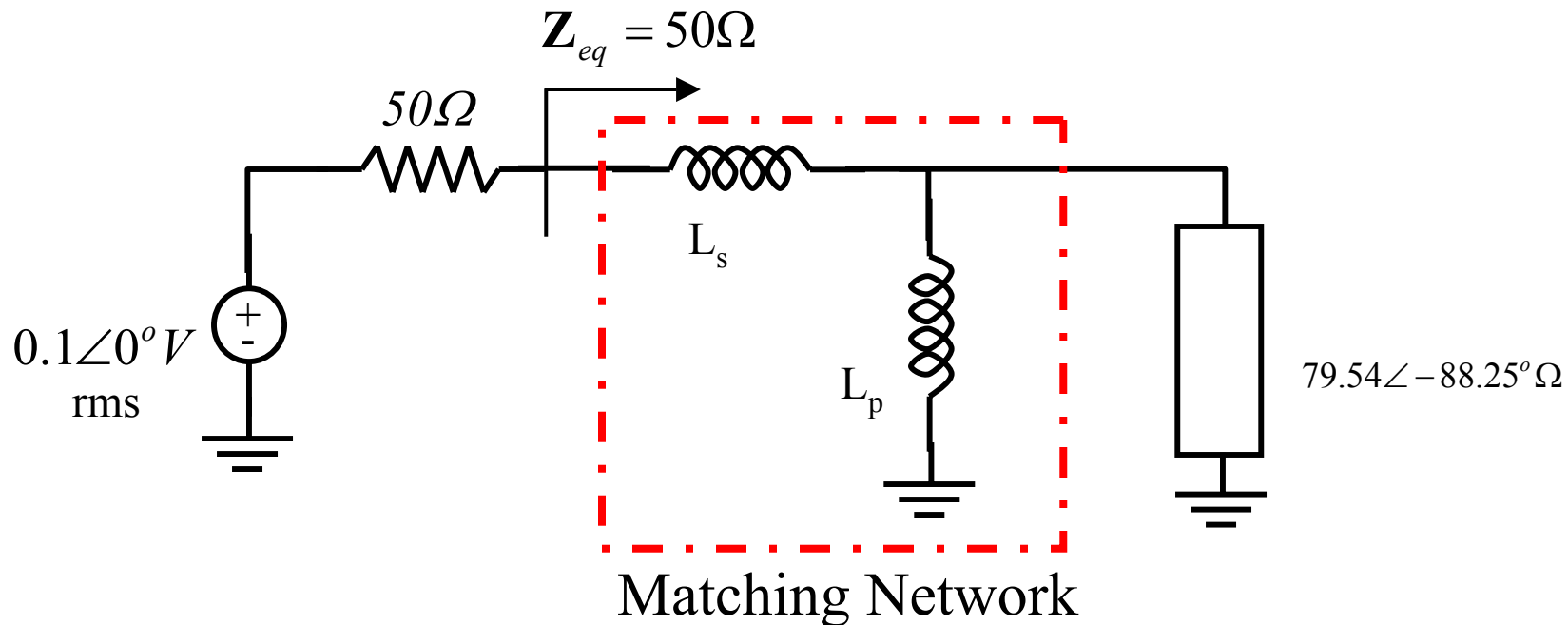


Add a matching network to transform the load impedance, such that the impedance Z_{eq} “seen” by the source is 50Ω .

Impedance Matching: Strategy

- Choose the value of the first inductor such that the parallel combination of the inductor and load results in an impedance of the form:

$$\mathbf{Z}_1 = 50 + jX_1 \Omega$$

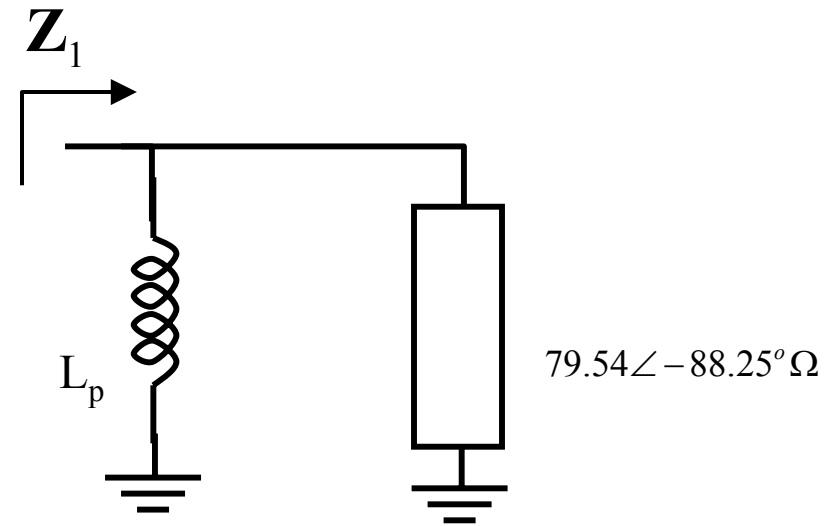


- The above impedance should have a real part of 50Ω and a **negative reactive part** (capacitive).
- Now choose the value of the series inductor to **cancel** the reactive component of the above impedance.

Impedance Matching: Strategy

$$\mathbf{Z}_L = 79.54 \angle -88.25^\circ \Omega$$

$$\mathbf{Y}_L = \frac{1}{79.54 \angle -88.25^\circ \Omega} = 0.384 + j12.57 \text{ mS}$$
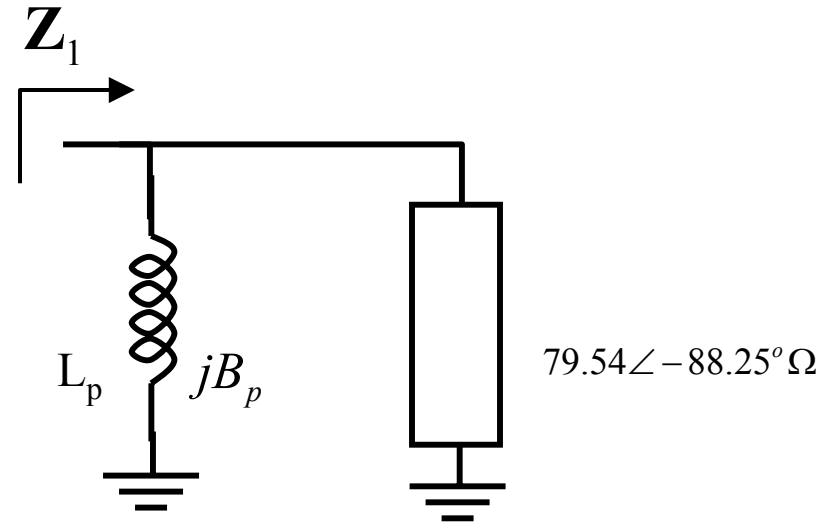
$$\mathbf{Y}_1 = 0.384 \times 10^{-3} + j(12.57 \times 10^{-3} + B_p)$$




$$\mathbf{Z}_1 = \frac{1}{0.384 \times 10^{-3} + j(12.57 \times 10^{-3} + B_p)} = \frac{0.384 \times 10^{-3} - j(12.57 \times 10^{-3} + B_p)}{(0.384 \times 10^{-3})^2 + (12.57 \times 10^{-3} + B_p)^2}$$

$$\text{Re}[\mathbf{Z}_1] = \frac{0.384 \times 10^{-3}}{(0.384 \times 10^{-3})^2 + (12.57 \times 10^{-3} + B_p)^2} = 50$$

$$7.68 \times 10^{-6} = (0.384 \times 10^{-3})^2 + (12.57 \times 10^{-3} + B_p)^2$$

quadratic

Impedance Matching: Strategy

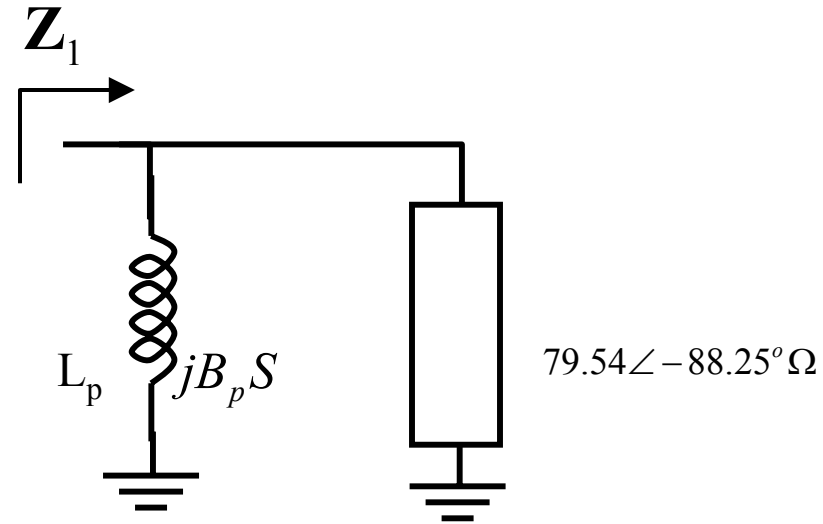

$$7.68 \times 10^{-6} = (0.384 \times 10^{-3})^2 + (12.57 \times 10^{-3} + B_p)^2$$

$$7.68 \times 10^{-6} = 147.5 \times 10^{-9} + 158 \times 10^{-6} + 25.14 \times 10^{-3} B_p + B_p^2$$

$$B_p^2 + 25.14 \times 10^{-3} B_p + 150.5 \times 10^{-6} = 0$$

$$B_p = \frac{-25.14 \times 10^{-3} \pm \sqrt{632 \times 10^{-6} - 4 \times 150.5 \times 10^{-6}}}{2}$$


$$B_p = -15.31 \times 10^{-3} S$$

$$B_p = -9.83 \times 10^{-3} S$$

Impedance Matching: Strategy


$$\left\{ \begin{array}{l} B_p = -15.31 \times 10^{-3} \text{ S} \\ \mathbf{Z}_1 = \left(-j15.31 \times 10^{-3} + \frac{1}{79.54 \angle -88.25^\circ} \right)^{-1} \\ = 49.86 + j356.9 \Omega \end{array} \right.$$
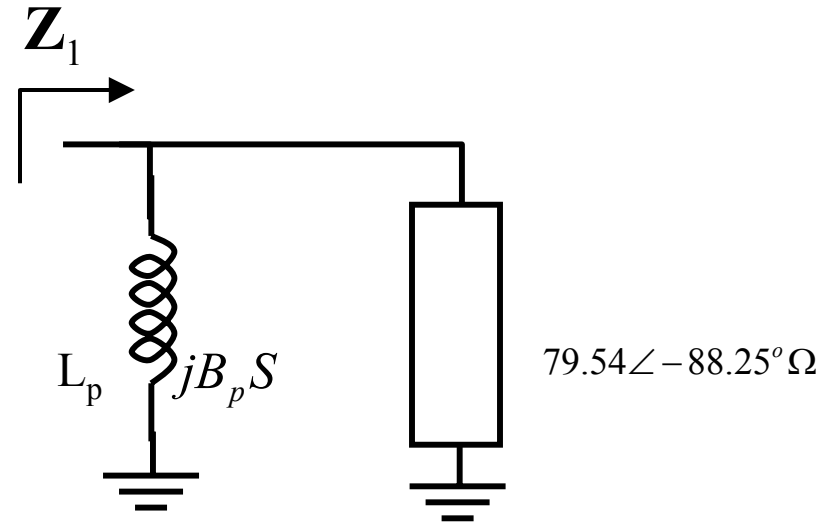
$$\left\{ \begin{array}{l} B_p = -9.83 \times 10^{-3} \text{ S} \\ \mathbf{Z}_1 = \left(-j9.83 \times 10^{-3} + \frac{1}{79.54 \angle -88.25^\circ} \right)^{-1} \\ = 50.28 - j358.4 \Omega \end{array} \right.$$



→ Choose second case (capacitive, negative reactance).

Impedance Matching: Strategy

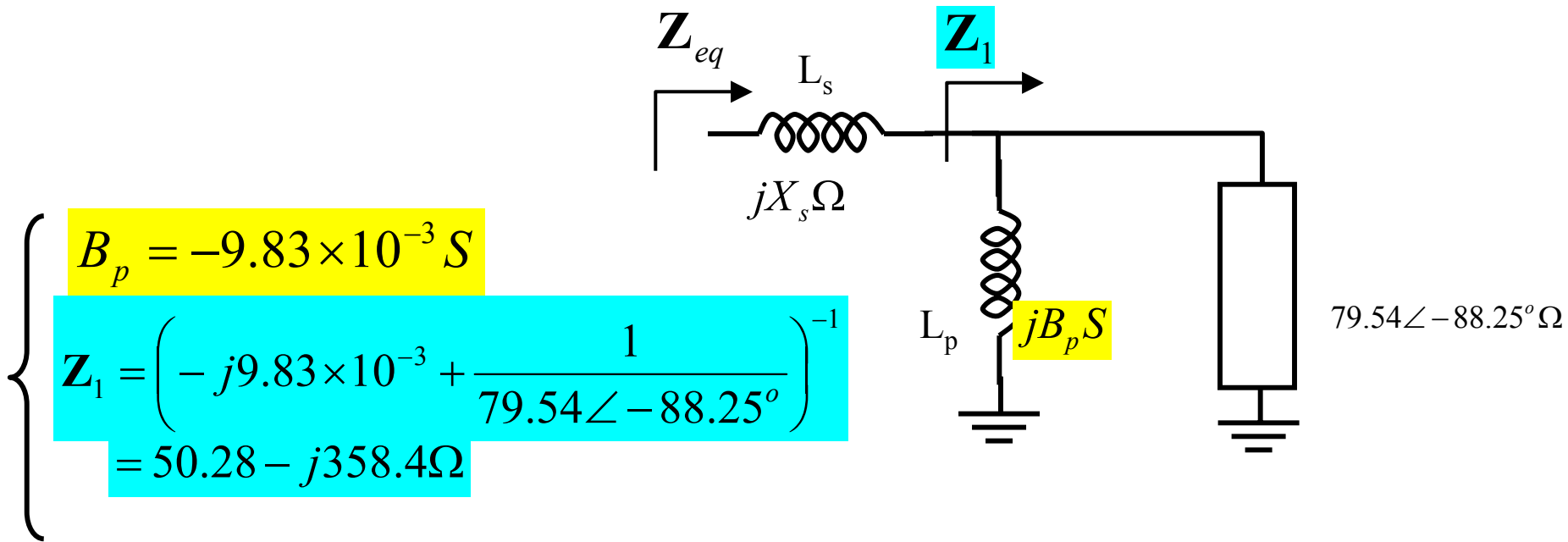

→ Use series inductor to cancel reactive part:

$$Z_{eq} = 50.28 - j358 + jX_s \quad \rightarrow \quad X_s = 358 \Omega$$

$$\rightarrow \quad Z_{eq} = 50.28 \cong 50 \Omega$$

Impedance Matching: Strategy

$$\begin{cases} B_p = -9.83 \times 10^{-3} \text{ S} \\ X_s = 358 \Omega \end{cases}$$


→ Find inductances:

$$jB_p = \frac{1}{j\omega L_p} = -j9.83 \times 10^{-3} \text{ S}$$

$$L_p = \frac{1}{(2\pi \times 10^9)(9.83 \times 10^{-3})} = 16.2 \text{ nH}$$

$$jX_s = j\omega L_s = j358 \Omega$$
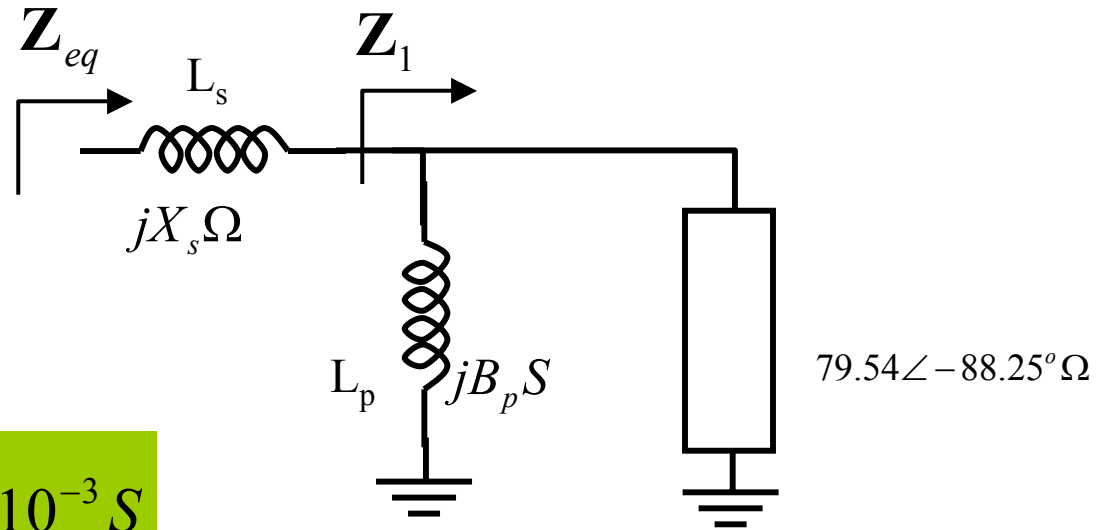
$$L_s = \frac{358}{2\pi \times 10^9} = 57 \text{ nH}$$



Impedance Matching: Summary

1. Any load can be matched to a 50Ω source.
2. This matching is only valid at one frequency.
3. The topology we have used (a parallel inductor and a series inductor) does not work for all cases. We will not worry about the choice of topologies.
4. The matching network is purely reactive and does not consume any average power.