


ECSE 210: Circuit Analysis

Lecture #18:

Three-Phase Circuits

Balanced Load Connections

Wye-Connected Load

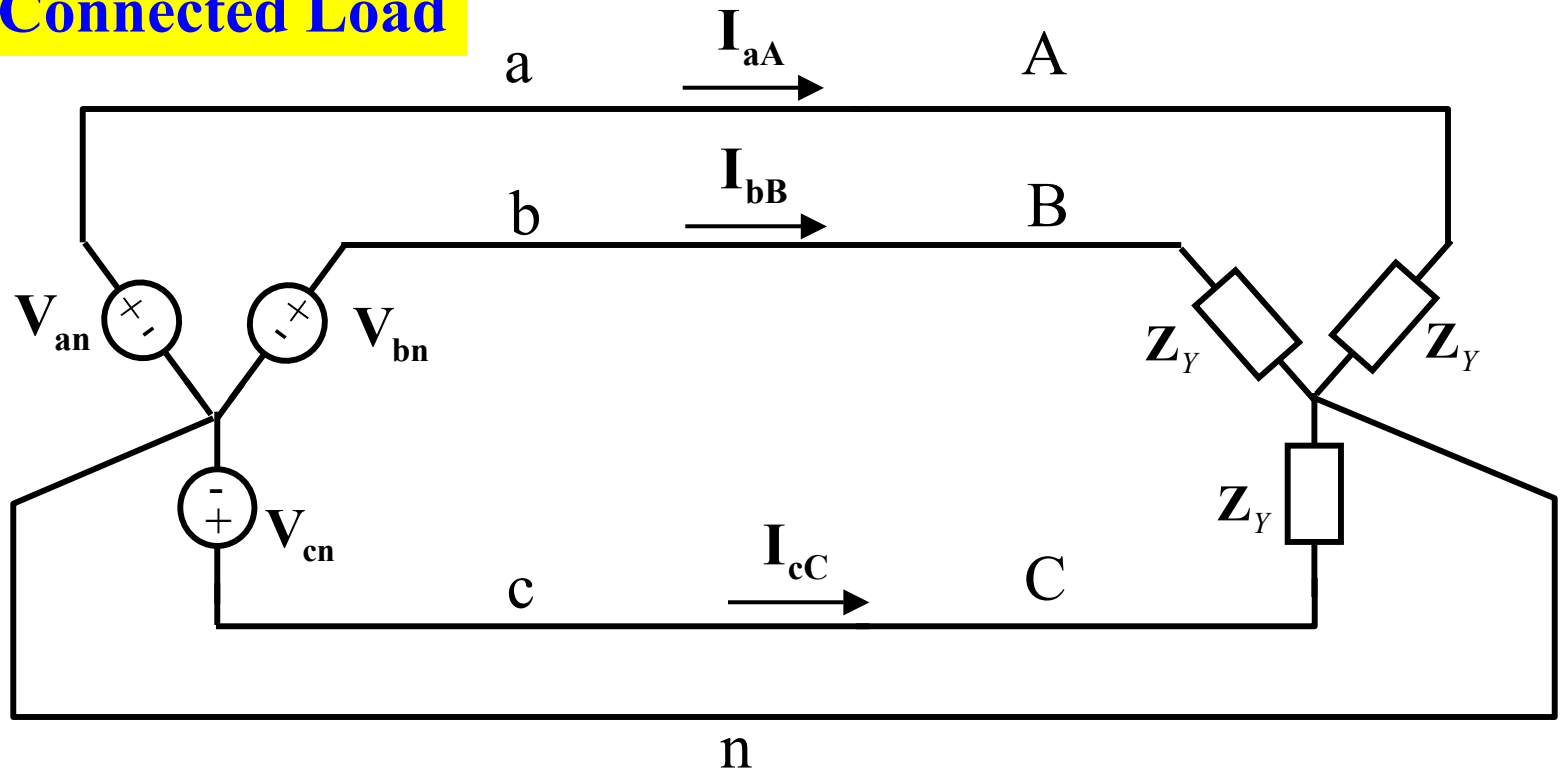

The above is also called the Wye-Wye configuration (Wye-connected source, Wye connected load).



→ For balanced circuit, current in neutral is zero.

Definitions

1. The *Phase Voltage* is the voltage that appears across the load.
2. The *Line Voltage* is the voltage difference from line to line.
3. The *Line Current* is the current through the transmission line.
4. The *Phase Current* is the current through the load.

Balanced Load Connections

Delta-Connected Load

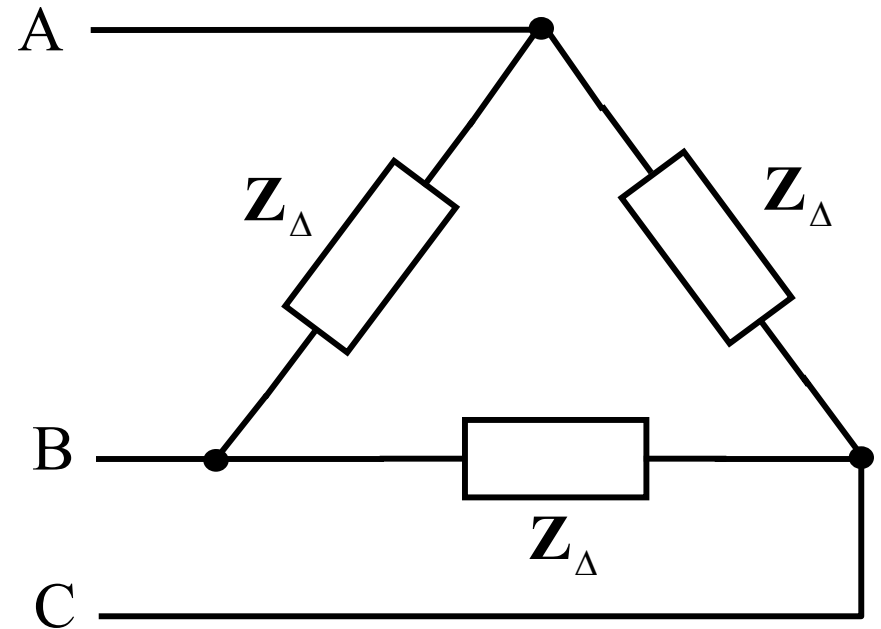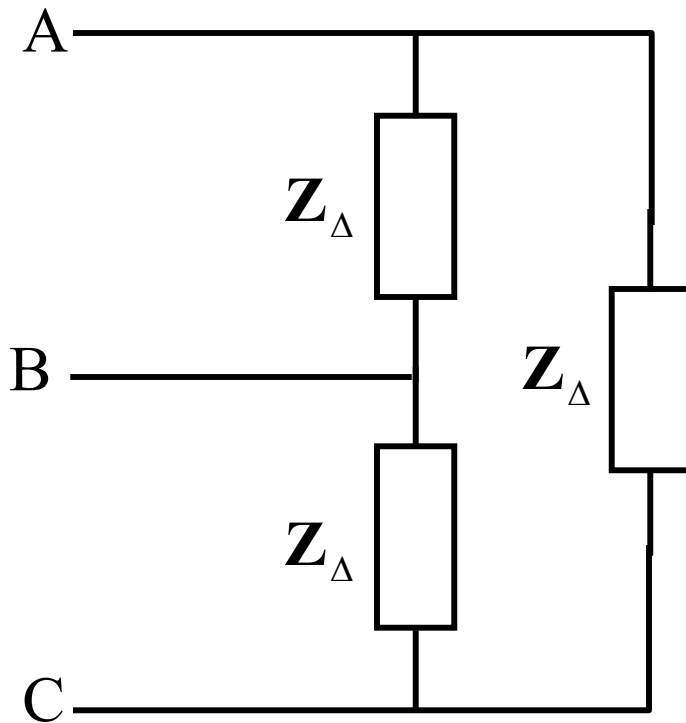

Note: Delta-connected load has no neutral line.

Balanced Load Connections (Y-Y)

The phase voltages are:

$$\mathbf{V}_{an} = V_p \angle 0^\circ$$

$$\mathbf{V}_{bn} = V_p \angle -120^\circ$$


$$\mathbf{V}_{cn} = V_p \angle +120^\circ$$

The line voltages are:

$$\mathbf{V}_{ab} = \mathbf{V}_{an} - \mathbf{V}_{bn} = \sqrt{3}V_p \angle 30^\circ$$

$$\mathbf{V}_{bc} = \mathbf{V}_{bn} - \mathbf{V}_{cn} = \sqrt{3}V_p \angle -90^\circ$$
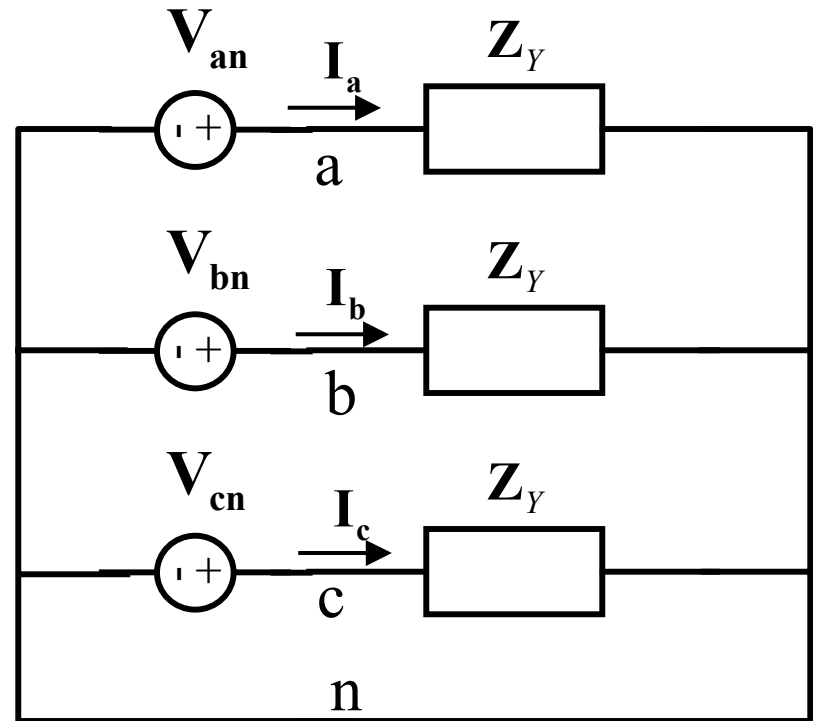
$$\mathbf{V}_{ca} = \mathbf{V}_{cn} - \mathbf{V}_{an} = \sqrt{3}V_p \angle -210^\circ = \sqrt{3}V_p \angle +150^\circ$$



Positive Phase Sequence


By Convention

Positive Phase Sequence (abc)

$$\mathbf{V}_{an} = V_p \angle 0^\circ$$

$$\mathbf{V}_{bn} = V_p \angle -120^\circ$$
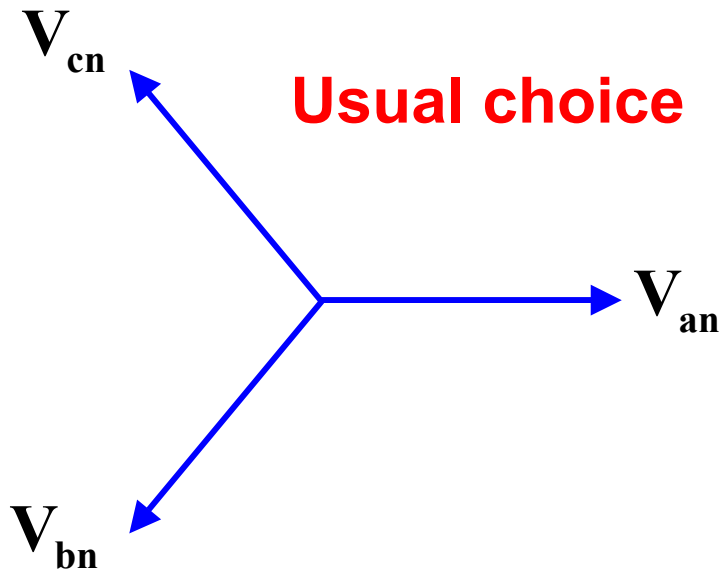
$$\mathbf{V}_{cn} = V_p \angle +120^\circ$$




Negative Phase Sequence (acb)


$$\mathbf{V}_{an} = V_p \angle 0^\circ$$

$$\mathbf{V}_{bn} = V_p \angle +120^\circ$$
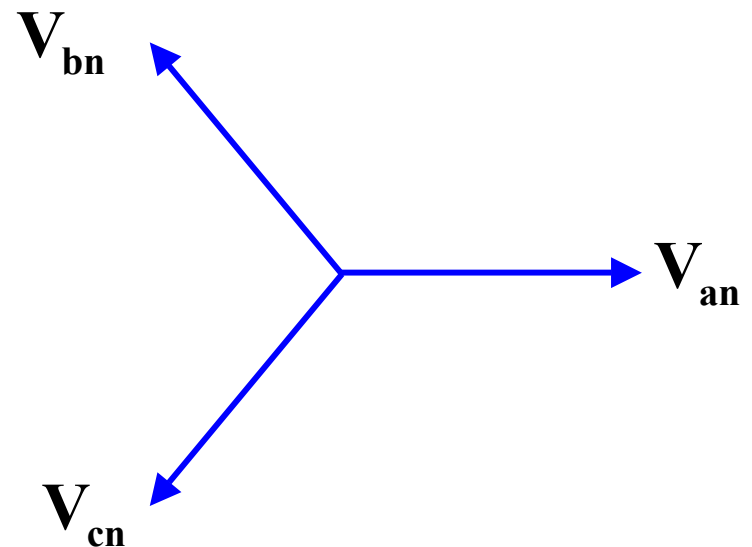
$$\mathbf{V}_{cn} = V_p \angle -120^\circ$$



Phase and Line Voltages of Wye Load

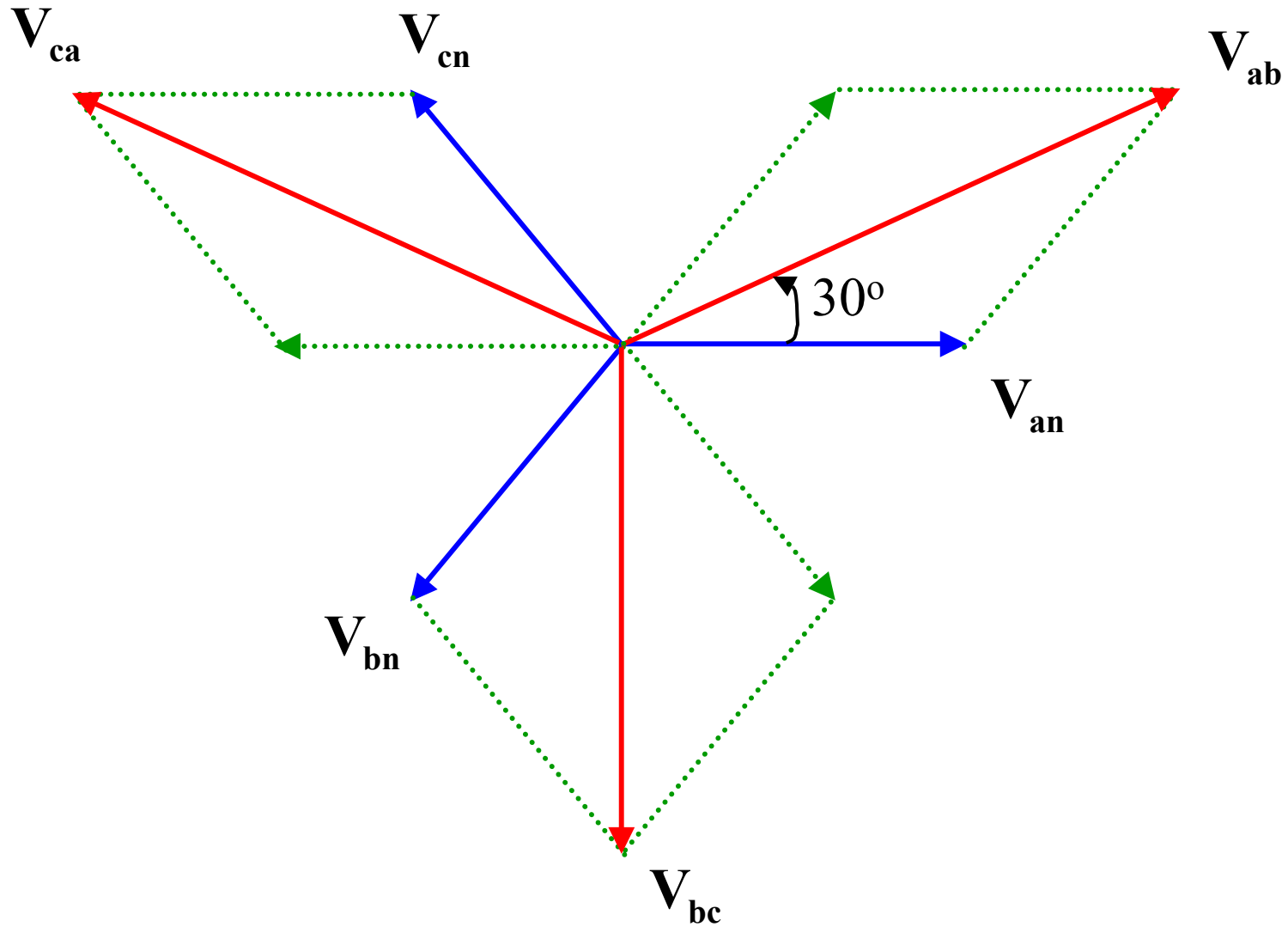

Balanced Currents

Line currents


$$\mathbf{I}_a = \frac{\mathbf{V}_{an}}{\mathbf{Z}_Y} = \frac{V_p \angle 0}{|\mathbf{Z}_Y| \angle \phi} = |\mathbf{I}_L| \angle -\phi$$

$$\mathbf{I}_b = \frac{\mathbf{V}_{bn}}{\mathbf{Z}_Y} = \frac{V_p \angle -120}{|\mathbf{Z}_Y| \angle \phi} = |\mathbf{I}_L| \angle (-\phi - 120)$$


$$\mathbf{I}_c = \frac{\mathbf{V}_{cn}}{\mathbf{Z}_Y} = \frac{V_p \angle +120}{|\mathbf{Z}_Y| \angle \phi} = |\mathbf{I}_L| \angle (-\phi + 120)$$

- Same amplitude
- Phases are 120 degrees apart
- Current in neutral is zero
- The neutral line can be removed from the circuit

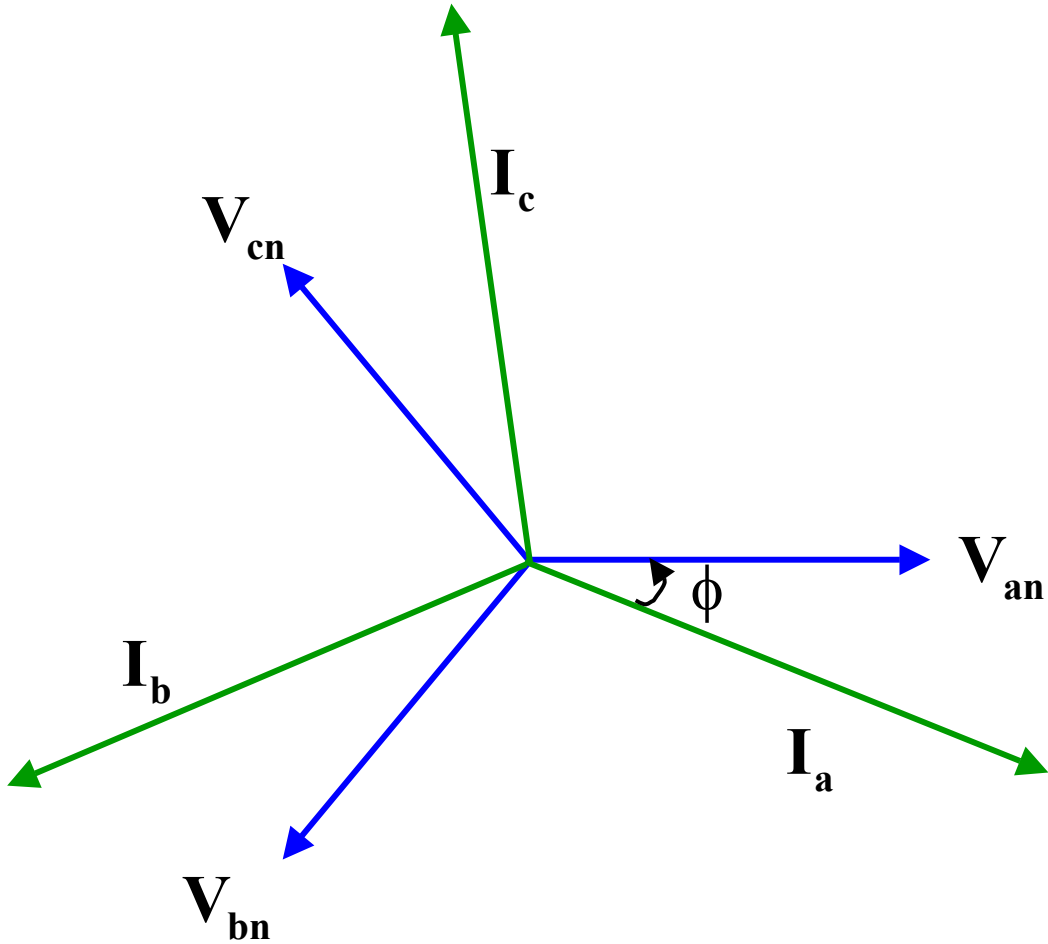Phase Voltages & Line Currents of Wye Load



Wye-Wye Connection with Line Impedance

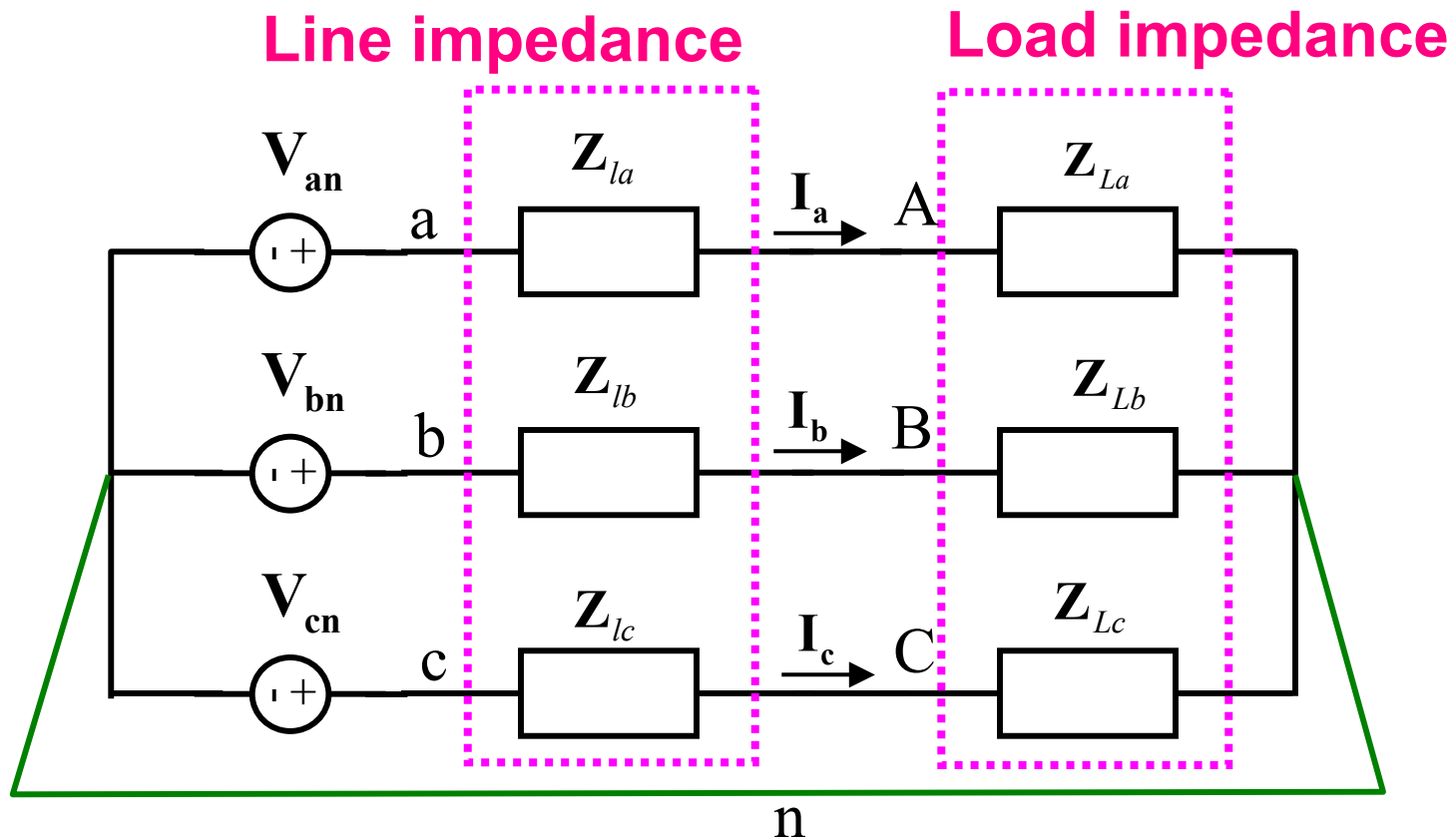

Balanced case: $|\mathbf{V}_{an}| = |\mathbf{V}_{bn}| = |\mathbf{V}_{cn}|$

$$\angle \mathbf{V}_{an} = \theta_a; \quad \angle \mathbf{V}_{bn} = \theta_a - 120; \quad \angle \mathbf{V}_{cn} = \theta_a - 240$$

$$\mathbf{Z}_{la} = \mathbf{Z}_{lb} = \mathbf{Z}_{lc}$$

$$\mathbf{Z}_{La} = \mathbf{Z}_{Lb} = \mathbf{Z}_{Lc}$$

Example 1

Assume that an abc-sequence three-phase voltage source connected in a balanced wye has a line voltage:

$$\mathbf{V}_{ab} = 208 \angle -30^\circ V \text{ rms}$$

Find the three phase voltages:

$$|\mathbf{V}_{an}| = |\mathbf{V}_{bn}| = |\mathbf{V}_{cn}| = V_p = \frac{|\mathbf{V}_{ab}|}{\sqrt{3}} = \frac{208}{\sqrt{3}} = 120V \text{ rms}$$

Recall graphical phase relation between phase and line voltages:

$$\mathbf{V}_{an} = 120 \angle -60^\circ V \text{ rms}$$

$$\mathbf{V}_{bn} = 120 \angle -180^\circ V \text{ rms}$$

$$\mathbf{V}_{cn} = 120 \angle 60^\circ V \text{ rms}$$

Example 2

Assume a wye-connected load is supplied by an abc-sequence balanced three-phase wye-connected source with a phase voltage of 120 V rms. Given the line impedance and load impedance per phase are $1+j\Omega$ and $20+10j\Omega$, respectively, determine the line current and load voltages.


Balanced circuit \rightarrow **Analyze one phase only!**

Phase voltages:

$$\mathbf{V}_{an} = 120 \angle 0^\circ \text{ V rms}$$

$$\mathbf{V}_{bn} = 120 \angle -120^\circ \text{ V rms}$$

$$\mathbf{V}_{cn} = 120 \angle +120^\circ \text{ V rms}$$

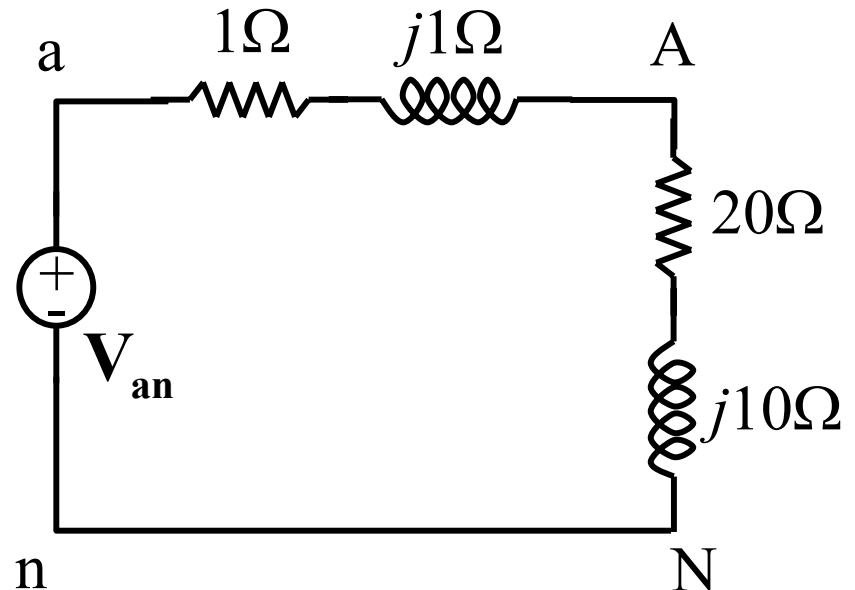

Example 2


Balanced circuit → **Analyze one phase only!**

Phase voltages:

$$\mathbf{V}_{an} = 120 \angle 0^\circ V \text{ rms}$$

$$\mathbf{V}_{bn} = 120 \angle -120^\circ V \text{ rms}$$
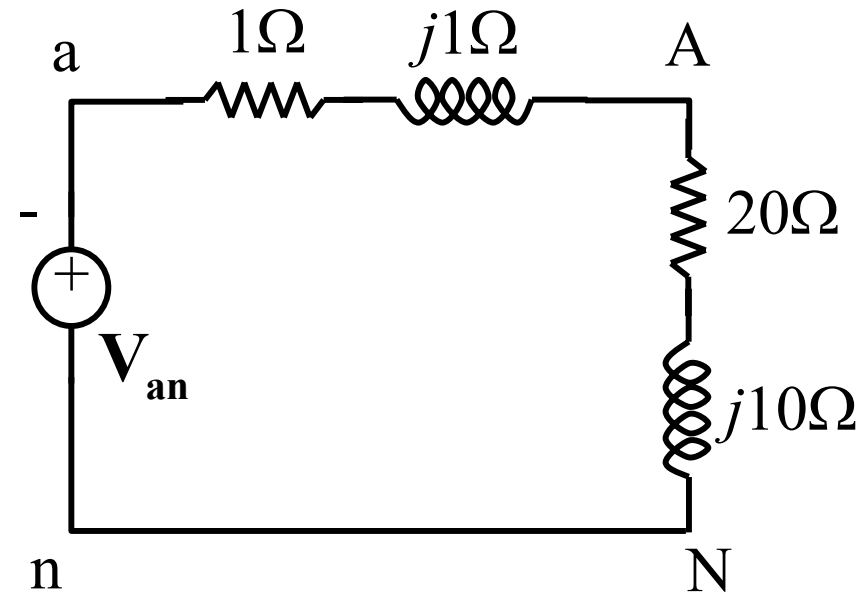
$$\mathbf{V}_{cn} = 120 \angle +120^\circ V \text{ rms}$$



$$\text{Line current (phase a): } \mathbf{I}_{aA} = \frac{120 \angle 0^\circ}{21 + j11} = 5.06 \angle -27.65^\circ A \text{ rms}$$

$$\begin{aligned} \text{Load voltage (phase a): } \mathbf{V}_{AN} &= (5.06 \angle -27.65^\circ)(20 + j10) \\ &= 113.15 \angle -1.08^\circ V \text{ rms} \end{aligned}$$

Example 2

Using the abc-sequence we can find phases b and c:

Line Currents:

$$\mathbf{I}_{bB} = 5.06 \angle -147.65^\circ \text{ A rms}$$

$$\mathbf{I}_{cC} = 5.06 \angle -267.65^\circ = 5.06 \angle 92.35^\circ \text{ A rms}$$

Load Voltages


$$\mathbf{V}_B = 113.15 \angle -121.08^\circ \text{ V rms}$$

$$\mathbf{V}_C = 113.15 \angle -241.08^\circ = 113.15 \angle 118.92^\circ \text{ V rms}$$

Note: For the wye-wye connection, line currents and phase currents are the same.

Balanced Wye-Delta Connection

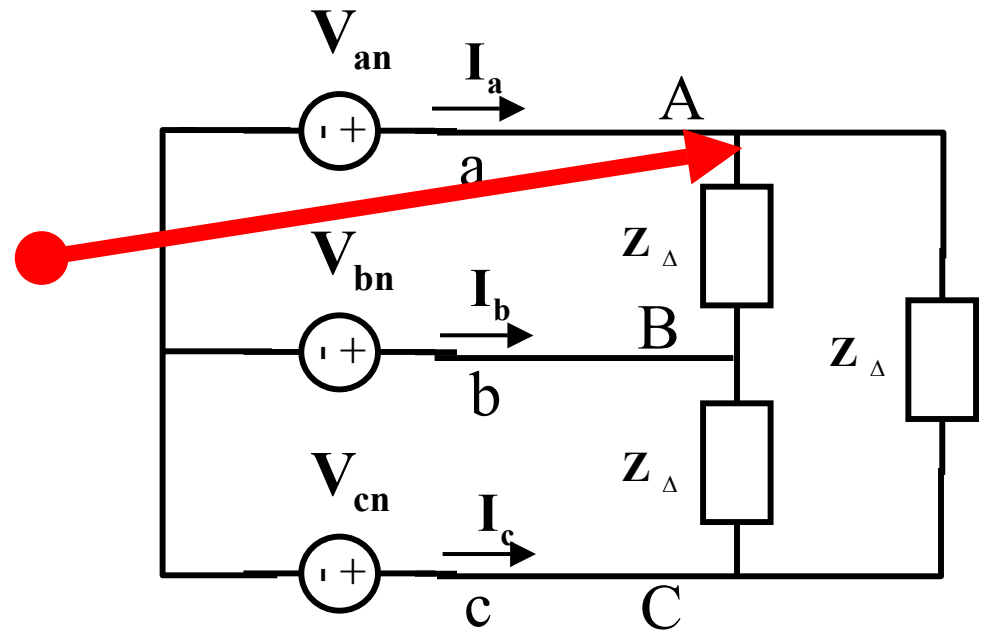Note: In this case, line voltages and phase voltages are the same!



For an abc-connected **source**, the **line-to-neutral** voltages are:

$$V_{an} = V_p \angle 0^\circ V \text{ rms}$$

$$V_{bn} = V_p \angle -120^\circ V \text{ rms}$$

$$V_{cn} = V_p \angle +120^\circ V \text{ rms}$$

Balanced Wye-Delta Connection

The *phase* or *line* voltages (**across the load**) are given by:

$$\mathbf{V}_{ab} = \sqrt{3}V_p \angle 30^\circ \text{ rms}$$

$$\mathbf{V}_{bc} = \sqrt{3}V_p \angle -90^\circ \text{ rms}$$

$$\mathbf{V}_{ca} = \sqrt{3}V_p \angle -210^\circ = \sqrt{3}V_p \angle 150^\circ \text{ rms}$$

For a load $\mathbf{Z}_\Delta = |\mathbf{Z}_\Delta| \angle \phi$ The *phase* currents at the load are:

$$\mathbf{I}_{AB} = \frac{\mathbf{V}_{AB}}{\mathbf{Z}_\Delta} = I_\Delta \angle 30^\circ - \phi$$

$$\mathbf{I}_{BC} = \frac{\mathbf{V}_{BC}}{\mathbf{Z}_\Delta} = I_\Delta \angle -90^\circ - \phi$$

$$\mathbf{I}_{CA} = \frac{\mathbf{V}_{CA}}{\mathbf{Z}_\Delta} = I_\Delta \angle 150^\circ - \phi$$

Balanced Wye-Delta Connection

The *line currents* can be found from the *phase currents* using KCL:

$$\mathbf{I}_{aA} = \mathbf{I}_{AB} - \mathbf{I}_{CA}$$

$$\mathbf{I}_{aA} = \sqrt{3}I_{\Delta} \angle -\phi$$

$$\mathbf{I}_{bB} = \sqrt{3}I_{\Delta} \angle -120 - \phi$$

$$\mathbf{I}_{cC} = \sqrt{3}I_{\Delta} \angle -240 - \phi$$