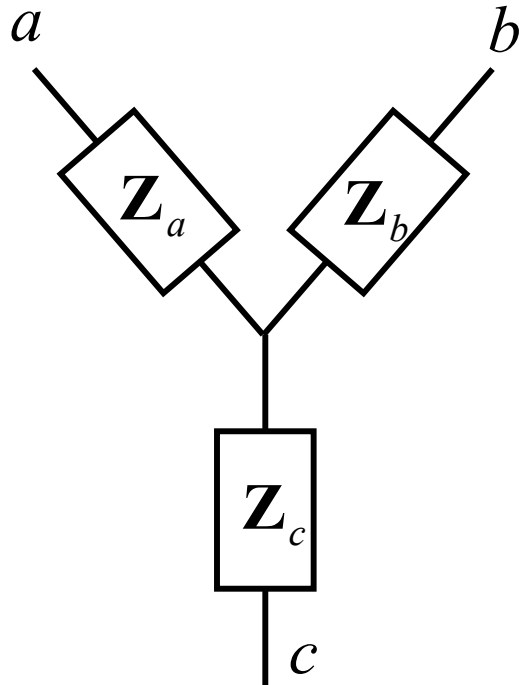


# **ECSE 210: Circuit Analysis**

**Lecture#19:**

**Three-Phase Circuits**


# Wye-Delta Transformation - Review



$$Z_a = \frac{Z_{ab} Z_{ac}}{Z_{ab} + Z_{ac} + Z_{bc}}$$

$$Z_b = \frac{Z_{ab} Z_{bc}}{Z_{ab} + Z_{ac} + Z_{bc}}$$
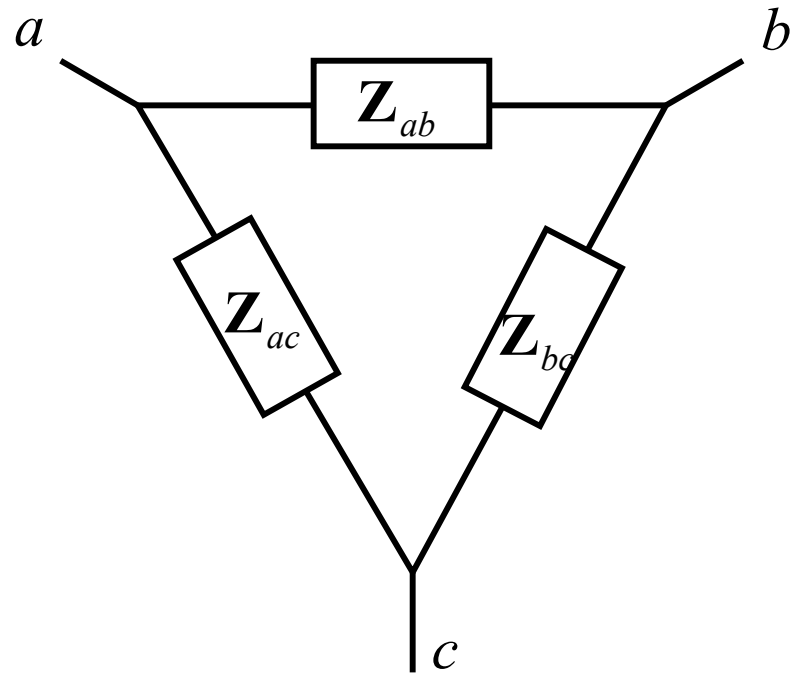
$$Z_c = \frac{Z_{ac} Z_{bc}}{Z_{ab} + Z_{ac} + Z_{bc}}$$




$$Z_{ab} = \frac{Z_a Z_b + Z_b Z_c + Z_c Z_a}{Z_c}$$


$$Z_{ac} = \frac{Z_a Z_b + Z_b Z_c + Z_c Z_a}{Z_b}$$

$$Z_{bc} = \frac{Z_a Z_b + Z_b Z_c + Z_c Z_a}{Z_a}$$

# Wye-Delta for Balanced Loads

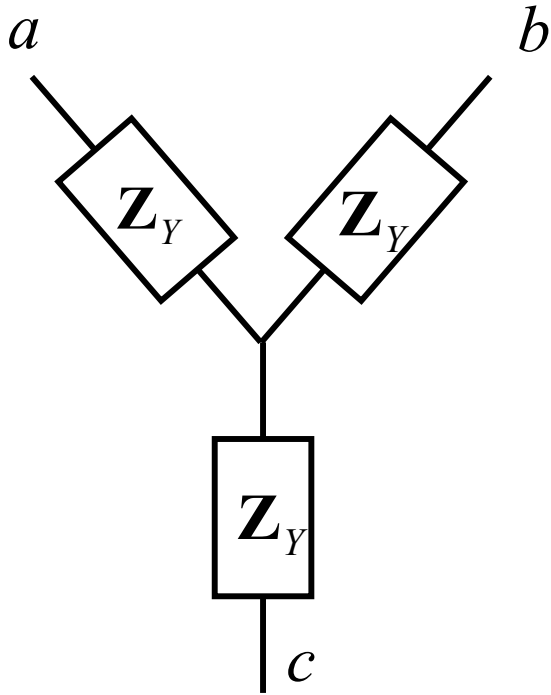


$$Z_Y = \frac{Z_{\Delta}}{3}$$

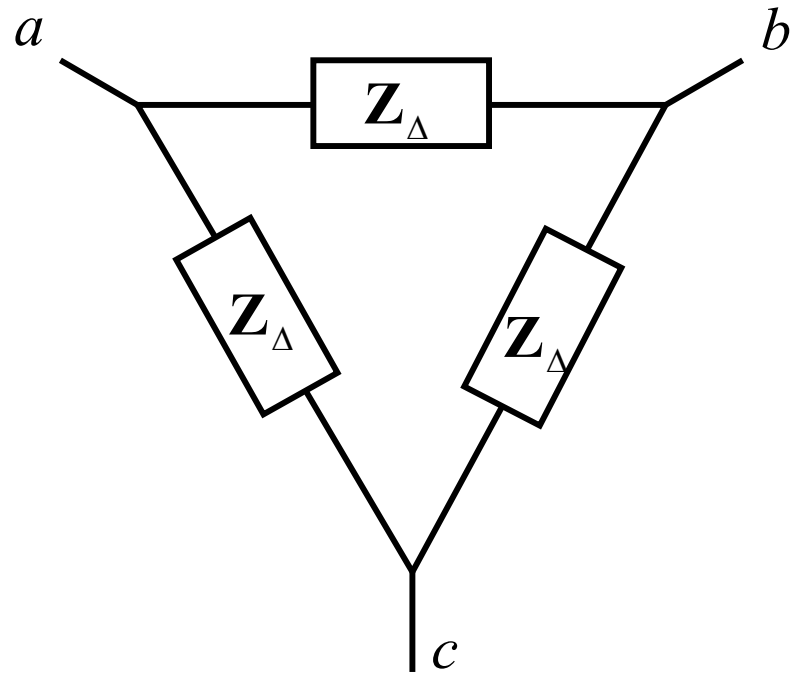

$$Z_{\Delta} = 3Z_Y$$

# Balanced Wye-to-Wye Connection

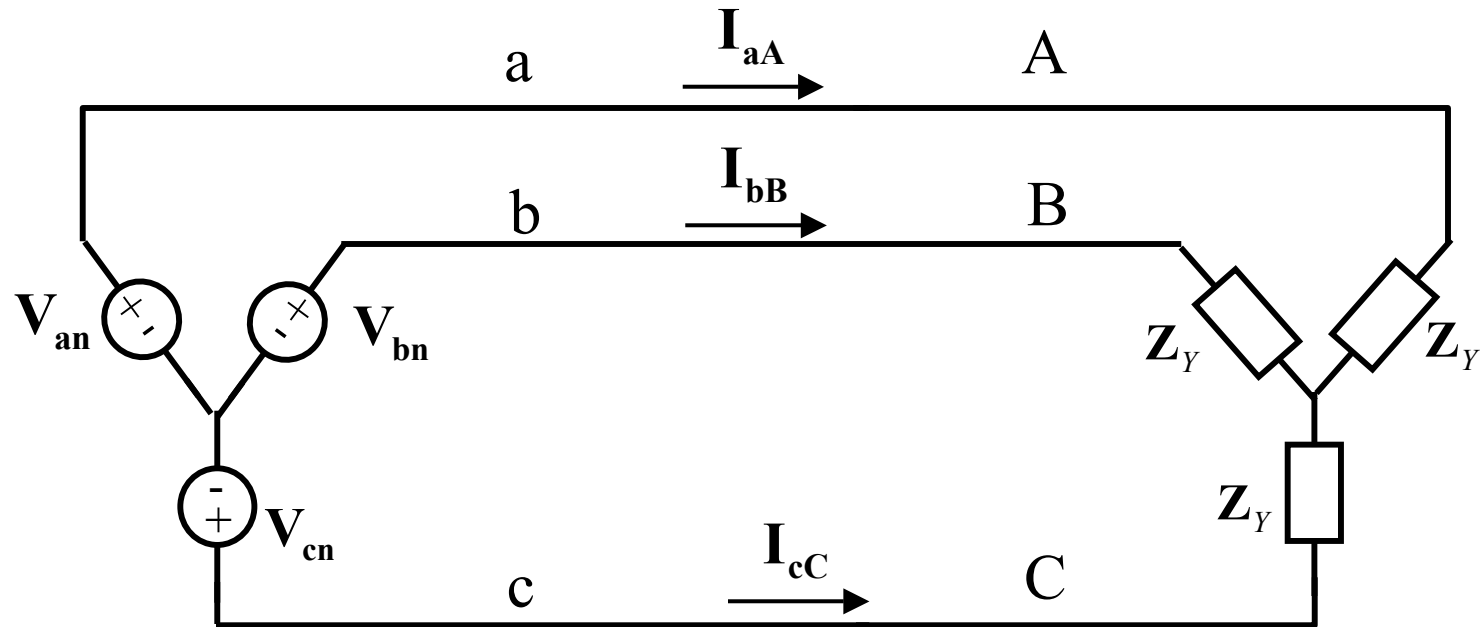

# Balanced Wye-to-Wye Connection

**Phase voltages:**  $V_a = V_p \angle 0^\circ$

$$V_b = V_p \angle -120^\circ$$

$$V_c = V_p \angle +120^\circ$$

**Line-to-line voltages (or line voltages):**

$$V_{ab} = V_L = \sqrt{3}V_p \angle 30^\circ \quad \mathbf{L \equiv line}$$

$$V_{bc} = \sqrt{3}V_p \angle -90^\circ$$

$$V_{ca} = \sqrt{3}V_p \angle -210^\circ = \sqrt{3}V_p \angle +150^\circ$$

# Balanced Wye-to-Wye Connection

**Currents:**

$$\mathbf{I}_L = \mathbf{I}_P \quad (\text{Line current} = \text{Phase current})$$


$$\mathbf{I}_{aA} = \frac{\mathbf{V}_a}{\mathbf{Z}_Y} = \frac{V_p \angle 0}{|\mathbf{Z}_Y| \angle \phi} = |\mathbf{I}_L| \angle -\phi = I_p \angle -\phi$$

$$\mathbf{I}_{bB} = |\mathbf{I}_L| \angle (-\phi - 120) = I_p \angle (-\phi - 120)$$

$$\mathbf{I}_{cC} = |\mathbf{I}_L| \angle (-\phi - 240) = I_p \angle (-\phi - 240)$$

**Phase voltage at the source is across the Y load impedance.**

# Balanced Wye-to-Delta Connection

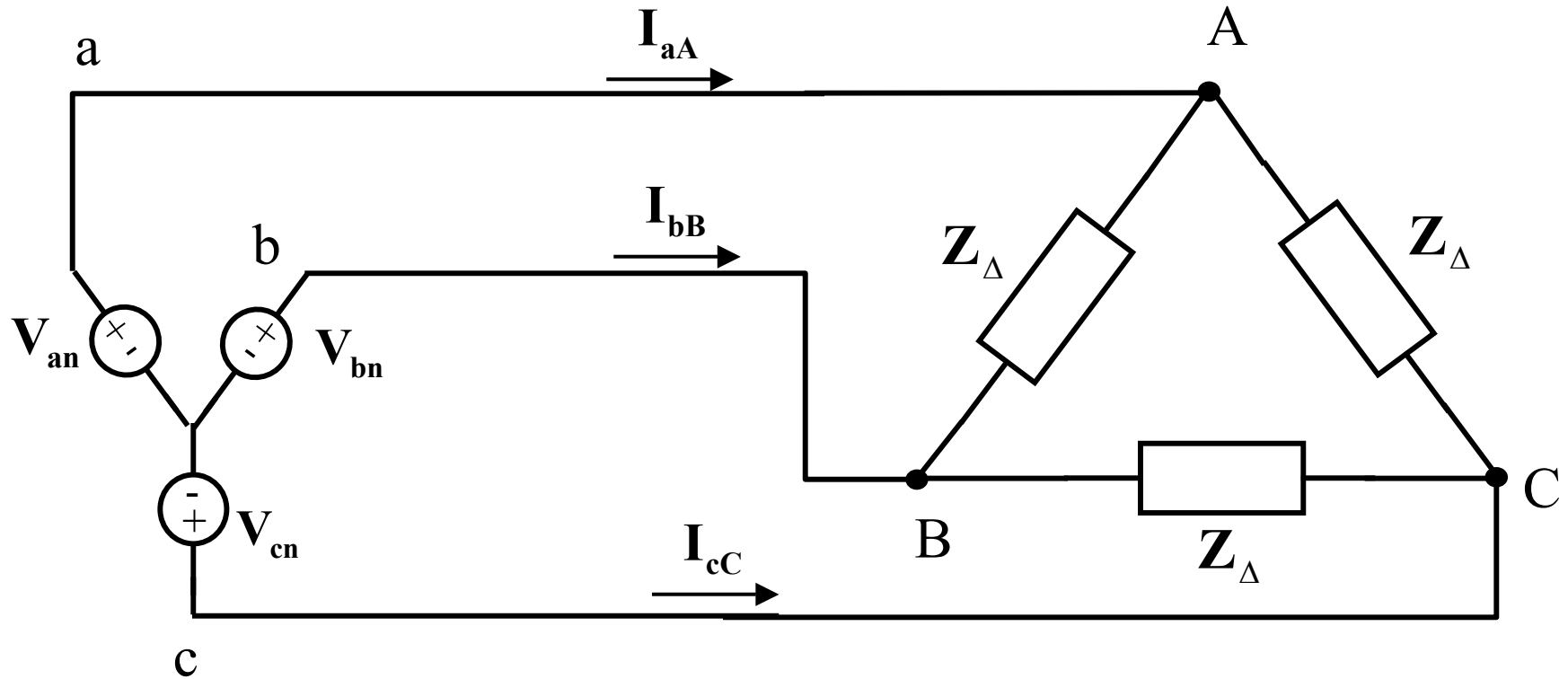


Phase voltages:  $V_{AB} = V_{AB} \angle 0^\circ = V_p \angle 0^\circ$

Line-to-line voltages (line voltages)

At the  $\Delta$   
load impedance.

# Balanced Wye-to-Delta Connection

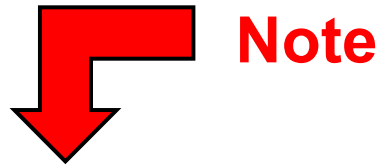

**Phase voltages:**  $V_{AB} = V_{AB} \angle 0^\circ = V_p \angle 0^\circ$

$$V_{BC} = V_p \angle -120^\circ$$

$$V_{CA} = V_p \angle -240^\circ$$

**At the  $\Delta$   
load impedance.**

**Line-to-line voltages (line voltages):**

$$V_{AB} = V_L \quad (\text{Line voltage} = \text{Phase voltage})$$


**Phase Currents:**  $I_{AB} = \frac{V_{AB}}{Z_\Delta} = I_p \angle -\phi$

$$I_{BC} = \frac{V_{BC}}{Z_\Delta} = I_p \angle -120 - \phi$$

$$I_{CA} = \frac{V_{CA}}{Z_\Delta} = I_p \angle -240 - \phi$$

$$Z_\Delta = Z_\Delta \angle \phi$$

**Note**

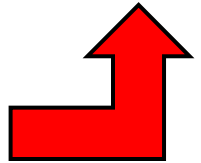



# Balanced Wye-to-Delta Connection

---

**Line Currents:**

$$\mathbf{I}_{aA} = \sqrt{3}I_p \angle -\phi - 30^\circ$$
$$\mathbf{I}_{bB} = \sqrt{3}I_p \angle -\phi - 150^\circ$$
$$\mathbf{I}_{cC} = \sqrt{3}I_p \angle -\phi + 90^\circ$$

# Example 1

Assume that an abc-sequence three-phase voltage source connected as a **wye** supplies power to a balanced **delta**-connected load. Given the load current  $\mathbf{I}_{AB}$ , find the line currents.

$$\mathbf{I}_{AB} = 4 \angle 20^\circ \text{ A rms}$$

---

$$\mathbf{I}_{aA} = 4\sqrt{3} \angle -10^\circ \text{ A rms}$$

$$\mathbf{I}_{bB} = 4\sqrt{3} \angle -130^\circ \text{ A rms}$$

$$\mathbf{I}_{cC} = 4\sqrt{3} \angle +110^\circ \text{ A rms}$$

**Line currents**

## Example 2

Assume a 60Hz abc-sequence three-phase voltage source connected in a balanced **wye** supplies power to a balanced **delta**-connected load. If  $\mathbf{V}_{an} = 120\angle 30^\circ$  V rms and the load contains a  $10\Omega$  resistance in series with a 20mH inductance in all three phases, what are the line and phase currents?

---

The load impedance per phase is:

$$\mathbf{Z}_{\Delta} = 10 + j(2\pi 60)(20\text{mH}) = 10 + j7.54\Omega$$

Since there is no line impedance:

$$\mathbf{V}_{AB} = \mathbf{V}_{ab} = 120\sqrt{3}\angle 60^\circ \text{ V rms}$$

$$\mathbf{I}_{AB} = \frac{120\sqrt{3}\angle 60^\circ}{10 + j7.54} = 16.6\angle 22.98^\circ \text{ A rms}$$

## Example 2

$$\mathbf{I}_{AB} = \frac{120\sqrt{3}\angle 60^\circ}{10 + j7.54} = 16.6\angle 22.98^\circ \text{ A rms}$$

**Load (phase) current**

$$\mathbf{I}_{aA} = 16.6\sqrt{3}\angle -7.02^\circ \text{ A rms}$$

**Line current**

Using the abc-sequence, the remaining phase and line currents are:

$$\mathbf{I}_{BC} = 16.6\angle -97.02^\circ \text{ A rms}$$

$$\mathbf{I}_{CA} = 16.6\angle 142.98^\circ \text{ A rms}$$


**Phase currents**

$$\mathbf{I}_{bB} = 16.6\sqrt{3}\angle -127.02^\circ \text{ A rms}$$

$$\mathbf{I}_{cC} = 16.6\sqrt{3}\angle 112.98^\circ \text{ A rms}$$

**Line currents**

# Three-Phase Power

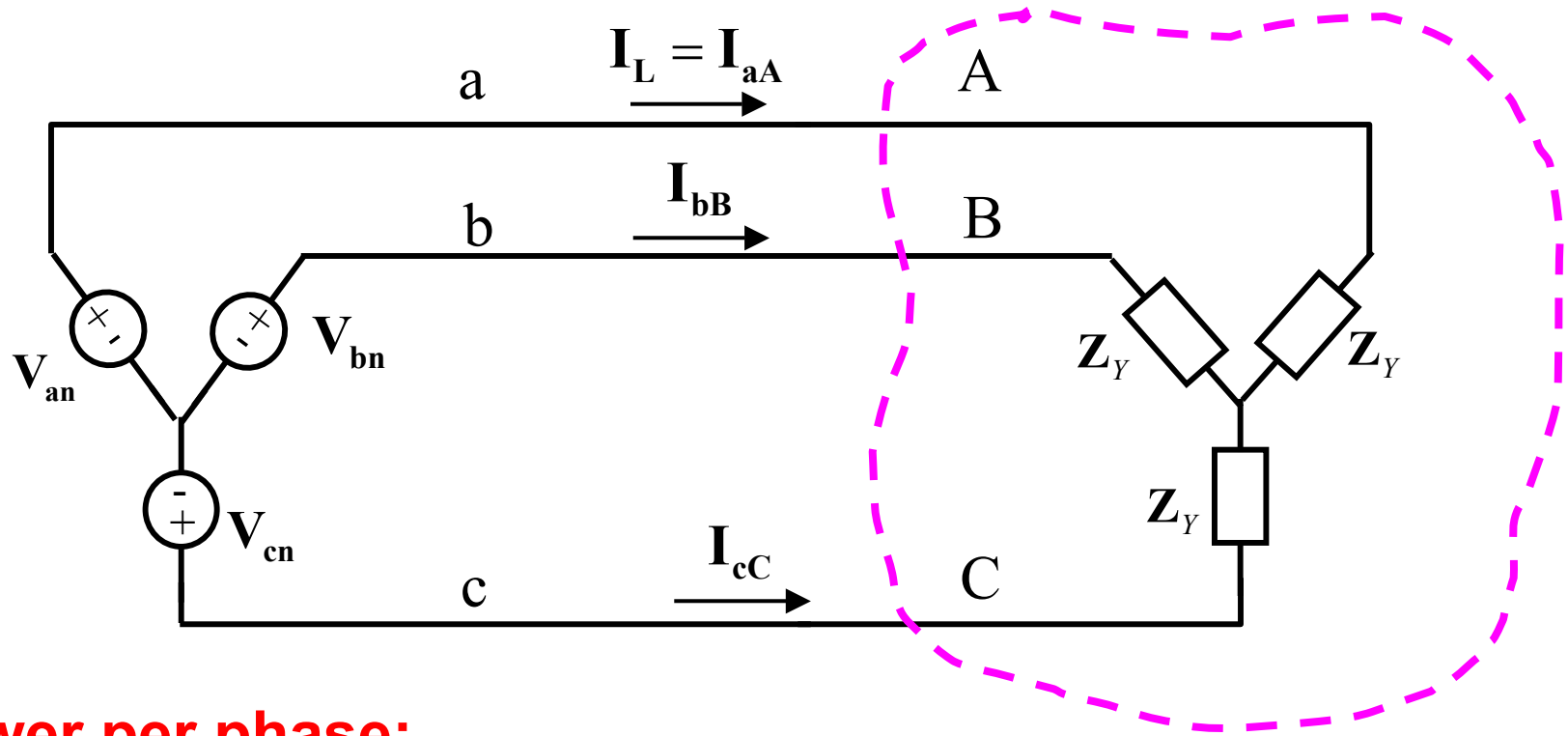

**Power per phase:**

$$P_p = |\mathbf{V}_{an}| |\mathbf{I}_L| \overbrace{\cos(\theta)}^{\text{Power factor}} \rightarrow \text{Average power}$$

$$Q_p = |\mathbf{V}_{an}| |\mathbf{I}_L| \sin(\theta) \rightarrow \text{Reactive power}$$

## Example 3

Assume a balanced three-phase **wye-delta** system has a line voltage of 208V rms. If the **total** real power (avg. power) absorbed by the load is **1200W**, and the load power factor angle is  $20^\circ$  lagging, determine the magnitude of the **line current** and the value of the **load impedance** per phase in the delta.

### Solution

Amplitude of **line-to neutral-voltage**:  $|\mathbf{V}_{an}| = \frac{208}{\sqrt{3}} V_{rms}$

$$\text{Per phase power} = \mathbf{400W} = \frac{208|\mathbf{I}_L|}{\sqrt{3}} \cos(20^\circ)$$

$$|\mathbf{I}_L| = 3.5 A_{rms} \quad \text{Line current}$$

## Example 3

---

$$|\mathbf{I}_L| = 3.5 \text{ A rms}$$

For a delta-connected load  $\rightarrow$  The phase current is:

$$|\mathbf{I}_V| = \frac{|\mathbf{I}_L|}{\sqrt{3}} = 2.04 \text{ A rms}$$

The magnitude of the impedance in each phase is:

$$|\mathbf{Z}_\Delta| = \frac{|\mathbf{V}_L|}{|\mathbf{I}_\Delta|} = \frac{208}{2.04} = 101.77 \Omega$$

Since the power factor angle is  $20^\circ$  lagging (means current is lagging):

$$\mathbf{Z}_\Delta = 101.77 \angle 20^\circ \Omega$$

## Example 4

---


Consider a balanced three-phase circuit consisting of:

- A wye-connected abc-sequence voltage **source** with  $V_{ab} = 208 \angle 30^\circ \text{ V rms}$ ;
- A **wye-connected load**, with per phase impedance  $10 + 6j \Omega$ , in parallel with a **delta-connected** load with per phase impedance  $24 + 9j \Omega$ ;
- A line impedance with per phase impedance  $1 + 0.5j \Omega$ .

Determine the line currents and the load phase voltages when the load is converted into **an equivalent wye**.



# Example 4

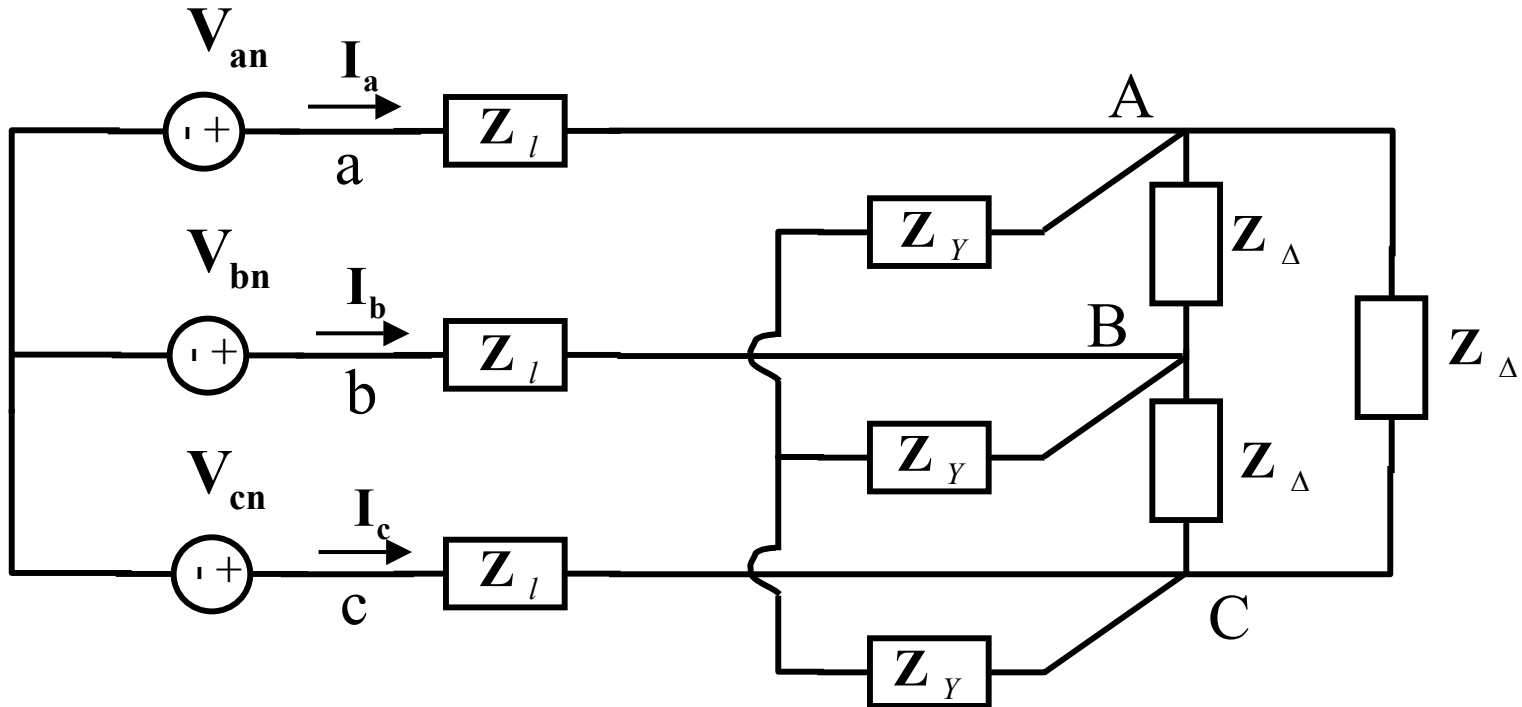

$$Z_l = 1 + 0.5j\Omega$$


$$Z_Y = 10 + 6j\Omega$$

$$Z_\Delta = 24 + 9j\Omega$$
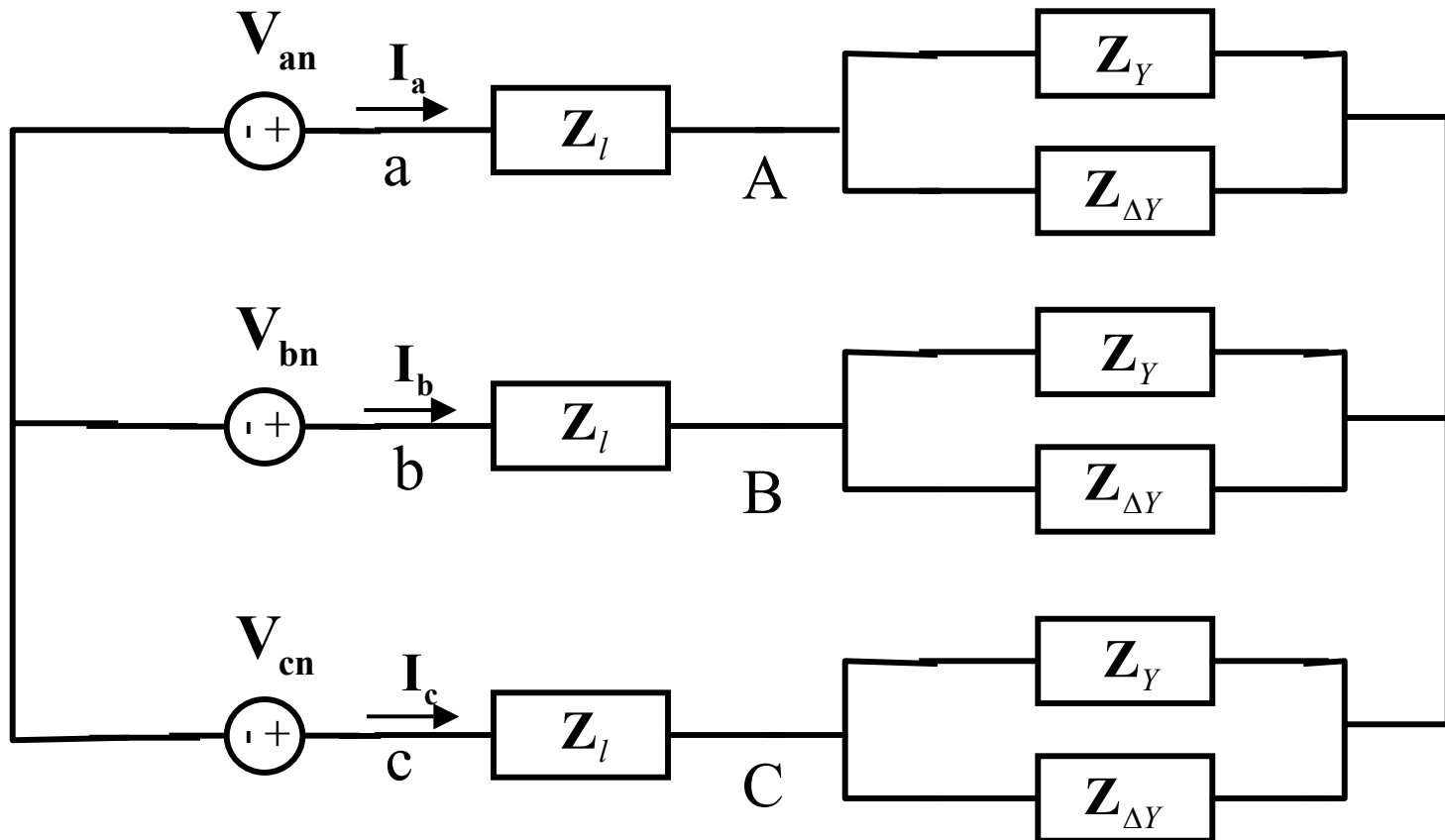
# Example 4


Delta to wye transformation:

$$\mathbf{Z}_{\Delta Y} = \frac{\mathbf{Z}_{\Delta}}{3} = 8 + 3j\Omega$$



# Example 4

Per-phase equivalent circuit:

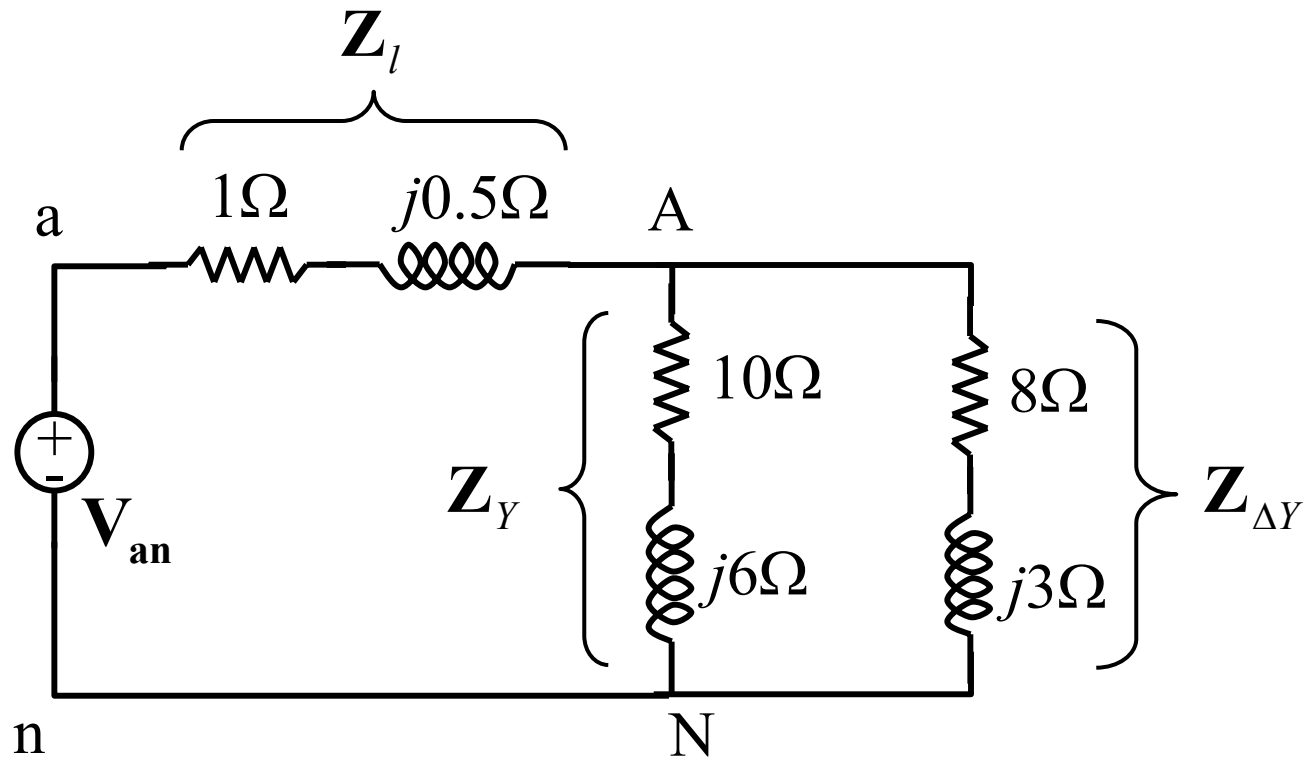

## Example 4

Line-voltage at the source is  $V_{ab} = 208 \angle 30^\circ$  V rms

**Given**

→ The **source phase voltage** is:

$$V_{an} = \frac{208}{\sqrt{3}} \angle 0^\circ \text{ V rms} = 120 \angle 0^\circ \text{ V rms}$$

→ The line current is:  $I_{aA} = \frac{V_{an}}{Z_{total}}$

where  $Z_{total} = Z_l + Z_Y \parallel Z_{\Delta Y} = 5.49 + 2.59 j \Omega$

$$\rightarrow I_{aA} = 19.77 \angle -25.26^\circ \text{ A rms}$$

→ The **phase voltage at the load** is:  $V_{AN} = I_{aA} Z_{load}$

where  $Z_{load} = Z_Y \parallel Z_{\Delta Y} = 4.49 + 2.09 j \Omega$

$$\rightarrow V_{AN} = 97.86 \angle -0.31^\circ \text{ V rms}$$

## Example 4

Therefore, the balanced three-phase **line currents** and **load phase voltages** are given by:

$$\mathbf{I}_{aA} = 19.77 \angle -25.26^\circ \text{ Arms}$$

$$\mathbf{V}_{AN} = 97.86 \angle -0.31^\circ \text{ V rms}$$

$$\mathbf{I}_{bB} = 19.77 \angle -145.26^\circ \text{ Arms}$$


$$\mathbf{V}_{BN} = 97.86 \angle -120.31^\circ \text{ V rms}$$

$$\mathbf{I}_{cC} = 19.77 \angle 94.74^\circ \text{ Arms}$$

$$\mathbf{V}_{CN} = 97.86 \angle 119.69^\circ \text{ V rms}$$

## Example 5

Consider the balanced circuit below:

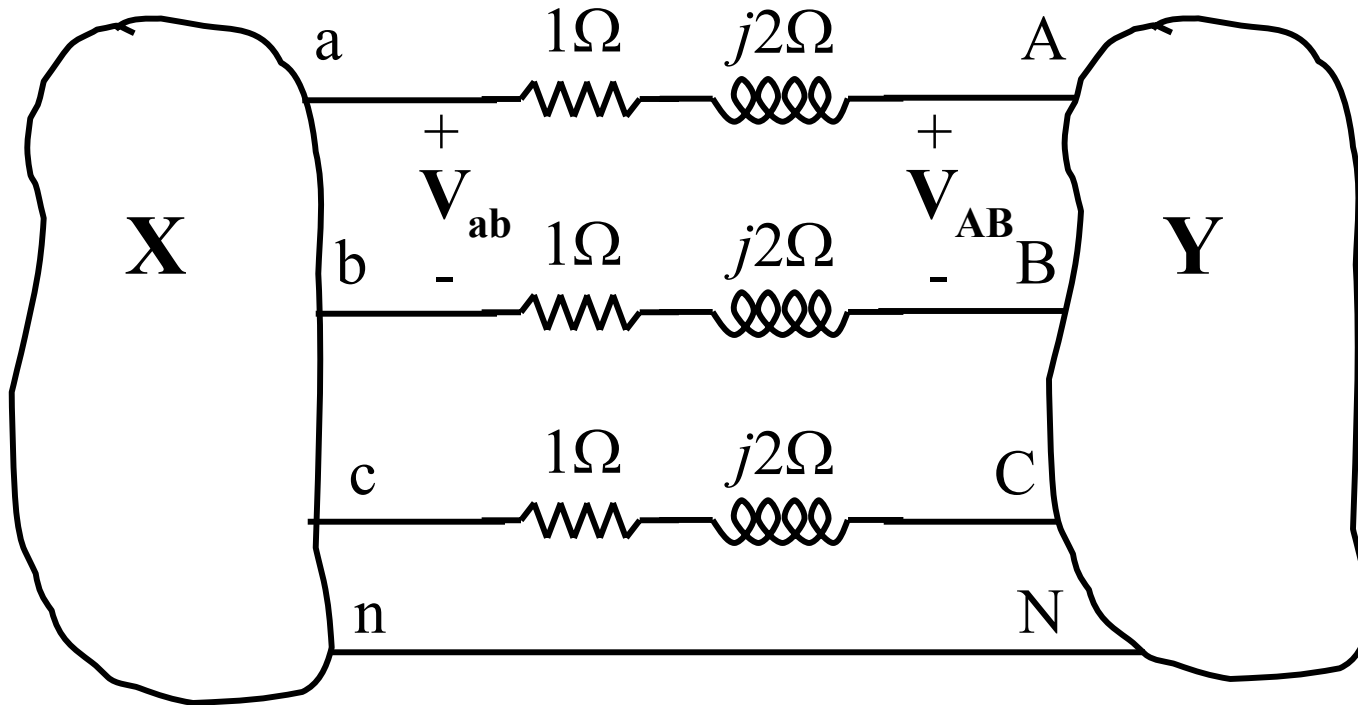

Determine which is the load and which is the source.

Given:


$$V_{ab} = 12\angle 0^\circ \text{ kV rms}$$

$$V_{AB} = 12\angle 5^\circ \text{ kV rms}$$

$$Z_{line} = 1 + 2j\Omega$$

## Example 5

The **per-phase** equivalent circuit is:

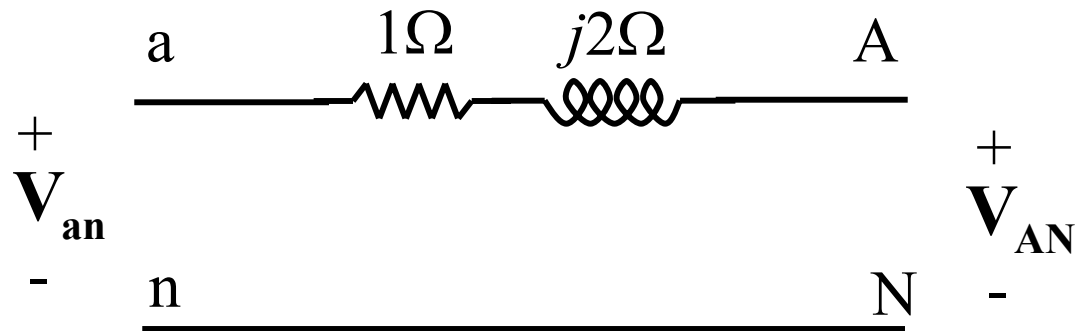

$$\mathbf{V}_{an} = \frac{12}{\sqrt{3}} \angle -30^\circ \text{ kV rms}$$

$$\mathbf{V}_{AN} = \frac{12}{\sqrt{3}} \angle -25^\circ \text{ kV rms}$$

The line current is given by:

$$\mathbf{I}_{aA} = \frac{\mathbf{V}_{an} - \mathbf{V}_{AN}}{\mathbf{Z}_{line}} = 270.3 \angle -180.93^\circ \text{ A rms}$$

## Example 5

→ The per-phase power supplied to system **Y** is:

$$P_{Yp} = |\mathbf{V}_{AN}| |\mathbf{I}_{aA}| \cos(-25 + 180.93) = -1.71 MW$$

The total power supplied to system **Y** is:

$$P_Y = 3P_{Yp} = -5.13 MW$$

**Thus system Y is not the load, it supplies 5.13MW.**

→ The per-phase power supplied to system **X** is:

$$P_{Xp} = -|\mathbf{V}_{an}| |\mathbf{I}_{aA}| \cos(-30 + 180.93) = 1.64 MW$$

The total power supplied to system **X** is:

$$P_X = 3P_{Xp} = 4.91 MW$$

→ Is power being conserved?