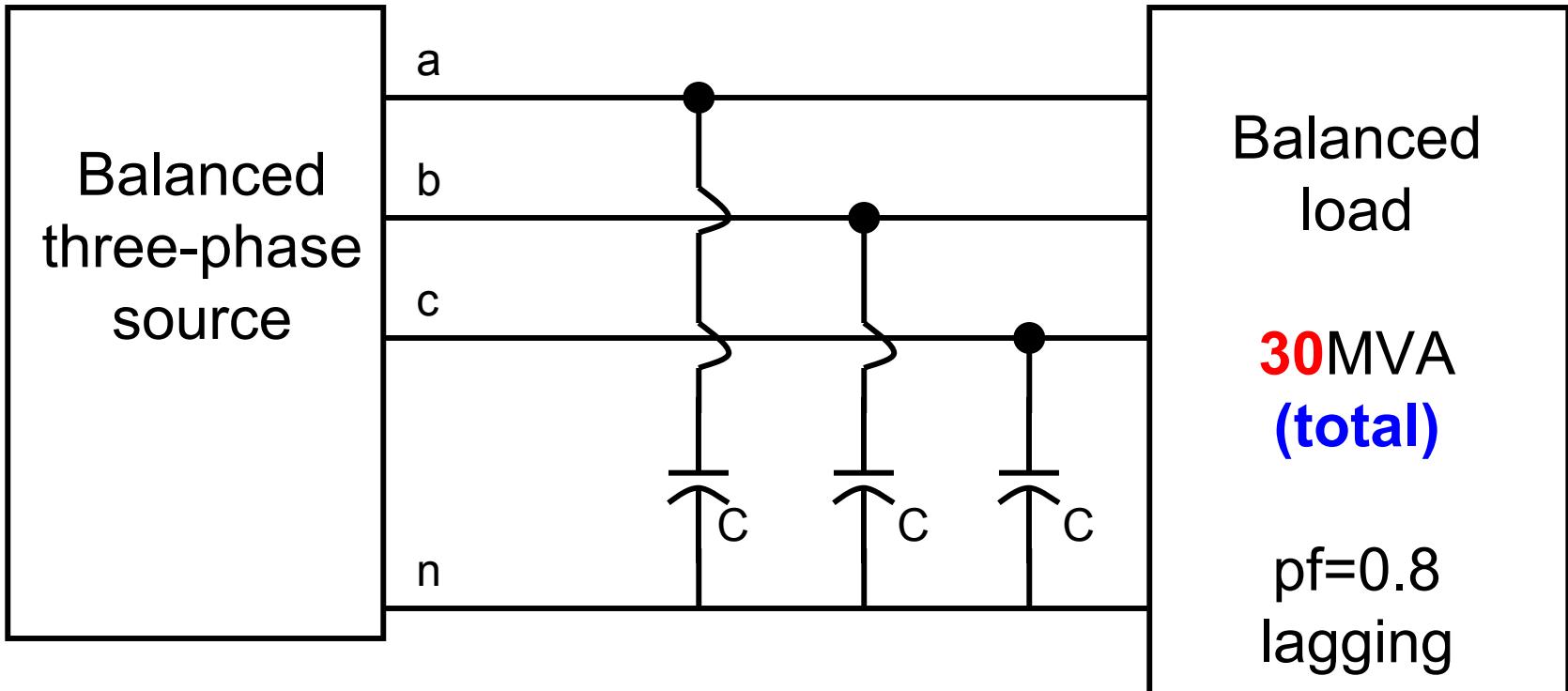


ECSE 210: Circuit Analysis

Lecture #20:
Three-Phase Circuits
Frequency Response

Power Factor Correction

- Line voltage is 40kV rms at 60Hz.
- Choose capacitors such that $\text{pf}=0.9$ lagging.




Power Factor Correction

→ The line to neutral voltage is given by:

$$|V_{an}| = \frac{40kV}{\sqrt{3}} = 23.09kV \text{ rms}$$

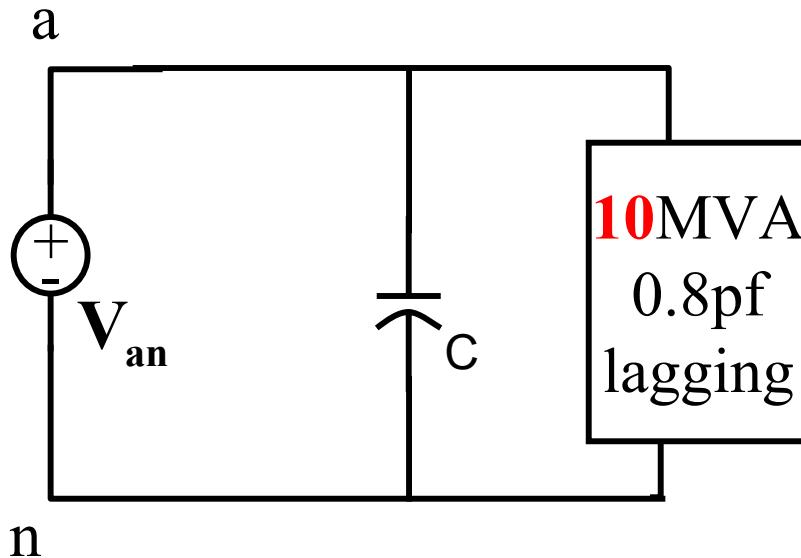→ The per-phase equivalent circuit is therefore:



$$S_{\text{old}} = 10 \angle \arccos(0.8) \text{ MVA}$$

$$= 10 \angle 36.87^\circ \text{ MVA}$$



$$\theta_V - \theta_I > 0$$

For the old pf:

$$S_{\text{old}} = 8 + 6j \text{ MVA}$$

Power Factor Correction

$$\mathbf{S}_{\text{old}} = 10 \angle 36.87^\circ \text{ MVA} = 8 + 6j \text{ MVA}$$

$$\theta_{\text{old}} = 36.87^\circ$$

$$\theta_{\text{new}} = \arccos(0.9) = 25.84^\circ$$


lagging pf $\rightarrow \theta_{\text{new}} > 0$

$$\mathbf{S}_{\text{new}} = 8 + j8 \tan(25.84^\circ) = 8 + j3.88 \text{ MVA}$$

$$\mathbf{S}_{\text{new}} = \mathbf{S}_{\text{cap}} + \mathbf{S}_{\text{old}} \quad \mathbf{S}_{\text{cap}} = \mathbf{S}_{\text{new}} - \mathbf{S}_{\text{old}} = -2.12j \text{ MVA}$$


$$\mathbf{S}_{\text{cap}} = \frac{V_{an}^2}{Z^*} = -j\omega C V_{an}^2$$
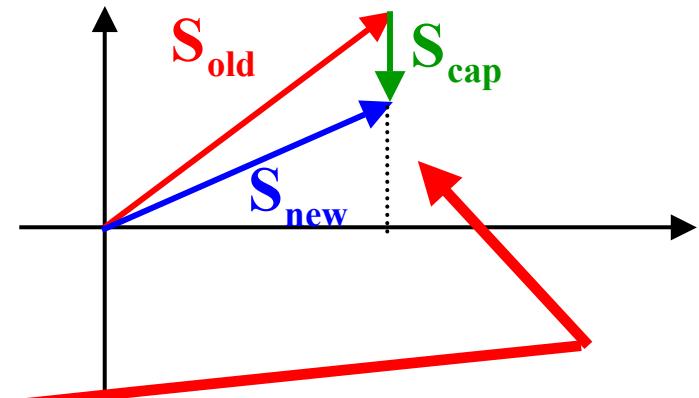
$$C = \frac{2.12 \times 10^6}{377(23.09 \times 10^3)^2} = 10.6 \mu F$$



Frequency Characteristics

→ What is V_o as a function of V_I ?

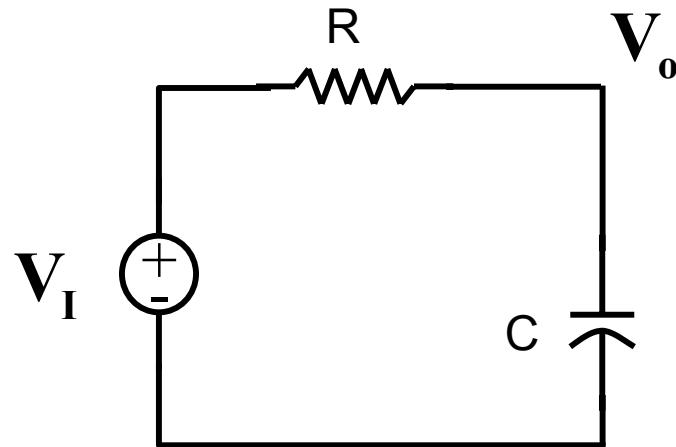

$$Z_C = \frac{1}{sC} \quad s = j\omega$$

$$Z_R = R$$

→ Voltage divider:


$$V_o = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} V_I = \frac{1}{1 + sRC} V_I = \frac{1}{1 + j\omega RC} V_I$$

Frequency Characteristics

$$V_o = \frac{1}{1 + sRC} V_I$$

- Input output relation is a function of frequency.
 - The input and output have the same frequency, but a different magnitude and phase.
- (This is a fundamental property of linear circuits.)**
- We define the transfer function:
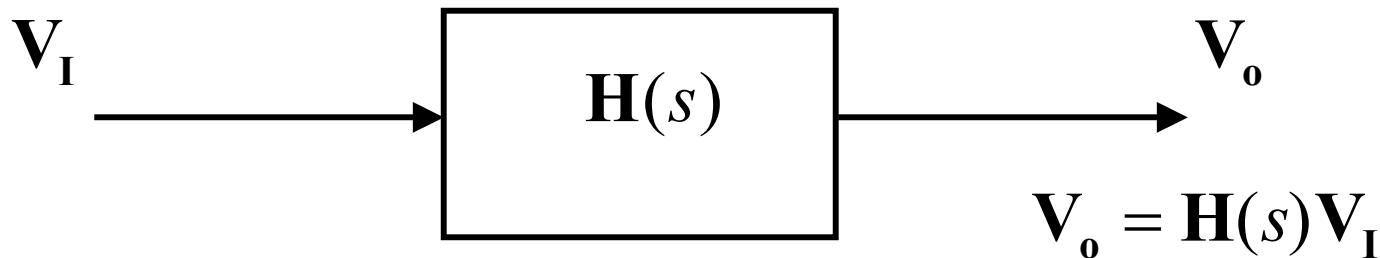
$$H(s) = \frac{V_o}{V_I} = \frac{1}{1 + sRC}$$




Frequency Response

→ At frequency ω :

$$\mathbf{V}_o = \mathbf{H}(j\omega) \mathbf{V}_I$$

$$|\mathbf{V}_o| \angle \theta_o = (|\mathbf{H}(j\omega)| \angle \theta_h)(|\mathbf{V}_I| \angle \theta_I)$$


$$|\mathbf{V}_o| \angle \theta_o = |\mathbf{H}(j\omega)| |\mathbf{V}_I| \angle \theta_I + \theta_h$$

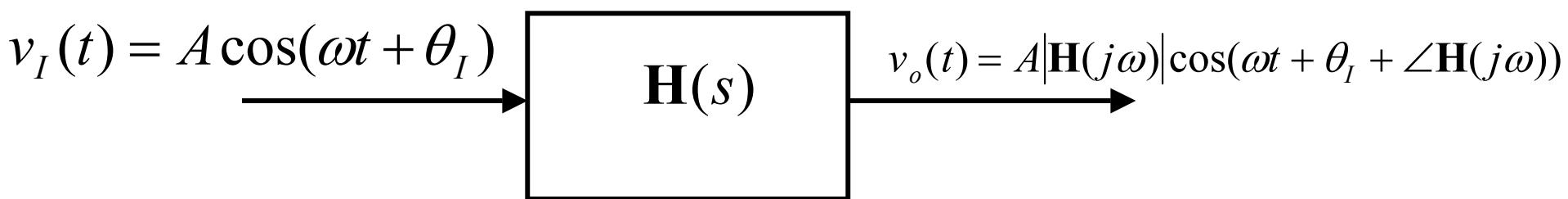

- Same frequency ω .
- Amplitude is multiplied by $|\mathbf{H}(j\omega)|$.
- Phase is shifted by the angle of $|\mathbf{H}(j\omega)|$.
- $\mathbf{H}(s)$ is not a phasor!

Network Function

- In general:

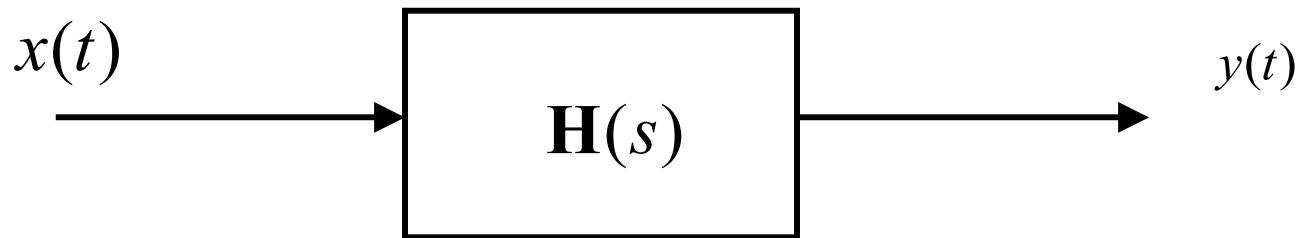

- $x(t)$ may be an input **voltage or current**.
- $y(t)$ may be a **voltage** at the “output” node *or* a **branch current**.
- This leads to four types of network transfer functions.

Network Function

$$(1) \quad x(t)=i(t); \quad y(t)=v(t) \rightarrow \quad \mathbf{Y}(s) = \mathbf{H}(s)\mathbf{X}(s); \quad \mathbf{V}(s) = \mathbf{H}(s)\mathbf{I}(s)$$
$$\mathbf{H}(s) = \mathbf{Z}(s)$$

Note: in this case $\mathbf{Z}(s)$ is a **transfer** impedance,
not a driving point impedance.

$$(2) \quad x(t)=v(t); \quad y(t)=i(t) \rightarrow \quad \mathbf{Y}(s) = \mathbf{H}(s)\mathbf{X}(s); \quad \mathbf{I}(s) = \mathbf{H}(s)\mathbf{V}(s)$$

$\mathbf{H}(s)$ is a **transfer** admittance.

$$(3) \quad x(t)=v_i(t); \quad y(t)=v_o(t) \rightarrow \quad \mathbf{Y}(s) = \mathbf{H}(s)\mathbf{X}(s); \quad \mathbf{V}_o(s) = \mathbf{H}(s)\mathbf{V}_I(s)$$
$$\mathbf{H}(s) = \mathbf{G}_V(s)$$

Note: $\mathbf{G}_V(s)$ is a **voltage gain**.


Network Function

$$(4) \quad x(t)=i_i(t); \quad y(t)=i_o(t) \rightarrow \mathbf{Y}(s) = \mathbf{H}(s)\mathbf{X}(s); \quad \mathbf{I}_o(s) = \mathbf{H}(s)\mathbf{I}_I(s)$$
$$\mathbf{H}(s) = \mathbf{G}_I(s)$$

Note: $\mathbf{G}_I(s)$ is a **current gain**.

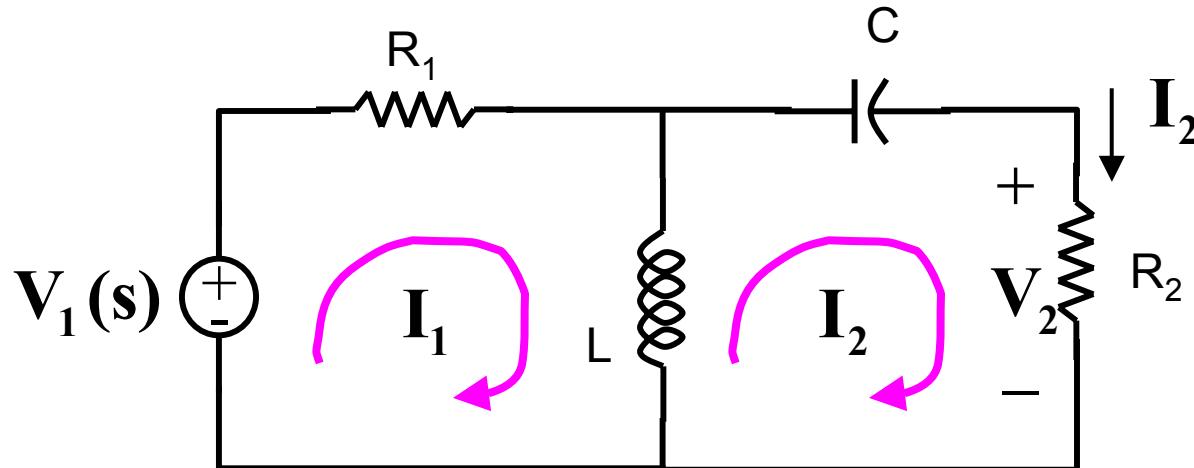Example 1

Find the transfer admittance $I_2(s)/V_1(s)$ and the voltage gain $V_2(s)/V_1(s)$ for the network provided below.



Mesh equations:

$$R_1 I_1(s) + sL(I_1(s) - I_2(s)) = V_1(s)$$

$$sL(I_2(s) - I_1(s)) + \frac{I_2(s)}{sC} + R_2 I_2(s) = 0$$

Example 1

$$\left\{ \begin{array}{l} (R_1 + sL)\mathbf{I}_1(s) - sL\mathbf{I}_2(s) = \mathbf{V}_1(s) \\ -sL\mathbf{I}_1(s) + \left(R_2 + sL + \frac{1}{sC} \right) \mathbf{I}_2(s) = 0 \end{array} \right. \quad \begin{array}{l} \star \\ \circledcirc \end{array}$$

→ Solve for \mathbf{I}_2 :

$$\circledcirc \rightarrow \mathbf{I}_1(s) = \frac{1}{sL} \left(R_2 + sL + \frac{1}{sC} \right) \mathbf{I}_2(s)$$

Substituting into $\star \rightarrow$

$$\frac{(R_1 + sL)}{sL} \left(R_2 + sL + \frac{1}{sC} \right) \mathbf{I}_2(s) - sL\mathbf{I}_2(s) = \mathbf{V}_1(s)$$

Example 1

$$\frac{(R_1 + sL)}{sL} \left(R_2 + sL + \frac{1}{sC} \right) I_2(s) - sL I_2(s) = V_1(s)$$

$$I_2(s) = \frac{sL V_1(s)}{(R_1 + sL) \left(R_2 + sL + \frac{1}{sC} \right) - s^2 L^2}$$

$$I_2(s) = \frac{LC s^2 V_1(s)}{(R_1 + R_2)LC s^2 + (L + R_1 R_2 C)s + R_1}$$

$$V_2(s) = \frac{\longrightarrow R_2 LC s^2 V_1(s)}{(R_1 + R_2)LC s^2 + (L + R_1 R_2 C)s + R_1}$$

Example 1


→ Transfer admittance:

$$Y(s) = \frac{I_2(s)}{V_1(s)} = \frac{LCs^2}{(R_1 + R_2)LCs^2 + (L + R_1R_2C)s + R_1}$$

→ Voltage gain:

$$G_v(s) = \frac{V_2(s)}{V_1(s)} = \frac{R_2LCs^2}{(R_1 + R_2)LCs^2 + (L + R_1R_2C)s + R_1}$$

Example 2: Integrator

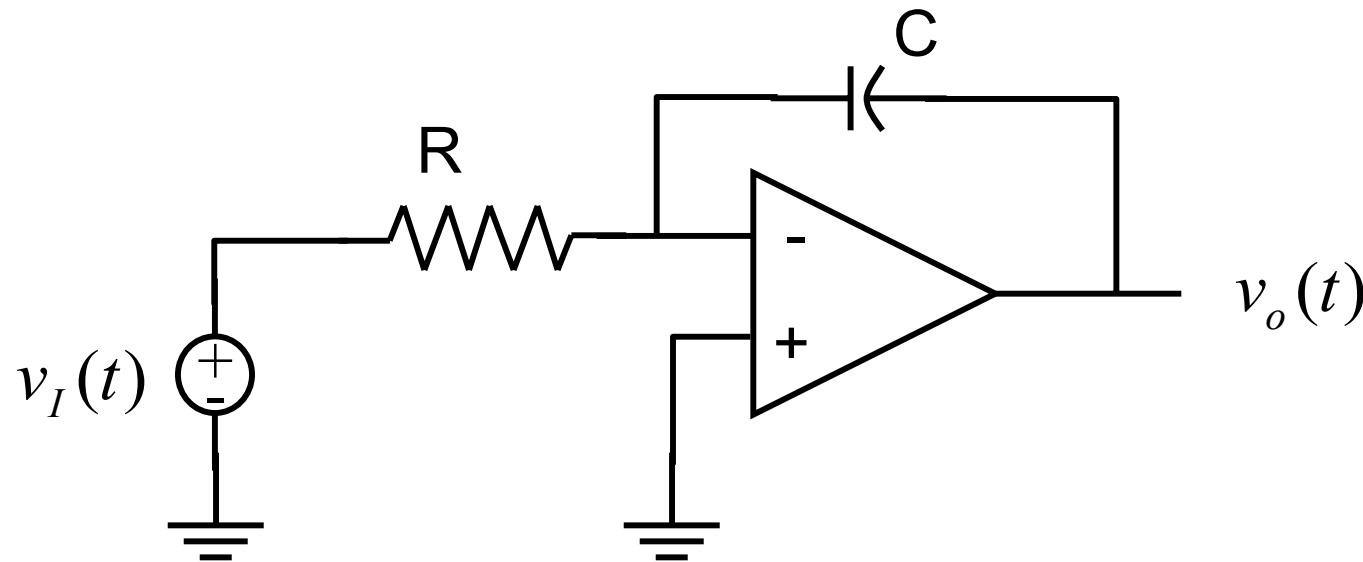


KCL in time domain

$$\frac{v_I(t)}{R} + C \frac{dv_o(t)}{dt} = 0 \quad \rightarrow \quad \frac{dv_o(t)}{dt} = -\frac{1}{RC} v_I(t)$$

$$v_o(t) = -\frac{1}{RC} \int_{0+}^t v_I(t) dt + v_o(0+) = -\frac{1}{RC} \int_{0+}^t v_I(t) dt$$

Assuming zero initial conditions.

Example 2: Integrator

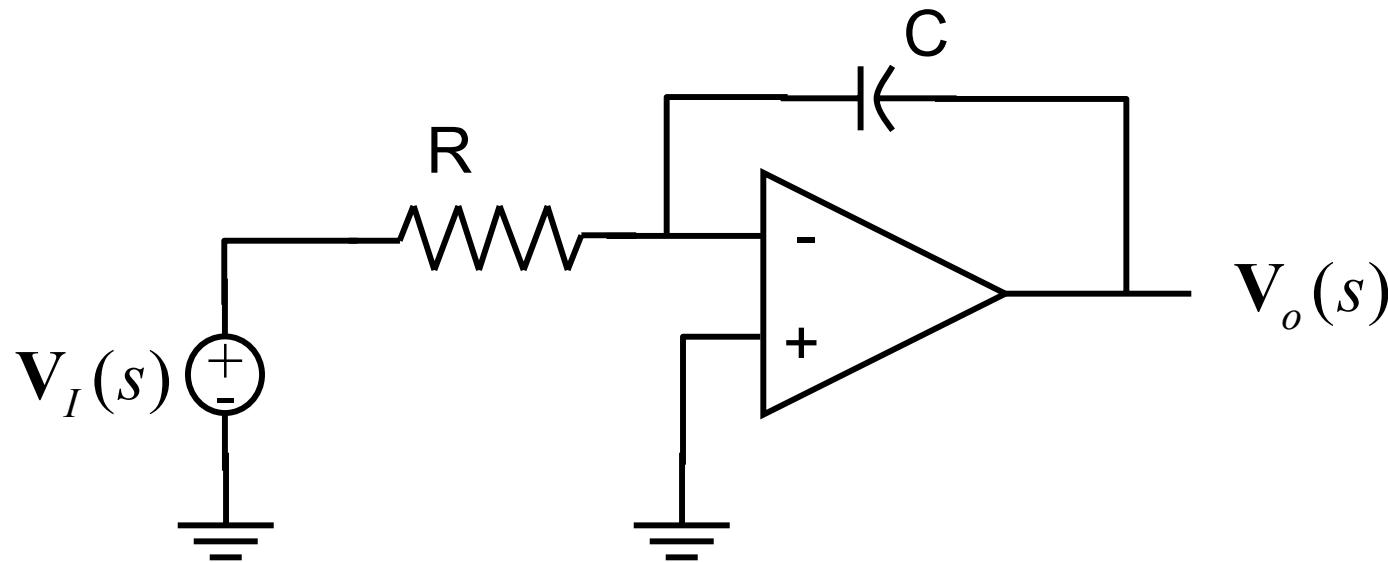


KCL in frequency domain

$$\frac{V_I(s)}{R} + sCV_o(s) = 0 \quad \rightarrow \quad V_o(s) = -\frac{1}{sRC} V_I(s)$$

→ Division by s is equivalent to integration

(Assuming zero initial conditions)

Example 3: Differentiator

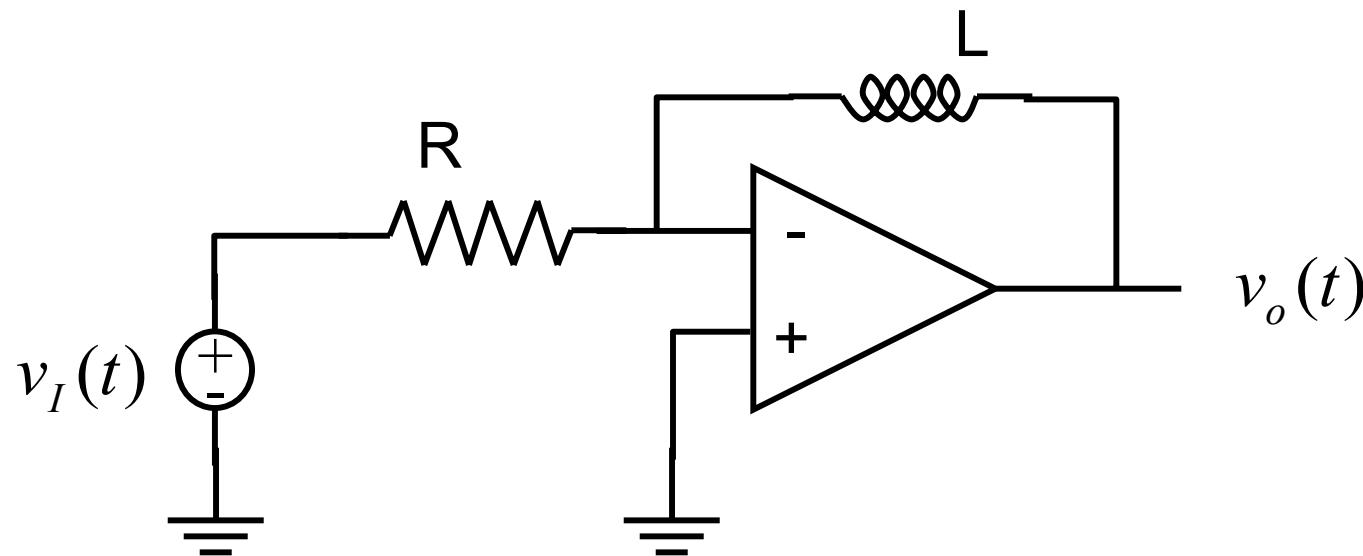


KCL in time domain

$$\frac{v_I(t)}{R} + \frac{1}{L} \int_{0+}^t v_o(t) dt + i_L(0+) = 0 \quad \rightarrow \quad \int_{0+}^t v_o(t) dt = -\frac{L}{R} v_I(t)$$

Assuming zero initial condition.

$$v_o(t) = -\frac{L}{R} \frac{dv_I(t)}{dt}$$

Example 3: Differentiator

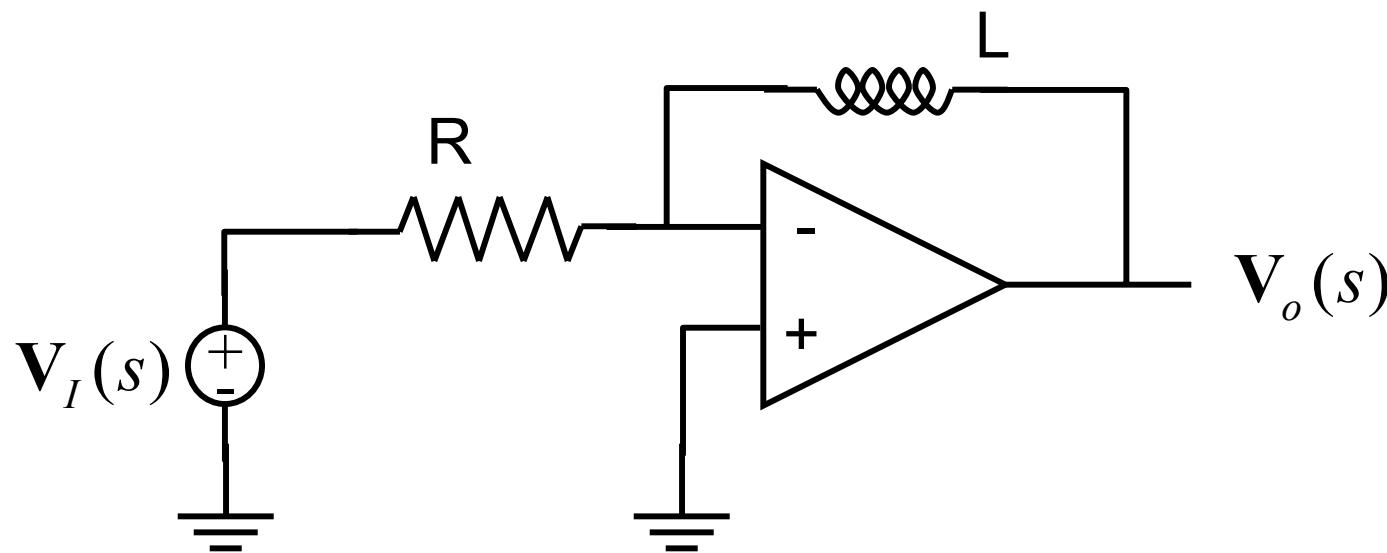

KCL in frequency domain

$$\frac{V_I(s)}{R} + \frac{V_o(s)}{sL} = 0 \quad \rightarrow \quad V_o(s) = -\frac{sL}{R} V_I(s)$$

→ Multiplication by s is equivalent to differentiation

(Assuming zero initial conditions)