

# **ECSE 210: Circuit Analysis**


**Lecture #21:**

**Frequency Response**

**Decibel Scale**
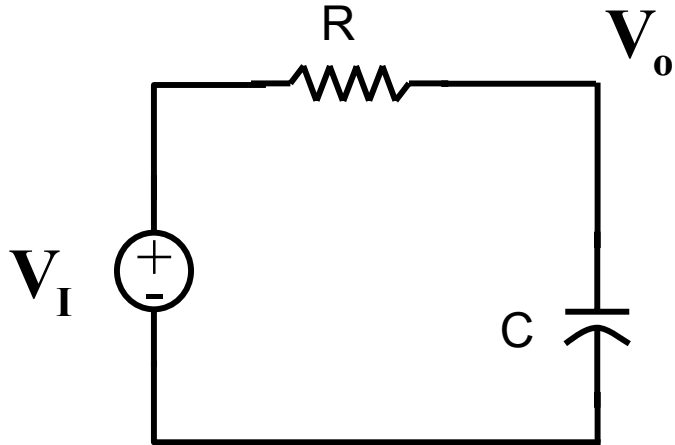
# Example

What is  $V_o$  as a function of  $V_i$ ?



$$Z_C = \frac{1}{sC} \quad s = j\omega$$

$$Z_R = R$$

→ Voltage divider:

$$V_o = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} V_i = \frac{1}{1 + sRC} V_i = \frac{1}{1 + j\omega RC} V_i$$

# Frequency Characteristics

$$\mathbf{H}(s) = \frac{\mathbf{V}_o}{\mathbf{V}_I} = \frac{1}{1 + sRC} = \frac{1/RC}{s + 1/RC} \quad R = 1k\Omega \quad \omega = 2\pi f$$


$$C = 1\mu F$$

$$\mathbf{H}(s) = \frac{\mathbf{V}_o}{\mathbf{V}_I} = \frac{1}{1 + sRC} = \frac{1000}{s + 1000}$$

$$\mathbf{H}(j\omega) = \frac{1000}{j\omega + 1000}$$


$f$	0	50	100	159	250	500	1000	10000	100000
$\omega$	0	314	628	1000	1570	3141	6283	62832	628320
$ \mathbf{H}(j\omega) $	1	0.95	0.85	0.707	0.54	0.3	0.16	0.016	0.0016
$\angle\mathbf{H}(j\omega)$	0	-17	-32	-45	-58	-72	-81	-89	-89.9

# Amplitude Plot

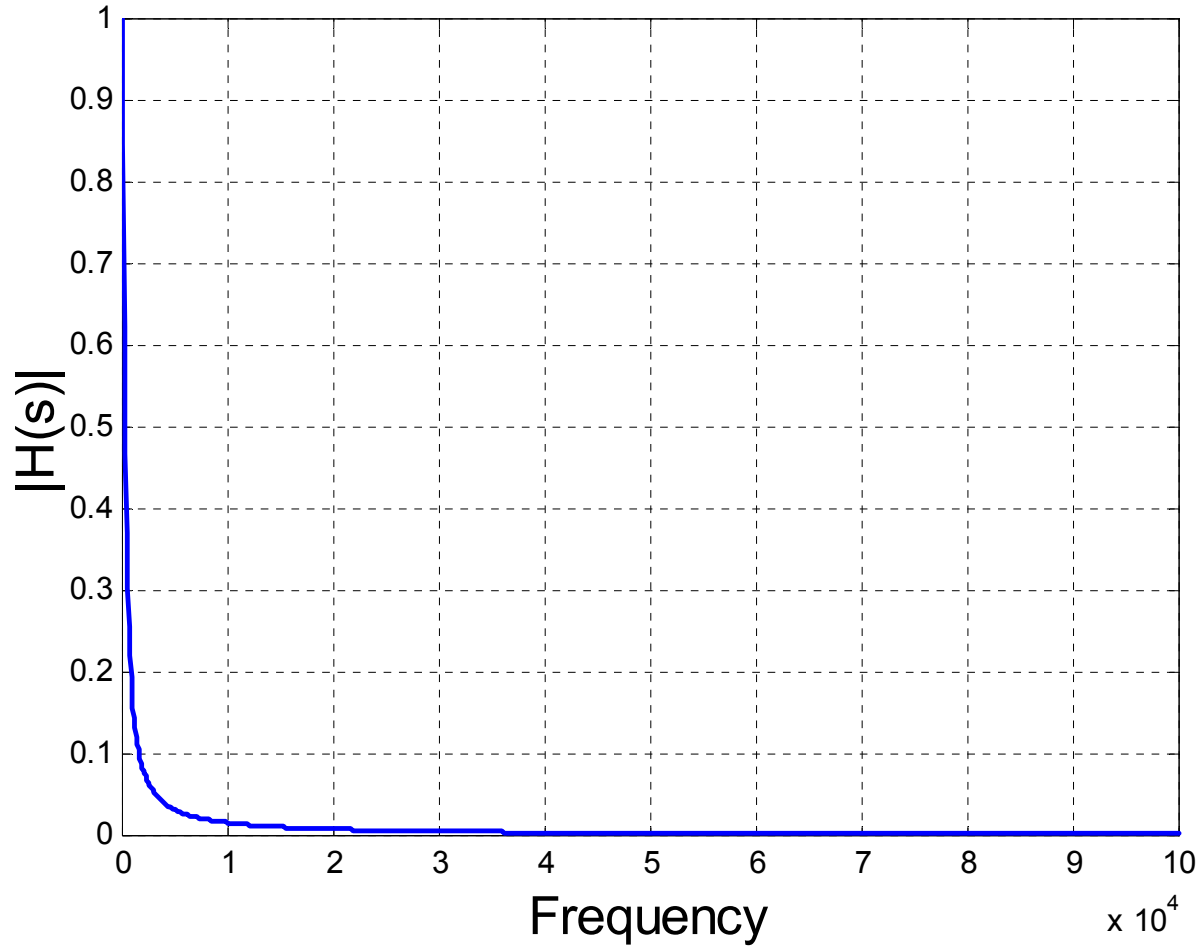


**Frequency on a linear scale**

# Amplitude Plot

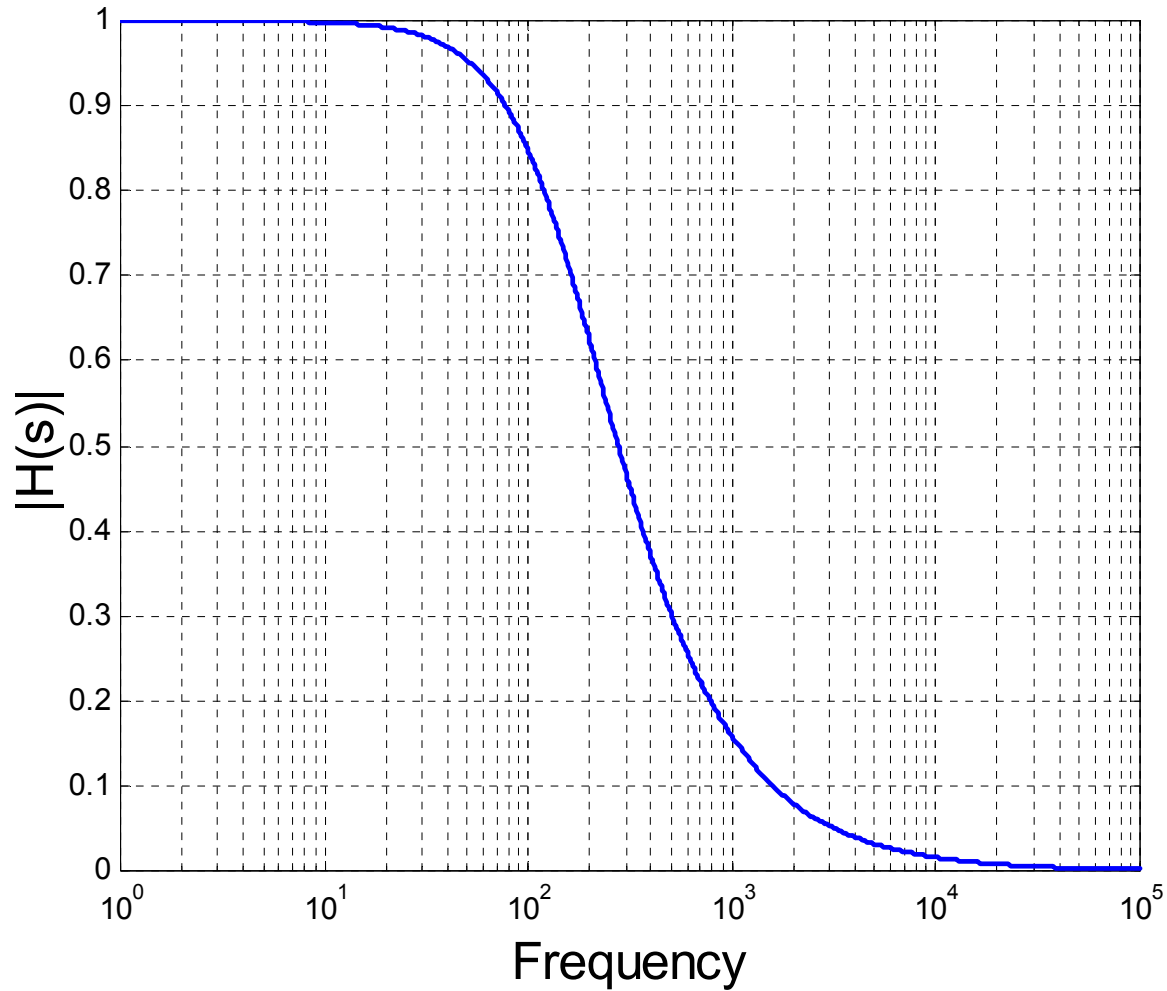

**Frequency on a log scale**

# Phase Plot

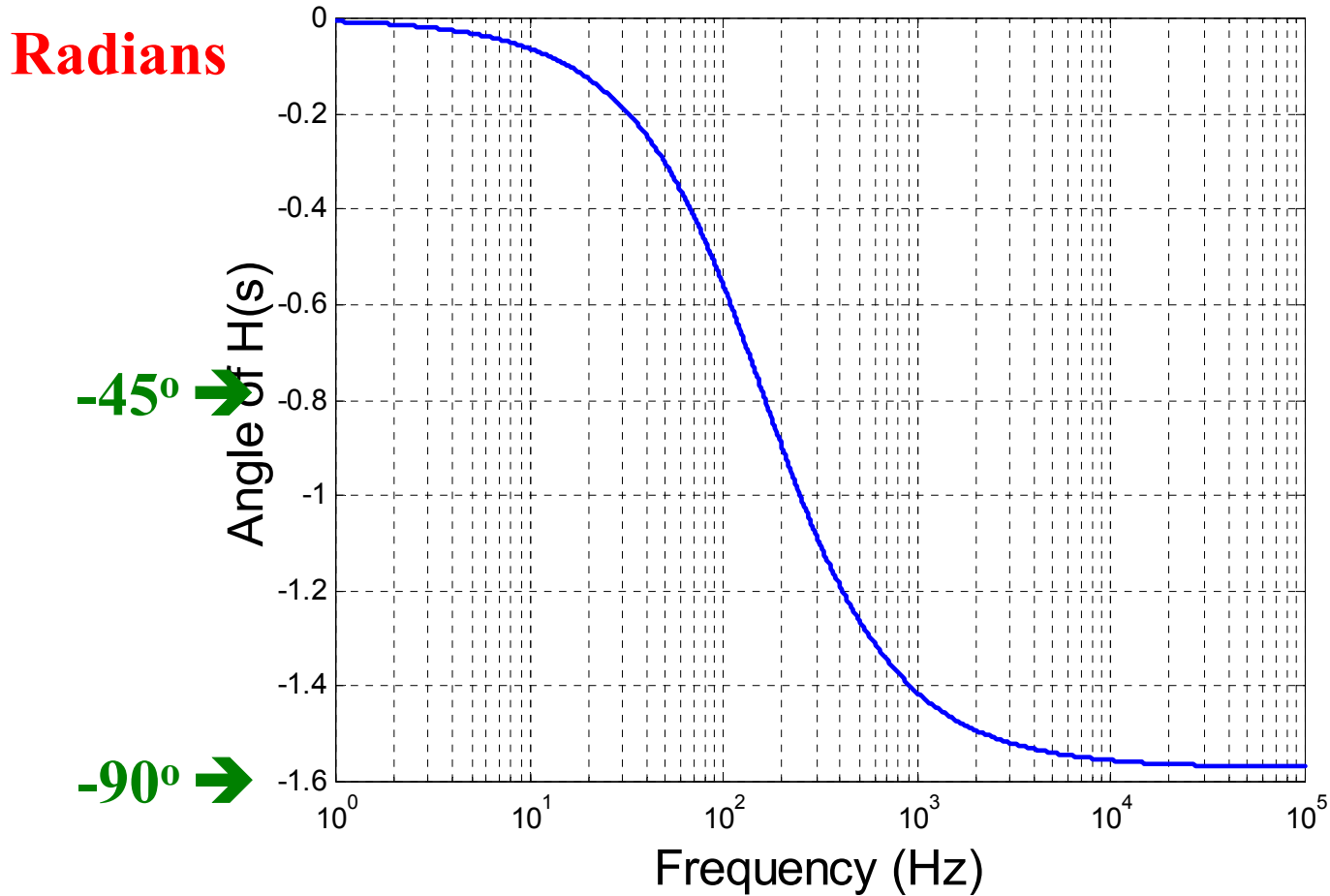

**Frequency on a log scale**

# Decibel Scale

---

- Experimental evidence shows that the human ear perceives loudness according to a logarithmic scale.
- The unit used to compare powers is the **decibel** which is defined as:

$$A(dB) = 10 \log_{10} \left( \frac{P_1}{P_2} \right)$$

where  $P_1$  and  $P_2$  are the powers to be compared.

# Example: Intensity of Sound

dB	Power ratio	Example
0	1	Threshold of hearing
20	$10^2$	Quiet room
30	$10^3$	Watch ticking at 1 m.
40	$10^4$	Quiet street
50	$10^5$	Quiet conversation
60	$10^6$	Quiet motor at 1 m.
70	$10^7$	Loud conversation
80	$10^8$	Door slamming
90	$10^9$	Busy typing room
100	$10^{10}$	Near loud motor / horn
110	$10^{11}$	Pneumatic drill
120	$10^{12}$	Near jet engine / <b>rock concert</b>
130	$10^{13}$	Threshold of pain



# dB Scale for Voltages

Compare two voltages  $V_1$  and  $V_2$ :

→ Choose a reference resistor  $R$

→ The power that  $V_1$  would dissipate in  $R$  is:

$$P_1 = \frac{V_1^2}{R}$$

→ The power that  $V_2$  would dissipate in  $R$  is:

$$P_2 = \frac{V_2^2}{R}$$

$$\begin{aligned} A(\text{dB}) &= 10 \log_{10} \left( \frac{P_1}{P_2} \right) = 10 \log_{10} \left( \frac{V_1^2}{R} \frac{R}{V_2^2} \right) \\ &= 10 \log_{10} \left( \frac{V_1}{V_2} \right)^2 = 20 \log_{10} \left( \frac{V_1}{V_2} \right) \end{aligned}$$

# dB Scale for a Transfer Function

Voltage transfer function:  $|H(j\omega)| = \frac{|V_o|}{|V_i|}$

$$A(dB) = 20 \log_{10}(|H(j\omega)|)$$


**Example:**  $H(j\omega) = \frac{1000}{j\omega + 1000}$        $|H(j\omega)| = \frac{1000}{\sqrt{\omega^2 + 1000^2}}$

$f$	0	50	100	159	250	500	1000	10000	100000
$\omega$	0	314	628	1000	1570	3141	6283	62832	628320
$ H(j\omega) $	1	0.95	0.85	0.707	0.54	0.3	0.16	0.016	0.0016
$dB$	0	-0.4	-1.4	-3	-5.3	-10.5	-15.9	-35.9	-55.9

# dB Scale for a Transfer Function

$$|\mathbf{H}(j\omega)| = \frac{1000}{\sqrt{\omega^2 + 1000^2}}$$

**Decibels**  
**(linear scale)**

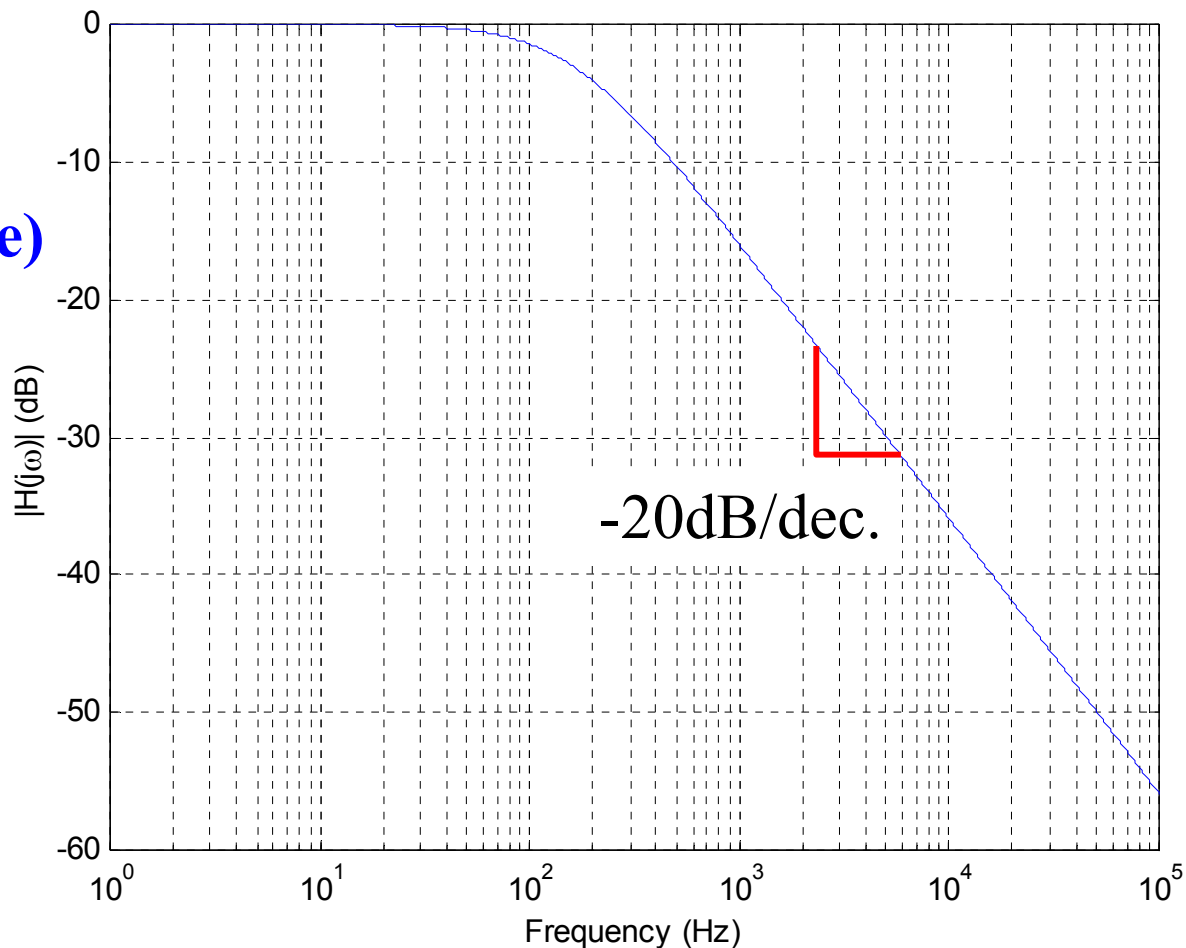

**Frequency (log scale)**

# dB Scale for a Transfer Function

$$\mathbf{H}(s) = \frac{k}{s-p} \quad \mathbf{H}(j\omega) = \frac{k}{j\omega-p} \quad |\mathbf{H}(j\omega)| = \frac{k}{\sqrt{\omega^2 + p^2}}$$

For  $\omega \gg p$

$$|\mathbf{H}(j\omega)| = \frac{k}{\omega}$$

$$A(\text{dB}) = 20 \log_{10} \left( \frac{k}{\omega} \right) = 20 \log_{10}(k) - 20 \log_{10}(\omega)$$

If we multiply  $\omega$  by 10  $\rightarrow$  We subtract 20 from A(dB)

$\rightarrow$  Slope is -20dB/decade.

# Poles and Zeros

---

In general, network functions can be expressed as the ratio of two polynomials in  $s$ :

$$\mathbf{H}(s) = \frac{N(s)}{D(s)} = \frac{a_m s^m + a_{m-1} s^{m-1} + \text{L} + a_1 s + a_o}{b_n s^n + b_{n-1} s^{n-1} + \text{L} + b_1 s + b_o}$$

where  $N(s)$  is the numerator polynomial of degree  $m$  and  $D(s)$  is the denominator polynomial of degree  $n$

It is common to factor  $N(s)$  and  $D(s)$  to yield:

$$\mathbf{H}(s) = \frac{K_o (s - z_1)(s - z_2) \text{L} (s - z_m)}{(s - p_1)(s - p_2) \text{L} (s - p_n)}$$

# Poles and Zeros

$$\mathbf{H}(s) = \frac{K_o (s - z_1)(s - z_2) \dots (s - z_m)}{(s - p_1)(s - p_2) \dots (s - p_n)}$$

where:  $K_o$  is a constant  
 $z_i$  are the roots of  $N(s)$   
 $p_i$  are the roots of  $D(s)$

Note:  $s = z_i \rightarrow \mathbf{H}(s) = 0$   
 $\rightarrow z_i$  are the *zeros* of  $\mathbf{H}(s)$

$\mathbf{H}(s) \rightarrow \infty$  as  $s \rightarrow p_i$   
 $\rightarrow p_i$  are the *poles* of  $\mathbf{H}(s)$

Note:  $z_i$  and  $p_i$  may be complex numbers

# Transfer Function

$$\mathbf{H}(s) = \frac{K_o (s - z_1)(s - z_2) \dots (s - z_m)}{(s - p_1)(s - p_2) \dots (s - p_n)} = \frac{K_o \prod_{i=1}^m (s - z_i)}{\prod_{i=1}^n (s - p_i)}$$

$$|\mathbf{H}(s)| = \frac{K_o \prod_{i=1}^m |(s - z_i)|}{\prod_{i=1}^n |(s - p_i)|}$$

$$\angle \mathbf{H}(s) = \sum_{i=1}^m \angle (s - z_i) - \sum_{i=1}^n \angle (s - p_i)$$

$$|\mathbf{H}(s)|(dB) = 20 \log_{10} (|\mathbf{H}(s)|) = 20 \log_{10} (K_o) + \sum_{i=1}^m 20 \log_{10} (|(s - z_i)|) - \sum_{i=1}^n 20 \log_{10} (|(s - p_i)|)$$

# Transfer Function

---

1. The amplitude and phase plots of a complex transfer function can be easily obtained by adding the factors forming the numerators and denominators.
2. Studying the behavior of first and second order circuits will allow us to handle more complex higher order circuits using the above technique.
3. The **amplitude (dB) and phase plots** on a log scale are called the Bode plots.