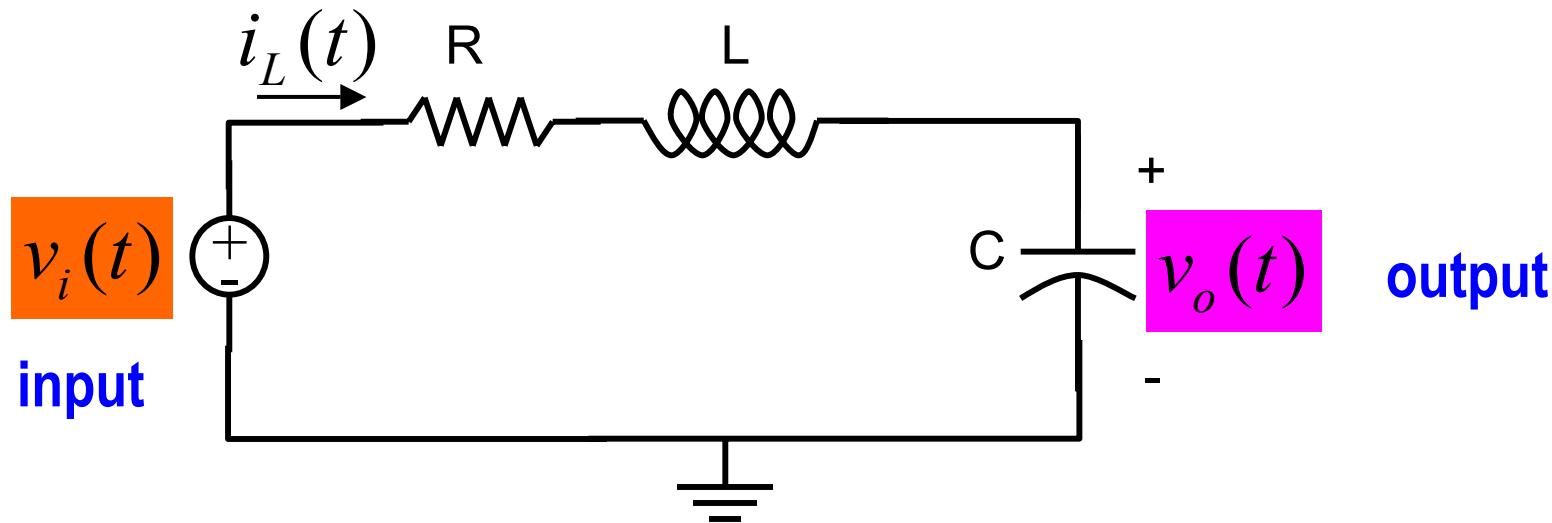


ECSE 210: Circuit Analysis

Lecture #24:
Complex Poles
Circuit Dynamics


Poles and Circuit Dynamics



$$\left\{ \begin{array}{l} \text{KCL} \rightarrow C \frac{dv_o}{dt} = i_L \quad \rightarrow \quad C \frac{d^2v_o}{dt^2} = \frac{di_L}{dt} \\ \text{KVL} \rightarrow Ri_L + L \frac{di_L}{dt} + v_o = v_i \end{array} \right.$$

→ $RC \frac{dv_o}{dt} + LC \frac{d^2v_o}{dt^2} + v_o = v_i$


Poles and Circuit Dynamics

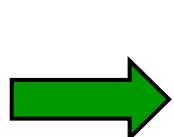

$$\frac{d^2v_o}{dt^2} + \frac{R}{L} \frac{dv_o}{dt} + \frac{1}{LC} v_o = \frac{v_i}{LC}$$

R=6Ω L=1H C=0.04F

$$v_i = 2 \cos(3t)$$

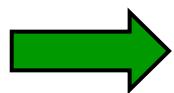

$$\frac{d^2v_o}{dt^2} + 6 \frac{dv_o}{dt} + 25v_o = 25v_i$$


- Second order circuit.
- Has a **forced** and **natural** response.

The input (forcing function) is:

$$v_i = 2 \cos(3t)$$

Poles and Circuit Dynamics

Natural response:

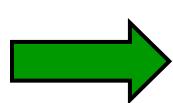

$$\frac{d^2v_o}{dt^2} + 6\frac{dv_o}{dt} + 25v_o = 0$$

$$R=6\Omega$$

$$L=1H$$

$$C=0.04F$$

$$v_i = 2 \cos(3t)$$

Characteristic polynomial: $s^2 + 6s + 25 = 0$

Roots: $s_{1,2} = \frac{-6 \pm \sqrt{36 - 100}}{2} = -3 \pm 4j$

→ Natural response of the form:

$$v_n = A_n e^{-3t} \cos(4t) + B_n e^{-3t} \sin(4t)$$

Poles and Circuit Dynamics

Forced response:

Input (forcing function): $v_i = 2 \cos(3t)$

→ Forced response of the form:

$$v_f = A_f \cos(3t) + B_f \sin(3t)$$

Total response:

$$\begin{aligned} v_o = v_n + v_f &= A_n e^{-3t} \cos(4t) + B_n e^{-3t} \sin(4t) \\ &\quad + A_f \cos(3t) + B_f \sin(3t) \end{aligned}$$


Poles and Circuit Dynamics

$$v_o = v_n + v_f = A_n e^{-3t} \cos(4t) + B_n e^{-3t} \sin(4t)$$
$$+ A_f \cos(3t) + B_f \sin(3t)$$

Determine the constants:

$$\frac{d^2 v_o}{dt^2} + 6 \frac{dv_o}{dt} + 25 v_o = 25 v_i$$

$$\frac{d^2(v_f + v_n)}{dt^2} + 6 \frac{d(v_f + v_n)}{dt} + 25(v_f + v_n) = 25 v_i$$
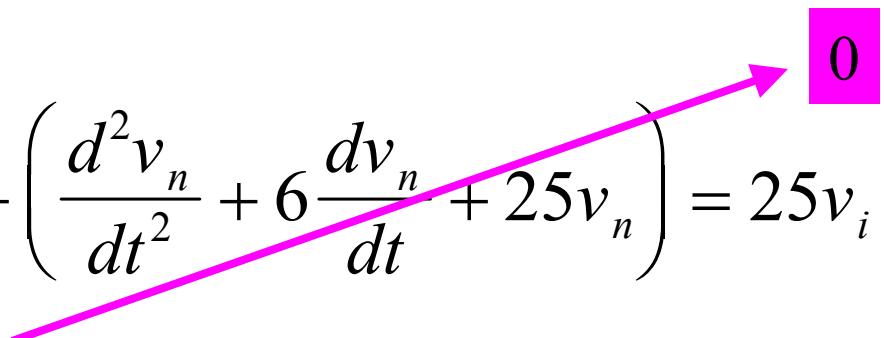
$$\left(\frac{d^2 v_f}{dt^2} + 6 \frac{dv_f}{dt} + 25 v_f \right) + \left(\frac{d^2 v_n}{dt^2} + 6 \frac{dv_n}{dt} + 25 v_n \right) = 25 v_i$$


Poles and Circuit Dynamics

Substituting

$$v_f = A_f \cos(3t) + B_f \sin(3t) \quad \text{and} \quad v_i = 2 \cos(3t)$$

into

$$\frac{d^2v_f}{dt^2} + 6\frac{dv_f}{dt} + 25v_f = 25v_i$$

gives:

$$(-9A_f \cos(3t) - 9B_f \sin(3t)) + 6(-3A_f \sin(3t) + 3B_f \cos(3t))$$

$$+ 25(A_f \cos(3t) + B_f \sin(3t)) = 50 \cos(3t)$$

$$\left. \begin{array}{l} 16A_f + 18B_f = 50 \\ -18A_f + 16B_f = 0 \end{array} \right\} \quad \begin{array}{l} A_f = 1.38 \\ B_f = 1.55 \end{array}$$

Poles and Circuit Dynamics

$$\left. \begin{array}{l} A_f = 1.38 \\ B_f = 1.55 \end{array} \right\} v_f = 1.38 \cos(3t) + 1.55 \sin(3t)$$

Equivalent more compact form:

$$v_f = V_f \cos(3t + \theta_f) = V_f \cos(\theta_f) \cos(3t) - V_f \sin(\theta_f) \sin(3t)$$

$$V_f = \sqrt{1.38^2 + 1.55^2} = 2.07$$

$$\left. \begin{array}{l} 2.07 \cos(\theta_f) = 1.38 \\ 2.07 \sin(\theta_f) = -1.55 \end{array} \right\} \theta_f = \arctan\left(-\frac{1.55}{1.38}\right) = -48.3^\circ$$

$$v_f = 2.07 \cos(3t - 48.3^\circ) \rightarrow \text{Forced response}$$

Poles and Circuit Dynamics

$$v_o = v_n + v_f = A_n e^{-3t} \cos(4t) + B_n e^{-3t} \sin(4t) \\ + 1.38 \cos(3t) + 1.55 \sin(3t)$$

Determine the constants (**zero initial conditions**):

$$v_o(0) = A_n + 1.38 = 0 \quad \rightarrow \quad A_n = -1.38$$

$$\frac{dv_o(0)}{dt} = -3A_n + 4B_n + 3 \times 1.55 = -3A_n + 4B_n + 4.65$$

KCL $C \frac{dv_o(0)}{dt} = i_L(0) = 0$

$$-3(-1.38) + 4B_n + 4.65 = 0$$



$$B_n = -2.2$$

Poles and Circuit Dynamics


$$v_o = v_n + v_f = \underbrace{-1.38e^{-3t} \cos(4t) - 2.2e^{-3t} \sin(4t)}_{\text{Natural response}} + \underbrace{1.38 \cos(3t) + 1.55 \sin(3t)}_{\text{Forced response}}$$

At $t=\infty$, the **natural** response dies out. Therefore :

- The **forced** response is the **steady-state** response.

- The **transient** response is due to both the forced and natural response.

Poles and Circuit Dynamics

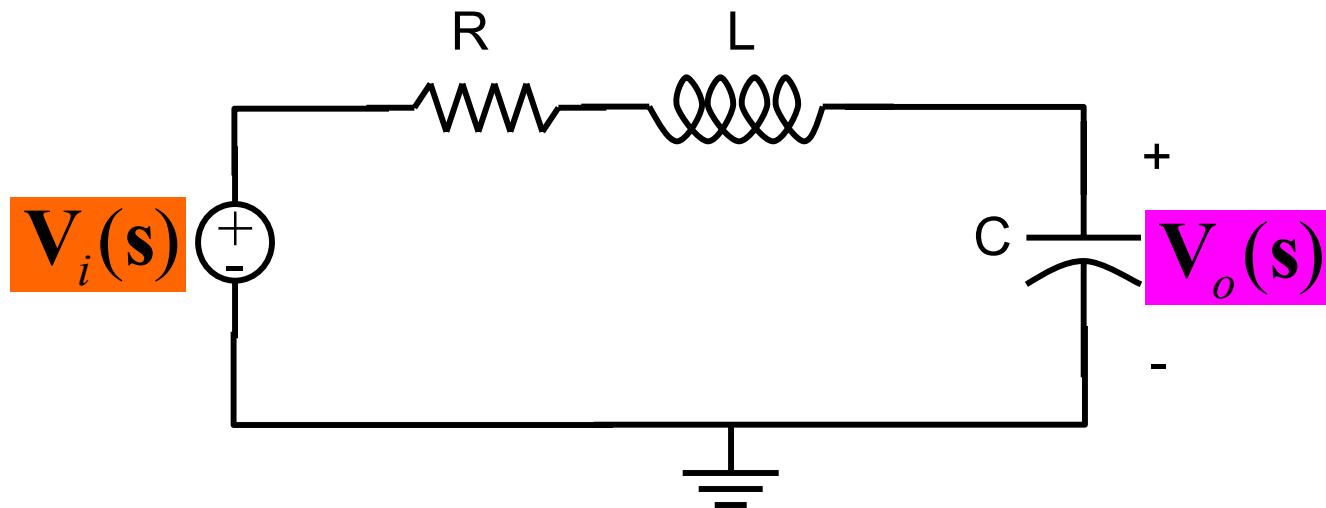


$$V_o(s) = \frac{1/\text{s}C}{R + \text{s}L + 1/\text{s}C} V_i(s) = \frac{1}{LC\text{s}^2 + RC\text{s} + 1} V_i(s)$$

$$H(\text{s}) = \frac{V_o(\text{s})}{V_i(\text{s})} = \frac{1/LC}{\text{s}^2 + \frac{R}{L}\text{s} + \frac{1}{LC}}$$

Poles and Circuit Dynamics
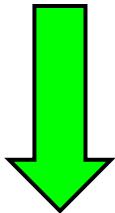
$$\left(\mathbf{s}^2 + \frac{R}{L}\mathbf{s} + \frac{1}{LC} \right) \mathbf{V}_o(\mathbf{s}) = \frac{1}{LC} \mathbf{V}_i(\mathbf{s})$$



$$\frac{d^2v_o}{dt^2} + \frac{R}{L} \frac{dv_o}{dt} + \frac{1}{LC} v_o = \frac{v_i}{LC}$$

Same as the differential equation
we derived in the time domain.

Poles and Circuit Dynamics

What is the **steady-state** response due to $v_i = 2 \cos(3t)$?

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{\frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$R=6\Omega$$

$$L=1H$$

$$C=0.04F$$

$$H(s) = \frac{25}{s^2 + 6s + 25}$$

$$H(j3) = \frac{25}{(j3)^2 + 6(j3) + 25} = 1.03 \angle -48^\circ$$

Steady state response:

$$v_o = 2 |H(j3)| \cos(3t + \angle H(j3)) = 2.06 \cos(3t - 48^\circ)$$

Same result
obtained using
ODE approach.

Poles and Circuit Dynamics

$$v_o = v_n + v_f = A_n e^{-3t} \cos(4t) + B_n e^{-3t} \sin(4t)$$

$$+ 1.38 \cos(3t) + 1.55 \sin(3t)$$

or

$$v_o = v_n + v_f = A_n e^{-3t} \cos(4t) + B_n e^{-3t} \sin(4t)$$

$$+ 2.07 \cos(3t - 48.3^\circ)$$

Next step:

Determine the constants (**zero initial conditions**).