


ECSE 210: Circuit Analysis

Lecture #25:

Generalized Phasors

Damped Sinusoids

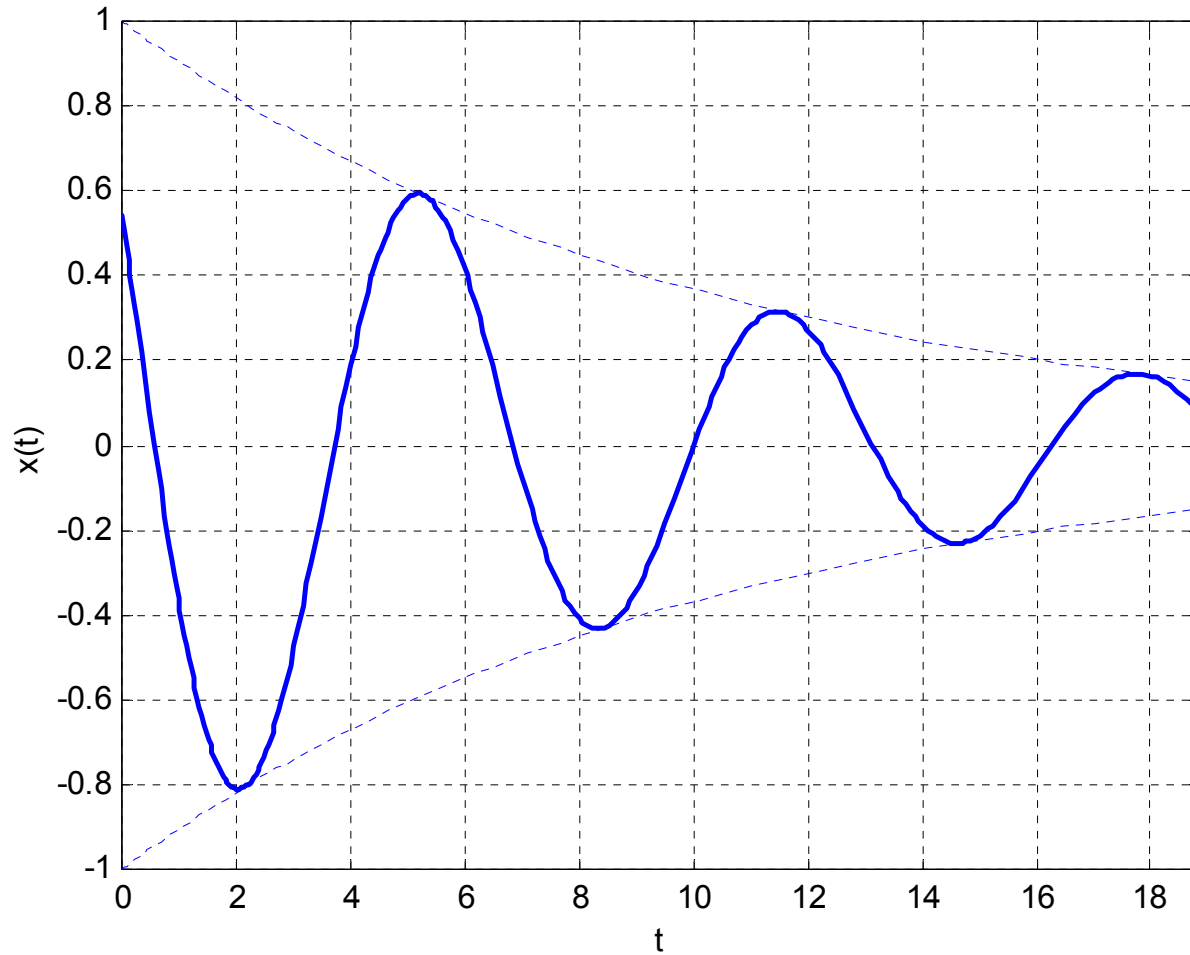
$$x(t) = X_m e^{\sigma t} \cos(\omega t + \phi)$$



$\sigma < 0$

Growing Sinusoids

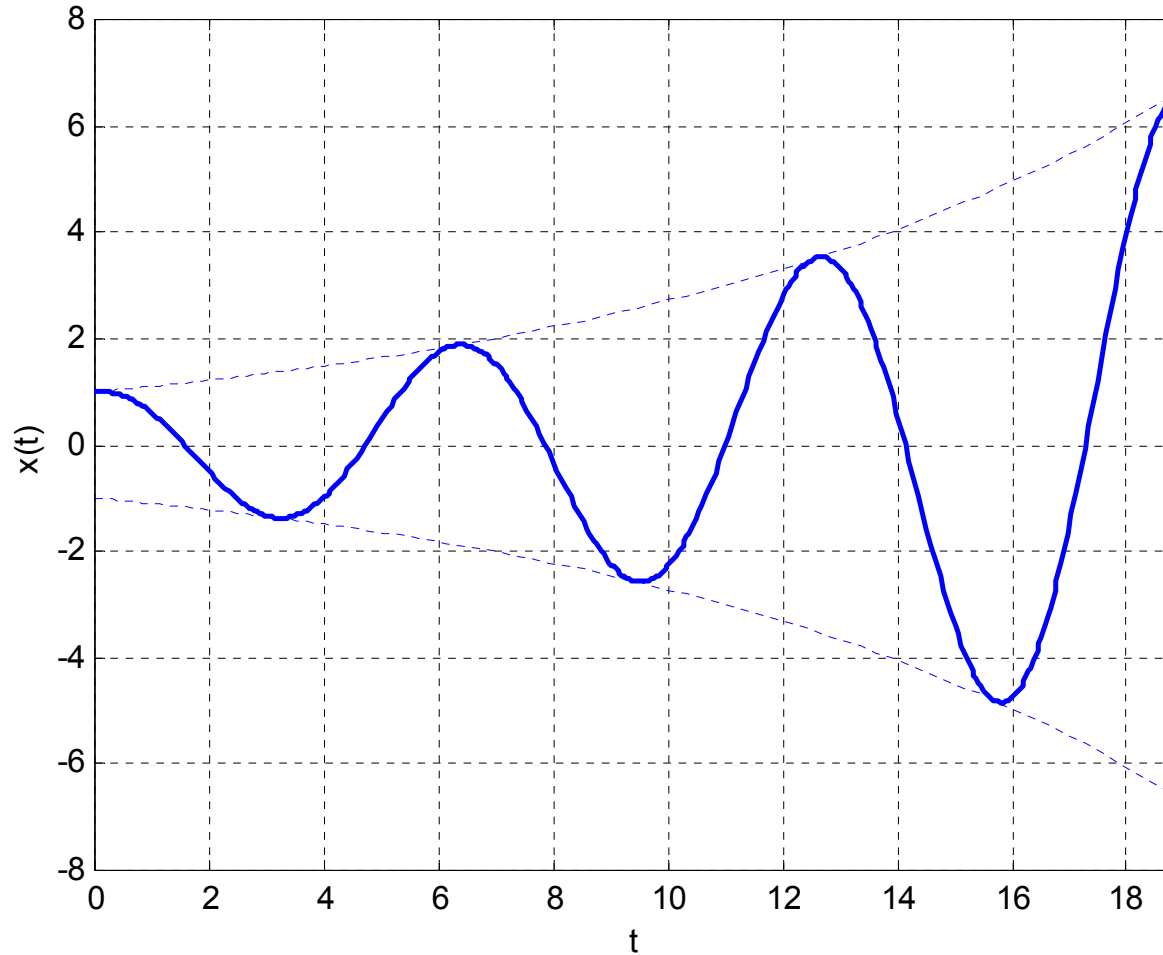
$$x(t) = X_m e^{\sigma t} \cos(\omega t + \phi)$$



$\sigma > 0$

Just Plain Sinusoids
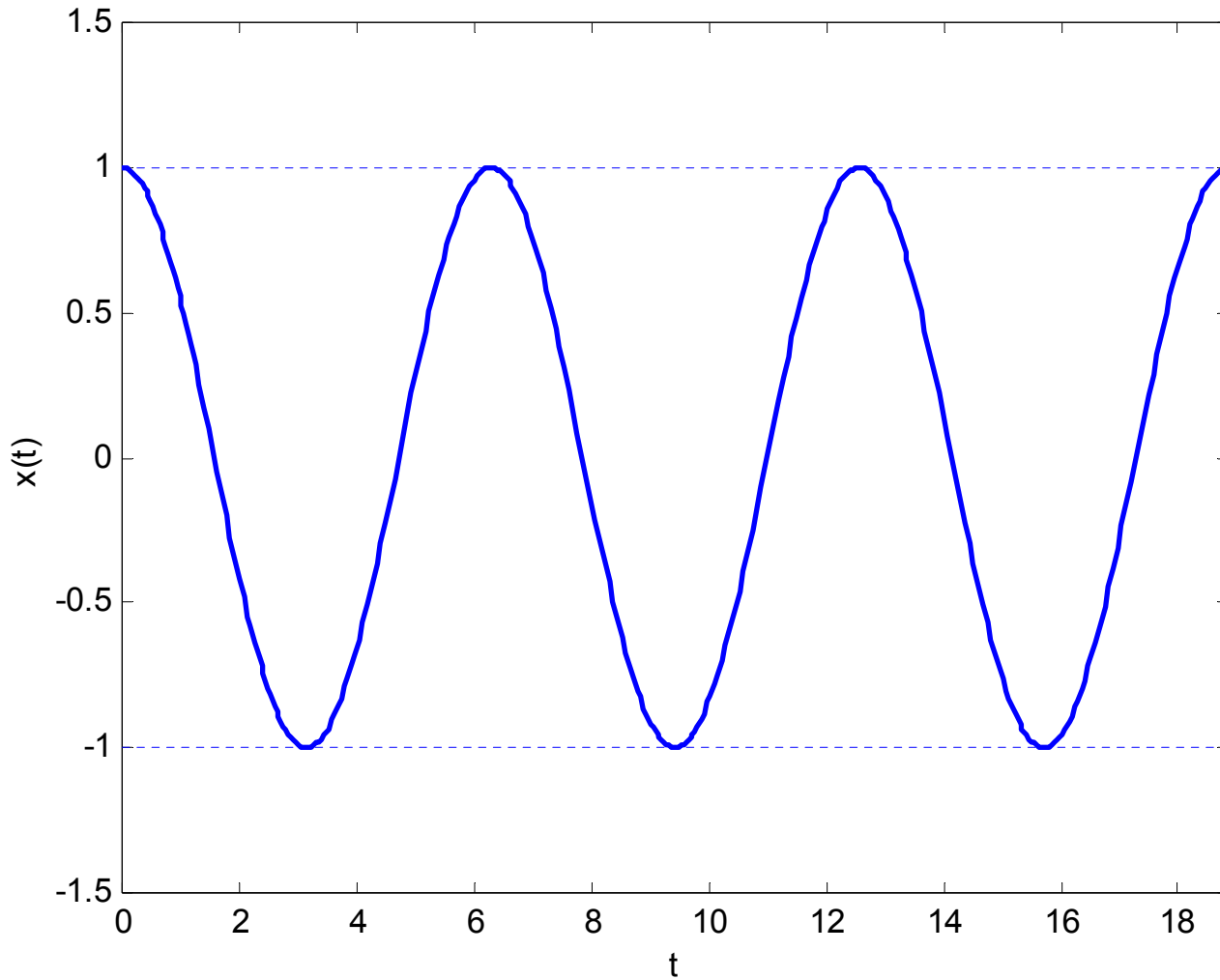
$$x(t) = X_m e^{\sigma t} \cos(\omega t + \phi)$$



$$\sigma = 0$$

Generalized Phasors

Can phasors describe damped sinusoids?

Recall: For $x(t) = X_m \cos(\omega t + \phi)$

$$\mathbf{X} = X_m e^{j\phi} = X_m \angle \phi$$

$$x(t) = \text{Re}[\mathbf{X} e^{j\omega t}]$$

Consider: $x(t) = X_m e^{\sigma t} \cos(\omega t + \phi)$

$$x(t) = \text{Re}[X_m e^{\sigma t} e^{j(\omega t + \phi)}]$$

$$= \text{Re}[X_m e^{j\phi} e^{(\sigma + j\omega)t}]$$

“complex” or
generalized
frequency

Thus $x(t) = \text{Re}[\mathbf{X} e^{st}]$ where $s = \sigma + j\omega$

Generalized Phasors

Example:

$$x(t) = 25e^{-t} \cos(2t + 30^\circ)$$

time domain

$$\mathbf{X}(s) = 25 \angle 30^\circ; \quad \mathbf{s} = -1 + 2j$$

frequency domain

Thus

$$x(t) = \operatorname{Re}[25 \angle 30^\circ e^{st}]; \quad s = -1 + 2j$$

Generalized Phasors

How many complex frequencies are there for:

$$x(t) = X_m e^{\sigma t} \cos(\omega t + \phi)$$

Recall: $\cos(\omega t + \phi) = \frac{1}{2} e^{j(\omega t + \phi)} + \frac{1}{2} e^{-j(\omega t + \phi)}$


$$\begin{aligned} x(t) &= \frac{X_m}{2} e^{\sigma t} e^{j(\omega t + \phi)} + \frac{X_m}{2} e^{\sigma t} e^{-j(\omega t + \phi)} \\ &= \frac{X_m}{2} e^{j\phi} e^{(\sigma + j\omega)t} + \frac{X_m}{2} e^{-j\phi} e^{(\sigma - j\omega)t} \\ &= \mathbf{X} e^{s_1 t} + \mathbf{X}^* e^{s_2 t} \end{aligned}$$

Two generalized complex frequencies s_1 and s_2 such that

$$s_1 = s_2^*$$

Transfer Function/System Response

Consider:

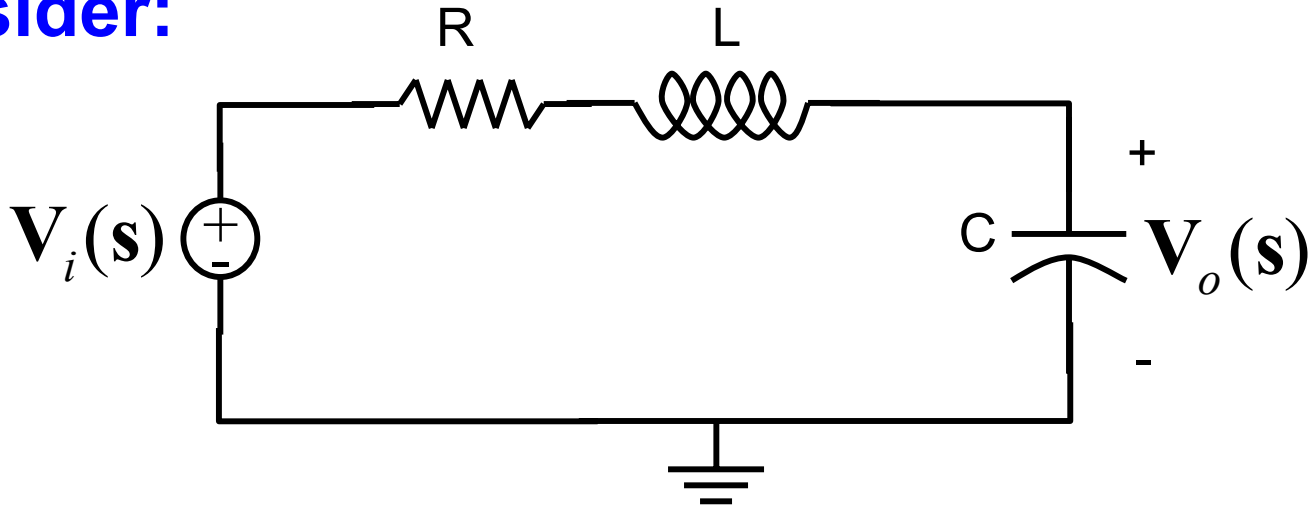

$$R=6\Omega$$

$$L=1\text{H}$$

$$C=0.04\text{F}$$

$$\mathbf{H(s)} = \frac{\mathbf{V_o(s)}}{\mathbf{V_i(s)}} = \frac{25}{s^2 + 6s + 25}$$

$$(s^2 + 6s + 25)V_o(s) = 25V_i(s)$$

Transfer Function/System Response

$$(s^2 + 6s + 25)V_o(s) = 25V_i(s)$$

Question: Is there a frequency s such that the above system has an output when the **input is zero**?

$$s^2 + 6s + 25 = 0$$

homogeneous equation

$$s_1 = -3 + 4j \quad s_2 = -3 - 4j$$

system poles

Thus

$$\begin{aligned} v_o(t) &= V_n e^{s_1 t} + V_n^* e^{s_2 t} \\ &= V_n e^{(-3+4j)t} + V_n^* e^{(-3-4j)t} \\ &= V_n e^{j\phi} e^{(-3+4j)t} + V_n e^{-j\phi} e^{(-3-4j)t} \end{aligned}$$

Transfer Function/System Response

$$\begin{aligned}v_o(t) &= V_n e^{j\phi} e^{(-3+4j)t} + V_n e^{-j\phi} e^{(-3-4j)t} \\&= V_n e^{-3t} \left(e^{j(4t+\phi)} + e^{-j(4t+\phi)} \right) \\&= 2V_n e^{-3t} \cos(4t + \phi) \\&= A_n e^{-3t} \cos(4t) + B_n e^{-3t} \sin(4t)\end{aligned}$$

- The poles of the system determine the **natural response**.
- For **stable systems** the poles are on the left half of the complex plane

Transfer Function/System Response

- The natural and forced responses of a circuit may be obtained from its network function in a straightforward manner.
- Consider a circuit with the following I/O relationship.

$$\begin{aligned} a_n \frac{d^n x_o}{dt^n} + a_{n-1} \frac{d^{n-1} x_o}{dt^{n-1}} + \dots + a_1 \frac{dx_o}{dt} + a_0 &= \\ &= b_m \frac{d^m x_i}{dt^m} + b_{m-1} \frac{d^{m-1} x_i}{dt^{m-1}} + \dots + b_1 \frac{dx_i}{dt} + b_0 \end{aligned}$$

Note: RHS terms = forcing function for ODE

Transfer Function/System Response

$$\mathbf{H}(s) = \frac{\mathbf{X}_o(s)}{\mathbf{X}_i(s)} = \frac{b_m s^m + b_{m-1} s^{m-1} + \dots + b_1 s + b_0}{a_n s^n + a_{n-1} s^{n-1} + \dots + a_1 s + a_0}$$

Hence, the characteristic polynomial (of unforced system):


$$a_n s^n + a_{n-1} s^{n-1} + \dots + a_1 s + a_0 = 0$$

Roots of the characteristic polynomial (poles of $H(s)$) yield the general solution to the homogeneous equation (natural response).


$$x_n(t) = A_1 e^{p_1 t} + A_2 e^{p_2 t} + \dots + A_n e^{p_n t}$$

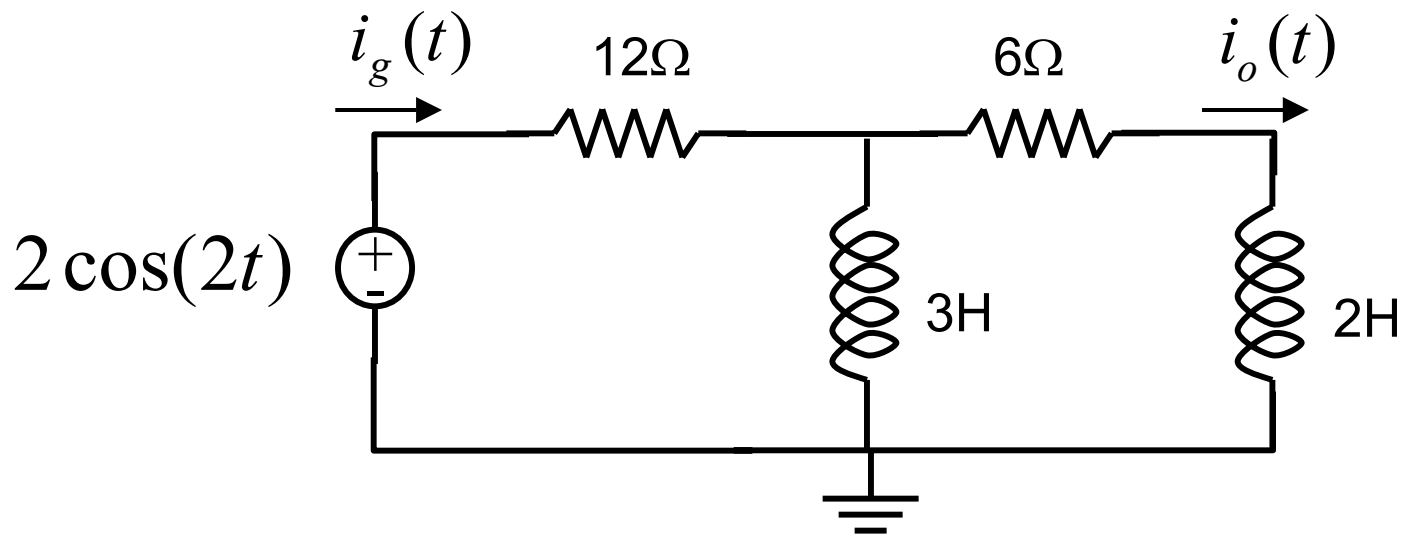Example

Assuming zero initial conditions, find $i_o(t)$.



Example

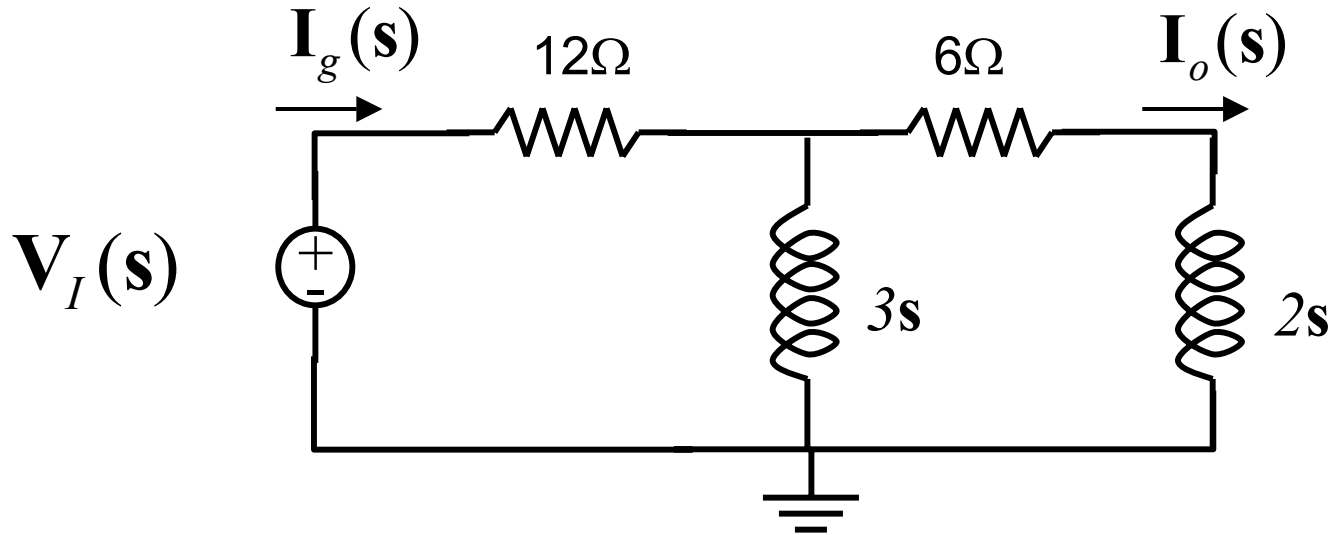

$$\mathbf{I}_g(\mathbf{s}) = \frac{\mathbf{V}_I(\mathbf{s})}{12 + 3\mathbf{s} \parallel (6 + 2\mathbf{s})} = \frac{(6 + 5\mathbf{s})\mathbf{V}_I(\mathbf{s})}{6\mathbf{s}^2 + 78\mathbf{s} + 72}$$

$$\mathbf{I}_o(\mathbf{s}) = \frac{3\mathbf{s}}{6 + 5\mathbf{s}} \mathbf{I}_g(\mathbf{s}) = \frac{\mathbf{s}\mathbf{V}_I(\mathbf{s})}{2(\mathbf{s} + 1)(\mathbf{s} + 12)}$$

Voltage divider

Example

$$\mathbf{I}_0(\mathbf{s}) = \frac{3\mathbf{s}}{6 + 5\mathbf{s}} \mathbf{I}_g(\mathbf{s}) = \frac{\mathbf{s}V_I(\mathbf{s})}{2(\mathbf{s} + 1)(\mathbf{s} + 12)}$$

From the poles we can write the **natural response** in the form:

$$i_n(t) = A_1 e^{-t} + A_2 e^{-12t}$$

Example

Forced response due to the input (forcing function):

$$v_i(t) = 3 \cos(2t)$$

$$\mathbf{H}(s) = \frac{\mathbf{I}_0(s)}{\mathbf{V}_I(s)} = \frac{s}{2(s+1)(s+12)}$$

$$\mathbf{H}(j2) = \frac{j2}{2(j2+1)(j2+12)} = 0.0368 \angle 17.1^\circ$$

$$\begin{aligned} i_f(t) &= 3 \times 0.0368 \cos(2t + 17.1^\circ) \\ &= 0.11 \cos(2t + 17.1^\circ) \end{aligned}$$

Example

Total response:

$$\begin{aligned}i(t) &= i_n(t) + i_f(t) = \\ &= A_1 e^{-t} + A_2 e^{-12t} + 0.11 \cos(2t + 17.1^\circ)\end{aligned}$$

- Need two boundary conditions to find the two undetermined parameters.
- For stable systems (**poles in the left half plane**), the forced response is the steady-state response.

Natural Frequencies

1. The natural frequencies of a circuit are the poles of the network function.
2. The natural frequencies of a circuit are the same for any response in the circuit.
3. To find the natural frequencies of a circuit you may consider any response of the circuit. (Choose the simplest one!)