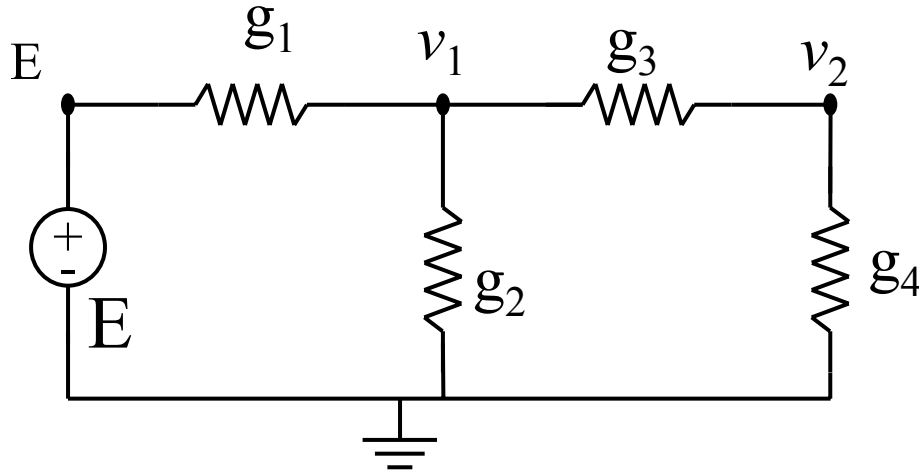


ECSE 210: Circuit Analysis

Lecture #3: Nodal & Mesh Analysis

Example with Voltage Source




$$\text{KCL at node 1: } (v_1 - E)g_1 + v_1g_2 + (v_1 - v_2)g_3 = 0$$

$$\text{KCL at node 2: } (v_2 - v_1)g_3 + v_2g_4 = 0$$

➡ 2 equations, 2 unknowns, → solve

➡ The voltage source allowed us to save one equation (but only if we chose the right reference node or ground).

Example With Two Voltage Sources

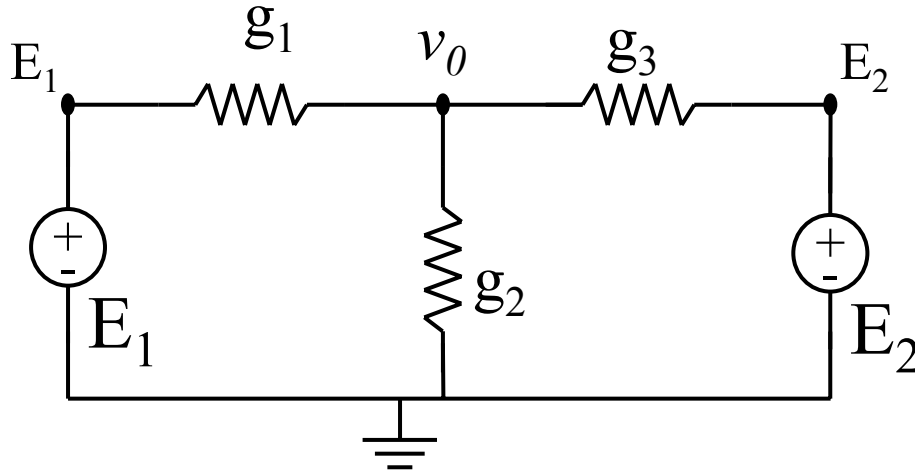


$$\text{KCL at node 0: } (v_0 - E_1)g_1 + v_0 g_2 + (v_0 - E_2)g_3 = 0$$

➡ 1 equations, 1 unknowns, → solve

➡ Try to choose the reference at a point where two or more voltage sources intersect. This eliminates more unknowns and therefore more equations.

Voltage Sources With No Common Nodes

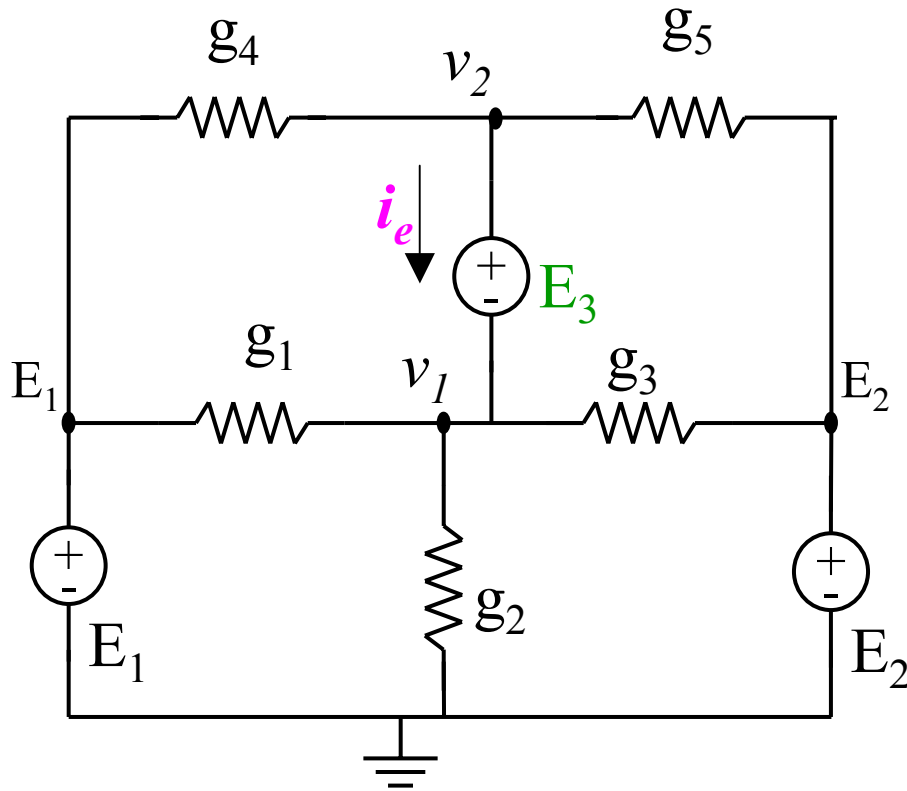

→ One extra variable
(the current in the
voltage source).

→ One extra equation
(the voltage relation
across the voltage
source).


$$\text{KCL at node 1: } (v_1 - E_1)g_1 + v_1g_2 + (v_1 - E_2)g_3 - i_e = 0$$

$$\text{KCL at node 2: } (v_2 - E_1)g_4 + (v_2 - E_2)g_5 + i_e = 0$$

$$\text{Voltage source relation: } v_2 = v_1 + E_3$$

3 equations
3 unknowns

Supernodes

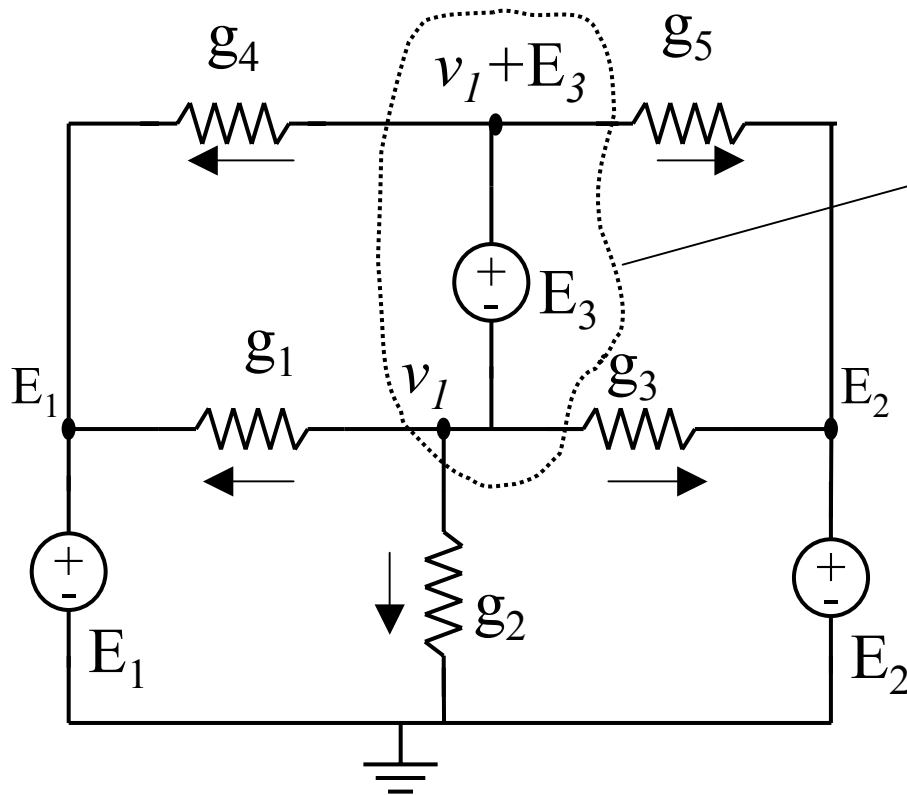


Supernode!
→ Apply KCL at supernode!
That is, sum the currents leaving the supernode.

KCL at supernode:

$$(v_I - E_1)g_1 + v_I g_2 + (v_I - E_2)g_3 + (v_I + E_3 - E_1)g_4 + (v_I + E_3 - E_2)g_5 = 0$$

Dependent Voltage Source

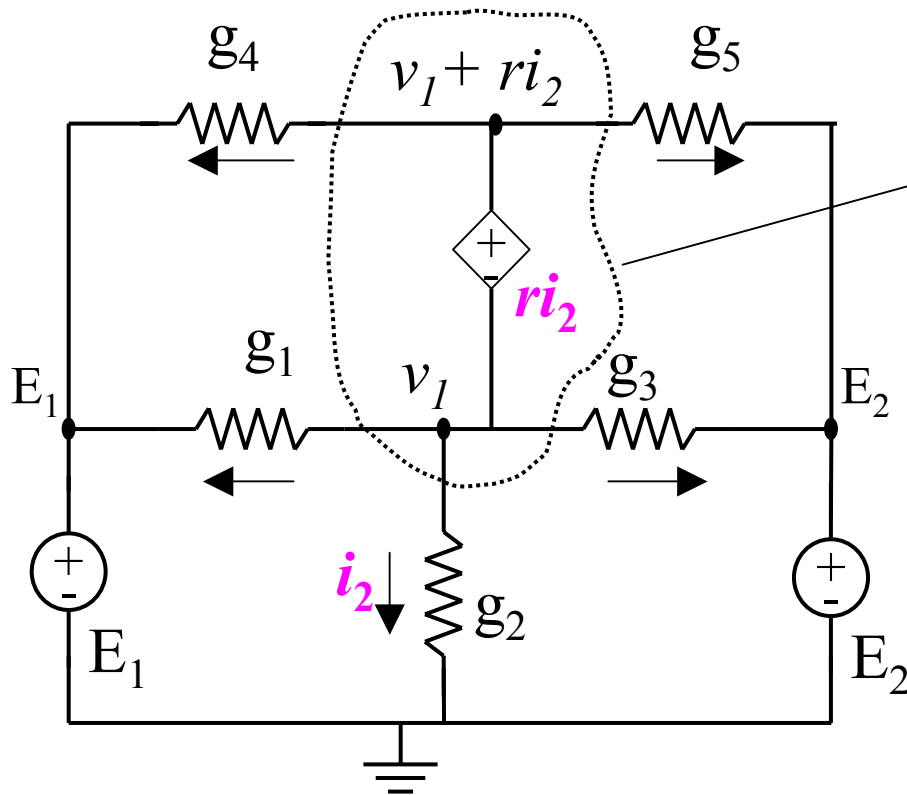

Supernode!
 → Apply KCL at super node!
 That is, sum the currents leaving the super node.


Note: $i_2 = v_1 g_2$; Controlled source = $ri_2 = rg_2 v_1$

KCL at super node:

One unknown v_1 → solve!

$$(v_1 - E_1)g_1 + v_1 g_2 + (v_1 - E_2)g_3 + (v_1 + rg_2 v_1 - E_1)g_4 + (v_1 + rg_2 v_1 - E_2)g_5 = 0$$

Dependent Voltage Source: Example

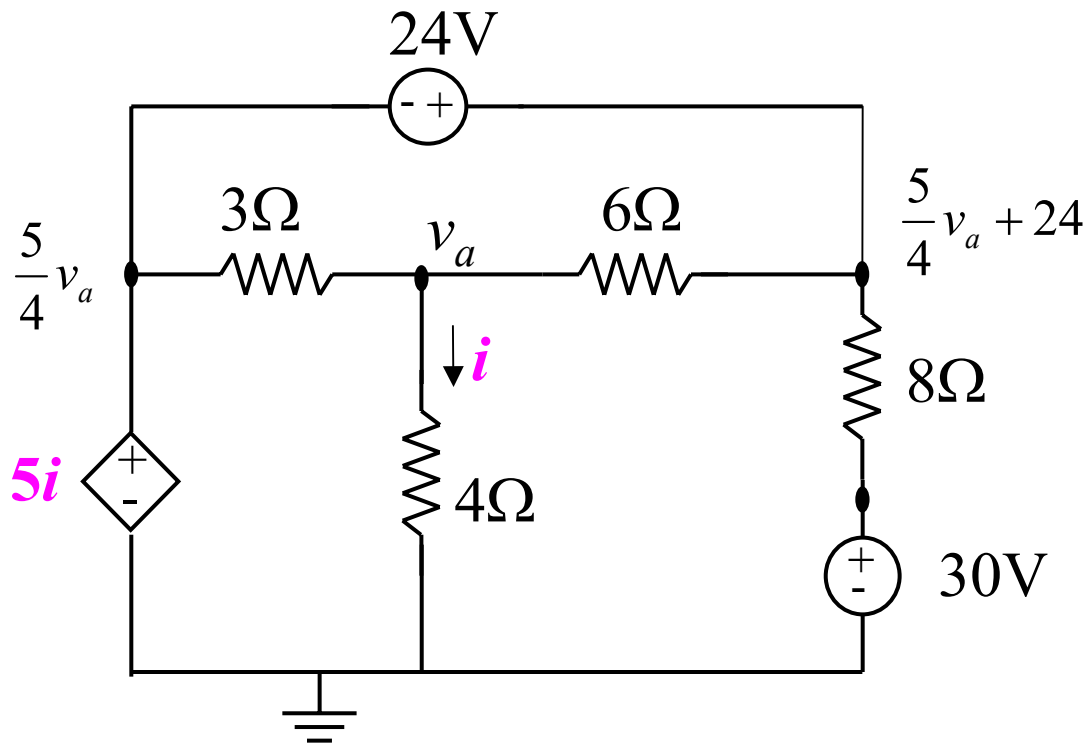

→ Find i

Note: $i = \frac{v_a}{4}$

$$5i = \frac{5}{4}v_a$$

$$3v_a = 96$$


$$v_a = 32V$$

$$i = \frac{32}{4} = 8A$$

$$\frac{v_a - \frac{5}{4}v_a}{3} + \frac{v_a}{4} + \frac{v_a - (\frac{5}{4}v_a + 24)}{6} = 0$$


$$-\frac{1}{12}v_a + \frac{v_a}{4} - \frac{1}{24}v_a = 4$$

What is a Mesh?

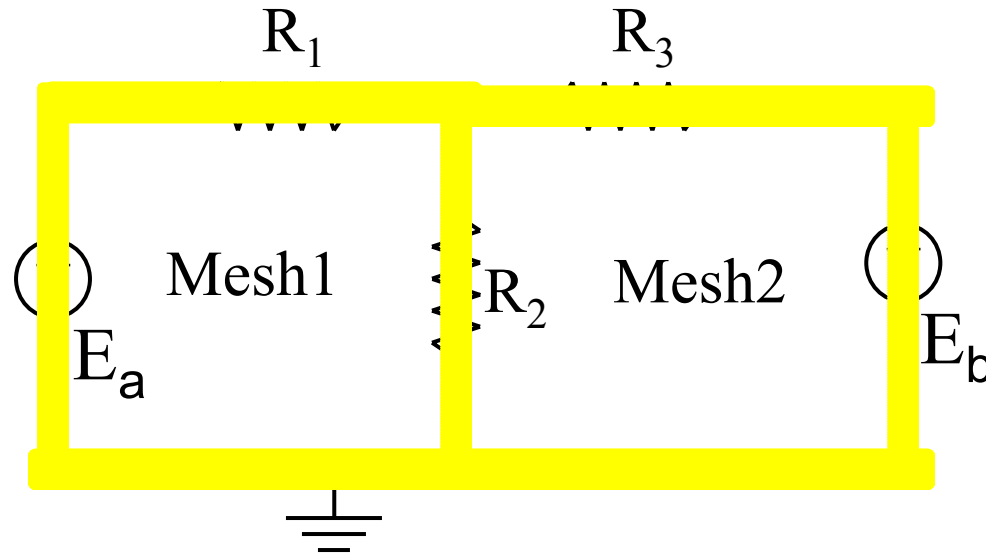


1. The circuit is divided into a collection of “smallest possible” loops.
2. Each small loop is a mesh.
3. A mesh is a loop that cannot be made smaller (i.e., divided into separate loops).
4. A mesh should not contain any elements inside it.
5. In this course we are restricted to “planar circuits”.

Mesh Current

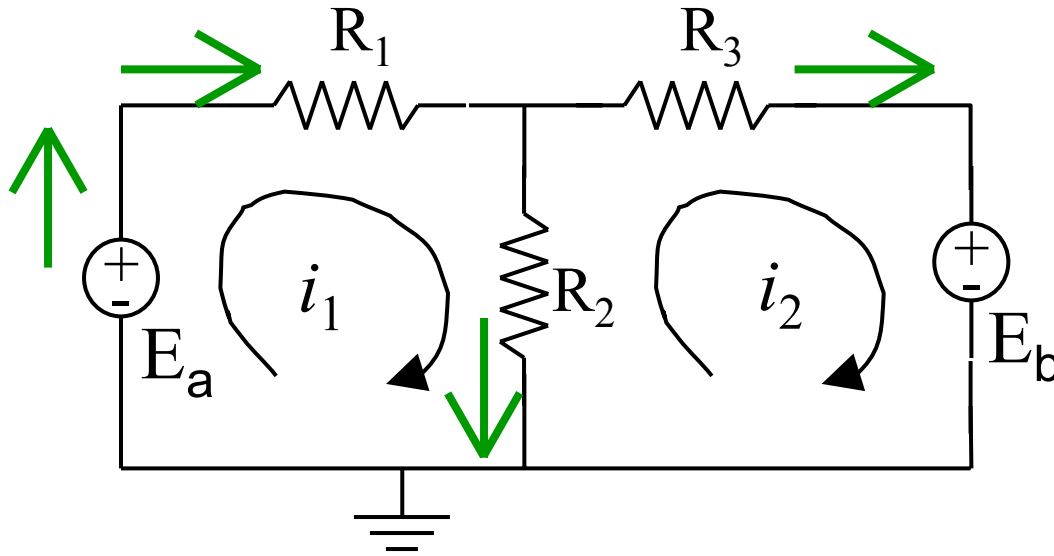


1. Each mesh is assigned a mesh current.
2. We will arbitrarily choose to define all mesh currents in a clockwise direction.
3. Do not confuse “mesh currents” and “branch currents.”

KVL equations

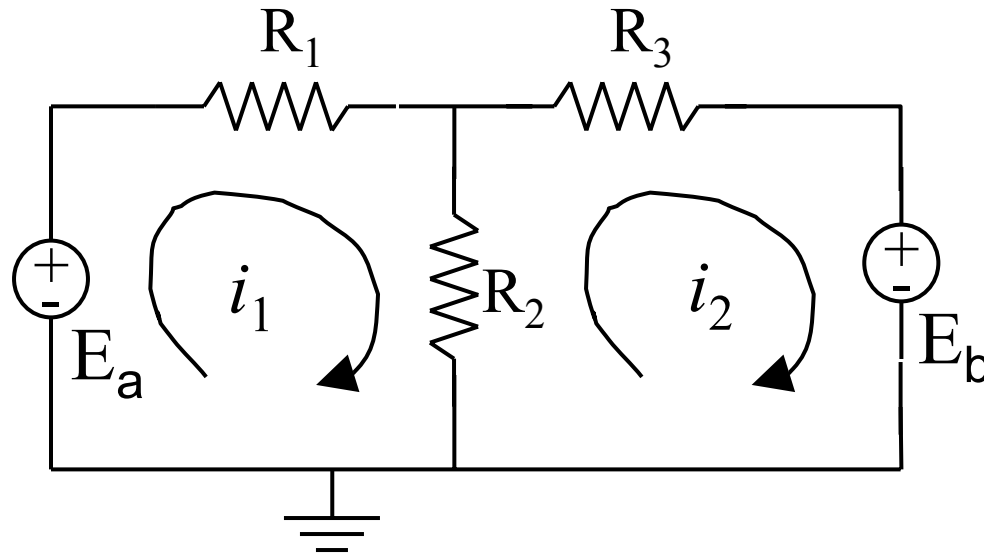

1. We choose to start from the lower left node and move clockwise.
2. We choose to add “voltage drops” across elements.
3. Be careful not to violate passive sign convention.
4. Again, do not confuse mesh currents with branch currents.

KVL equations

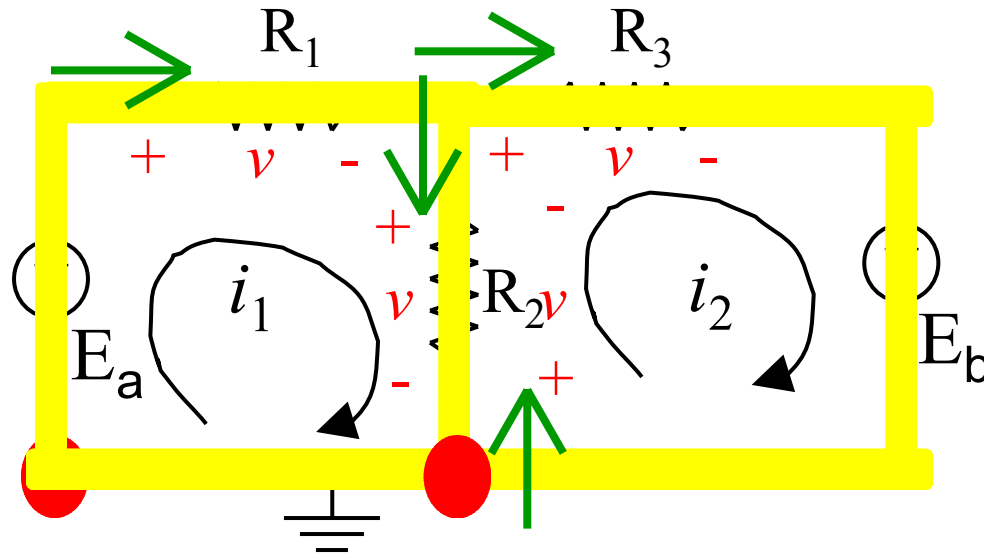


$$-E_a + R_1 i_1 + R_2(i_1 - i_2) = 0$$

$$R_2(i_2 - i_1) + R_3 i_2 + E_b = 0$$

➔ Two equations, two unknowns

Current Source

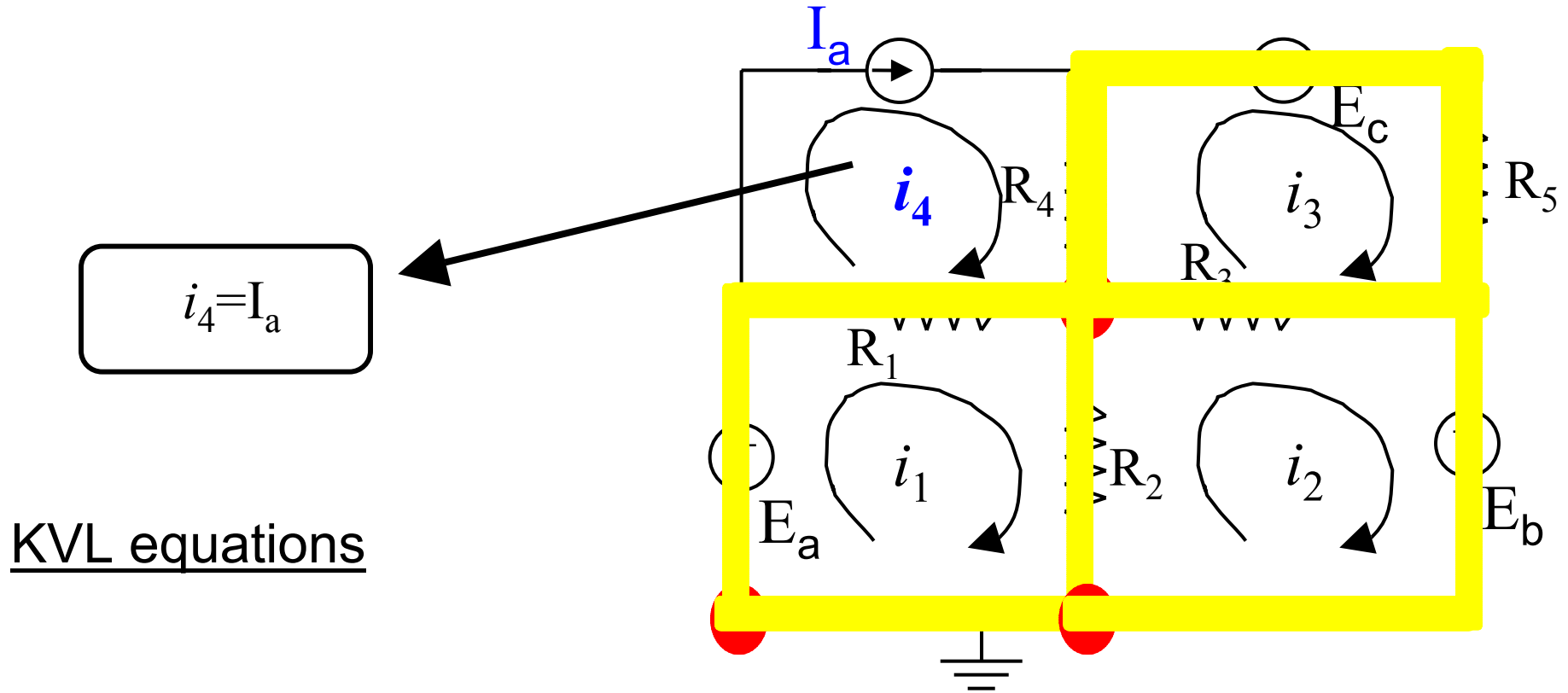

$$i_4 = I_a$$

KVL equations


$$-E_a + R_1(i_1 - i_4) + R_2(i_1 - i_2) = 0$$

$$R_2(i_2 - i_1) + R_3(i_2 - i_3) + E_b = 0$$

$$R_4(i_3 - i_4) + E_c + R_5 i_3 + R_3(i_3 - i_2) = 0$$

3 equations, 3 unknowns
(i_4 is not an unknown!)

Current Source: Example 2

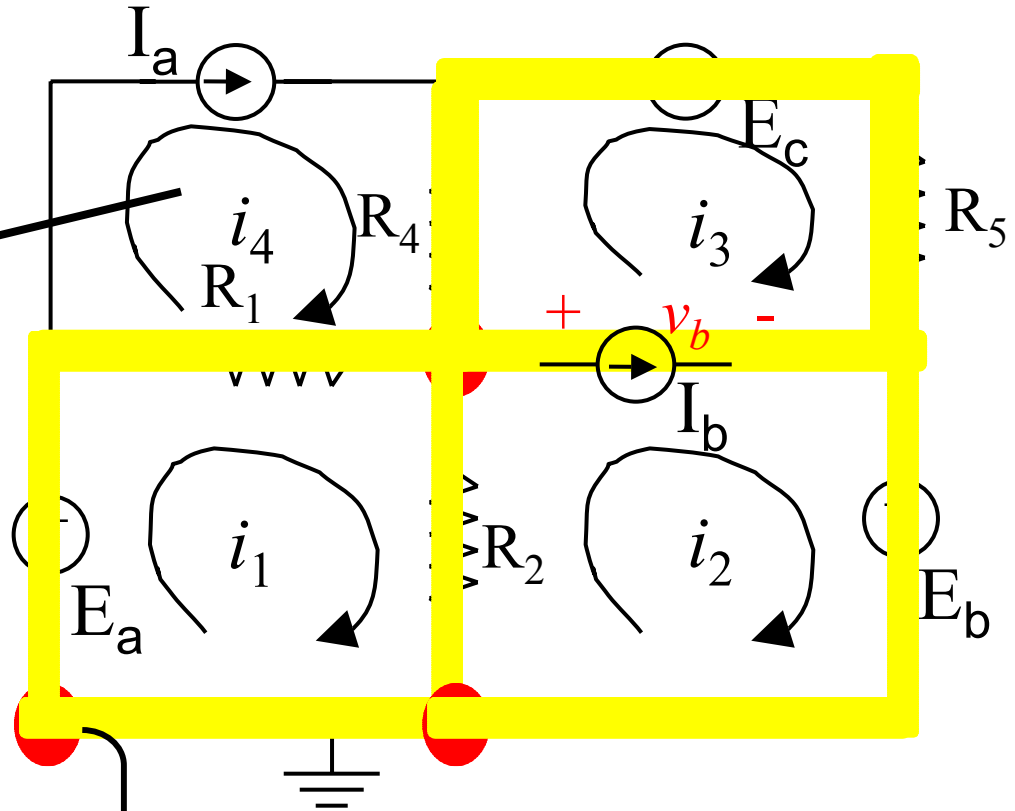

$$i_4 = I_a$$

KVL equations

$$-E_a + R_1(i_1 - i_4) + R_2(i_1 - i_2) = 0$$

$$R_2(i_2 - i_1) + v_b + E_b = 0$$


$$R_4(i_3 - i_4) + E_c + R_5 i_3 - v_b = 0$$

$$i_2 - i_3 = I_b$$

4 equations

4 unknowns: i_1, i_2, i_3, v_b
 (i_4 is not an unknown!)

Supermesh: Open Circuit Current Sources

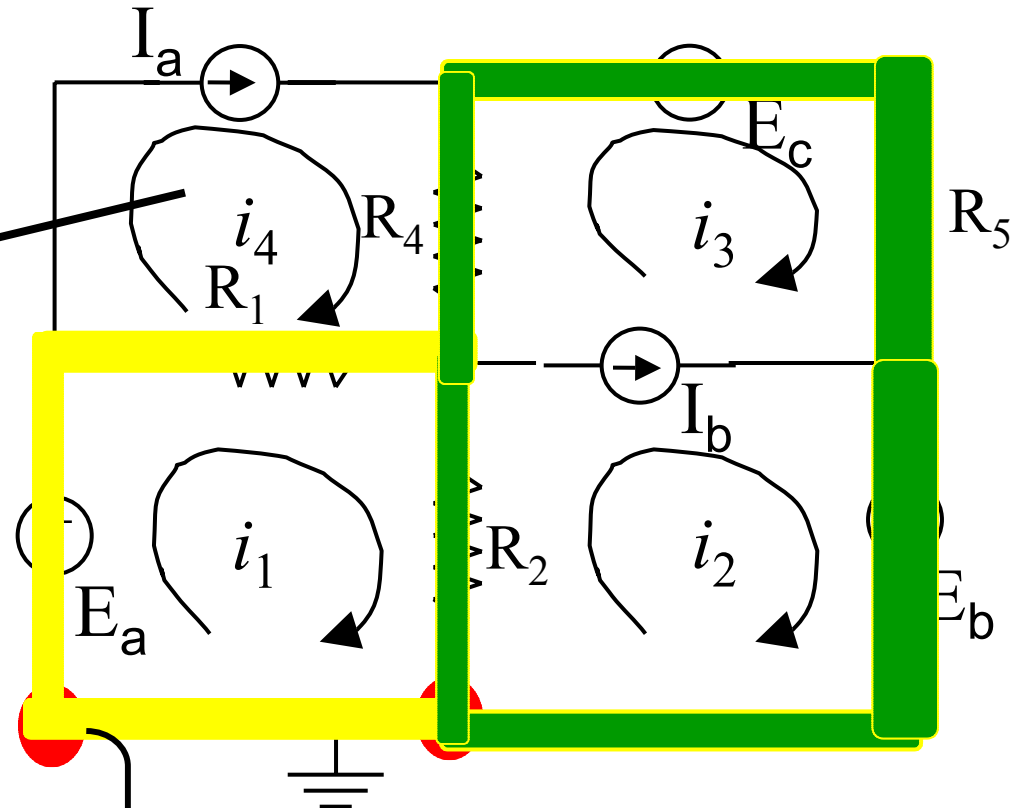

$$i_4 = I_a$$

KVL equations

$$-E_a + R_1(i_1 - i_4) + R_2(i_1 - i_2) = 0$$


$$R_2(i_2 - i_1) + R_4(i_3 - i_4) + E_c + R_5 i_3 + E_b = 0$$

$$i_2 - i_3 = I_b$$

3 equations, 3 unknowns
(i_4 is not an unknown!)

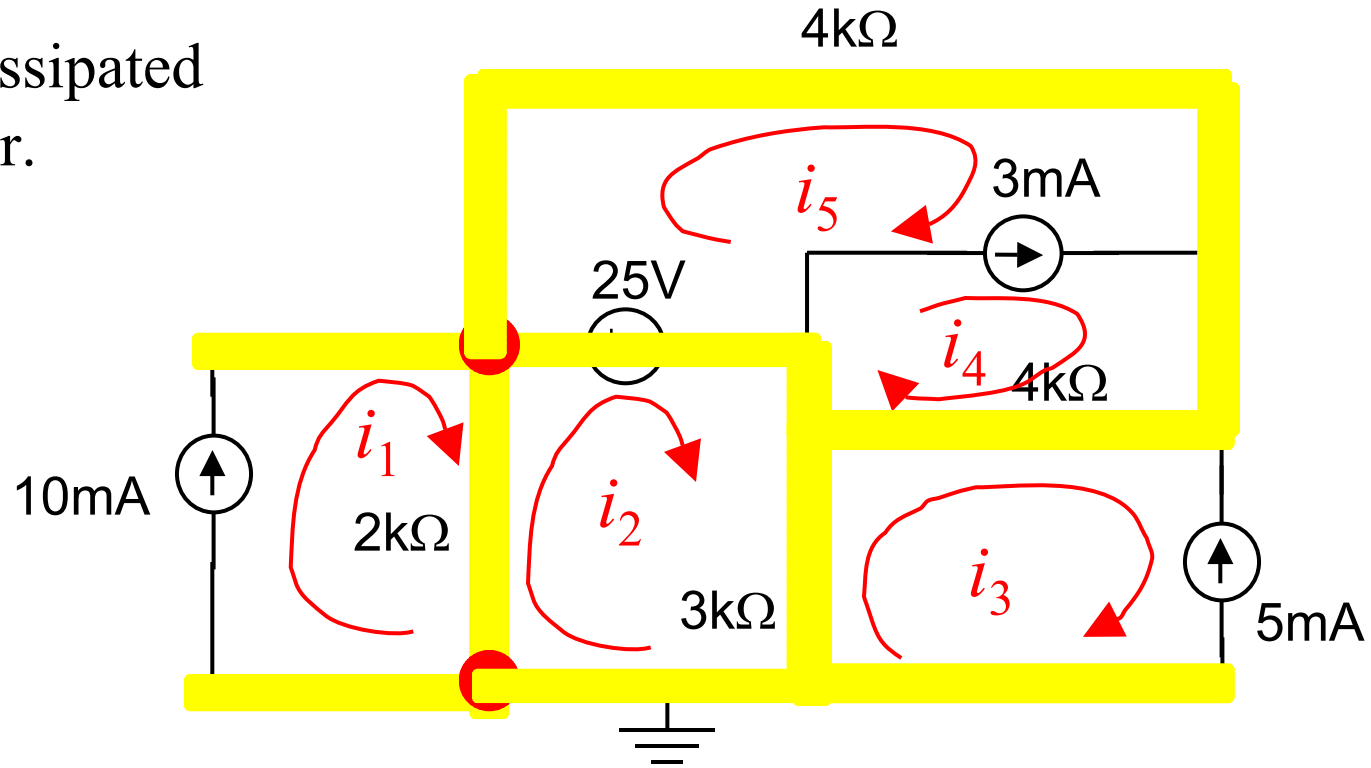Example

Find the power dissipated in the $3k\Omega$ resistor.



Constraints

$$i_1 = 10\text{mA}$$

$$i_3 = -5\text{mA}$$

$$i_4 - i_5 = 3\text{mA}$$

$$2(i_2 - i_1) + 25 + 3(i_2 - i_3) = 0$$

$$4i_5 + 4(i_4 - i_3) - 25 = 0$$

$$i_2 = -4\text{mA}$$

Power =

$$(i_2 - i_3)^2 R_3 = (1\text{mA})^2 (3k\Omega) = 3\text{mW}$$

Be careful with units.