

CIRCUIT ANALYSIS

304-210B

Test 2

Test 2

Time: 10:30-11:30

Mon. 15 March, 1999

Professor: Martin D. Levine

- CLOSED BOOK TEST -

Name Solutions

Student # _____

INSTRUCTIONS

1. Answer all questions.
2. Write your answers in the space at the bottom of each page.


QUESTION #	Q1	Q2	Q3	Q4	TOTAL
MARKS	3 Points	4.5 Points	4.5 Points	3 Points	15 Points

Remarks:

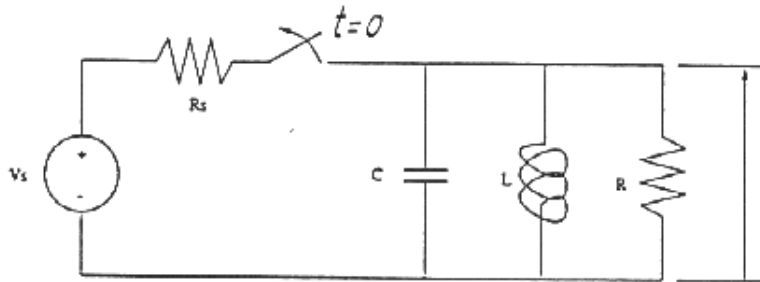
Question 1

For the circuit shown below, assume steady-state for $t < 0$:

- Find the differential equation associated with the voltage v , for $t \geq 0$.
- If $R = \infty$, find $v(t)$ for $t \geq 0$.
- For the equation obtained in part A., find R such that $v(t)$ is critically damped.



A. $t \geq 0$
(1.4pt)

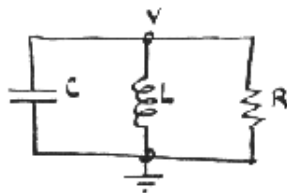

By KCL @ Node (v):

$$i_c + i_L + i_R = 0$$

$$C \frac{dv}{dt} + i_L + \frac{v}{R} = 0 \quad (1)$$

Voltage across the inductor: $v = L \frac{di_L}{dt} \quad (2)$

Differentiating (1): $C \ddot{v} + \frac{di_L}{dt} + \frac{\dot{v}}{R} = 0 \quad (3)$

Replacing $\frac{di_L}{dt}$ from (2) in (3):

$$C \ddot{v} + \frac{v}{L} + \frac{\dot{v}}{R} = 0 \rightarrow \ddot{v} + \frac{1}{RC} \dot{v} + \frac{1}{LC} v = 0 \quad (4)$$

B. (i) For $t < 0$

(1pt) Initial Conditions

$$v_c(0^-) = 0 \quad i_L(0^-) = 0$$

$$v_L(0^-) = 0 \quad v_L(0^-) = L \frac{di_L(0^-)}{dt} = 0 \quad (\text{since } v_s = \text{constant}).$$

In steady-state:

- Capacitor \rightarrow Open circuit

- Inductor \rightarrow Short circuit (and the rate of change of the current through it is zero, i.e. $i_L(0^-) = \text{constant}$).

(ii) From eq. (4) in A., with $R = \infty$.

$$\ddot{V} + \frac{1}{LC} V = 0$$

Roots of the characteristic equation: $s^2 + \frac{1}{LC} = 0 \rightarrow s = \pm j \frac{1}{\sqrt{LC}}$

$$\therefore v(t) = A_1 \sin\left(\frac{1}{\sqrt{LC}} t\right) + A_2 \cos\left(\frac{1}{\sqrt{LC}} t\right)$$

$$\left. \begin{array}{l} v(0) = 0 = A_2 \\ \frac{dv(0)}{dt} = \frac{i_L(0)}{C} = 0 = \frac{A_1}{\sqrt{LC}} \end{array} \right\} \therefore A_1 = A_2 = 0$$

$$\underline{v(t) = 0 \text{ [V], } t \geq 0}$$

C. (0.6 pt) Critically damped \Rightarrow Discriminant = 0

From eq. (4) in A., the discriminant is:

$$\sqrt{\left(\frac{1}{RC}\right)^2 - \frac{4}{LC}} = 0 \rightarrow \frac{1}{RC} = \frac{2}{\sqrt{LC}} \rightarrow \underline{R = \frac{1}{2} \sqrt{\frac{L}{C}} \text{ } [\Omega]}$$


ANS.: A. $\underline{\ddot{V} + \frac{1}{RC} \dot{V} + \frac{1}{LC} V = 0}$

B. $v(t) = \underline{0 \text{ [V]}}$

C. $R = \underline{\frac{1}{2} \sqrt{\frac{L}{C}} \text{ } [\Omega]}$


Question 2

Find the steady-state voltage $v(t)$.

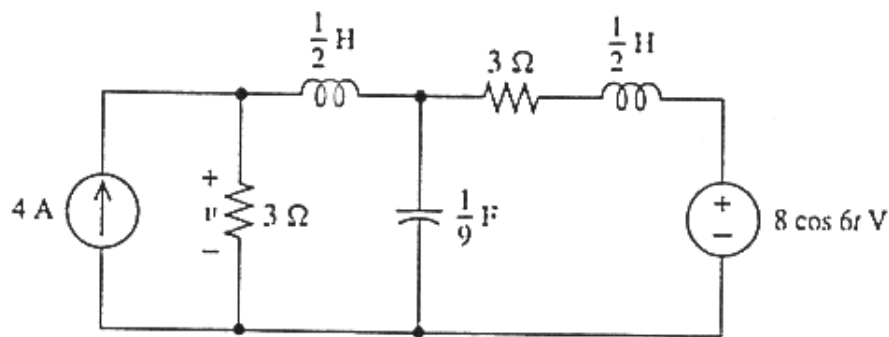

Different frequency sources \rightarrow Apply SUPERPOSITION (0.5)

(i) Killing the ac-voltage source

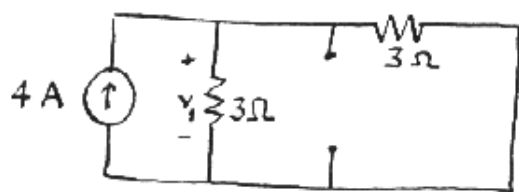


In steady-state (dc)

$$v_1 = 3 \cdot \left(\frac{I}{2}\right) = 3 \cdot 2 = 6 \text{ [V]} \quad (1)$$

(ii) Killing the dc-current source.

In steady-state (ac) with $\omega = 6$

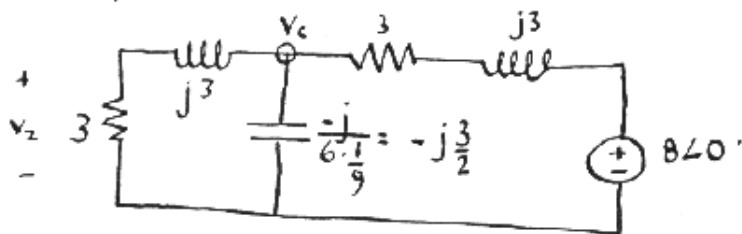

By voltage divider

$$v_2 = \frac{3}{3+j3} v_c = \frac{1}{1+j} v_c \quad (2)$$

$$\text{And } v_c = \frac{(3+j3) \cdot (-j\frac{3}{2})}{3+j3 - j\frac{3}{2}} \cdot 8\angle 0^\circ$$

$$= \frac{(3+j3)(-j\frac{3}{2})}{3+j3 - j\frac{3}{2}} \cdot 8 = \frac{\cancel{3}(1+j)(-j\frac{3}{2})}{\cancel{3}(1+j)(-j\frac{3}{2}) + \cancel{3}(1+j)(3+j\frac{3}{2})} \cdot 8 = \frac{-j\frac{3}{2}}{3} 8 = -j4 \quad (1.5)$$


$$\therefore V_2 = \frac{1}{1+j} V_c = \frac{-j4}{1+j} = \frac{4 \angle -90^\circ}{\sqrt{2} \angle 45^\circ} = 2\sqrt{2} \angle -135^\circ \text{ [V]}$$

$$\begin{aligned} \therefore v(t) &= v_1(t) + v_2(t) \\ &= 6 + 2\sqrt{2} \cos(6t - 135^\circ) \quad (0.5) \end{aligned}$$

$$\text{ANS.: } v(t) = \underline{6 + 2\sqrt{2} \cos(6t - 135^\circ)} \text{ [V]}$$

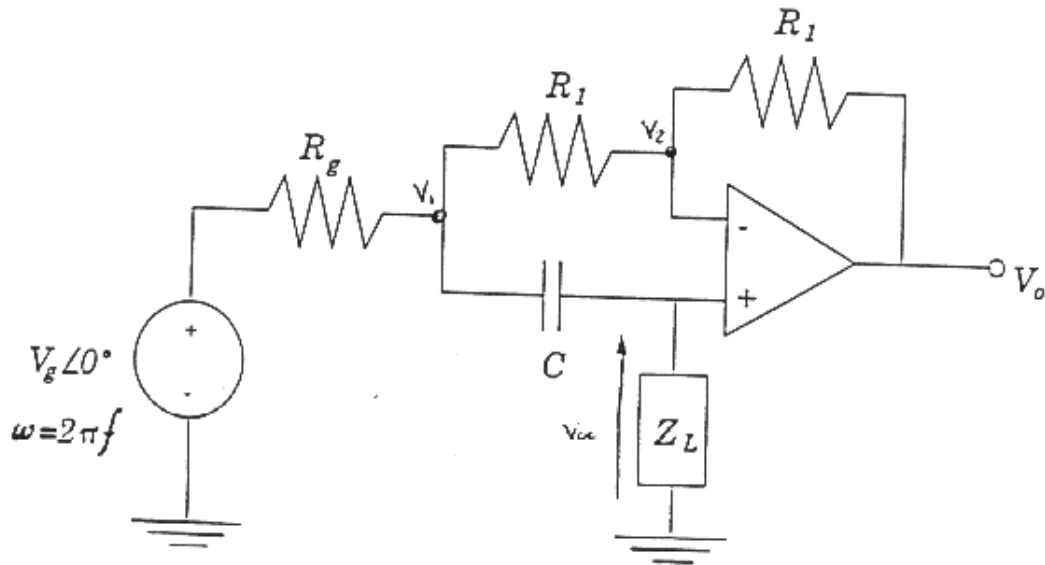Question 3

Find the load Z_L so that it absorbs maximum power.



OP.AMP. \rightarrow Dependent Source $\rightarrow Z_{TH} = \frac{V_{oc}}{I_{sc}}$ (0.3p)

(i) V_{oc}

$$V_{oc} = V_2 \quad (\text{since } V^- = V^+)$$

$$I_+ = 0 \Rightarrow I_+ = \frac{V_1 - V_2}{\frac{-j}{\omega C}} = 0 \Rightarrow V_1 = V_2 \Rightarrow I_{R_1} = 0$$

$$\text{Then, since } I_{source} = I_{R_1} + I_+ = 0 \rightarrow V_2 = V_g \angle 0^\circ$$

$$\therefore \underline{V_{oc} = V_g} \quad (1.2p)$$

(ii) I_{sc}

$$V^+ = V_2 = 0$$

$$I_{sc} = \frac{V_1}{\frac{-j}{\omega C}} \quad (\text{since } I_+ = 0)$$

$$\underline{\text{KCL @ } V_1} \quad \frac{V_g - V_1}{R_g} = \frac{V_1 - 0}{R_1} + \frac{V_1}{\frac{-j}{\omega C}} \quad (\text{eq 1})$$

From eq. (1):

$$\frac{V_g}{R_g} = \left(\frac{1}{R_g} + \frac{1}{R_1} + j\omega C \right) V_1$$

$$V_1 = \frac{V_g}{R_g \left(\frac{1}{R_g} + \frac{1}{R_1} + j\omega C \right)}$$

$$I_{sc} = \frac{V_1}{\frac{-j}{\omega C}} = j\omega C V_1 = \frac{j\omega C V_g}{R_g \left(\frac{1}{R_g} + \frac{1}{R_1} + j\omega C \right)} \quad (1.8)$$

$$Z_{TH} = \frac{V_{oc}}{I_{sc}} = \frac{R_g}{j\omega C} \left(\frac{1}{R_g} + \frac{1}{R_1} + j\omega C \right) = \frac{(R_1 + R_g)}{j\omega C R_1} + R_g$$

$$Z_{TH} = R_g - j \frac{(R_1 + R_g)}{\omega C R_1}$$

For maximum
power

$$\underline{Z_L = Z_{TH}^* = R_g + j \frac{(R_1 + R_g)}{\omega C R_1}} \quad (1.2p)$$

$$\text{ANS.: } Z_L = \underline{R_g + j \frac{(R_1 + R_g)}{\omega C R_1}}$$

Question 4

A 7.46 kW motor operates from a 480 V_{rms}, 60 Hz source with 0.8 lagging power factor. Determine the parallel capacitor C required so that the power factor is changed to 0.922 lagging.

$$P = 7.46 \text{ kW}$$


$$V = 480 \text{ [V}_{rms}]$$

$$p.f._0 = 0.8 \text{ (lagging)} \rightarrow \theta_0 = \arccos(p.f._0) = 36.8699^\circ \text{ (0.5p)}$$

$$p.f._1 = 0.922 \text{ (")} \rightarrow \theta_1 = \arccos(p.f._1) = 22.7798^\circ \text{ (0.5p)}$$

$$Q_0 = P \tan(\theta_0) = 7.46 \cdot 0.75 = 5.595 \text{ kVAR (0.5p)}$$
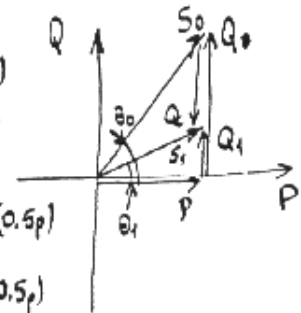
$$Q_1 = P \tan(\theta_1) = 7.46 \cdot 0.4199 = 3.133 \text{ kVAR (0.5p)}$$



P-Q Diagram


$$Q_c = Q_1 - Q_0 = -2.4622 \text{ kVAR (0.5p)}$$

$$S_c = V_{rms} \cdot I_c^* = V_c \cdot \left(\frac{V_c}{Z_c}\right)^* = \frac{V_{rms}^2}{Z_c^*}, \quad Z_c = \frac{-j}{\omega C}$$

$$S_c = jQ_c \Rightarrow -j V_{rms}^2 \cdot C \cdot \omega = jQ_c$$

$$\therefore C = \frac{-Q_c}{2\pi f V_{rms}^2} = \frac{2.4622 \cdot 10^3}{2\pi \cdot 60 \cdot (480)^2} \text{ (0.5p)}$$

$$\underline{C = 28.3472 \mu F}$$

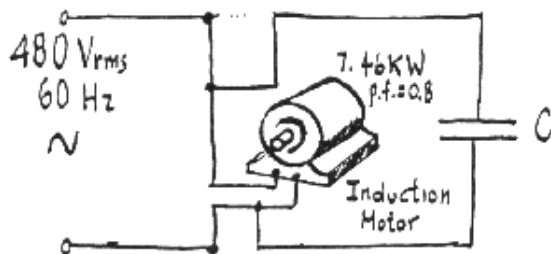

ANS.: $C = \underline{28.3472 \mu F}$