


Tutorial 5

Part 1 (From Tutorial 4)

Truth Table for Full Adder:

C_{in}	A	B	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Implementation of Full Adder:

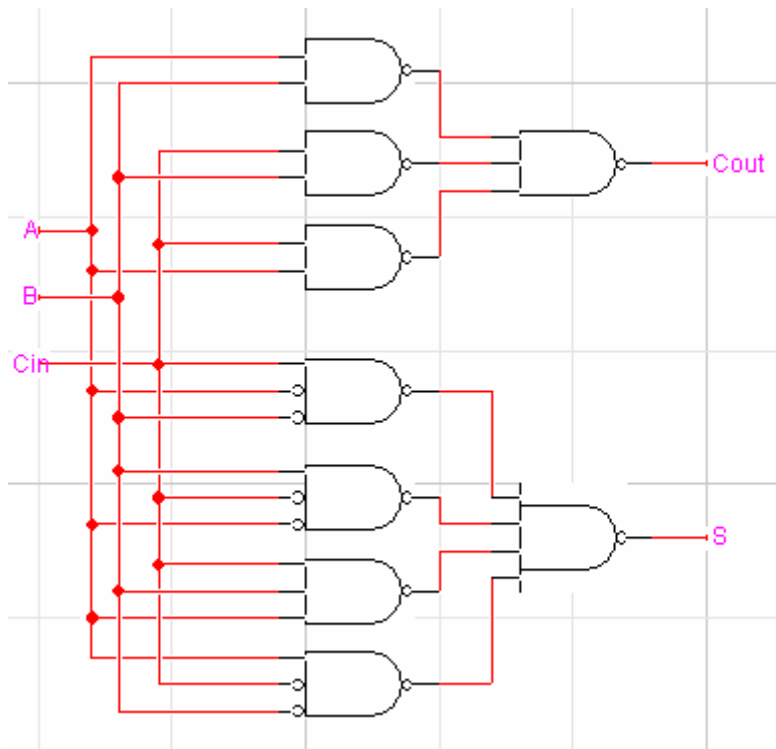


Testing Full Adder:

Test using a timing file (tab delimited, with column labeled \$T (time) \$D (delay) and \$I (input) - make sure to use the same names for inputs as the labels you used on the wires in your circuit:

\$T	\$D	\$I Cin	\$I A	\$I B
0	100	0	0	0
	100	0	0	1
	100	0	1	0
	100	0	1	1
	100	1	0	0
	100	1	0	1
	100	1	1	0
	100	1	1	1

 Simulation->Import Timing...,
Files of type: All Files
Navigate to your timing file.



Now, look at Cout and S

- they are the same as Cout (0 0 0 1 0 1 1 1) and S (0 1 1 0 1 0 0 1) from the original truth table
- so the circuit works properly.

Part 2
From Tutorial 4...
Karnaugh Maps for functions with four inputs

Given a function:

$$F = \sum \{ 0, 2, 3, 5, 7, 8, 10 \}$$

Create a truth table:

A	B	C	D	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

Karnaugh maps and minimizations:

Sum of Products:

		CD			
		00	01	11	10
AB	00	1	0	1	1
	01	0	1	1	0
	11	0	0	0	0
	10	1	0	0	1

$$F = \overline{B}\overline{D} + \overline{A}BD + \overline{A}CD$$

Product of Sums:


		CD			
		00	01	11	10
AB	00	1	0	1	1
	01	0	1	1	0
	11	0	0	0	0
	10	1	0	0	1

$$F = (\bar{B} + D)(\bar{A} + \bar{D})(B + C + \bar{D})$$

Part 3 Implementing the Function from Part 2

 A) NOR-NOR Logic:

Notice how labeling the wires simplifies the circuit:




Create a timing file:

\$T	\$D	\$I A	\$I B	\$I C	\$I D
0	100	0	0	0	0
	100	0	0	0	1
	100	0	0	1	0
	100	0	0	1	1
	100	0	1	0	0
	100	0	1	0	1
	100	0	1	1	0
	100	0	1	1	1
	100	1	0	0	0
	100	1	0	0	1
	100	1	0	1	0
	100	1	0	1	1
	100	1	1	0	0
	100	1	1	0	1


100	1	1	1	0
100	1	1	1	1
100	0	0	0	0
100	0	0	0	1
100	0	0	1	0
100	0	0	1	1
100	0	1	0	0
100	0	1	0	1
100	0	1	1	0
100	0	1	1	1
100	1	0	0	0
100	1	0	0	1
100	1	0	1	0
100	1	0	1	1
100	1	1	0	0
100	1	1	0	1
100	1	1	1	0
100	1	1	1	1

 Import the timing file, this is the result:



We could directly check F against the truth table - but it is hard to be sure it is correct since there are now 16 cases to check.

 
An easier way is to create a circuit that can test F against the expected value of F, F_e:



Add a column to the timing file, F_e, which gives the expected value of F:

\$T	\$D	\$I A	\$I B	\$I C	\$I D	\$I F_e
0	100	0	0	0	0	1
	100	0	0	0	1	0
	100	0	0	1	0	1
	100	0	0	1	1	1
	100	0	1	0	0	0
	100	0	1	0	1	1
	100	0	1	1	0	0
	100	0	1	1	1	1
	100	1	0	0	0	1
	100	1	0	0	1	0
	100	1	0	1	0	1
	100	1	0	1	1	0
	100	1	1	0	0	0
	100	1	1	0	1	0
	100	1	1	1	0	0
	100	1	1	1	1	0
	100	0	0	0	0	1
	100	0	0	0	1	0
	100	0	0	1	0	1
	100	0	0	1	1	1
	100	0	1	0	0	0
	100	0	1	0	1	1
	100	0	1	1	0	0
	100	0	1	1	1	1
	100	1	0	0	0	1
	100	1	0	0	1	0
	100	1	0	1	0	1
	100	1	0	1	1	0
	100	1	1	0	0	0
	100	1	1	0	1	0
	100	1	1	1	0	0
	100	1	1	1	1	0

 
Now, run the circuit with the new timing file. This is the result:




By looking at the Success line, we can see that the circuit always works.

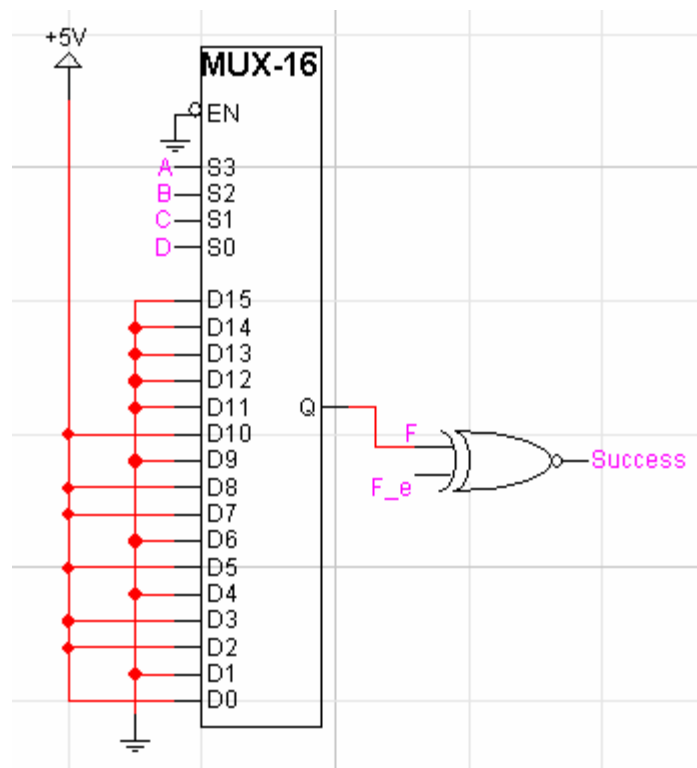B) MUX-16:

Can implement any circuit with n inputs using a multiplexer with 2^n lines, with each line connected to 0 or 1 according to the truth table. So, for this circuit, we will need an MUX-16. Since logicworks doesn't have one, you can make one using two MUX-8's (you don't need to encapsulate it, but so as not to give everything away I've encapsulated one for the purposes of the tutorial):



 Here's the resulting timing file: it works!



C) MUX-8:


Note that the truth table can be grouped into twos, as follows:

A	B	C	D	F	
0	0	0	0	1	D'
0	0	0	1	0	
0	0	1	0	1	1
0	0	1	1	1	
0	1	0	0	0	D
0	1	0	1	1	
0	1	1	0	0	D
0	1	1	1	1	
1	0	0	0	1	D'
1	0	0	1	0	
1	0	1	0	1	D'
1	0	1	1	0	
1	1	0	0	0	0
1	1	0	1	0	
1	1	1	0	0	0
1	1	1	1	0	

So, could use an MUX-8 with A, B, and C as the select lines, and then connect 0, 1, D, or D' for each combination of A, B, and C.

 D) PROM:


Use the PROM wizard to create a PROM with 4 address lines, and 1 bit output:



Here's the contents of the PROM:

```
1 0 1 1
0 1 0 1
1 0 1 0
0 0 0 0
```

And here's the resulting timing file:

 

It works!