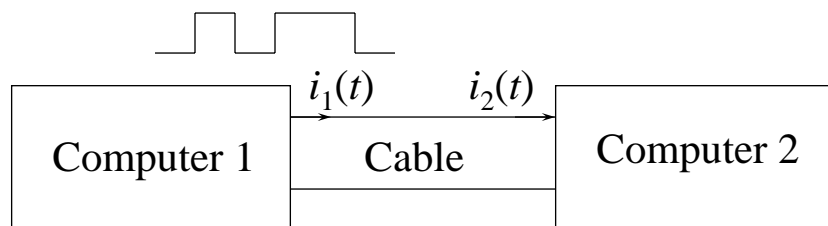


Electrostatics, section 01

Distributed Capacitance

Electrostatics_01_DistributedCapacitance: 1

Computer Communication




Is $i_1(t) = i_2(t)$?

Electrostatics_01_DistributedCapacitance: 2

No, because of *distributed capacitance*.

A better model for the cable is:

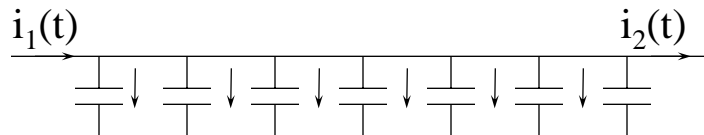

Electrostatic analysis can give us a value for the *capacitance per meter*, C'

Electrostatics_01_DistributedCapacitance: 3

Example

$$C' = 2\text{pF /m}$$

Cable length, $l = 2\text{m}$


Input resistance of computer 2, $R = 50\text{ Ohms}$

$$i_1(t) = 2\text{ns pulse}$$

Electrostatics_01_DistributedCapacitance: 4

Total (lumped) capacitance of cable, C

$$= C'l = 4 \text{ pF}$$

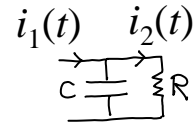


Time constant

$$= CR$$


$$= 4 \times 50 \text{ ps}$$

$$= 0.2 \text{ ns}$$

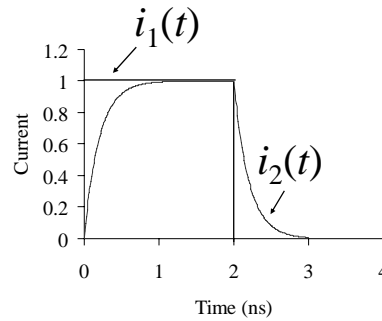


Electrostatics_01_DistributedCapacitance: 5

Two-wire line

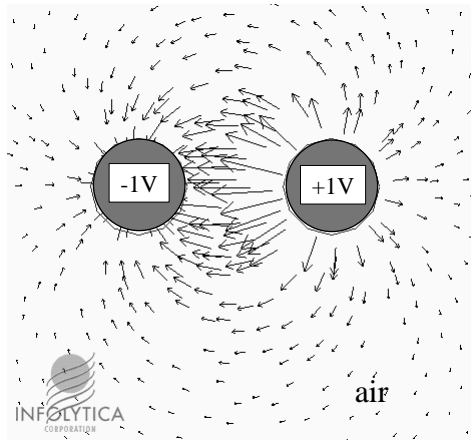



Electrostatics_01_DistributedCapacitance: 6

Coaxial cable

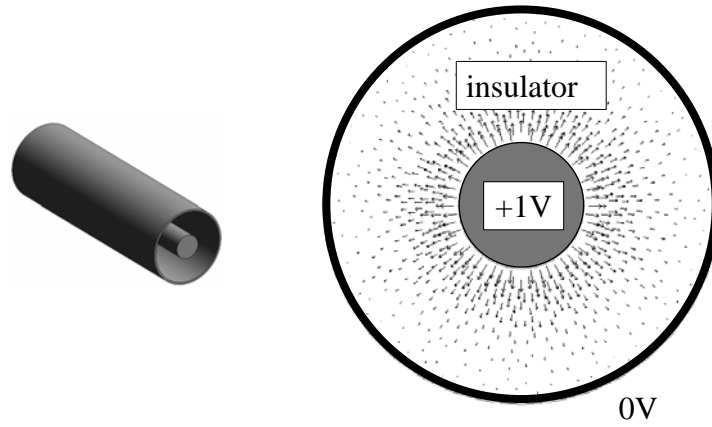

Electrostatics_01_DistributedCapacitance: 7

Printed Circuit Board (PCB)

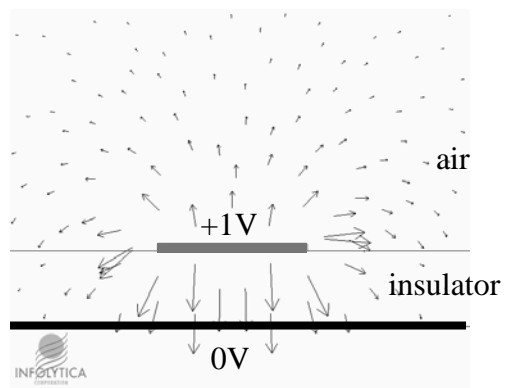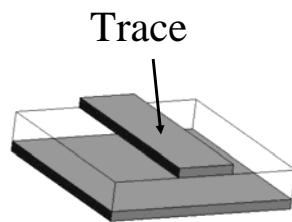

Electrostatics_01_DistributedCapacitance: 8