

Problem Set 9

Solutions

ProblemSet_09: 1

1.
(9-10)

a)

$$Z_0 = \sqrt{\frac{L}{C}}$$

$$L = \frac{\mu}{\pi} \cosh^{-1}\left(\frac{D}{2a}\right)$$

$$C = \frac{\pi \epsilon}{\cosh^{-1}(D/2a)}$$

$$Z_0 = \sqrt{\frac{\frac{\mu}{\pi} \cosh^{-1}(D/2a)}{\pi \epsilon \cosh^{-1}(D/2a)}} = \sqrt{\frac{\mu}{\pi^2 \epsilon} (\cosh^{-1}(D/2a))^2}$$

ProblemSet_09: 2

$$Z_0 = \frac{1}{\pi} \sqrt{\frac{\mu}{\epsilon}} \cosh^{-1}\left(\frac{D}{2a}\right) = 300 \Omega$$

$$= \frac{120}{\sqrt{\epsilon_r}} \ln \left[\frac{D}{2a} + \sqrt{\left(\frac{D}{2a}\right)^2 - 1} \right] = 300$$

$$\frac{D}{2a} = 21.27 \rightarrow \boxed{D = 25.5 \times 10^{-3} \text{ m}}$$

ProblemSet_09: 3

b) For a coax,

$$L = \frac{\mu}{2\pi} \ln \frac{b}{a}$$

$$C = \frac{2\pi\epsilon}{\ln(b/a)}$$

$$Z_0 = \sqrt{\frac{\frac{\mu}{2\pi} \ln(b/a)}{\frac{2\pi\epsilon}{\ln(b/a)}}} = \frac{1}{2\pi} \sqrt{\frac{\mu}{\epsilon}} \ln(b/a)$$

$$= \frac{40}{\sqrt{\epsilon_r}} \ln\left(\frac{b}{a}\right) = 75$$

$$\frac{b}{a} = 6.52 \rightarrow \boxed{b = 3.91 \times 10^{-3} \text{ m}}$$

ProblemSet_09: 4

(9-18)

2.

$$Z_L = 40 + j30 \Omega$$

$$Z_0 = 50 \Omega$$

$$f = 200 \text{ MHz}$$

$$l = 2 \text{ m}$$

$$\beta l = \frac{2\pi f}{c} \cdot l = \frac{8\pi}{3} = 480^\circ$$


$$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l}$$

$$= 50 \frac{(40 + j30) + j50(-1.732)}{50 + j(40 + j30)(-1.732)}$$

$$Z_{in} = 26.3 - j9.87 \Omega$$

ProblemSet_09: 5

3. (9-30)

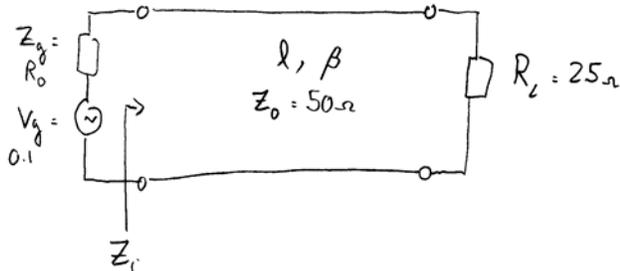

$$(a) \quad Z_i = R_0 \left[\frac{R_L + R_0 j \tan \beta l}{R_0 + R_L j \tan \beta l} \right]$$
$$= R_0 \left[\frac{1 + 2j \tan \beta l}{2 + j \tan \beta l} \right]$$

ProblemSet_09: 6

$$\text{Then } V_i = \frac{Z_i}{Z_i + Z_g} V_g = \frac{(1 + Z_i \tan \beta l)}{3(1 + j \tan \beta l)} \times 0.1$$

$$I_i = \frac{V_i}{Z_i} = \frac{2 + j \tan \beta l}{3(1 + j \tan \beta l)} \times 2 \times 10^{-3}$$

$$\left. \begin{array}{l} V_i = V^+ + V^- \\ R_o I_i = V^+ - V^- \end{array} \right\} \Rightarrow V^+ = \frac{V_i + R_o I_i}{2}$$

$$= \frac{1}{2} \cdot 0.1 \frac{(3 + 3j \tan \beta l)}{3(1 + j \tan \beta l)} = 0.05 V$$

ProblemSet_09: 7

$$\text{At load: } V_L^+ = V^+ e^{-j\beta l} = 0.05 e^{-j\beta l}$$

$$\text{Then } V_L^- = \Gamma_L V_L^+ = \left(\frac{Z_L - Z_o}{Z_L + Z_o} \right) 0.05 e^{-j\beta l}$$

$$= -\frac{0.05}{3} e^{-j\beta l}$$

$$V_L = V_L^+ + V_L^- = \frac{0.1}{3} e^{-j\beta l} = 0.0333 e^{-j\beta l}$$

$$I_L = \frac{V_L}{Z_L} = \frac{0.1}{3 \times 25} e^{-j\beta l} = (1.33 \times 10^{-3}) e^{-j\beta l}$$

ProblemSet_09: 8

$$(b) \text{ SWR} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} = \frac{1 + \frac{1}{3}}{1 - \frac{1}{3}} = 2$$

$$(c) \text{ POWER} = \frac{1}{2} \operatorname{Re} V_L I_L^* \\ = \frac{1}{2} \operatorname{Re} \frac{0.1}{3} \times \frac{0.1}{3 \times 25} = 0.0222 \text{ mW}$$

ProblemSet_09: 9

If $R_L = 50$ (matched load):


$$V_L = V_i = \frac{R_o}{R_o + R_o} V_g = \frac{V_g}{2} = \frac{0.1}{2} \text{ V}$$

$$\text{POWER} = \frac{1}{2} \operatorname{Re} V_L \frac{V_L^*}{R_o} = \frac{1}{2} \frac{1}{50} \left| \frac{0.1}{2} \right|^2 \\ = 0.025 \text{ mW}$$

i.e. more power to load when load
is matched

ProblemSet_09: 10

4. (a)

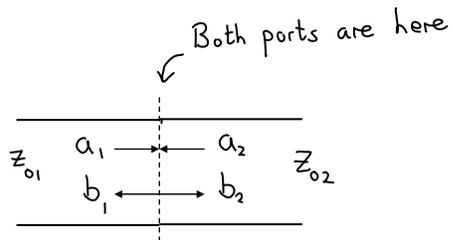


Step 1: Set $a_2=0$, $a_1=1$. Then

$$\begin{aligned} V_1 &= \sqrt{Z_{01}} (1 + S_{11}) & V_2 &= \sqrt{Z_{02}} S_{21} \\ I_1 &= (1 - S_{11}) / \sqrt{Z_{01}} & I_2 &= -S_{21} / \sqrt{Z_{02}} \end{aligned}$$

ProblemSet_09: 11

Step 2:

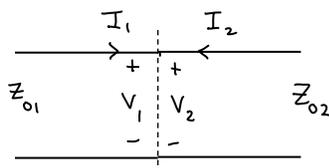

$$V_1 = V_2$$

$$I_1 = -I_2$$

Step 3: Substitute:

$$\sqrt{Z_{01}} (1 + S_{11}) = \sqrt{Z_{02}} S_{21}$$

$$(1 - S_{11}) / \sqrt{Z_{01}} = + S_{21} / \sqrt{Z_{02}}$$

ProblemSet_09: 12

Step 4: Solve

$$\begin{aligned}\sqrt{z_{01}}(1+S_{11}) &= \sqrt{z_{02}}S_{21} \\ (1-S_{11})/\sqrt{z_{01}} &= + S_{21}/\sqrt{z_{02}}\end{aligned}$$

$$1+S_{11} = r S_{21} \quad \text{where } r = \sqrt{\frac{z_{02}}{z_{01}}}$$

$$1-S_{11} = \frac{1}{r} S_{21}$$

$$\Rightarrow \left(r + \frac{1}{r}\right) S_{21} = 2 \Rightarrow S_{21} = \frac{2r}{1+r^2} = \frac{2\sqrt{z_{01}z_{02}}}{z_{02}+z_{01}}$$

$$S_{11} = \frac{2r^2}{1+r^2} - 1 = \frac{r^2-1}{r^2+1} = \frac{z_{02}-z_{01}}{z_{02}+z_{01}}$$

ProblemSet_09: 13

$$\begin{aligned}\text{Step 5: } S_{12} &= S_{21} \text{ (passive)} \\ &= \frac{2\sqrt{z_{01}z_{02}}}{z_{02}+z_{01}}\end{aligned}$$

$$\begin{aligned}S_{22} &= S_{11} \text{ (symmetric)} \\ &= \frac{z_{02}-z_{01}}{z_{02}+z_{01}}\end{aligned}$$

$$S_0 = \begin{bmatrix} \frac{z_{02}-z_{01}}{z_{02}+z_{01}} & \frac{2\sqrt{z_{01}z_{02}}}{z_{02}+z_{01}} \\ \frac{2\sqrt{z_{01}z_{02}}}{z_{02}+z_{01}} & \frac{z_{02}-z_{01}}{z_{02}+z_{01}} \end{bmatrix}$$

ProblemSet_09: 14

$$[S] = \begin{bmatrix} \frac{z_{02} - z_{01}}{z_{02} + z_{01}} & \frac{2\sqrt{z_{01}z_{02}}}{z_{02} + z_{01}} \\ \frac{2\sqrt{z_{01}z_{02}}}{z_{02} + z_{01}} & \frac{z_{02} - z_{01}}{z_{02} + z_{01}} \end{bmatrix}$$

Check the case $z_{01} = z_{02}$:

$$[S] = \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix} \quad \text{Is this right?}$$

With $z_{01} = 100$, $z_{02} = 50$:

$$[S] = \begin{bmatrix} -\frac{1}{3} & \frac{2\sqrt{2}}{3} \\ \frac{2\sqrt{2}}{3} & -\frac{1}{3} \end{bmatrix}$$

ProblemSet_09: 15

4 (b) For a lossless device: $|S_{11}|^2 + |S_{21}|^2 = 1$
 $|S_{12}|^2 + |S_{22}|^2 = 1$


Here:

$$|S_{11}|^2 + |S_{21}|^2 = \frac{1}{9} + \frac{8}{9} = 1$$

$$|S_{12}|^2 + |S_{22}|^2 = \frac{8}{9} + \frac{1}{9} = 1$$

ProblemSet_09: 16

4 (c)

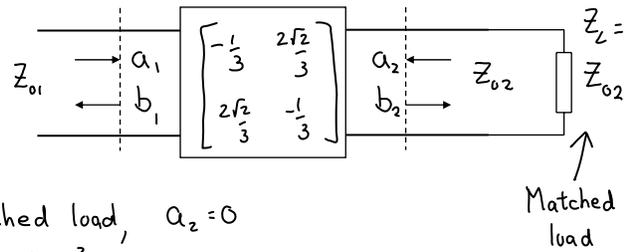

With matched load, $a_2 = 0$

$$P_{\text{inc}} = \frac{1}{2} |a_1|^2$$


$$P_{\text{absorbed}} = \frac{1}{2} |b_2|^2$$

$$b_2 = S_{21} a_1 + S_{22} a_2 = S_{21} a_1 = \frac{2\sqrt{2}}{3} a_1$$

$$\text{So } \frac{P_{\text{absorbed}}}{P_{\text{inc}}} = \frac{|b_2|^2}{|a_1|^2} = \frac{8}{9} //$$

ProblemSet_09: 17

5.

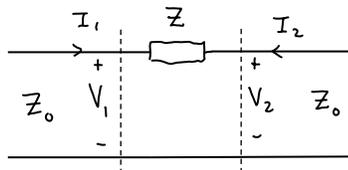

Step 1: Set $a_2 = 0$, $a_1 = 1$. Then

$$\begin{aligned} V_1 &= \sqrt{Z_0} (1 + S_{11}) & V_2 &= \sqrt{Z_0} S_{21} \\ I_1 &= (1 - S_{11}) / \sqrt{Z_0} & I_2 &= -S_{21} / \sqrt{Z_0} \end{aligned}$$

Step 2: $I_1 = -I_2$

$$V_1 = V_2 + I_1 Z$$

ProblemSet_09: 18

Step 3: Substitute

$$I_1 = -I_2 \quad \Rightarrow \quad (1-S_{11})\sqrt{Z_0} = +S_{21}\sqrt{Z_0}$$

$$V_1 = V_2 + I_1 Z \quad \Rightarrow \quad \sqrt{Z_0}(1+S_{11}) = \sqrt{Z_0}S_{21} + (1-S_{11})\frac{Z}{\sqrt{Z_0}}$$

Step 4: Solve

$$1-S_{11} = S_{21} \quad r = Z/Z_0$$

$$1+S_{11} = S_{21} + r(1-S_{11})$$

$$\Rightarrow S_{11} = \frac{r}{2}(1-S_{11}) \Rightarrow \left(1 + \frac{r}{2}\right)S_{11} = \frac{r}{2} \Rightarrow S_{11} = \frac{r}{2+r} = \frac{Z}{Z+2Z_0}$$

$$S_{21} = 1-S_{11} = \frac{2Z_0}{Z+2Z_0}$$

ProblemSet_09: 19

$$\text{Step 5} \quad S_{12} = S_{21} \quad (\text{passive})$$

$$S_{22} = S_{11} \quad (\text{symmetry})$$

$$[S] = \begin{bmatrix} \frac{Z}{Z+2Z_0} & \frac{2Z_0}{Z+2Z_0} \\ \frac{2Z_0}{Z+2Z_0} & \frac{Z}{Z+2Z_0} \end{bmatrix}$$

ProblemSet_09: 20