

PROBLEM SET 10

74



9-33, 9-34, 9-35, 9-36

9-33



$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{1 - \frac{Z_0}{Z_L}}{1 + \frac{Z_0}{Z_L}} = +1$$

$$\Gamma_g = \frac{Z_g - Z_0}{Z_g + Z_0} = \frac{-Z_0}{Z_0} = -1$$

a) $0 < t < T (= \frac{L}{v})$

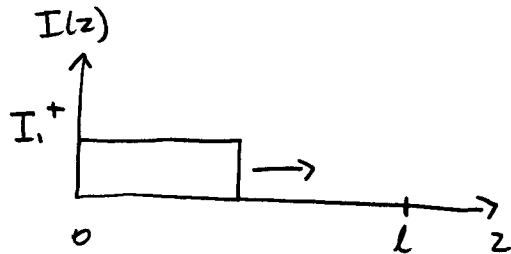
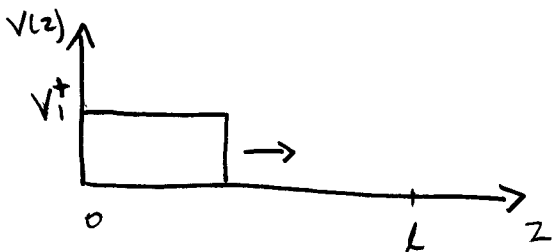


b) $T < t < 2T$

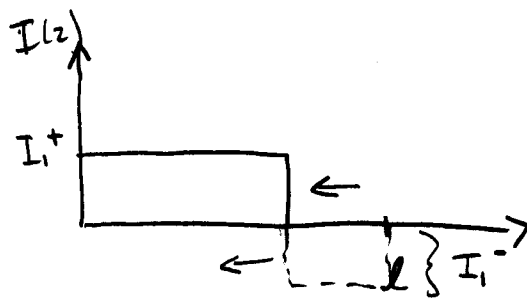
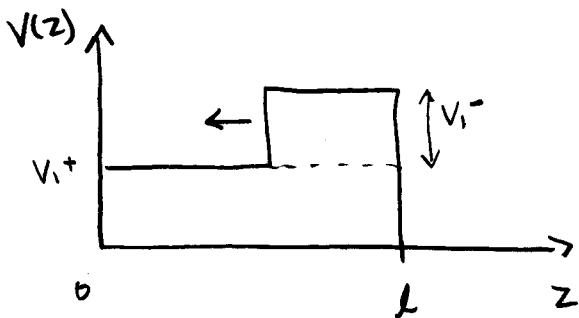


c) $2T < t < 3T$

75

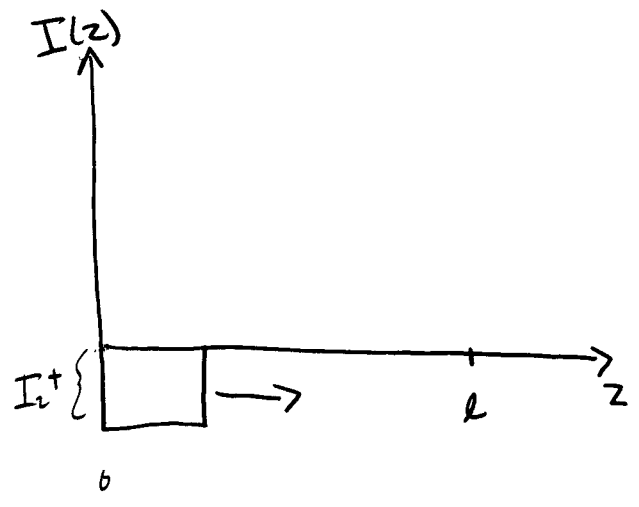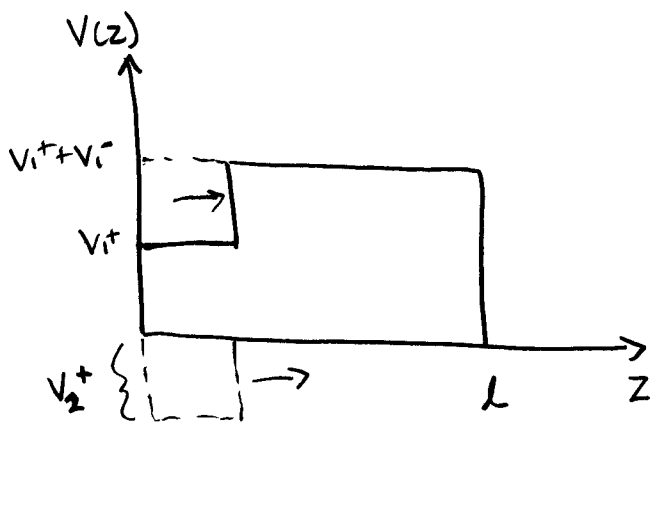

d) $3T < t < 4T$

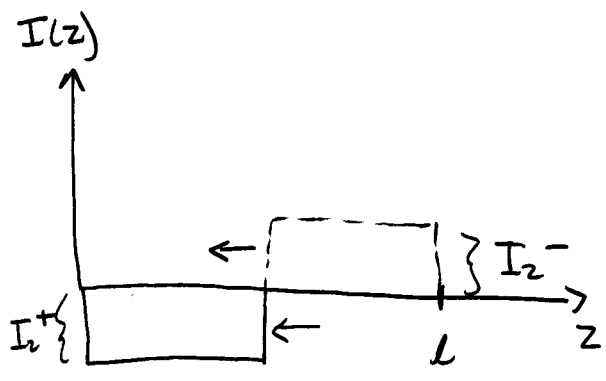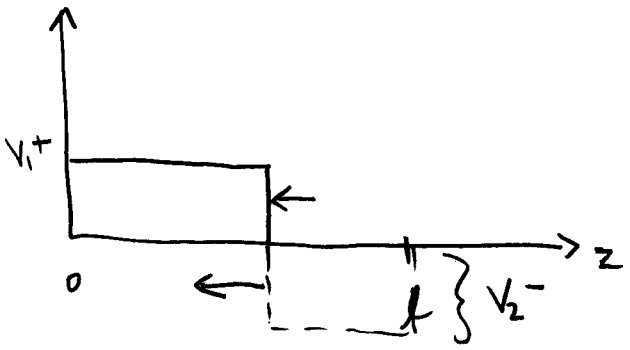

$$V_1^+ = V_0, \quad V_1^- = V_1^+ = V_0$$

$$V_2^+ = -V_1^- = -V_0$$

$$V_2^- = V_2^+ = -V_0$$

$$I_1^+ = \frac{V_0}{R_0}, \quad I_1^- = -I_1^+ = -\frac{V_0}{R_0}$$


$$I_2^+ = I_1^- = -\frac{V_0}{R_0}$$

$$I_2^- = -I_2^+ = \frac{V_0}{R_0}$$


At $t=4T$, both $V(z)$ & $I(z)$ revert back to the conditions at $t=0$. and the cycle repeats itself with a period $4T$.

9-34

76

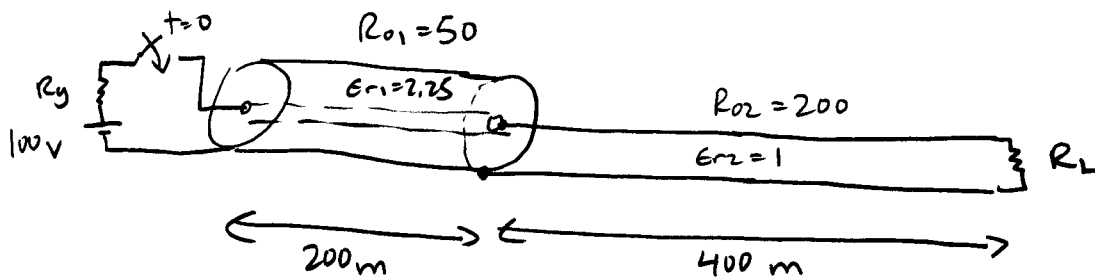

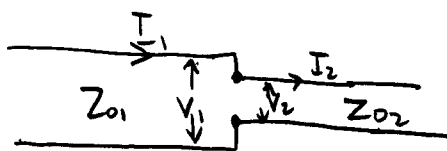At junction of 2 lines w/ Z_{01} & Z_{02}



$$V_1 = V_2 \rightarrow V_1^+ + V_1^- = V_2^+$$

$$I_1 = I_2 \rightarrow I_1^+ + I_1^- = \frac{(V_1^+ - V_1^-)}{Z_{01}} = \frac{V_2^+}{Z_{02}}$$

$$V_1^- = \frac{Z_{02} - Z_{01}}{Z_{02} + Z_{01}} V_1^+, \quad V_2^+ = \frac{2Z_{02}}{Z_{02} + Z_{01}} V_1^+$$

$$I_1^- = - \frac{Z_{02} - Z_{01}}{Z_{02} + Z_{01}} I_1^+, \quad I_2^+ = \frac{2Z_{01}}{Z_{02} + Z_{01}} I_1^+$$

$$I_2^+ = \frac{2Z_{01}}{Z_{02} + Z_{01}} I_1^+$$

$$I_1^- = - \frac{Z_{02} - Z_{01}}{Z_{02} + Z_{01}} I_1^+$$



$$a) \quad V_1^+ = \frac{V_g}{2} = 50 \text{ V} \quad I_1^+ = \frac{V_g}{50+50} = 1 \text{ A} \quad (77)$$

$$V_1^- = \frac{200-50}{200+50} V_1^+ = 30 \text{ V} \quad I_1^- = \frac{200-50}{200+50} I_1^+ = -0.6 \text{ A}$$



$$V_2^+ = \frac{2 \times 200}{200+50} V_1^+ = 80 \text{ V} \quad I_2^+ = \frac{2 \times 50}{200+50} I_1^+ = 0.4 \text{ A}$$

No transient waves on coaxial cable after V_1^- and I_1^- reach input terminals (at $2t_1 = 2 l_1/v_1 = 400/2 \times 10^8 = 2 \mu\text{s}$) and no transient waves on two-wire line after V_2^+ and I_2^+ reach the load R_L (at $t_2 = t_1 + l_2/v_2 = 1 \times 10^{-6} + 400/3 \times 10^8 = 2.33 \mu\text{s}$).

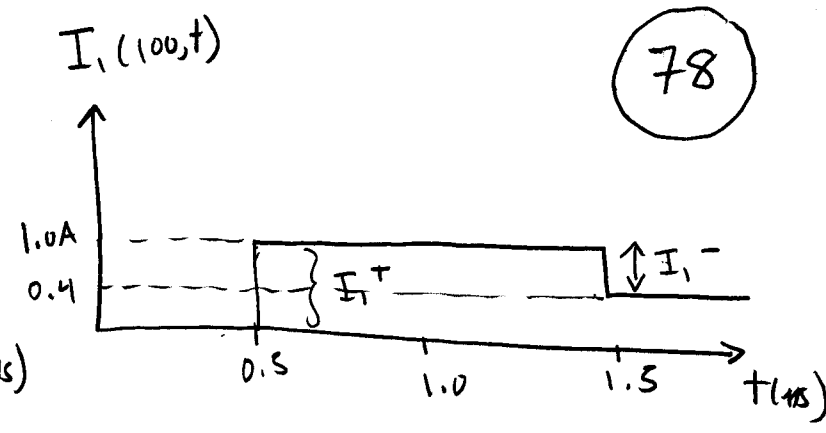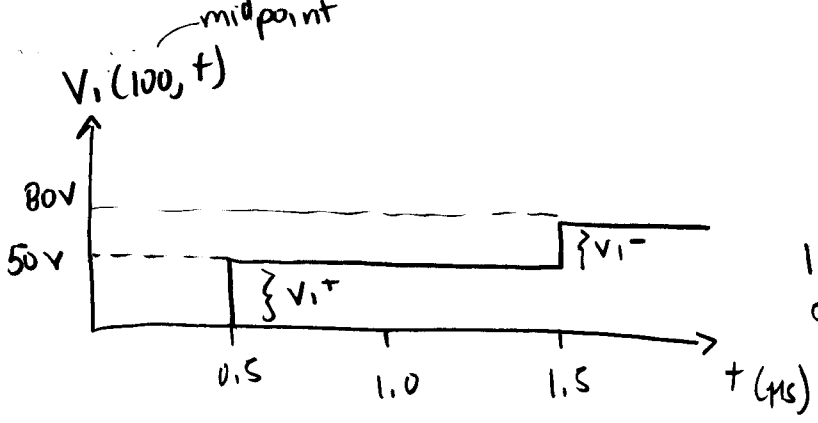b) On the coaxial cable, it takes $t_{1/2} = 0.5 \mu\text{s}$ for V_1^+ & I_1^+ to reach midpoint ($x=100\text{m}$). The reflected waves V_1^- and I_1^- arrive at the midpoint at $t = 3t_{1/2} = 1.5 \mu\text{s}$. There are no changes after that.



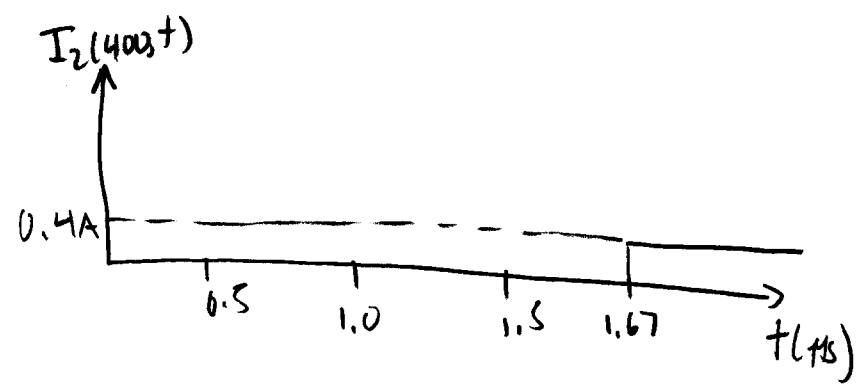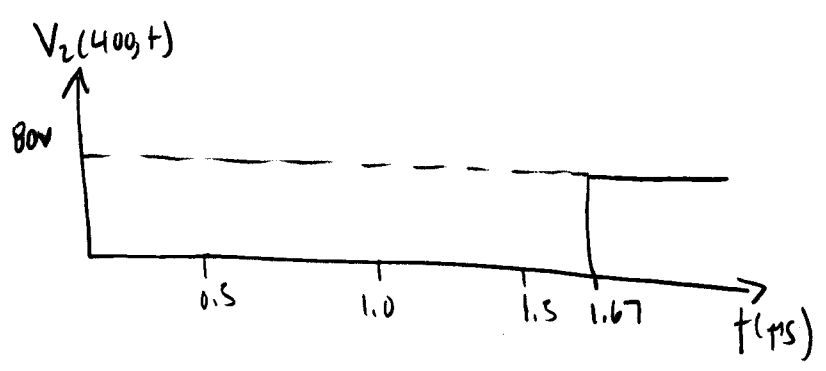c) On two wire system, steady state is reached at $t = t_1 + \frac{200}{3 \times 10^8} = 1.67 \mu s$ distance to midpoint from junction!



9-35

$$R_g = \frac{R_0}{2} \rightarrow$$

$$\Gamma_g = \frac{\frac{R_0}{2} - R_0}{\frac{R_0}{2} + R_0} = \frac{-\frac{1}{2}R_0}{\frac{3}{2}R_0} = -\frac{1}{3}$$

(79)

$$R_L = \infty \rightarrow \Gamma_L = 1$$

$$T = \frac{l}{u}$$


$$V_1^+ = \frac{R_0}{R_0 + \frac{R_0}{2}} V_0 = \frac{2}{3} V_0$$

$$I_1^+ = \frac{V_1^+}{R_0} = \frac{2}{3} \frac{V_0}{R_0}$$


$$t_1 = \frac{1}{2} \frac{l}{2u} = \frac{l}{4u}$$

a)



Voltage Reflection Diagram

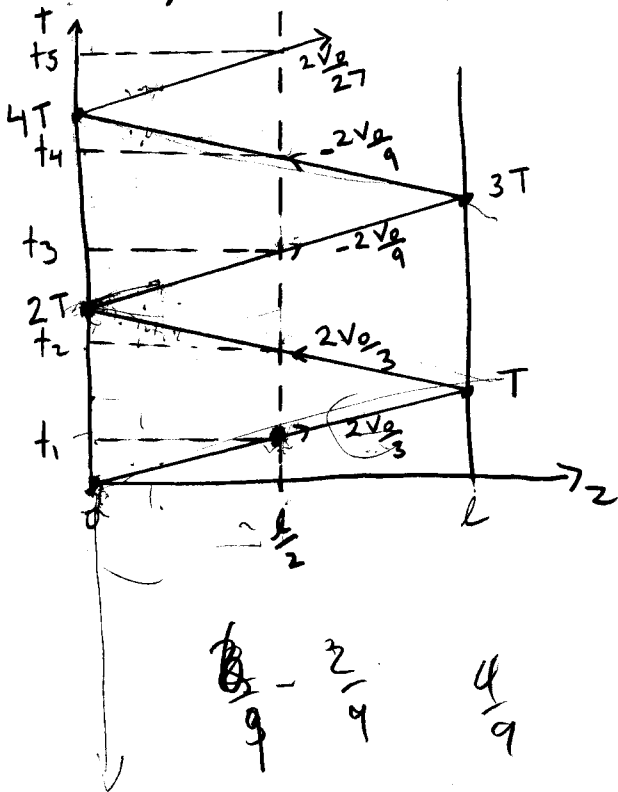



Current Reflection Diagram

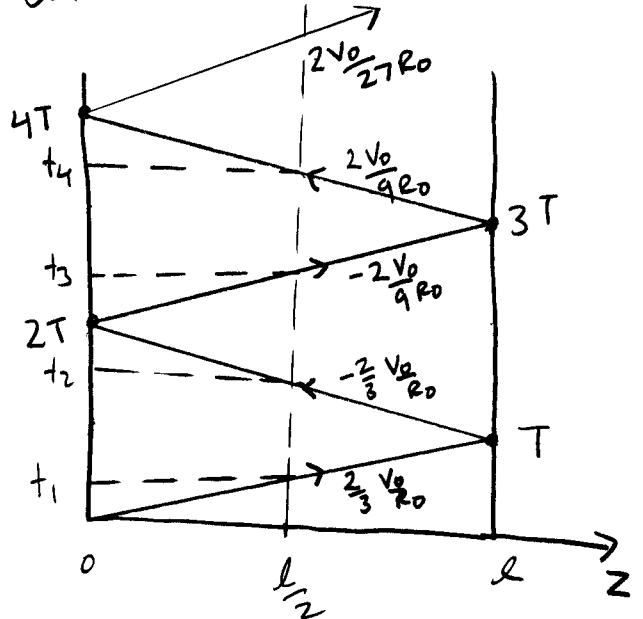

b)

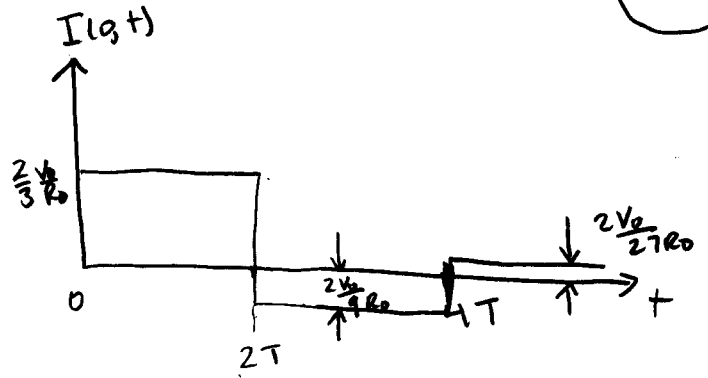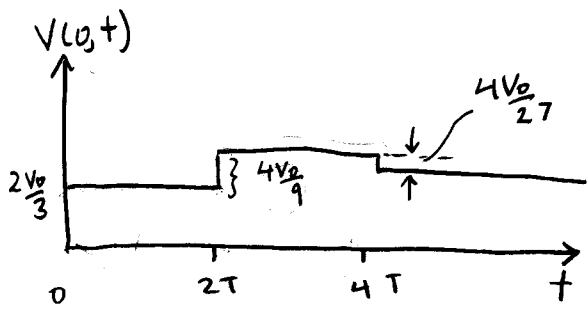

c)

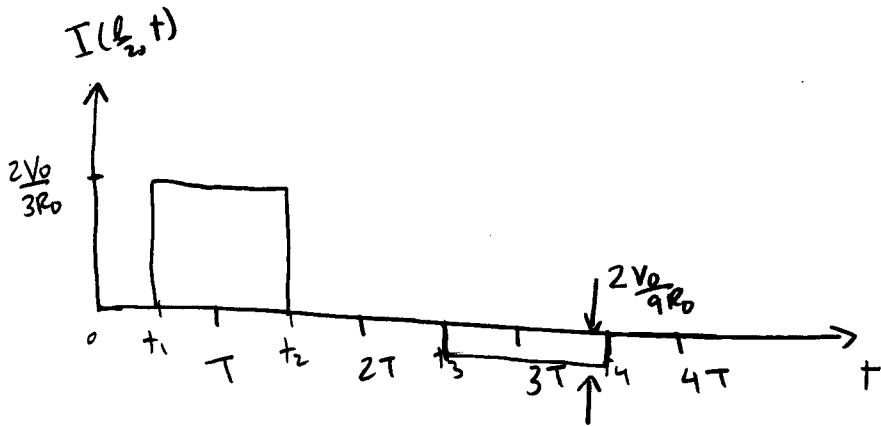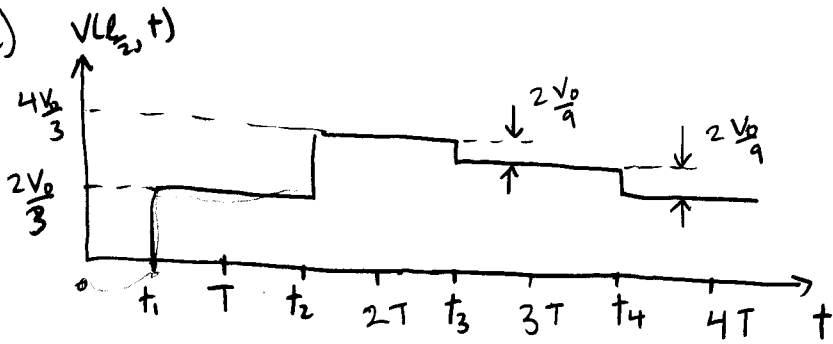

9-3b

$$R_L = 2R_0 \quad R_g = 0 \rightarrow \Gamma_g = -1$$

$$L \rightarrow \Gamma_L = \frac{1}{3} \quad T = \frac{L}{u}$$



$$V_1^+ = V_0$$

$$I_1^+ = \frac{V_0}{R_0}$$



81

a)

Voltage Reflection Diagram

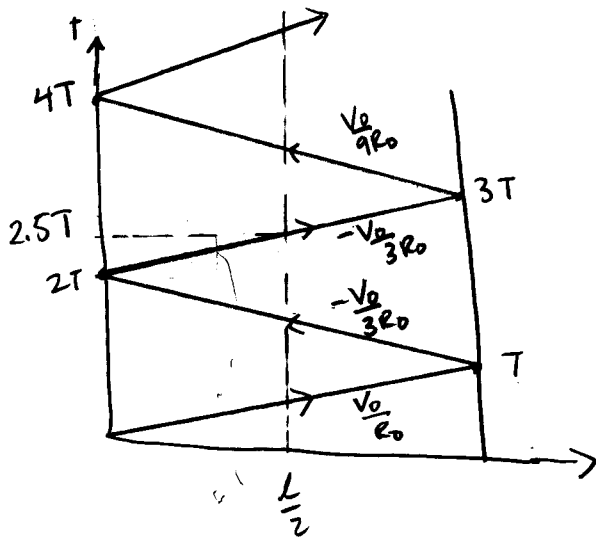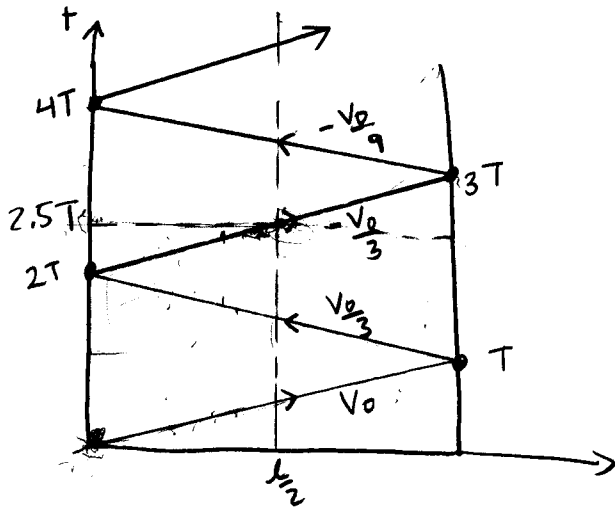

b)

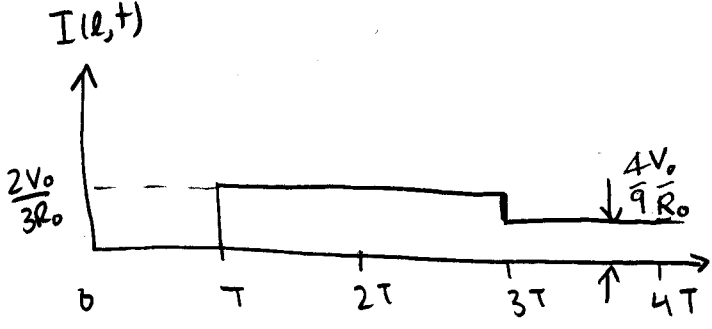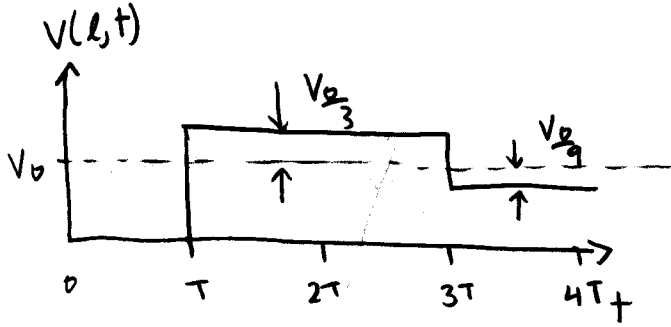

c)

