

McGill University
Department of Electrical and Computer Engineering

Course: ECSE-323 Digital System Design

Winter 2008

Assignment #11 Solutions

TOPIC: Datapath/Controller System Design

Tuesday Tutorial Session

Design a datapath/controller system that computes the *arithmetic-geometric mean* of two inputs x and y , using the following iterative process:

$$a_1 = \frac{x + y}{2}$$

$$g_1 = \sqrt{xy}.$$

$$a_{n+1} = \frac{a_n + g_n}{2}$$

$$g_{n+1} = \sqrt{a_n g_n}.$$

As this process is iterated many times the two values a and g will converge to the same number, which is known as the arithmetic-geometric mean.


Assume that in addition to the two inputs x and y , your system has an asynchronous **START** input, an asynchronous **RESET** input, and an input **N_ITER** indicating the number of iterations to be done. The outputs of the system should be the values a and g , and a signal **DONE** which goes high once **N_ITER** iterations have been done.

- a) Write down a pseudo-code description of the process to be implemented.
- b) Draw the datapath, assuming that only one adder module, one multiplier module, and one square root module are available. You can use as many other modules as you see fit.
- c) Draw the state transition diagram for the controller (use a Moore machine approach).


a)

1. wait for START to go low
2. wait for START to go high
3. $a = x$; $g = y$; $n=0$; -- initialize
4. $a = (a+g)/2$; $g = \text{square_root}(a*g)$; $n = n+1$;
5. if $n < N_ITER$ go to step 4
6. else assert DONE and go to step 1

b) Datapath:

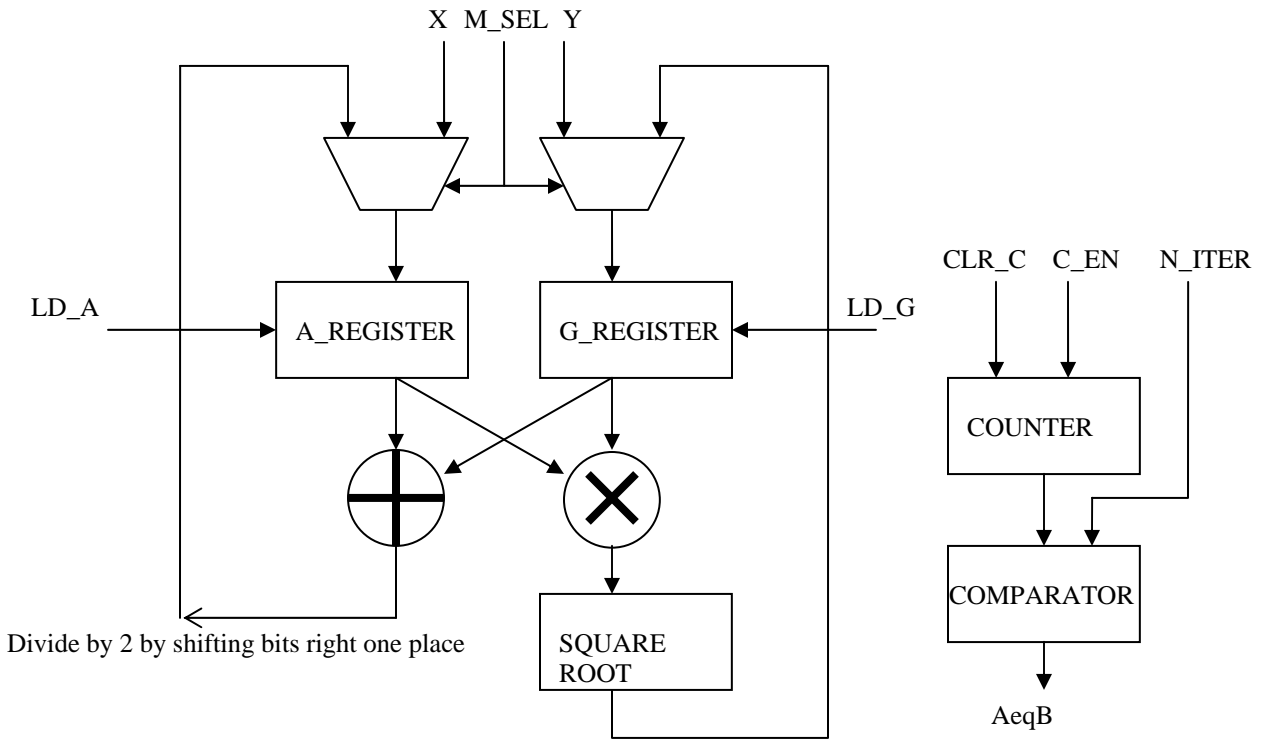

c) State Diagram:

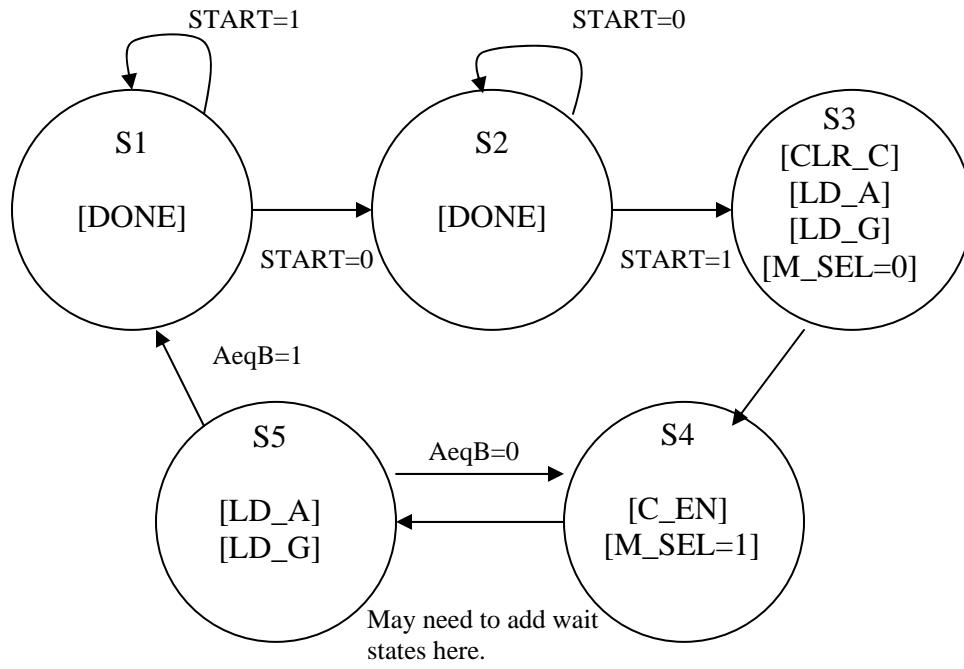

Wednesday Tutorial Session

Design a datapath/controller system that computes the natural logarithm of a number (assumed to lie in the range 1 to 2) using the following third order power series approximation:

$$\ln(1+x) = \sum_{n=1}^{\infty} \frac{(-1)^{n+1}}{n} x^n = x - \frac{x^2}{2} + \frac{x^3}{3} - \dots \quad \text{for } |x| \leq 1 \quad \text{unless } x = -1$$


- Write down a pseudo-code description of the process to be implemented. Assume that you only need to implement the terms shown above.
- Draw the datapath, assuming that only one adder/subtractor module and one multiplier module are available. You can use as many other modules as you see fit. Implement the division by 3 by a multiplication by 21 and a division by 64.
- Draw the state transition diagram for the controller (use a Moore machine approach). Your system should have as input the number y , an asynchronous *START* signal, and an asynchronous *reset* signal. The system output should be the natural log of y and a *DONE* signal, which should go high once a valid result is available.

a)

- wait for START to go low
- wait for START to go high
- $P = 1; L = 0;$
- $L = L+Y;$
- $L = L-1; X = L; -- X \text{ and } L \text{ are now } Y-1$
- $P = X*P; -- P \text{ is now } X$
- $P = X*P; -- P \text{ is now } X^2$
- $L = L-P/2; -- L \text{ is now } X-X^2/2$
- $P = X*P; -- P \text{ is now } X^3$
- $X = 21;$
- $P = X*P;$
- $L = L+P/64; -- L \text{ is now } X-X^2/2+X^3/3$
- assert DONE and go to step 1

Note that the multiplier operands are always X and P . The output of the multiplier always gets loaded into P . One operand to the adder/subtractor is always L . The output of the adder/subtractor always gets loaded into L . Whether the add/sub module adds or subtracts is determined by the control signal ADD/SUB.

b) Datapath:

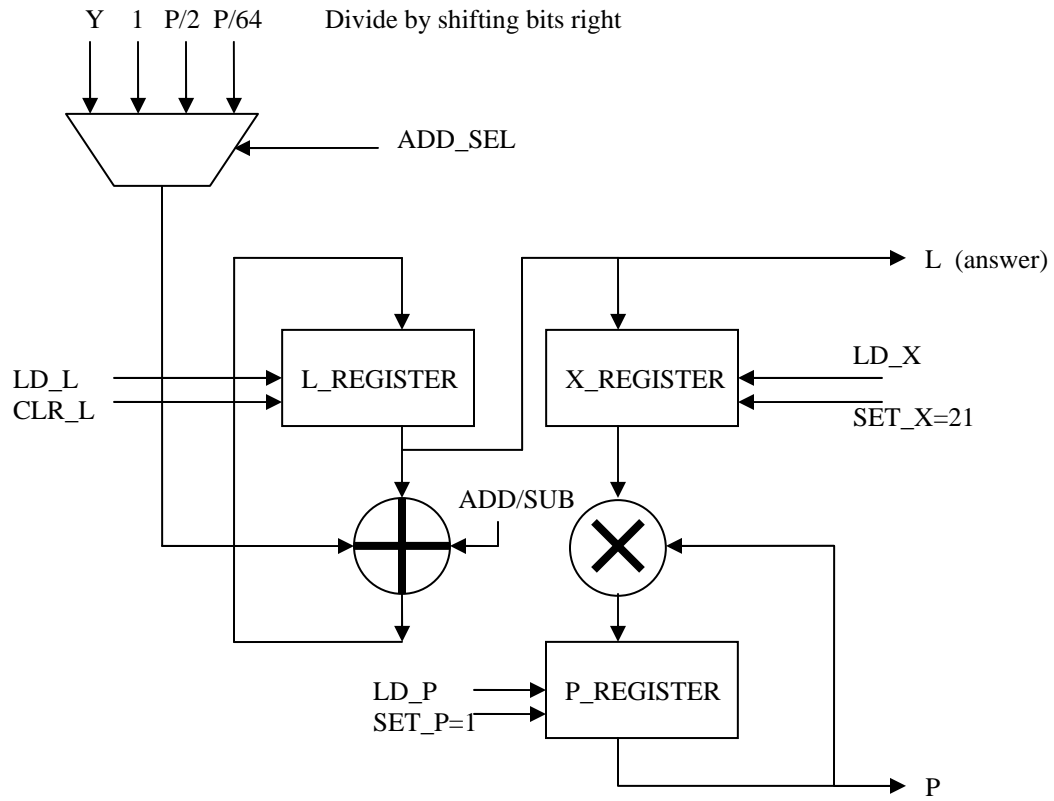

c) State Diagram:

