



Outline of Chapter 5, Section 5.8-5.9

- 1- High-Frequency Model of BJT
- 2- Frequency Response of CEA
- Note: Frequency response of CBA and CCA are covered in EC2



High-Frequency Model

- The small signal model discussed was assumed to be instantaneous and no reactive element was included.
- We add the capacitive effects due to the pn junctions to the hybrid- π model
- The average time that a charge carrier spends in crossing the base is called **forward base-transit time** τ_F
 - This represent the small-signal diffusion capacitance C_{de}

$$C_{de} = \tau_F g_m = \tau_F \frac{I_C}{V_T}$$

- The total BEJ capacitance is called C_π and is composed of two parts:

$$C_\pi = C_{de} + C_{je}$$



High-Frequency Model

- There is also the Base-Emitter junction capacitance in the forward bias C_{je}

$$C_{je} \cong 2C_{je0}$$

- Where C_{je0} is the value of C_{je} when zero voltage is applied to EBJ
- CBJ is reverse biased and its junction depletion capacitance is


$$C_{\mu} = \frac{C_{\mu0}}{\left(1 + \frac{V_{CB}}{V_{0c}}\right)^m} \quad 0.2 \leq m \leq 0.5$$

- Where V_{0c} is the CBJ built-in voltage (0.75V), $C_{\mu0}$ is the value of C_{μ} when zero voltage is applied and m is the grading coefficient



High-Frequency Hybrid- π Model

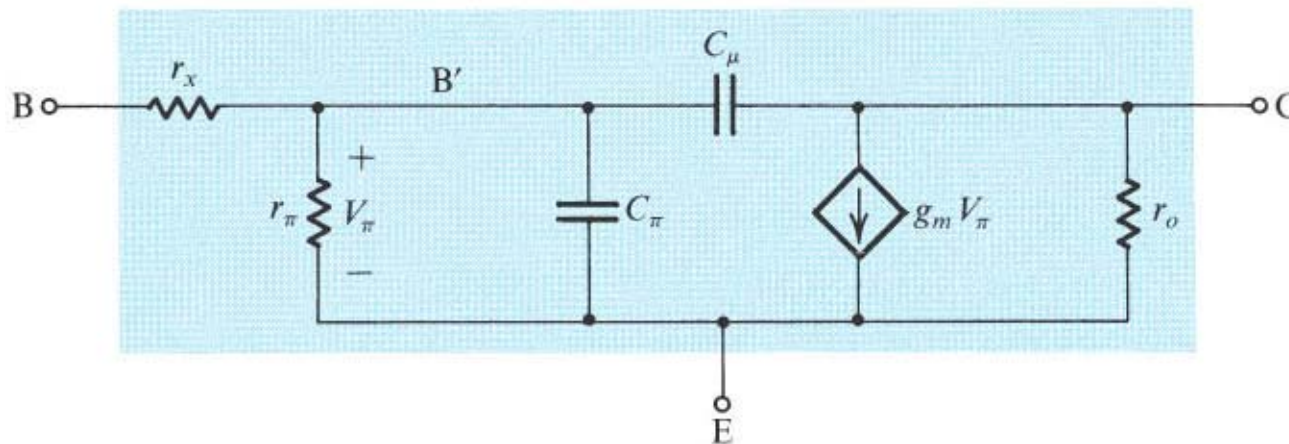- Two capacitances: Capacitance C_π is usually larger than C_μ (Fig. 5.67):




- Note: There is new high-frequency component, resistor r_x
 - r_x represents the resistance of the Silicon in the base region.
 - It is a few tens of Ohms.
- Since $r_x \ll r_\pi$, it is neglected at low frequencies



BJT Unity-Gain Bandwidth

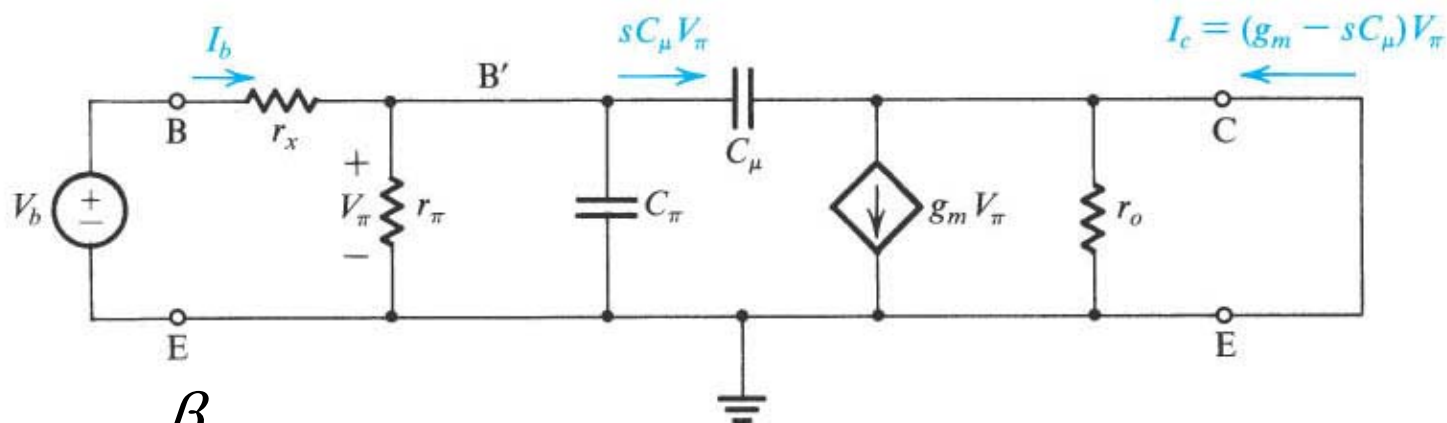- Unity-gain bandwidth, f_T , is a figure of merit for high-frequency operation.
- It is found from the short circuit current gain of CEA, $h_{fe} = I_c / I_b$




$$h_{fe} = \frac{\beta_0}{1 + s(C_\pi + C_\mu)r_\pi}$$

Lowpass STC

$$\omega_{3dB-cutoff} = \omega_\beta = \frac{1}{(C_\pi + C_\mu)r_\pi}$$




BJT Unity-Gain Bandwidth

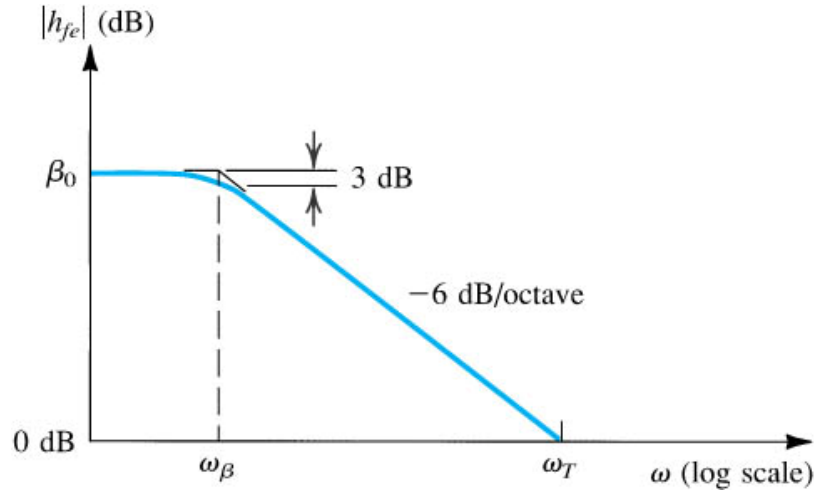

$$\omega_T = \beta_0 \omega_\beta$$

$$f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)}$$

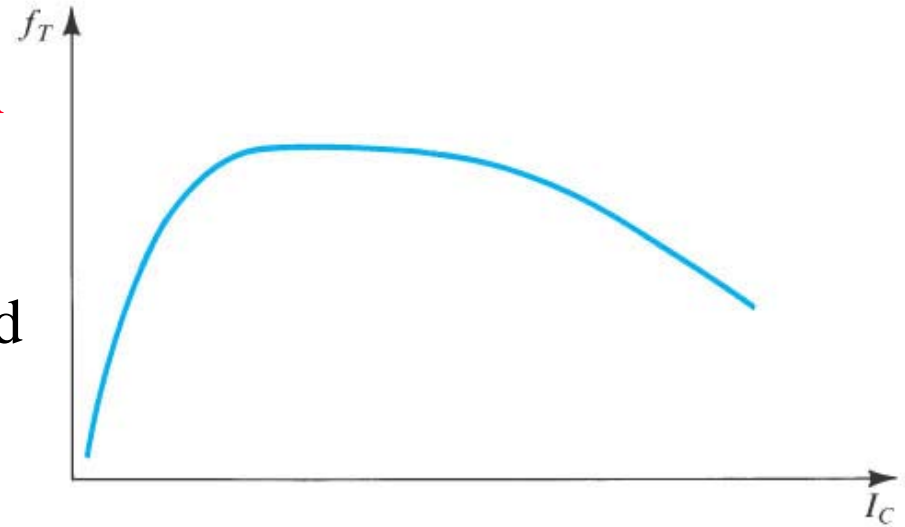- f_T is called **the unity-gain bandwidth**
- It is given as function of I_C in data sheets
- The behavior is due to few combined effects
- f_T is from 100 MHz to tens of GHz







Frequency Response of CEA

- Midband gain:
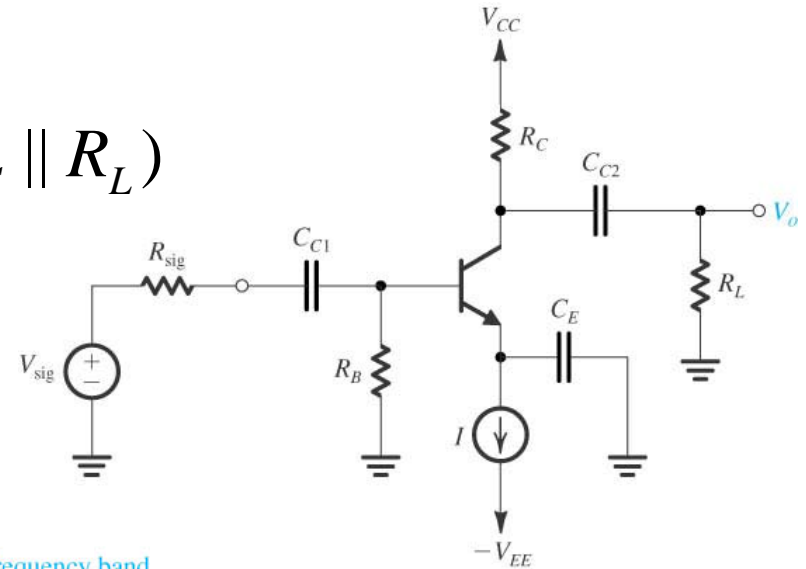
$$A_M = \frac{V_o}{V_{sig}} = - \frac{(R_B \parallel r_\pi)}{(R_B \parallel r_\pi) + R_{sig}} g_m (r_o \parallel R_C \parallel R_L)$$



(a)

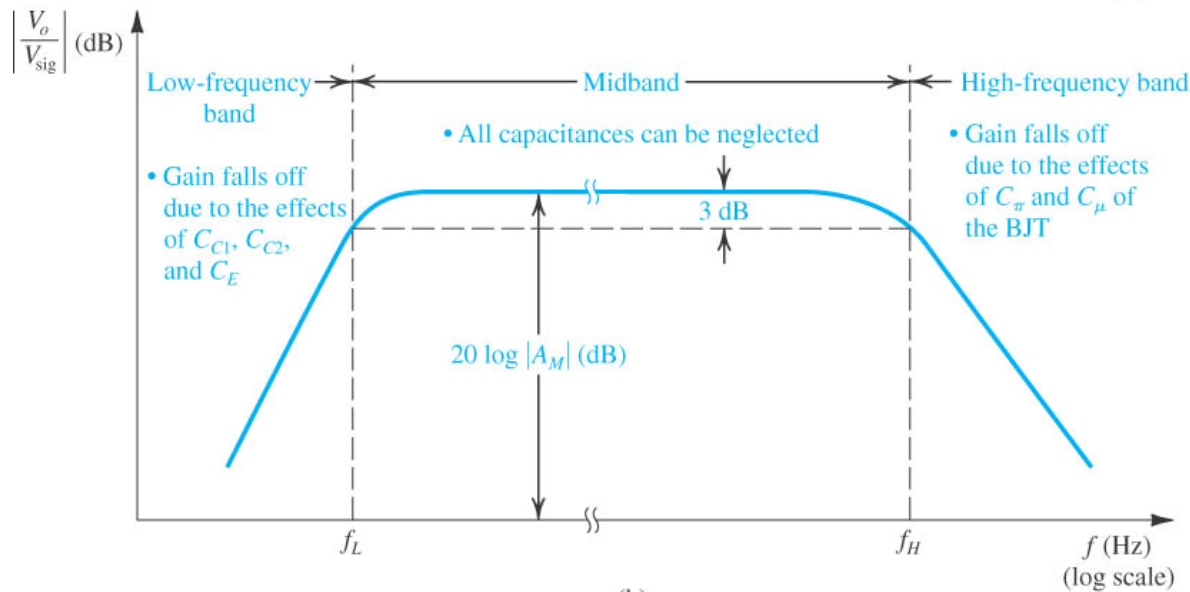

(b)



High-Frequency Response (CEA)

- f_H and f_L are frequencies at which gain is 3 dB lower than the midband value $|gain| = |A_M| / \sqrt{2}$
- 3dB bandwidth is:

$$BW \equiv f_H - f_L$$


- If $f_L \ll f_H$ then $BW \cong f_H$
- A figure of merit for an amplifier is gain-bandwidth product

$$GB \equiv |A_M| BW$$




High-Frequency Response (CEA)

- CEA

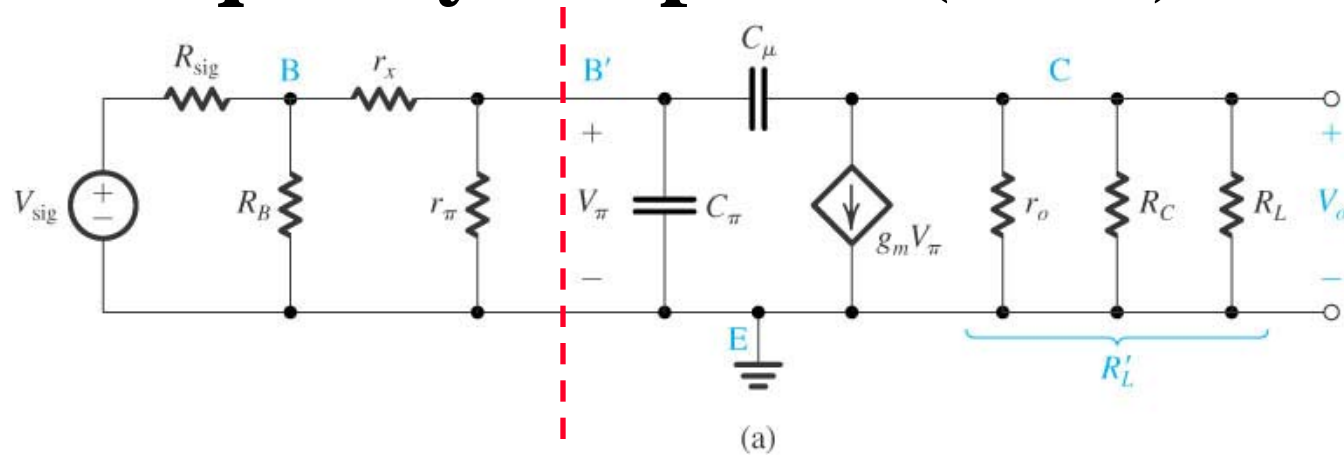

- Using Thevenin Theorem

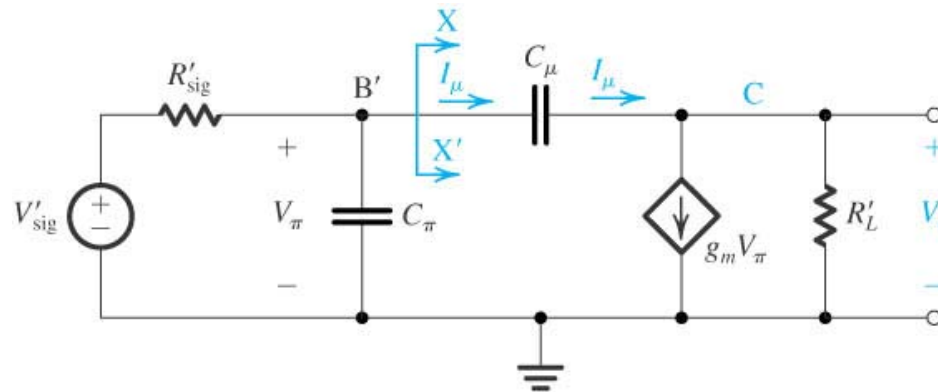

$$V'_{sig} = V_{sig} \frac{R_B}{R_B + R_{sig}} \frac{r_{\pi}}{r_{\pi} + r_x + (R_{sig} // R_B)}$$

$$R'_L = r_o // R_C // R_L$$

$$R'_{sig} = r_{\pi} // [r_x + (R_B // R_{sig})]$$

(b)




High-Frequency Response (CEA)

- Find equivalent for C_μ


Miller Effect

Miller Multiplier = $(1 + g_m R'_L)$

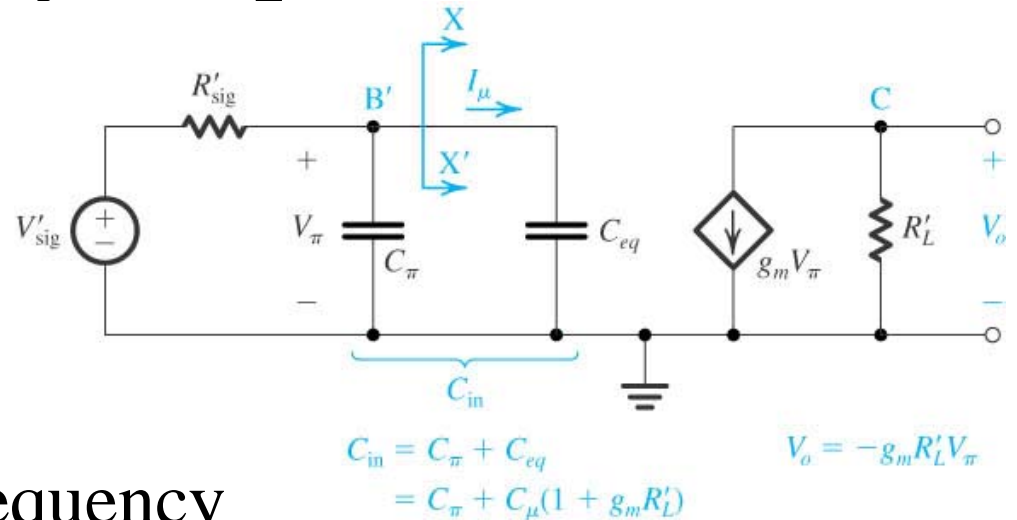

- Lowpass STC: Corner frequency
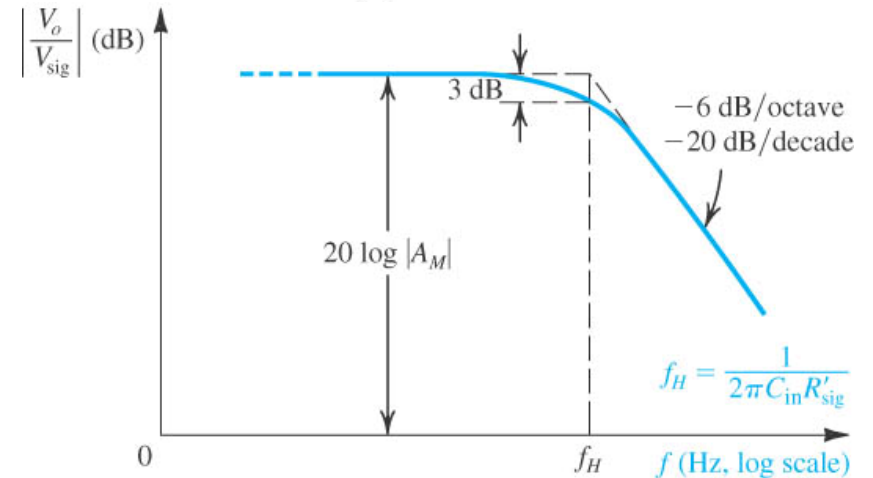
$$\omega_H = \omega_0 = \frac{1}{C_{in} R'_{sig}} = \frac{1}{(C_\pi + C_{eq}) R'_{sig}}$$



- High-frequency gain of CEA


$$\frac{V_o}{V_{sig}} = \frac{A_M}{1 + \frac{s}{\omega_H}}$$

(d)





Low-Frequency Response (CEA)

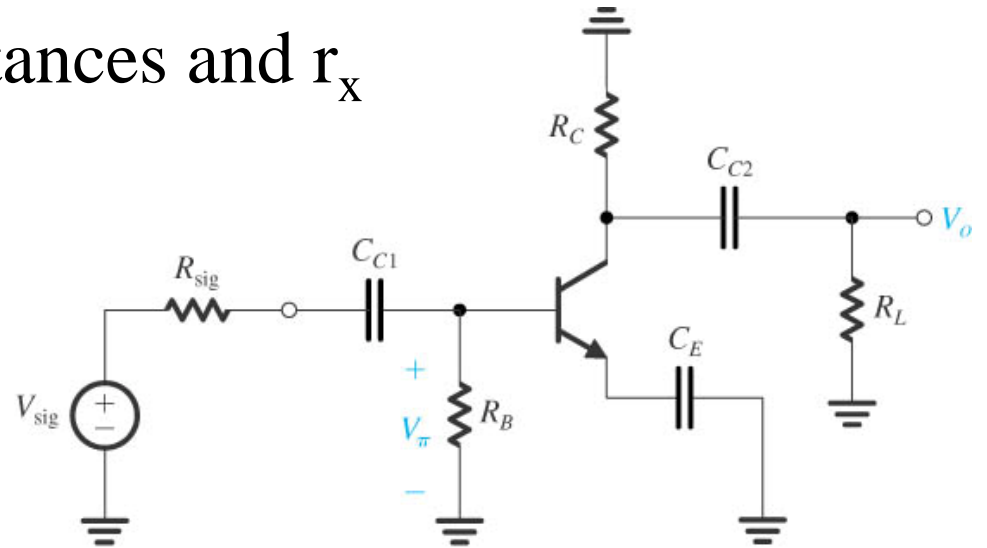- Ignoring internal capacitances and r_x
- Consider:
 - Other Cs are sort circuit
 - V_{sig} is zero



$$f_{P1} = \frac{1}{2\pi C_{C1} (R_B \parallel r_\pi + R_{sig})}$$

Highpass STC

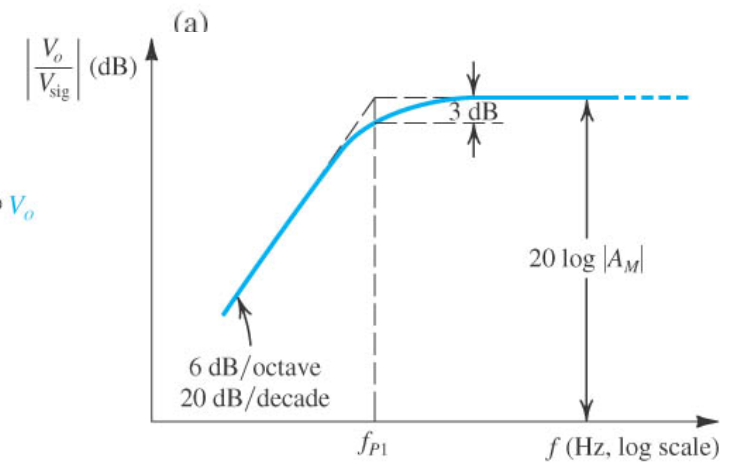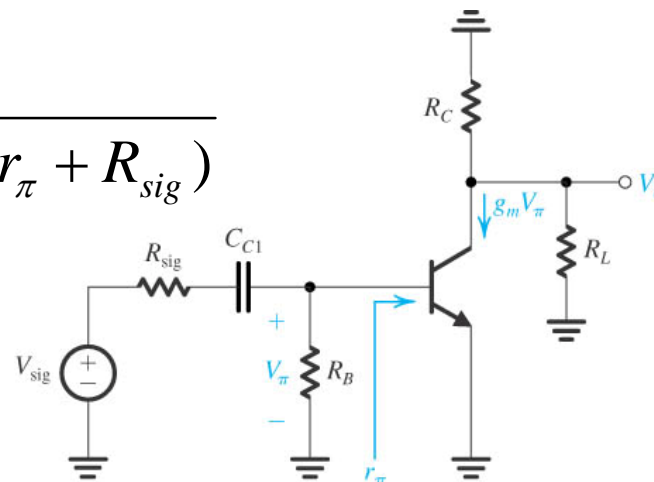



$$f_{P1} = 1/2\pi C_{C1} [(R_B \parallel r_\pi) + R_{sig}]$$

(b)



Low-Frequency Response (CEA)

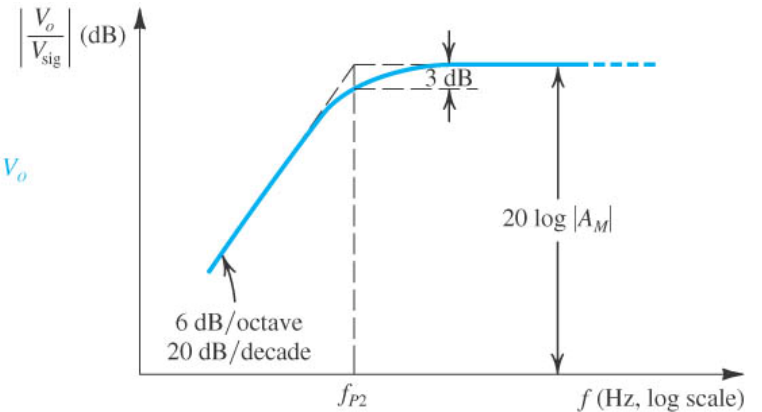
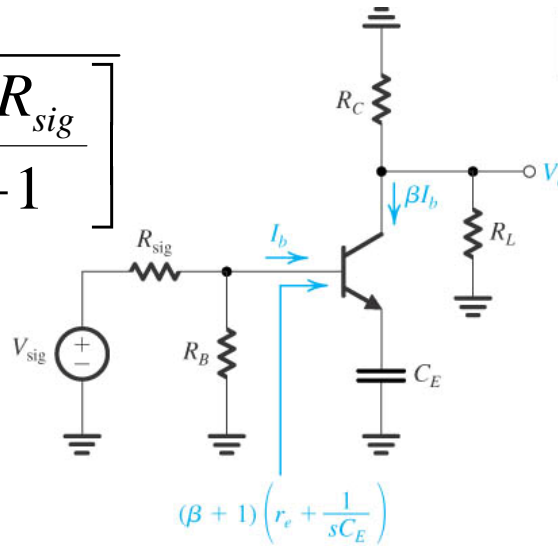
$$f_{P2} = \frac{1}{2\pi C_E \left[r_e + \frac{R_B \parallel R_{sig}}{\beta + 1} \right]}$$



$$f_{P2} = 1/2\pi C_E \left[r_e + \frac{R_B \parallel R_{sig}}{\beta + 1} \right]$$

Highpass STC
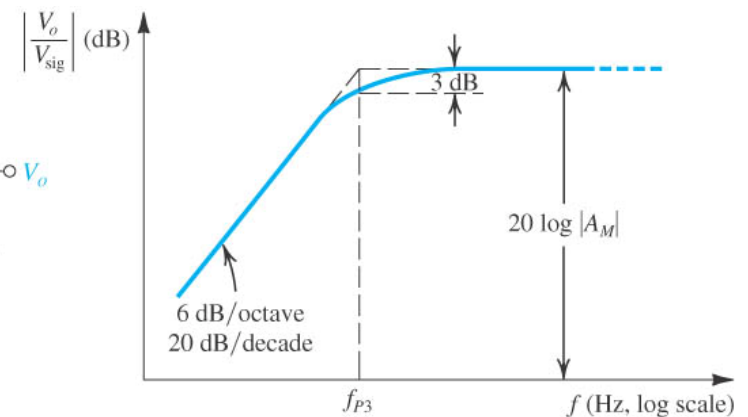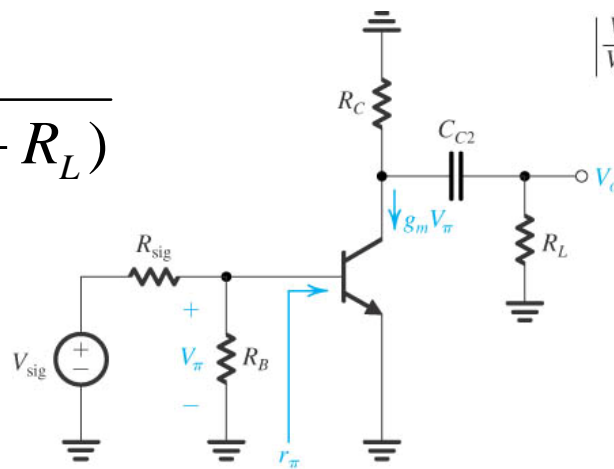
$$f_{P3} = \frac{1}{2\pi C_{C2} (R_C + R_L)}$$



$$f_{P3} = 1/2\pi C_{C2} (R_C + R_L)$$


(c)

(d)



Low-Frequency Response (CEA)

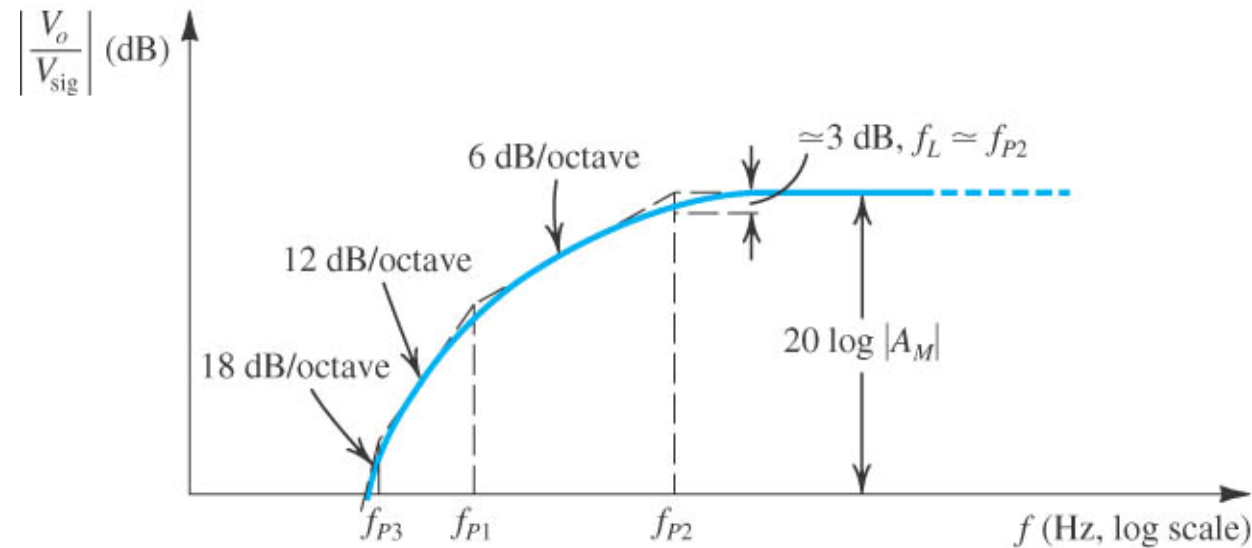- To find the time constant for poles f_{p1} , f_{p2} and f_{p3}
 - Set source to zero
 - Consider each C separately (others are short circuit)
 - Find the total resistance seen between the two terminals of C



(e)



Low-Frequency Response (CEA)

- When all three Cs are present and do not interact;

$$\frac{V_o}{V_{sig}} = -A_M \frac{s}{s + \omega_{P1}} \frac{s}{s + \omega_{P2}} \frac{s}{s + \omega_{P3}}$$

- The f_L is determined by the highest f_P (Often f_{P2})
- When the three Cs interact, the f_L is considered as the summation of f_{P1}, f_{P2}, f_{P3} for approximate hand calculations or SPICE simulations are used to find it.
- If it is not mentioned in the problem, consider that the Cs do not interact