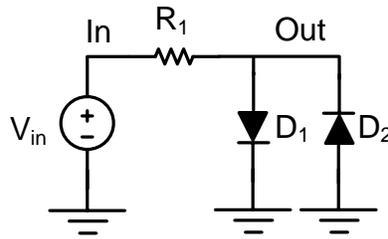


Let's say that you want to implement the following circuit in PSPICE:



R_1 is 1KOhm and D_1 and D_2 are identical diodes with the following PSPICE model:

```
.model diode d(Is=2.68n n=1.8)
```

1) To find the voltage transfer characteristic of the above limiter you need to define a DC input and perform a DC sweep on the input and look at the output voltage:

Create a new txt file and type in the following code:

Diode limiter

* the first line is ALWAYS assumed to be the title and if you define a component on the first line of your code it is ignored.

*circuit description. It is usually very helpful if you assign names (rather than numbers) to different nodes

R1 in out 1K

* you don't need to mention the unit. PSICE already knows that a resistor is being defined. If you are defining a capacitor of "one Farad" don't write 1F since PSPICE will assume that it's a 1fF capacitor

D1 out 0 diode

D2 0 out diode

```
.model diode d(Is=2.68n n=1.8)
```

Vi in 0 DC 0

```
.op
```

*to report the DC operating point in the output file

```
.DC Vi -5 5 0.01
```

*performing the DC sweep


```
.probe
```

*to open a data window and be able to look at different voltages vs Vi

```
.end
```

*anything written after this line is ignored

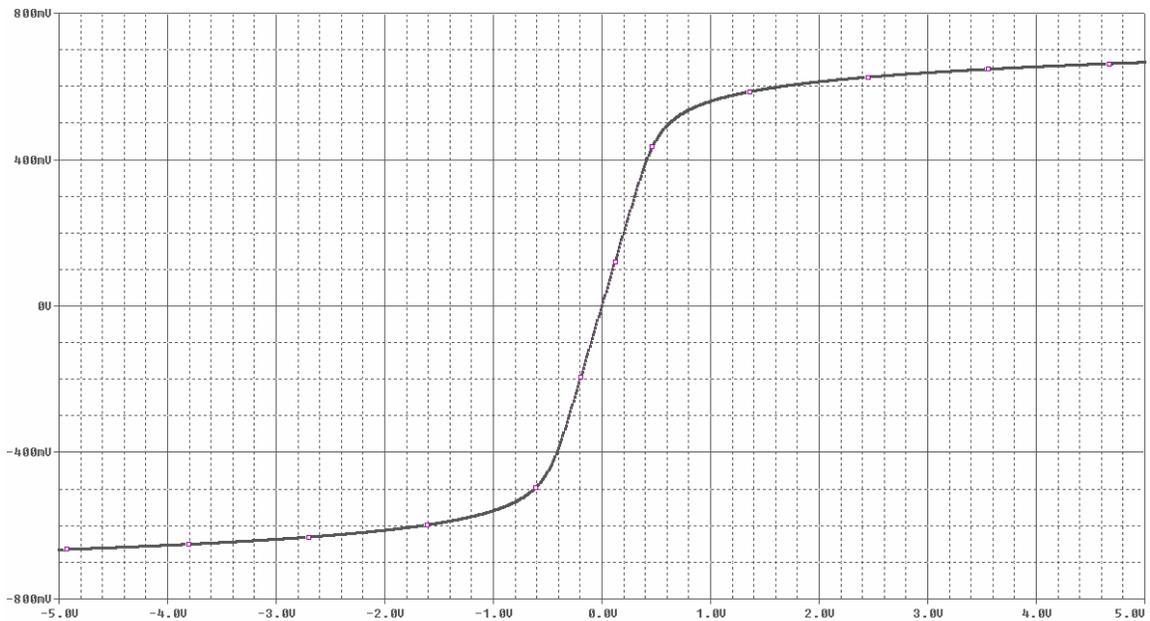- I. Save the file as “filename.cir”.
- II. Click on “Simulation Queue” button on the left. PSPICE Simulation Manager window will open.
- III. In this window filename.cir appears under “Simulation” (if you don’t see the filename you may need to close PSPICE and rerun it).
- IV. Click on filename.cir in the simulation manager window and click on “run”.
- V. “data display” window will open.
- VI. In the data display window go to “add trace”.
- VII. You can choose V(out) (voltage at node “out”). You can also choose certain functions of the voltages at different nodes (for example you can plot $20 \cdot \log_{10}(V(\text{out})/V(\text{in}))$ if you are doing an AC sweep and want to draw the bode plot of the gain). If you choose V(out) you will see the following voltage transfer characteristic:



2) To find the gain at zero DC bias vs frequency you can define an AC input and perform an AC sweep:

Diode limiter

R1 in out 1K
D1 out 0 diode
D2 0 out diode

.model diode d(Is=2.68n n=1.8)


Vi in 0 AC 1m

.op
.AC LIN 1000 10k 10meg

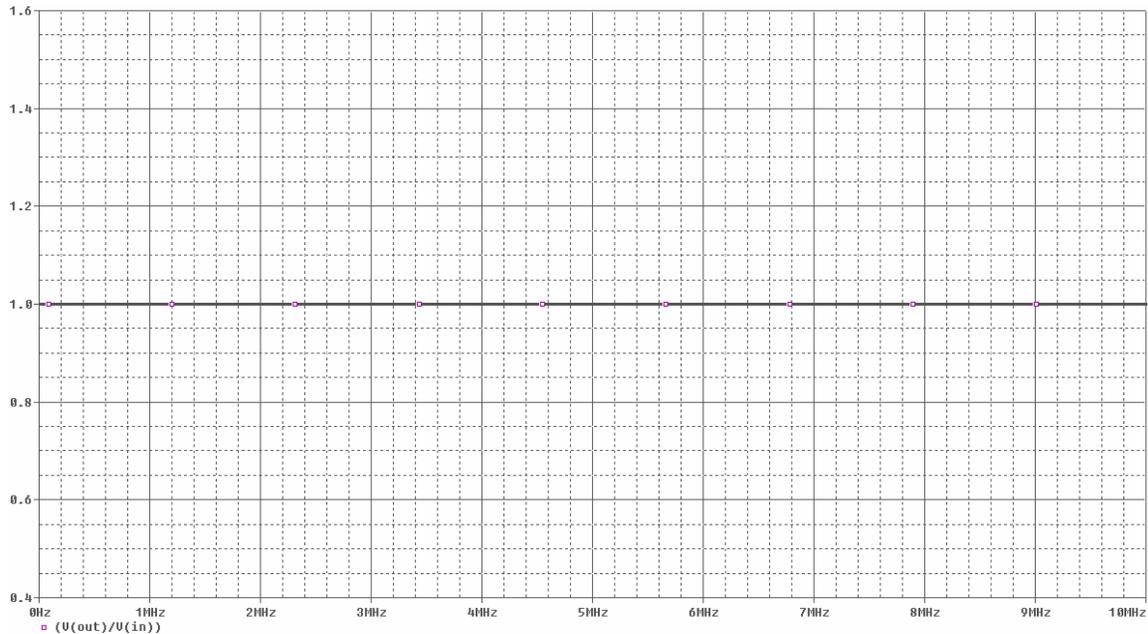***performing the AC sweep**

```
.probe  
.end
```

Repeat steps I-VII from the previous section. If you choose $V(\text{out})/V(\text{in})$ you will see the following plot:



3) There is also another way to find the gain at one particular frequency and that is to look at the output waveform when the input is a small-signal sinusoid. To do this you need to perform a transient simulation:

Diode limiter

```
R1 in out 1K  
D1 out 0 diode  
D2 0 out diode
```

```
.model diode d(Is=2.68n n=1.8)
```

```
Vi in 0 sin(0 1m 10k)
```

```
.op  
.tran 1u 0.5m 0 1u  
*performing the transient simulation  
.probe  
.end
```

Repeat steps I-VII from the previous section. If you choose V(out) you will see the following output voltage waveform:

