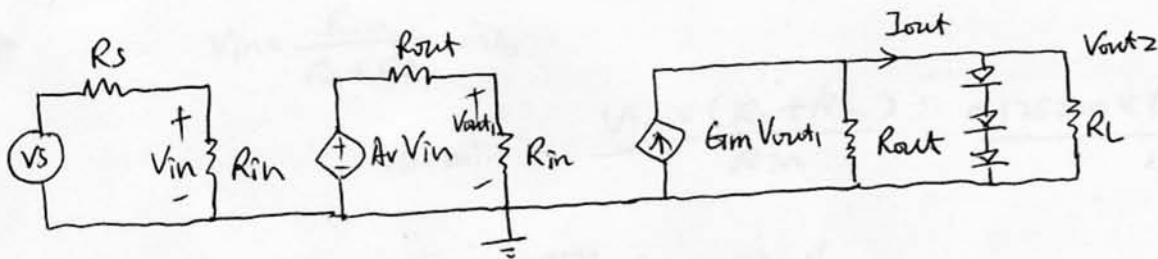


Q1.

a)



b) All diodes OFF.

$$V_{in} = \frac{R_{in}}{R_{in} + R_s} \cdot V_s \quad (1)$$

$$V_{out1} = \frac{A_v R_{in}}{R_{out} + R_{in}} \cdot V_{in} \quad (2)$$

$$I_{out} = \frac{R_{out}}{R_{out} + R_L} \times G_m V_{out1} \quad (3)$$

Combine (1)(2)(3)

$$I_{out} = \frac{R_{out}}{R_{out} + R_L} \times G_m \cdot \frac{A_v \cdot R_{in}}{R_{out} + R_{in}} \times \frac{R_{in}}{R_{in} + R_s} V_s$$

$$G_{m-tot} = \frac{I_{out}}{V_s} = \frac{R_{in}^2 R_{out} \cdot A_v G_m}{(R_{out} + R_L)(R_{in} + R_{out})(R_{in} + R_s)}$$

Since $R_{in} = R_{out}$

$$G_{m-tot} = \frac{R_{in}^2 A_v G_m}{2(R_{in} + R_s)(R_{out} + R_L)}$$

c) $I_d = 5 \text{ mA}$ $V_{out2} = 3 \times 0.7 = 2.1 \text{ V}$.

$$I_L = \frac{V_{out2}}{R_L} = \frac{2.1 \text{ V}}{2 \text{ k}} = 1.05 \text{ mA}$$

$$I_{out} = I_d + I_L = 5 + 1.05 = 6.05 \text{ mA}$$

(Note that since diodes are ON, the equation derived in part b) is not valid any more.)

The current flow through the output resistance R_{out2} is I_{Rout}

$$I_{Rout} = \frac{V_{out2}}{R_{out}} = \frac{2.1}{10 \text{ k}} = 0.21 \text{ mA}$$

$$\therefore G_m V_{out1} = I_{Rout} + I_{out} = 6.26 \text{ mA}$$

$$\Rightarrow V_{out1} = \frac{6.26m}{500m} = 0.01252V = 12.52mV.$$


$$A_v V_{in} = 2V_{out1} \quad V_{in} = \frac{2V_{out1}}{A_v} = 0.1252mV.$$

$$V_{in} = \frac{R_{in}}{R_s + R_{in}} \cdot V_s.$$

$$\therefore V_{s-min} = \frac{V_{in} \times (R_s + R_{in})}{R_{in}} = \frac{0.1252m \times (10K + 1K)}{10K}$$

$$V_{s-min} = 0.13772 \approx 0.138mV.$$

d).

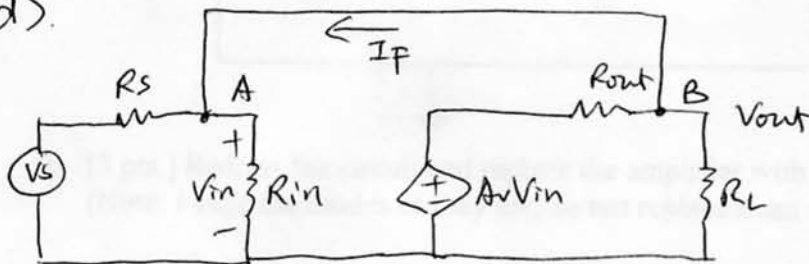

KCL @ node A.

$$\frac{V_s - V_{in}}{R_s} + I_F = \frac{V_{in}}{R_{in}}$$

↓

$$I_F = \frac{V_{in}}{R_{in}} - \frac{V_s - V_{in}}{R_s}$$

KCL @ node B.

$$\frac{A_v V_{in} - V_{out}}{R_{out}} = \frac{V_{out}}{R_L} + I_F$$

$$I_F = \frac{A_v V_{in} - V_{out}}{R_{out}} - \frac{V_{out}}{R_L}$$

$$\frac{V_{in}}{R_{in}} - \frac{V_s - V_{in}}{R_s} = \frac{A_v V_{in} - V_{out}}{R_{out}} - \frac{V_{out}}{R_L}$$

$$V_{in} = V_{out}$$

$$\frac{1}{R_{in}} - \frac{\frac{V_s}{V_{out}} - 1}{R_s} = \frac{A_v - 1}{R_{out}} - \frac{1}{R_L}$$

$$\frac{1}{R_{in}} - \frac{A_v - 1}{R_{out}} + \frac{1}{R_L} + \frac{1}{R_s} = \frac{1}{R_s} \cdot \frac{V_s}{V_{out}}$$


$$\frac{V_{out}}{V_s} = \frac{1}{R_s} \left[\frac{1}{R_{in}} + \frac{1}{R_L} + \frac{1}{R_s} - \frac{A_v - 1}{R_{out}} \right]^{-1}$$

Put all numbers in:

~~$$\frac{V_{out}}{V_s} = \frac{1}{1K} \left[\frac{1}{10K} + \frac{1}{2K} + \frac{1}{1K} - \frac{200-1}{10K} \right]^{-1}$$~~

Q2:

a)

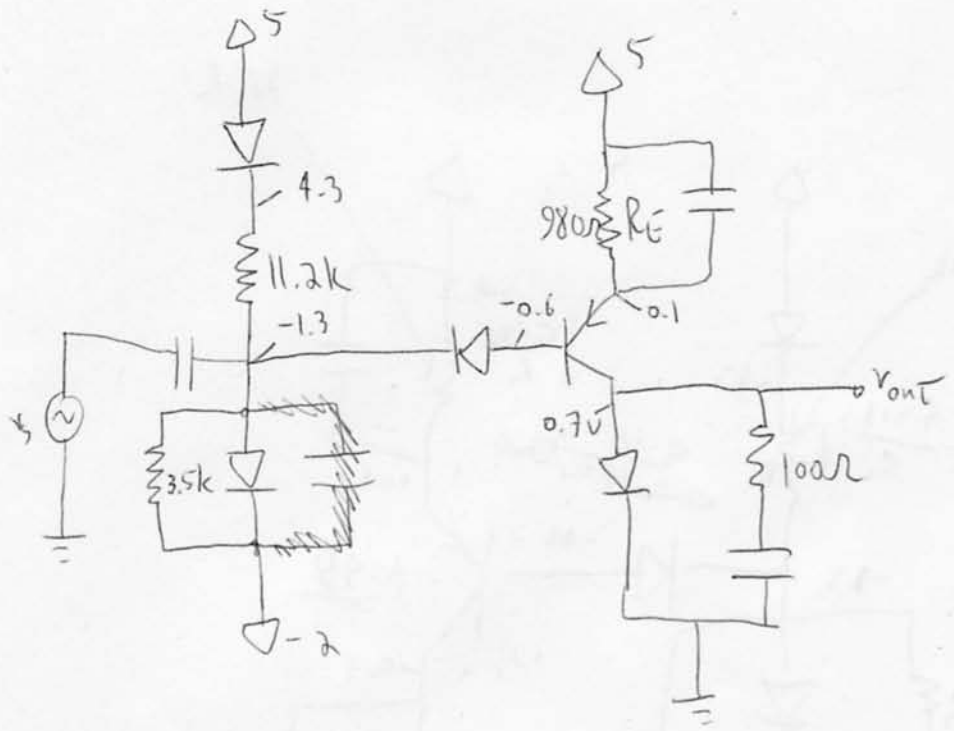

-assume all ON

$$I_E = \frac{5 - 0.1}{980} = 5 \mu A \rightarrow I_{D4} = \alpha I_E = 4.9 \mu A$$


$$I_{D3} = \frac{I_E}{\beta + 1} = 0.1 \mu A$$

$$I_{D1} = I_{11.2k} = \frac{4.3 - (-1.3)}{11.2k} = 0.5 \mu A \quad \text{and} \quad I_{3.5k} = \frac{0.7}{3.5k} = 0.2 \mu A$$

$$\therefore I_{D2} = I_{D3} + I_{D1} - I_{3.5k} = 0.4 \mu A$$

b) require $\frac{0.7}{R_2} \leq 0.6 \mu A$ so $R_2 \geq 1.167 k$

c)

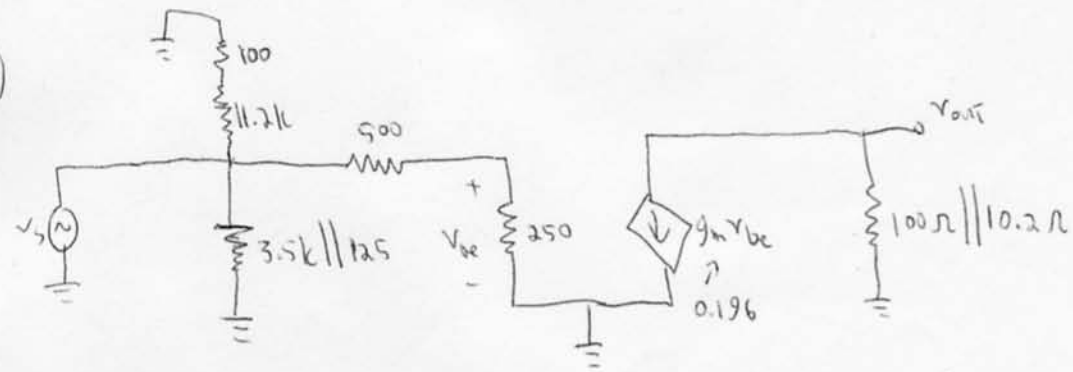

d) $\frac{V_{out}}{V_s} = \left(\frac{250}{750}\right) (-0.196 \times 9.256) = -0.605 V/V$

e) decrease \rightarrow load in parallel with resistances!

Question 3

a) Assume saturation for all transistors

$$\textcircled{1} I_{M1} = I_{M2} = \frac{1}{2} K_p' \frac{W}{L} (V_{GS} - V_{t1})^2$$

$$1 \text{ mA} = \frac{1}{2} \cdot \frac{250 \mu\text{A}}{\text{V}^2} \cdot 12.5 (V_{GS} + 0.7)^2$$

$$\Rightarrow V_{GS} = -1.5 \text{ V}$$

$$V_1 = V_{CM} - V_{GS} = 3 + 1.5 = \boxed{4.5 \text{ V}}$$

$$\textcircled{2} I_{M3} = \frac{1}{2} K_n' \frac{W}{L} (V_{GS} - V_{t1})^2$$

$$1 \text{ mA} = \frac{1}{2} \cdot 500 \frac{\mu\text{A}}{\text{V}^2} \cdot 4 (V_{GS} - 0.7)^2$$

$$\Rightarrow V_{GS} = 1.7 \text{ V}$$

$$V_2 = \boxed{1.7 \text{ V}}$$

$$\textcircled{3} V_{DS1} = V_{DS2} = -2.8 \text{ V} < V_{GS1} - V_{t1} < -1.5 \text{ V} - 0.7 \text{ V} < -2.2 \text{ V} \text{ OK!}$$

$$V_{DS3} = V_{DS4} = V_{GS3} = 1.7 \text{ V} > V_{GS3} - V_{t1} > 1.7 \text{ V} - 0.7 \text{ V} > 1 \text{ V} \text{ OK!}$$

All transistors in saturation!

b) For M2

$$\text{Boundary at } V_{DS2} = V_{GS2} - V_{t2}$$

$$V_3 - V_1 = -0.8 \text{ V}$$

$$\Rightarrow V_3 = 3.7 \text{ V}$$

$$\infty \quad 1 \text{ V} \leq V_3 \leq 3.7 \text{ V}$$

For M4


$$\text{Boundary at } V_{DS4} = V_{GS4} - V_{t4}$$

$$V_3 - 0 = 1 \text{ V}$$

$$\Rightarrow V_3 = 1 \text{ V}$$

For saturation.

c)

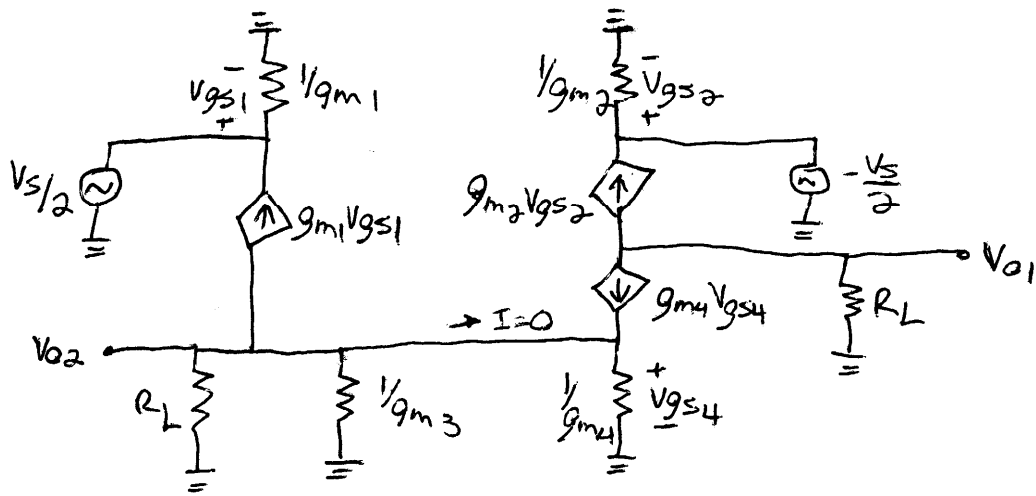

$$d) \quad g_{m1} = \sqrt{2k'_p} \sqrt{\frac{W}{L}} \sqrt{I_{D1}} \quad g_{m2} = g_{m1}$$

$$= \sqrt{2 \cdot \frac{250 \mu A}{V_0}} \sqrt{12.5} \sqrt{1 \text{ mA}}$$

$$= 2.5 \times 10^{-3} \frac{\text{A}}{\text{V}}$$

$$g_{m3} = \sqrt{2k'_n} \sqrt{\frac{W}{L}} \sqrt{I_{D3}} \quad g_{m4} = g_{m3}$$

$$= \sqrt{2 \cdot \frac{500 \mu A}{V_0}} \sqrt{4} \sqrt{1 \text{ mA}}$$

$$= 2 \times 10^{-3} \frac{\text{A}}{\text{V}}$$

$$e) \quad V_{gs1} = \frac{V_s}{2}$$

$$V_{o2} = -g_{m1} V_{gs4} (R_L \parallel 1/g_{m3})$$

$$\frac{V_{o2}}{V_s} = -\frac{g_{m1}}{2} \left(\frac{R_L}{1+g_{m3}R_L} \right) = \frac{-g_{m1}R_L}{2(1+g_{m3}R_L)} = \frac{-6.25}{11} = -0.57 \frac{\text{V}}{\text{V}}$$



$$f) \quad V_{gs2} = -\frac{V_s}{2} \quad V_{gs4} = V_{o2}$$

$$V_{o1} = -(g_{m2}V_{gs2} + g_{m4}V_{gs4}) \cdot R_L$$

$$= \left(\frac{g_{m2}}{2} + \frac{g_{m1}g_{m4}R_L}{2(1+g_{m3}R_L)} \right) \cdot R_L = (1.25 \times 10^{-3} + 1.136 \times 10^{-3}) \cdot 5000 = 11.93 \frac{\text{V}}{\text{V}}$$

Q4

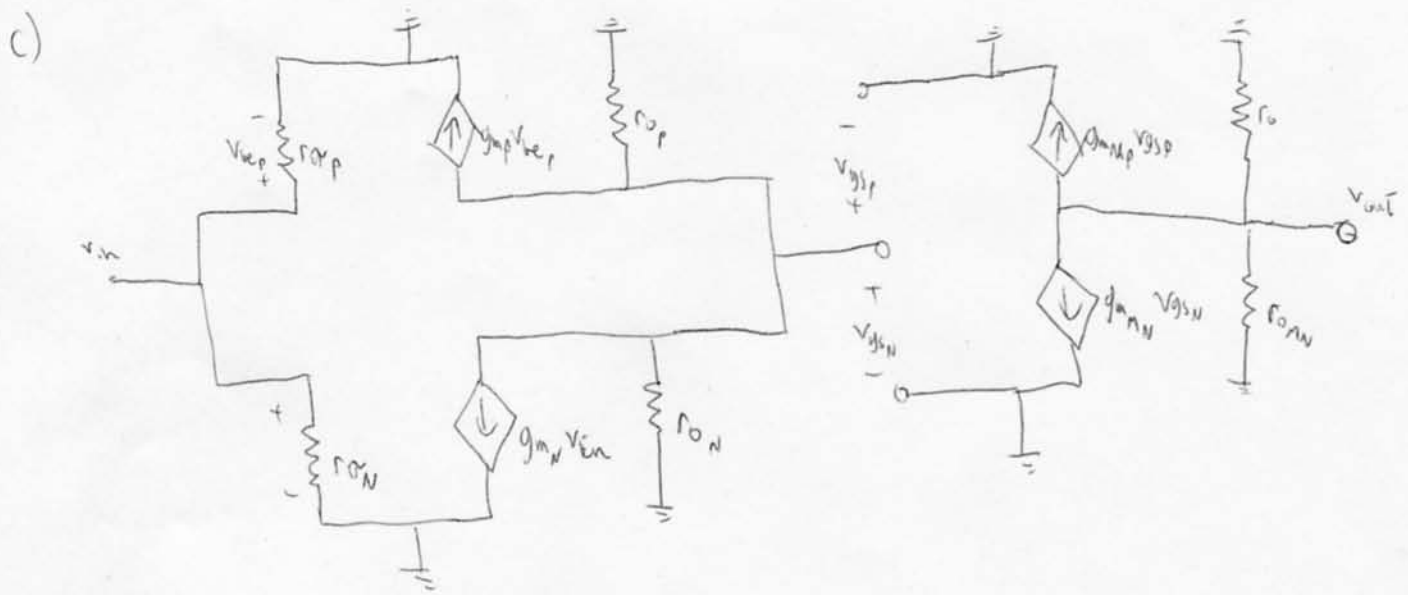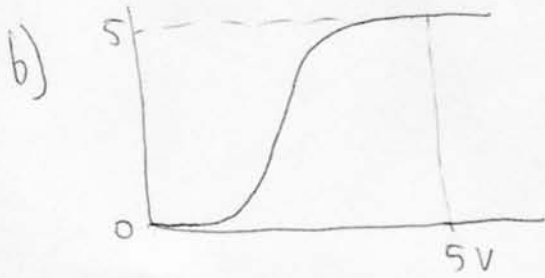- a) Q_p - sat M_p - cut-off
 Q_n - cut-off M_n - Triode



d) $v_{DSN} = v_{DSP} = -g_{mN} r_{oN} v_{in}$ and $v_{out} = -g_{mM} v_{DSN} r_{oM}$

$$\frac{v_{out}}{v_{in}} = g_{mN} \cdot g_{mM} \cdot r_{oN} \cdot r_{oM}$$


e) $g_{mN} \cdot r_{oN} = \frac{V_A}{V_T}$; independent of biasing!

$g_{mM} \cdot r_{oM} = \frac{1}{\lambda(V_{DS} - V_T)}$ depends on the DC biasing...

#5

a) CGA CDA CSA

b)

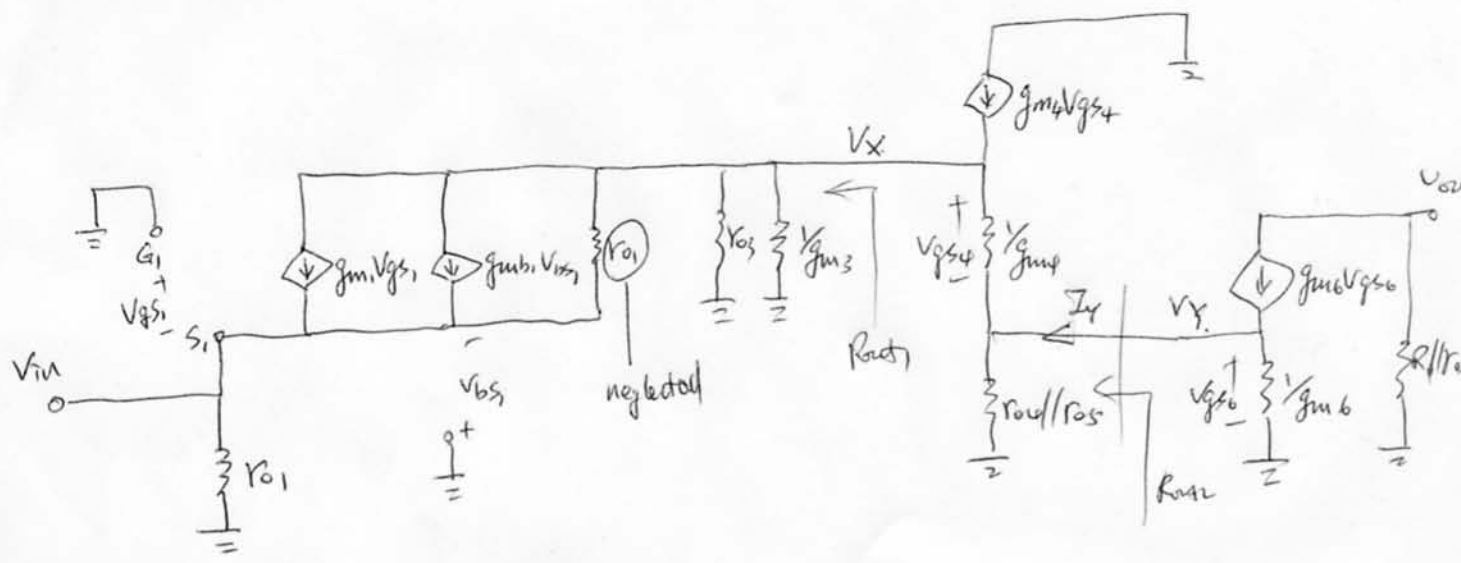

c)
$$\frac{V_x}{V_{in}} = \frac{-(g_{m1} V_{gs1} + g_{m2} V_{bs1}) (R_{02} // \frac{1}{g_{m3}})}{V_{in}}$$

& $V_{gs1} = -V_{in} \quad V_{bs1} = -V_{in} \quad \therefore \frac{V_x}{V_{in}} = + (g_{m1} + g_{m2}) (R_{02} // \frac{1}{g_{m3}})$

a)
$$\frac{V_y}{V_x} = \frac{g_{m4} V_{gs4} \times (R_{out1} // R_{05})}{V_x} = \frac{g_{m4} (V_x - V_y) (R_{out1} // R_{05})}{V_x}$$

$$\Rightarrow \frac{V_y}{V_x} = \frac{g_{m4} R_{out1} // R_{05}}{1 + g_{m4} R_{out1} // R_{05}}$$

e)
$$\frac{V_{out}}{V_y} = g_{m6} R_{in} // R_{06}$$

f)
$$R_{out1} = R_{03} // \frac{1}{g_{m3}}$$

g)
$$R_{out2} = \frac{V_y}{I_y} = \frac{(I_y + g_{m6} V_{gs6}) \cdot (R_{out1} // R_{05})}{I_y} = \frac{(I_y - g_{m6} V_y) (R_{out1} // R_{05})}{I_y}$$

$$= (1 - g_{m6} \frac{V_y}{I_y}) (R_{out1} // R_{05})$$

$$R_{in} = \frac{V_y}{I_y} = \frac{(R_{out1} // R_{05})}{1 + g_{m6} R_{out1} // R_{05}}$$

Question 6

a) Edge of Triode/saturation

$$V_{DS} = V_{GS} - V_t = -1.3 + 0.6 = -0.7$$

$$\Rightarrow V_{D1} = 2.6 \text{ V}$$

$$I_D = \frac{1}{2} K_p' \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$$

$$1 \text{ mA} = \frac{1}{2} \cdot 0.47285 \cdot K_p' \frac{W}{L} \quad K_p' = 500 \frac{\mu\text{A}}{\text{V}^2}$$

$$\frac{W}{L} = \boxed{8.46}$$

b) saturation

$$c) \textcircled{1} I_{M2} = \frac{1}{2} K_n' \frac{W}{L} (V_{GS} - V_t)^2$$

$$1 \text{ mA} = \frac{1}{2} \cdot \frac{1 \text{ mA}}{V_{D1}} \cdot 1 (V_{GS} - V_t)^2$$

$$= V_{GS_{M2}} = 2.01 \text{ V}$$

$$V_{DS} = 2.6 - 0.99 = 1.61 \geq V_{GS} - V_t$$

$$\geq 2.01 - 0.6$$

$$\geq 1.41$$

OK!

$$\textcircled{2} V_{S2} = V_{GS} - V_{GS_{M2}} = 3 - 2.01 = 0.99 \text{ V}$$

$$\textcircled{3} V_{EQ2} = V_{S2} - 0.7 \text{ V} = 0.29 \text{ V}$$

$$\textcircled{4} I_{EQ2} = \frac{0.29 \text{ V}}{\frac{200}{500} \Omega} = 1.45 \text{ mA} = I_{CQ1} \quad (\beta = 100)$$


$$\textcircled{5} V_{\text{max-sym}} = \frac{3.3 + 2.1}{2} = 2.7 \text{ V}$$

$$\textcircled{6} R_3 = \frac{2.7 \text{ V}}{1.45 \text{ mA}} \Rightarrow V_{CC} - R_3 I_{C1} = 2.7$$

$$\Rightarrow R_3 = \frac{0.6}{1.45 \text{ mA}} = 413.8 \Omega$$

d)
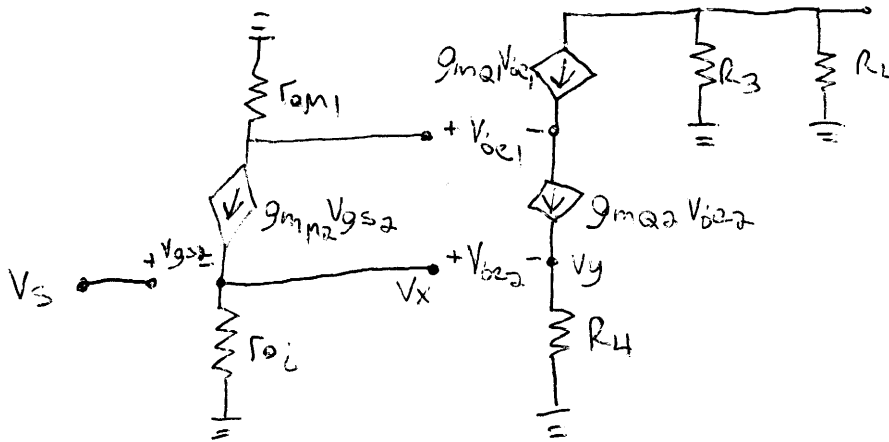
$$\beta = \infty \Rightarrow r_{\pi} = \infty$$



e)

$$① V_{out} = -g_{m1} V_{be1} (R_3 // R_L)$$

$$② g_{m1} V_{be1} = g_{m2} V_{be2} \Rightarrow V_{be1} = \frac{g_{m2} V_{be2}}{g_{m1}}$$

$$③ V_{be2} = V_x - V_y$$

$$④ V_y = g_{m2} (V_x - V_y) R_4 \Rightarrow V_y = \frac{g_{m2} R_4}{1 + g_{m2} R_4} V_x$$

$$⑤ V_{gs2} = V_s - V_x$$

$$⑥ V_x = g_{m2} (V_s - V_x) r_{o2} \Rightarrow V_x = \frac{g_{m2} r_{o2}}{1 + g_{m2} r_{o2}} V_s$$

$$⑦ V_{be2} = \frac{g_{m2} r_{o2}}{1 + g_{m2} r_{o2}} \left[\frac{1 - g_{m2} R_4}{1 + g_{m2} R_4} \right] V_s$$

$$⑧ \frac{V_{out}}{V_s} = -g_{m1} (R_3 // R_L) \frac{g_{m2}}{g_{m1}} \left(\frac{g_{m2} r_{o2}}{1 + g_{m2} r_{o2}} \right) \left(\frac{1 - g_{m2} R_4}{1 + g_{m2} R_4} \right)$$

$$= -g_{m2} (R_3 // R_L) \left(\frac{g_{m2} r_{o2}}{1 + g_{m2} r_{o2}} \right) \left(\frac{1 - g_{m2} R_4}{1 + g_{m2} R_4} \right)$$