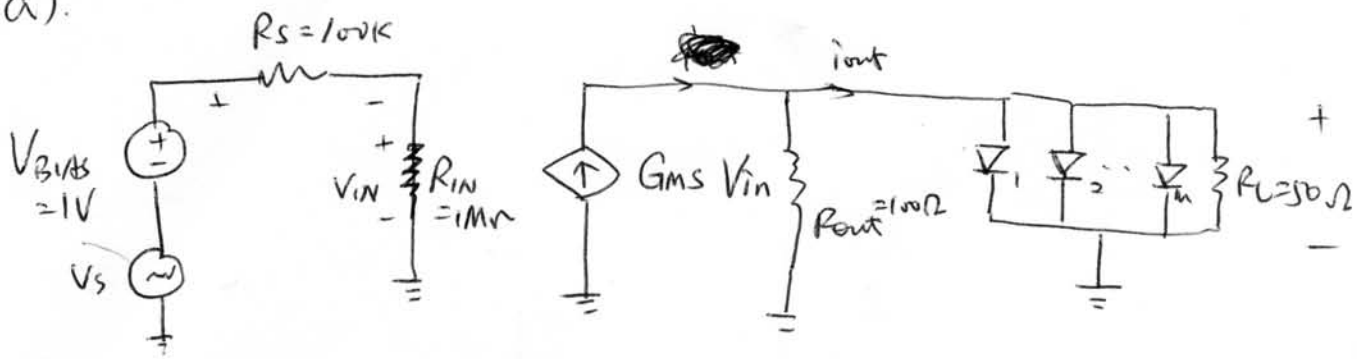


Solutions 2003

Q 1.

a).



For all the diodes to be conduct, assuming CVDM.

$$V_{out} = 0.7V.$$

$$V_{IN} = \frac{R_{IN}}{R_s + R_{IN}} \cdot V_{BIAS} = 0.91V.$$

Assuming on the conducting boundary. $I_{DM} = 0$.

So:

$$G_{MS} V_{IN} = \frac{0.7}{R_{out}} + \frac{0.7}{R_L}$$

$$G_{MS} \times 0.91 = \frac{0.7}{100} + \frac{0.7}{50} \Rightarrow G_{MS} = 23.1 \text{ mA/V.}$$


b). $G_{MS} = 50 \text{ mA/V.}$ assuming CVDM.

$$G_{MS} \times V_{IN} = \frac{0.7}{100} + \frac{0.7}{50} + I_D \times M.$$

$$50 \times 10^{-3} \times 0.91 = 0.7 \times \frac{3}{100} + I_D \times M$$

$$I_D = \frac{0.0245}{M} = \frac{24.5 \text{ mA}}{M}$$

c).

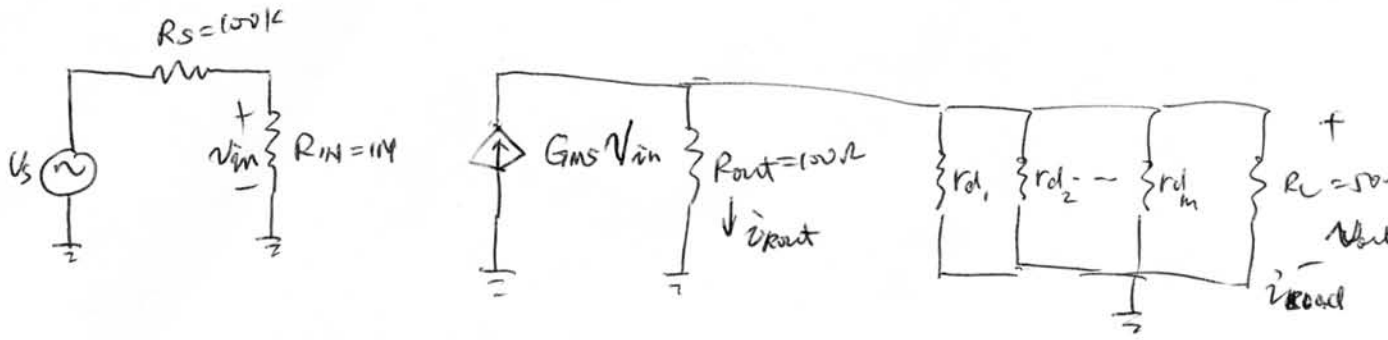

$$r_{d1} = \frac{n \cdot V_T}{I_D}$$

$$I_D = \frac{24.5 \mu\text{A}}{M}$$

$$r_{d1} = \frac{2 \times 25 \text{ mV}}{24.5 \mu\text{A}} \cdot M = 2.04 \text{ M}$$

d). $V_{in} = \frac{R_{in}}{R_{in} + R_s} \cdot V_s = 0.91 |V_s| \sin(\omega t)$.

$$G_m V_{in} = 50 \times 10^{-3} \times 0.91 |V_s| \sin(\omega t) = 0.0455 |V_s| \sin(\omega t)$$

Small signal output = $45.5 |V_s| \sin(\omega t) \text{ mA}$.

$$V_{out} = R_L \times 100 \sin(\omega t) \mu\text{A} = 5 \sin(\omega t) \text{ mV}$$

$$i_{Roact} = \frac{V_{out}}{R_{out}} = \frac{5 \sin(\omega t)}{100} = 50 \sin(\omega t) \mu\text{A}$$

$$i_{load} = 100 \sin(\omega t) \mu\text{A}$$

$$M i_d = G_m V_{in} - i_{Roact} - i_{load}$$

$$i_d = \frac{45.5 \times 10^3 |V_s| \sin(\omega t) - 150 \sin(\omega t)}{M}$$


$$i_d = \frac{V_{out}}{r_{d1}} = \frac{5 \sin(\omega t) \times 10^3}{2.04 \text{ M}} = \frac{2451}{M} \sin(\omega t) \mu\text{A}$$

$$45.5 \times 10^3 |V_s| - 150 = 2451$$

$$|V_s| = 0.057 \text{ V} = 57 \text{ mV}$$

P2

Q2.

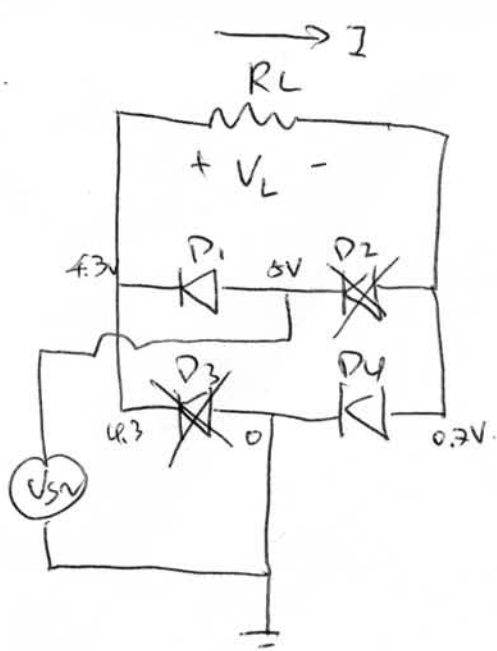


CUDM $n=1$.

a). D_1, D_4 is ON
 D_2, D_3 off. $V_s = 5V$.

$$I = \frac{4.3 - 0.7}{R_L} = \frac{3.6}{R_L} \quad V_{D_2} = -4.3V \quad V_{D_3} = -4.3V$$

D_2, D_3 are reversly biased.

$$V_L = IR_L = 3.6V$$

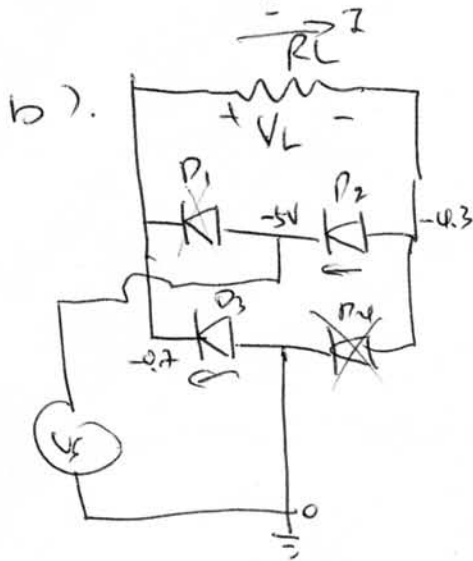


$V_s = -5V$

D_2, D_3 ON
 D_1, D_4 off

$$I = \frac{-4.3 + 0.7}{R_L}$$

$V_{D_1} = -4.3V$
 $V_{D_4} = -4.3V$ > Reversely biased.

$$V_L = 3.6V$$

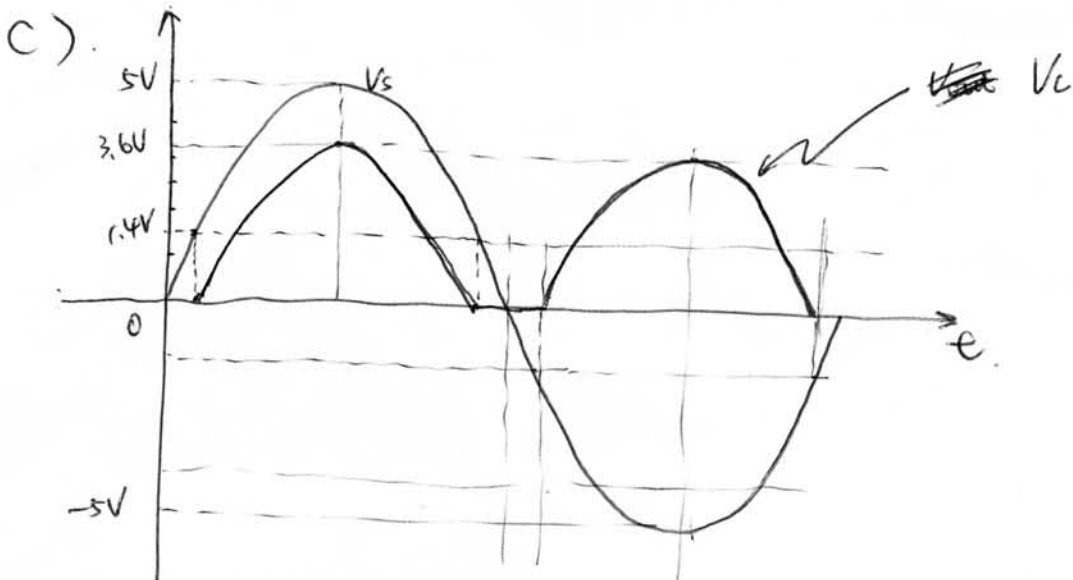

P3


Q2. d). The swing is from -10mV to 10mV . No diodes can be on. $V_L = 0$ always.

e). $V_s = 5\text{V} + 10\sin(\omega t)\text{mV}$.

The DC BIAS is 5V .

So. D_2, D_3 off. D_1, D_4 ON.

DC current CVDN

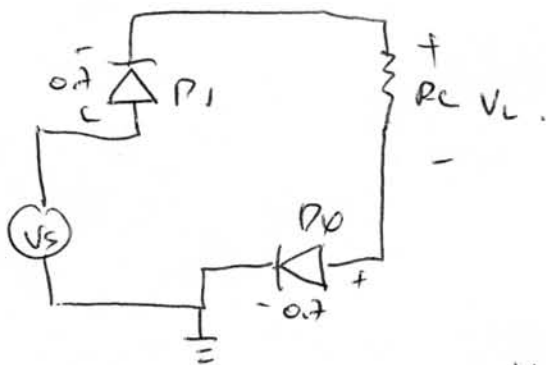

$$I_D = \frac{5 - 1.4}{R_L} = \frac{3.6}{R_L} \quad V_L = 3.6\text{V}$$

$$r_d = \frac{nVT}{I_D} = \frac{1 \times 25\text{mV}}{3.6} \times R_L = 7 \times 10^{-3} R_L$$

$$V_L = \frac{R_L}{R_L + 2r_d} \times V_s$$



$$V_L = 3.6\text{V} + \frac{R_L}{R_L + 2r_d} \times 10\sin(\omega t)\text{mV}$$

$$= 3.6\text{V} + \frac{1}{1 + 1.4 \times 10^{-2}} \times 10\sin(\omega t)\text{mV}$$

$$= 3.6\text{V} + 9.862\sin(\omega t)\text{mV}$$


P4

Final 2003 Fall, Solutions Q3, Q7.

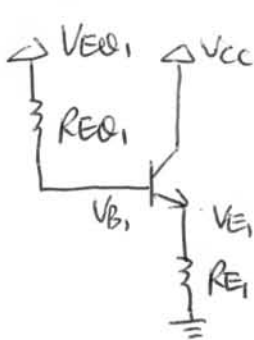Q3

$$a) V_{EQ1} = \frac{R_{B2}}{R_{B2} + R_{B1}} \times V_{CC} = \frac{40K}{40K + 120K} \times 12 = 3V$$

$$R_{EQ1} = R_{B1} \parallel R_{B2} = 120K \parallel 40K = 30K \Omega$$



$$\begin{cases} I_{B1} = \frac{V_{EQ1} - V_{B1}}{R_{EQ1}} \\ I_{E1} = \frac{V_{E1}}{R_{E1}} \\ I_{E1} = (\beta + 1) I_{B1} \\ V_{B1} = V_{E1} + 0.7 \end{cases} \Rightarrow \frac{V_{E1}}{R_{E1}} = (\beta + 1) \frac{V_{EQ1} - V_{E1} - 0.7}{R_{EQ1}} \quad (*)$$

$$\frac{V_{E1}}{3K} = 50 \times \frac{3 - 0.7 - V_{E1}}{30K}$$


$$\boxed{V_{E1} = 1.92V}$$

$$\boxed{I_{C1} = \frac{\beta}{\beta + 1} I_{E1} = \frac{49}{50} \times \frac{1.92V}{3K\Omega} = 0.627mA}$$

For Q2.

$$V_{EQ2} = \frac{R_{B4}}{R_{B3} + R_{B4}} \times V_{CC} = \frac{20K}{120K + 20K} \times 12 = 1.714V$$
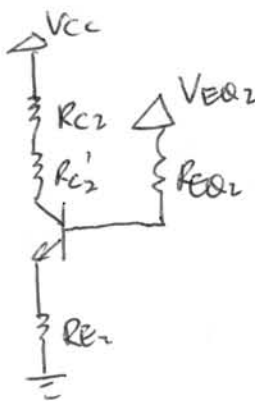
$$R_{EQ2} = R_{B3} \parallel R_{B4} = 17.14K \Omega$$



Use (*)

$$\frac{V_{E2}}{1K} = 50 \times \frac{1.714 - V_{E2} - 0.7}{17.14K}$$

$$\boxed{V_{E2} = 0.755V}$$


$$\boxed{I_{C2} = \frac{\beta}{\beta + 1} I_{E2} = \frac{49}{50} \times \frac{0.755}{1K} = 0.74mA}$$

No other solutions, must be the same as the value specified here.

Q3

b)

Without R_{c2} , take (-0.25)

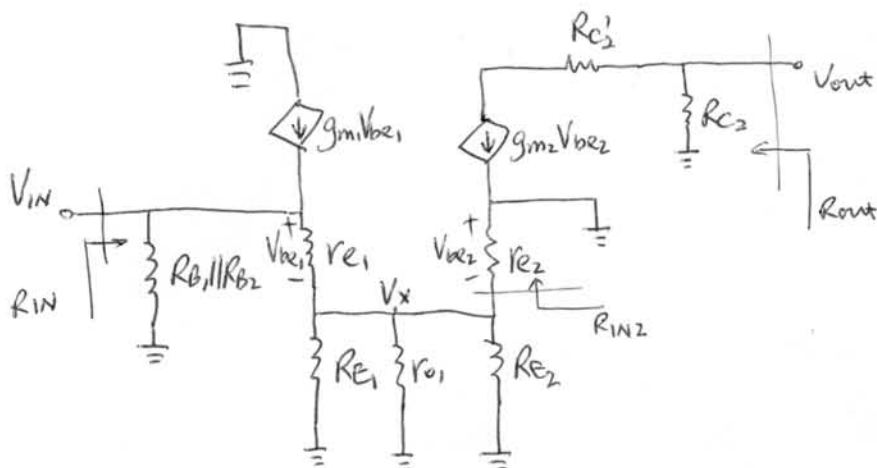

c)

$$R_{IN} = R_{B1} \parallel R_{B2} \parallel (\beta+1) [r_{e1} + R_{E1} \parallel r_{o1} \parallel R_{E2} \parallel r_{e2}]$$

d) $R_{IN2} = r_{e2}$

e) $R_{out} = R_{C2}$

f) $V_{out} = -g_{m2} V_{be2} (R_{C2} \parallel R_L)$

$V_{be2} = -V_x$

$$V_x = V_{in} \cdot \frac{R_{E2} \parallel R_{E1} \parallel r_{e2}}{r_{e1} + R_{E1} \parallel R_{E2} \parallel r_{e2}}$$

$g_m = \frac{I_c}{V_T} = 0.032 \text{ A/V}$

$r_e = \frac{\alpha}{g_m} = 30.625 \Omega$

neglect Early effect.

$$\frac{V_{out}}{V_{in}} = \frac{g_{m2} (R_{C2} \parallel R_L) \cdot R_{E2} \parallel R_{E1} \parallel r_{e2}}{r_{e1} + R_{E1} \parallel R_{E2} \parallel r_{e2}}$$


if R_L is not connected. open circuit gain is

$$A_v = \frac{0.032 \times 10K \times 3K \parallel 1K \parallel 30.625}{30.625 + 3K \parallel 1K \parallel 30.625} = 156.8 \text{ V/V}$$

Q4

	Body Eff.	CLM
M1	N	Y
M2	Y	N
M3	N	Y

a)

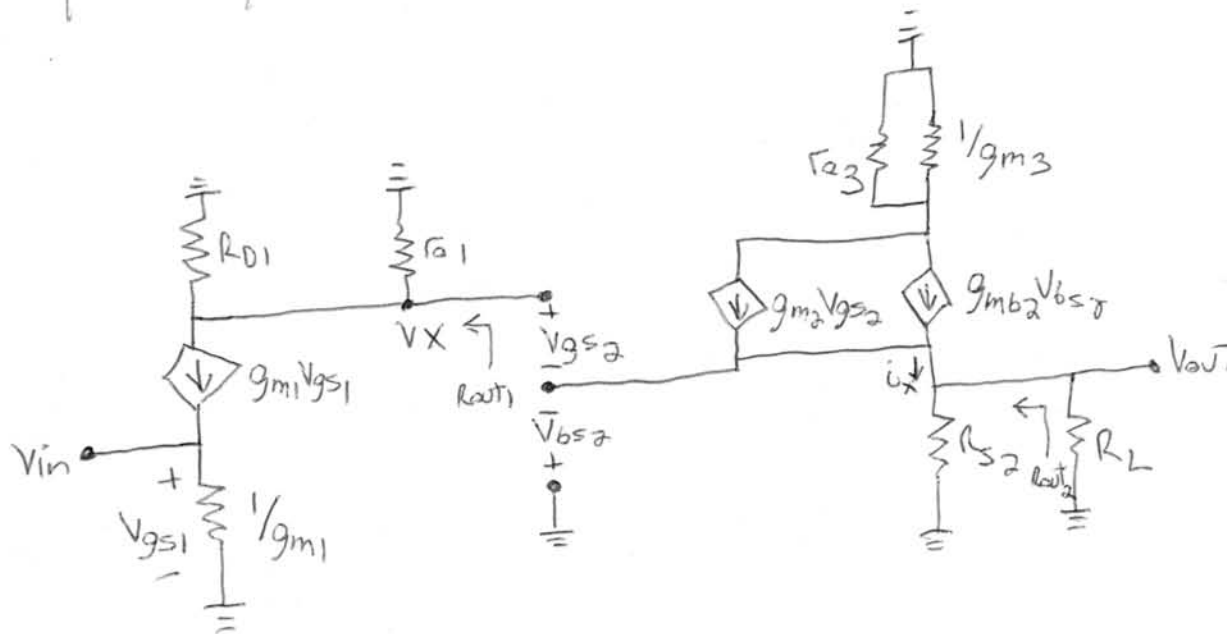

b)

$$\frac{V_x}{V_{in}} = -g_m (r_{o1} \parallel R_{D1})$$

c)

$$V_x = V_{gs2} + V_{out} ; V_{gs2} = V_x - V_{out}$$

$$V_{bs2} = -V_{out}$$

$$\textcircled{1} i_x = g_{m2} V_{gs2} - g_{mb2} V_{out} \Rightarrow \textcircled{2} i_x = \frac{V_{out}}{R_{S2} \parallel R_L}$$

$$\Rightarrow \frac{V_{out}}{R_{S2} \parallel R_L} = g_{m2} V_{gs2} - g_{mb2} V_{out}$$


$$\Rightarrow \frac{V_{out}}{R_{S2} \parallel R_L} + g_{mb2} V_{out} = g_{m2} (V_x - V_{out})$$

$$\Rightarrow \frac{V_{out}}{R_{S2} \parallel R_L} + g_{mb2} V_{out} + g_{m2} V_{out} = g_{m2} V_x \Rightarrow \frac{V_{out}}{V_x} = \frac{g_{m2}}{\frac{1}{R_{S2} \parallel R_L} + g_{m2} + g_{mb2}}$$

$$d) \frac{V_{out}}{V_{in}} = \frac{V_x}{V_{in}} \cdot \frac{V_{out}}{V_x} = \left[-g_{m1} (r_{o1} \parallel R_{D1}) \right] \left[\frac{g_{m2}}{\frac{1}{R_{S2} \parallel R_L} + g_{m2} + g_{mb2}} \right]$$

$$e) R_{out1} = r_{o1} \parallel R_{D1}$$

f)

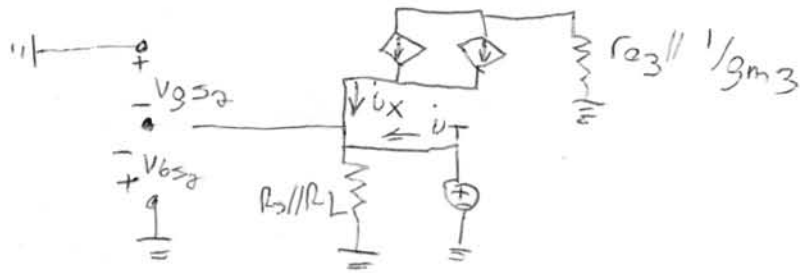

$$\frac{V_{out}}{R_S \parallel R_L} = i_T + i_x \quad ; \quad V_x = 0V \quad V_{gs} = -V_{out}$$

$$= i_T + g_{m2} V_{gs2} + g_{mb2} V_{bs2}$$

$$= i_T + g_{m2} V_{gs2} - g_{mb2} V_{out}$$

$$\frac{V_{out}}{R_S \parallel R_L} + g_{mb2} V_{out} = i_T - g_{m2} V_{out} \Rightarrow i_T = \frac{V_{out}}{R_S \parallel R_L} + g_{mb2} V_{out} + g_{m2} V_{out}$$

$$\Rightarrow R_{out} = \frac{V_{out}}{i_T} = \boxed{\frac{1}{\frac{1}{R_S \parallel R_L} + g_{m2} + g_{mb2}}}$$

Q#5

a) BOUNDARY: $V_{BE} = 0.7$; $V_B = V_C$
(3PTS)

$$V_{B_1} = V_{B_2} = 1.8V$$

$$V_{C_1} = V_{C_2} = 1.8V$$


$$I_{C_1} = I_{C_2} = \frac{V_{CC} - V_{C_1}}{R_{C_1}} = \frac{3.3 - 1.8}{R_{C_1}} = \frac{1.5}{R_{C_1}}$$

SINCE $V_{in} = 0$ $V_{E_1} = V_{E_2} \rightarrow$ NO DC CURRENT THROUGH R_E

$$I_{E_1} = I_{E_2} = 1mA$$

$$I_{C_1} = \alpha I_{E_1} = \frac{99}{100} \times 1mA = 0.99mA$$
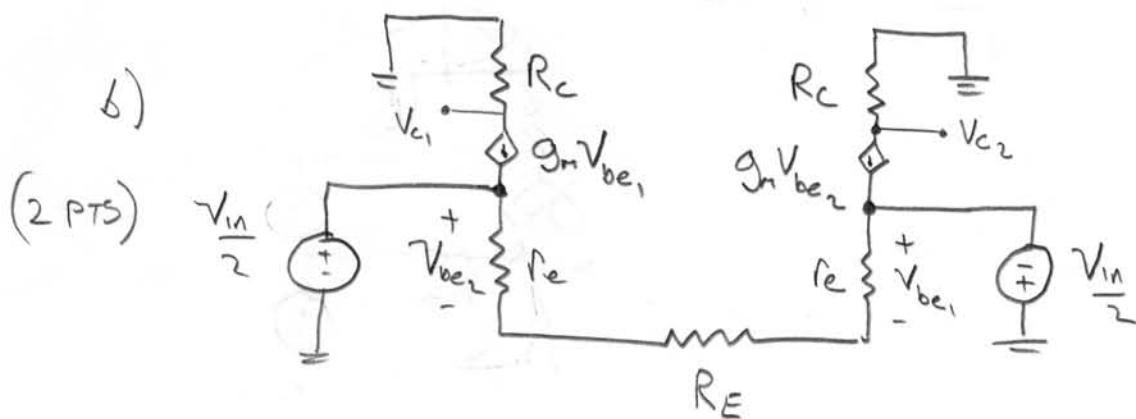
$$R_{C_1} = R_{C_2} = \frac{1.5V}{0.99} = 1.515K\Omega$$



c) (2PTS)


$$V_{C_1} - V_{C_2} = -g_m R_C (V_{be_1} - V_{be_2})$$

KVL: $\frac{V_{in}}{2} - V_{be_1} - V_{RE} + V_{be_2} + \frac{V_{in}}{2} = 0$

$$V_{in} - V_{RE} = V_{be_1} - V_{be_2}$$

VOLATAGE DIVIDER
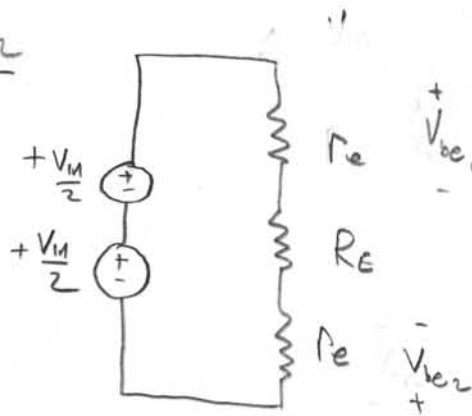
$$V_{RE} = V_{IN} \left(\frac{R_E}{2r_e + R_E} \right)$$



$$V_{be1} - V_{be2} = V_{IN} - V_{RE}$$

$$= V_{IN} \left(1 - \frac{R_E}{2r_e + R_E} \right) = V_{IN} \left[\frac{2r_e}{2r_e + R_E} \right]$$

$$\frac{V_{c1} - V_{c2}}{V_{IN}} = -g_m R_c \left(\frac{2r_e}{2r_e + R_E} \right)$$

$$= \frac{-g_m R_c 2r_e}{2r_e + (\beta + 1) R_E}$$

d) $R_{in} \equiv \frac{V_{IN}}{i_b} = \frac{V_{IN}}{-g_m V_{be} + i_e} = \frac{V_{IN}}{i_e (1 - g_m r_e)}$

(3PTS)

$$i_e = \frac{V_{RE}}{R_E} = \frac{1}{R_E} \left[V_{IN} \left(\frac{R_E}{2r_e + R_E} \right) \right] = \frac{V_{IN}}{2r_e + R_E}$$

$$R_{in} = \frac{\left(\frac{V_{IN}}{1 - g_m r_e} \right)}{\frac{V_{IN}}{2r_e + R_E}} = \frac{2r_e + R_E}{1 - g_m r_e} = (\beta + 1)(2r_e + R_E)$$

$$R_{in} = (\beta + 1)(2r_e + R_E)$$

$$R_{in} = 2r_e + (\beta + 1) R_E$$

Q6

$$a) I_{M1} = \frac{1}{2} K_n' \frac{3W}{L} (V_{S1} - V_t)^2 = 3I_{M2}$$

$$I_{C1} = I_{M1} = 3I_{M2}$$

$$I_{B1} = \frac{I_{C1}}{\beta} = \frac{3I_{M2}}{\beta}$$

$$I_{E1} = \frac{I_{C1}(\beta+1)}{\beta} = \frac{3(\beta+1)}{\beta} I_{M2}$$

$$I_{M3} = I_{M2}$$

$$\begin{aligned} b) V_{out} &= V_{CC} - R_D(I_{M1} + I_{M2}) \\ &= 10 - 1k\Omega(3I_{M2} + I_{M2}) \\ &= 10 - 4k\Omega \cdot I_{M2} \end{aligned}$$

$$\begin{aligned} c) V_{out} &= 10 - 4k\Omega \cdot 1mA \\ &= 6V \end{aligned}$$


$$I_{M2} = I_{M3} \Rightarrow \frac{1}{2} K_n' \frac{W}{L} (6 - V_{S2} - 1)^2 = \frac{1}{2} K_n' \frac{W}{L} (3.03 - 1)^2 \left(1 + \frac{1}{4} V_{S2}\right)$$

$$25 - 10V_{S2} + V_{S2}^2 = 4.122 + 1.0305V_{S2}$$

$$\Rightarrow V_{S2}^2 - 11.03V_{S2} + 20.878 = 0$$

$$\Rightarrow V_{S2} = 2.426V$$

d)

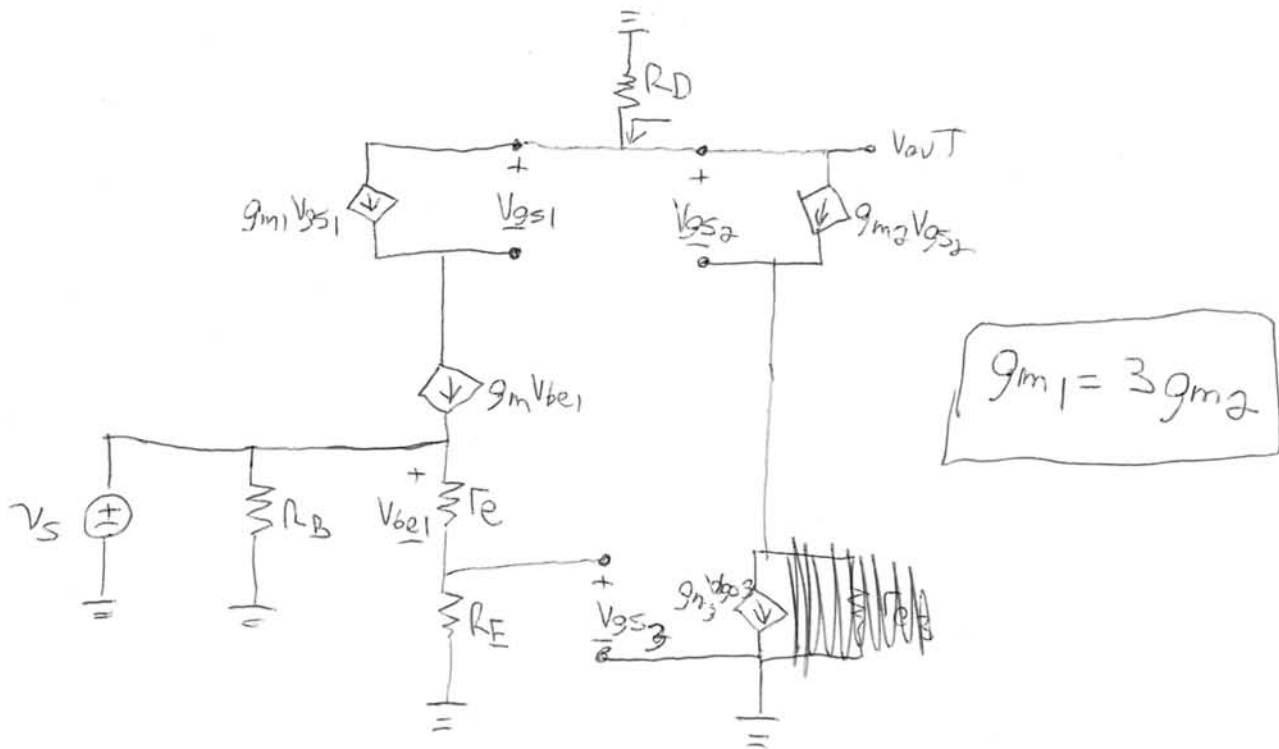


e) $R_{IN} = R_B // (\beta + 1)(r_{e1} + R_E)$

f) $-\frac{V_{out}}{R_D} = g_{m1}V_{be1} + g_{m3}V_{gs3} = g_{m1} + g_{m3}V_{g3}$

$$V_{g3} = V_S \left(\frac{R_E}{r_{e1} + R_E} \right)$$

$$V_{be1} = V_S \left(\frac{r_{e1}}{r_{e1} + R_E} \right)$$
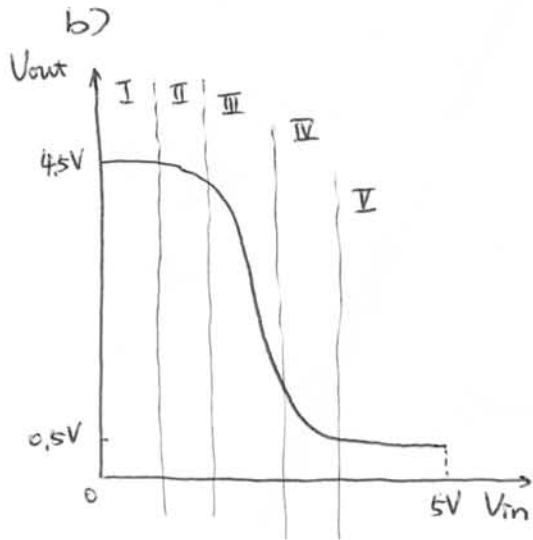
$$\frac{V_{out}}{V_S} = -R_D \left(g_{m1} \frac{r_{e1}}{r_{e1} + R_E} + g_{m3} \cdot \frac{R_E}{R_E + r_{e1}} \right)$$




	I	II	III	IV	V
M_P	T	T	S	S	C
M_N	C	S	S	T	T
M_{PL}	C	C/S	S	S	S
M_{NL}	S	S	S	C/S	C

T: triode

S: Saturation

C: cutoff.

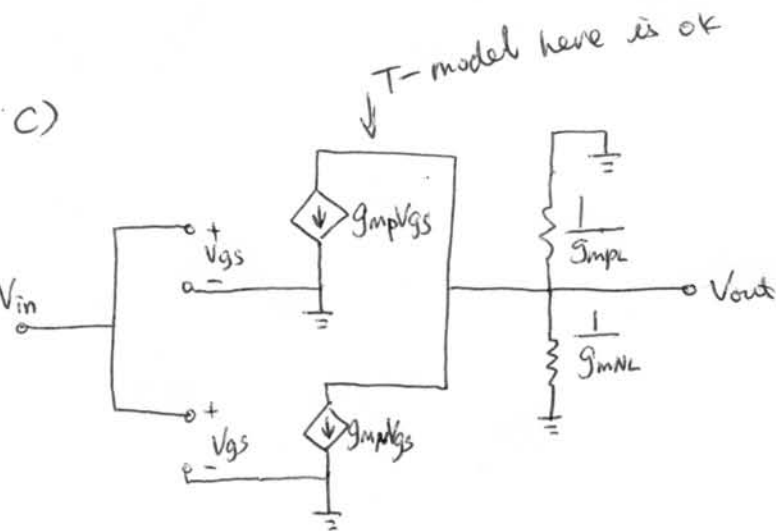

d)

$$V_{out} = -2 g_{mN} V_{gs} \times \left(\frac{1}{g_{mPL}} \parallel \frac{1}{g_{mNL}} \right)$$

$$\frac{V_{out}}{V_{in}} = -2 g_{mN} \times \frac{1}{2g_{mPL}} = -\frac{g_{mN}}{g_{mPL}}$$

$$V_{out} = 2.5V + \left(-10 \times \frac{g_{mN}}{g_{mPL}} \sin \omega t \right) mV \quad \leftarrow$$

DC: $V_{in} = 2.5V$. $g_{mN} = g_{mP} = g_{mPL} = g_{mNL}$.

$$V_{out} = 2.5V + (-10 \sin \omega t)$$

$$= 2.5V - 10 \sin \omega t$$