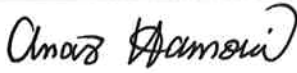



*McGill University -*  
*Faculty of Engineering*  
*Department of Electrical and Computer Engineering*  
**ECSE 334 - Introduction to Microelectronics**  
**Final Examination (April 11, 2006)**  
**3 hours (2:00PM-5:00PM)**

---

**Examiner:** Prof. Anas A. Hamoui   
**Co-Examiner:** Prof. Mourad N. El-Gamal 

**□ INSTRUCTIONS/NOTES:**

- This is a closed-book examination. Only the faculty-approved calculators are permitted.
- The examination includes 3 questions and consists of 9 pages, including this cover page.
- A summary of the BJT and MOSFET characteristics is attached (4 pages).
- Make sure you have total of 13 pages, BEFORE you start solving this examination.
- **All questions have equal weight.**
- State any assumptions you find *necessary* to complete your answers.
- For full credit, you must show the **steps** you followed to answer the questions and you must clearly indicate the **units** in your answers.
- **Answer all questions in the exam books provided. Underline your answers.**
- Write your name on this cover page and on top of each question which you want marked. Place the sheets which you want to be marked inside your exam booklet.
- **Return ALL pages of this of this examination to the Invigilator.**  
 You are NOT allowed to leave this room with any examination paper.

**Student Last Name:** \_\_\_\_\_

**Student First Name:** \_\_\_\_\_

**McGill Student ID:** \_\_\_\_\_

Question #	1	2	3	4	Total
Mark	/25	/25	25	/25	/100

**DEVICE PARAMETERS****□ MOSFET Parameters:**

For a MOSFET in the saturation region and having  $L = 0.5 \mu m$ :

	<b>NMOS Transistor</b>	<b>PMOS Transistor</b>
$ V_{t0} $	$0.6 V$	$0.65 V$
$\lambda$	$0.25 V^{-1}$	$0.40 V^{-1}$
$\mu C_{ox}$	$200 \mu A/V^2$	$50 \mu A/V^2$
$C_{ox}$	$5 fF/\mu m^2$	$5 fF/\mu m^2$
$L_{ov} C_{ox}$	$0.625 fF/\mu m$	$0.625 fF/\mu m$

**□ BJT Parameters:**

	<b>nnp BJT</b>	<b>pnp BJT</b>
$ V_{BEon} $	$0.7 V$	$0.7 V$
$ V_{BCon} $	$0.4 V$	$0.4 V$
$ V_{CEsat} $	$0.3 V$	$0.3 V$
$\beta = h_{fe}$	120	50
$C_{\mu}$	$5 fF$	$15 fF$
$r_x$	$400 \Omega$	$200 \Omega$
$ V_A $	$35 V$	$30 V$
$V_T$	$25 mV$	$25 mV$

**□ Note:**  $1 fF = 10^{-3} pF = 10^{-15} F$

 


Figure 1

**Question 1: Frequency Compensation [25 marks]**

Consider the two-stage opamp shown in Figure 1.

Its open-loop transfer function  $A(s) = V_o(s)/V_i(s)$  has:

- a dc gain of  $A_0 = A_1A_2 = 60$  dB;
- poles at  $f_{p1} = 1$  MHz,  $f_{p2} = 10$  MHz, and  $f_{p3} = 100$  MHz.

The 1<sup>st</sup> pole (at  $f_{p1}$ ) is formed at node 1 and the 2<sup>nd</sup> pole (at  $f_{p2}$ ) is formed at node 2.

The total capacitance at node 1 is  $C_1 = 7$  pF.

The dc gains of the individual stages are  $A_1 = 50$  V/V and  $A_2 = 20$  V/V.

The opamp is to be connected in a negative-feedback loop via a feedback network whose feedback factor  $B$  is frequency independent.

It is required to compensate the opamp, so that it is stable with a phase margin of  $PM = 45^\circ$  for a feedback factor  $B = 1$ .

**Consider the following 3 compensation schemes:**

**a) Compensation Scheme 1:** the opamp is compensated by introducing a new dominant pole.

- Find the frequency  $f_D$  at which the new pole must be placed.

**b) Compensation Scheme 2:** the opamp is compensated by placing an additional capacitance  $C_C$  at node 1 to reduce the frequency of the 1<sup>st</sup> pole.

- Find the frequency  $f_{p1}'$  to which the 1<sup>st</sup> pole must be shifted. Assume that the frequencies of the other poles remain unchanged.
- Find the required size for capacitor  $C_C$ .

**c) Compensation Scheme 3:** the opamp is to be compensated by connecting a compensating capacitor  $C_C$  between nodes 1 and 2.

- Find the frequency  $f_{p1}'$  to which the 1<sup>st</sup> pole must be shifted. Assume that such frequency compensation will also shift the 2<sup>nd</sup> pole (at  $f_{p2}$ ) to a frequency  $f_{p2}' \gg f_{p3}$ .
- Find the required size for capacitor  $C_C$ .

**Specifications**  
 $R_S = 5\text{ k}\Omega$   
 $R_F = 5\text{ k}\Omega$   
 $R_L = 2\text{ k}\Omega$

 


Figure 2 (a)

 


Figure 2 (b)

**Question 2: Feedback Amplifiers [25 marks]**

The series-shunt feedback amplifier in Figure 2(a) is implemented as shown in Figure 2(b).

Assume that:

- the signal source  $v_s$  has a **dc** component of 0 V and the bias voltage level at the output is stabilized by feedback to about 0 V;
- the **dc** base currents of the BJTs are negligible;
- current source  $I_{bias}$  is ideal;
- the incremental output resistances of sources  $I_C$  and  $I_D$  are  $R_c$  and  $R_d$ , respectively.

For simplicity, write your expressions using the variables previously derived, together with the BJT small-signal parameters, the incremental output resistance of the current sources ( $R_c, R_d$ ), and the external resistors ( $R_S, R_F, R_L$ ).

**Refer to the  $\beta$  of the BJT as  $h_{fe}$ . Use subscripts to associate each small-signal parameter with its corresponding transistor number.**

 


Figure 2 (c)

a) Use feedback analysis to write the expression for:

- i) the feedback factor  $B$
- ii) the open-loop gain  $A$
- iii) the closed-loop gain  $A_f \equiv v_o / v_s$
- iv) the input resistance  $R_{in}$
- v) the output resistance  $R_{out}$

of the feedback amplifier in Figure 2(b).

b) Write the expression for

- $R_1$
- $R_2$
- $A_0$

in Figure 2(c), such that the voltage amplifier model in Figure 2(c) is equivalent to the feedback amplifier circuit in Figure 2(b).

 


Figure 3 (a)

**Question 3: High-Frequency Response [25 marks]**

Consider the active-loaded common-emitter (CE) amplifier in Figure 3(a).

In the following, assume that:

- all BJTs are biased in the active region;
- **the signal voltage at the base of transistors Q2 and Q3 is zero.**

Do NOT neglect  $r_x$  in the BJT small-signal models.

For simplicity, write your expressions using the variables previously derived, together with the BJT small-signal parameters. **Use subscripts to associate each small-signal parameter with its corresponding transistor number.**

a) For the CE amplifier in Figure 3(a), write the expression for:

- its midband gain  $A_{Ma} = v_o / v_s$ ;
- its 3-dB frequency  $\omega_{H\omega}$ , assuming a dominant pole is formed at node IN.

 


Figure 3 (b)

 


Figure 3 (c)

- b) To increase the 3-dB frequency of the CE amplifier in Figure 3(a), a common-base transistor  $Q4$  is placed at the collector of  $Q1$ , as shown in Figure 3(b).

For the cascode amplifier in Figure 3(b), write the expression for:

- its midband gain  $A_{Mb} = v_o / v_s$ ;
- the high-frequency pole  $\omega_{INb}$  associated with node IN;
- the high-frequency pole  $\omega_{Xb}$  associated with node X
- the high-frequency pole  $\omega_{OUTb}$  associated with node OUT.

- c) To increase the input resistance of the CE amplifier in Figure 3(a), a resistor  $R_E$  is placed in the emitter of  $Q1$ , as shown in Figure 3(c).

For the CE amplifier in Figure 3(c), write the expression for:

- its midband gain  $A_{Mc} = v_o / v_s$ ;
- its 3-dB frequency  $\omega_{Hc}$ , assuming a dominant pole is formed at node IN.

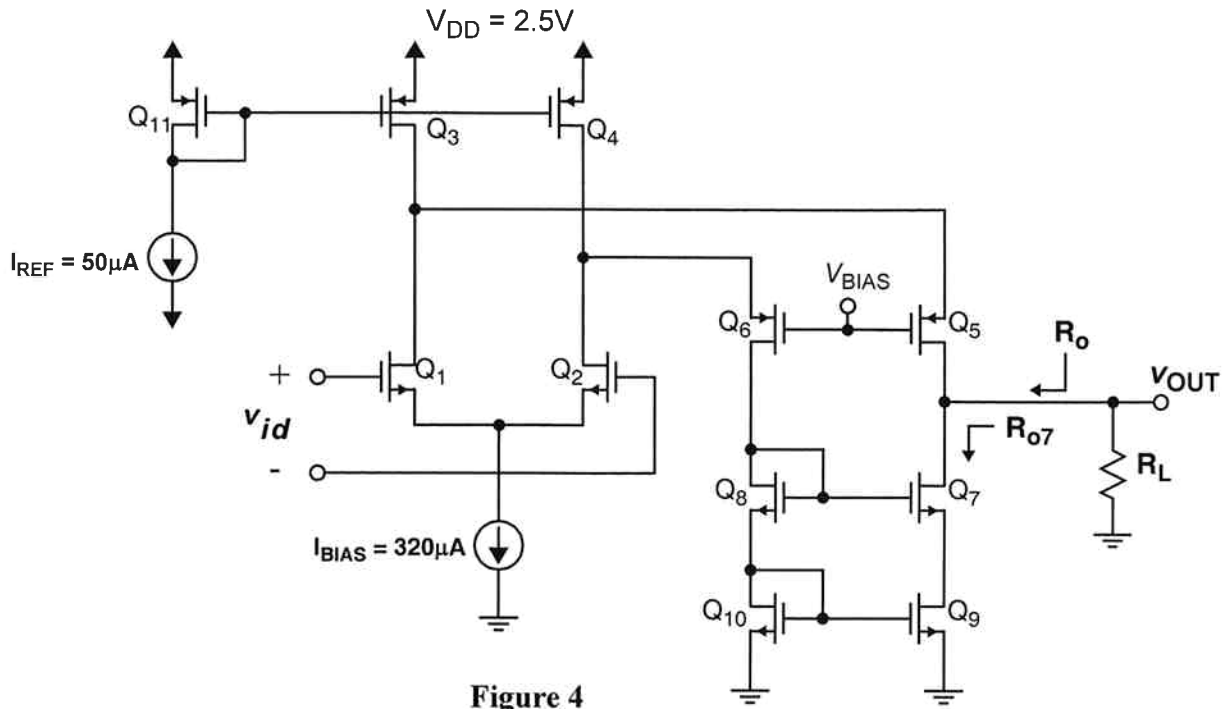


Figure 4

**Question 4: Differential and Cascode Amplifiers [25 marks]**

Figure 4 shows a folded-cascode differential CMOS opamp.

The MOSFET parameters are listed on page 2. Ignore the body effect.

Assume that:

- $\gamma = 0$  and  $\lambda = 0$  in your dc calculations;
- all MOSFETs are biased in the saturation region and operate at  $|V_{OV}| = 0.25\text{ V}$ ;

For simplicity, write your expressions using the variables previously derived, together with the MOSFET small-signal parameters. **Use subscripts to associate each small-signal parameter with its corresponding transistor number.**

- a) Specify the aspect ratio ( $W/L$ ) of transistors  $Q_3$  and  $Q_4$ , such that the ratio of the bias input currents to the cascode currents is:  $I_{D1,2}/I_{D5,6} = 4$ .
- b) Write the expression for the output resistance  $R_o$ .  
Note: The output resistance of the cascode current mirror ( $Q_7$ - $Q_{10}$ ) is  $R_{o7} \cong (g_{m7}r_{o7})r_{o9}$ .
- c) Write the expression for the short-circuit transconductance  $G_m \equiv |i_{out}/v_{id}|_{R_L=0}$  and draw the equivalent transconductance circuit model of the opamp.
- d) Write the expression for the open-circuit differential voltage gain  $A_d \equiv (v_{out}/v_{id})_{R_L=\infty}$ .



- e) Let  $V_{\text{out, min}}$  denote the smallest value of output voltage  $V_{\text{out}}$  for proper operation of the CMOS opamp, with all its transistors in saturation.
- Write the expression for  $V_{\text{out, min}}$ . Find its value.
- f) Let  $V_{\text{out, max}}$  denote the largest value of output voltage  $V_{\text{out}}$  for proper operation of the CMOS opamp, with all its transistors in saturation.
- Write the expression for  $V_{\text{BIAS}}$ , which maximizes  $V_{\text{out, max}}$ . Find its value.
  - Write the expression for the resulting  $V_{\text{out, max}}$ . Find its value.

## SUMMARY OF BJT CHARACTERISTICS

### □ BJT Current-Voltage Relationships in the Active Mode

- For the **npn** BJT:

$$i_C = I_S e^{v_{BE}/V_T} \left( 1 + \frac{v_{CE}}{V_A} \right)$$



$$i_B = \frac{i_C}{\beta} = (1 - \alpha) i_E = \frac{i_E}{\beta + 1}$$

$$i_E = \frac{i_C}{\alpha} = (\beta + 1) i_B$$

$$i_C = \alpha i_E = \beta i_B$$

$$i_E = i_B + i_C$$

  where  $V_T = \frac{kT}{q} \cong 25mV$  at room temperature



- For the **pnp** BJT: reverse the polarity of all terminal voltages

- Relationships between  $\alpha$  and  $\beta$ :

$$\alpha = \frac{\beta}{\beta + 1} \quad \beta = \frac{\alpha}{1 - \alpha} \quad \beta + 1 = \frac{1}{1 - \alpha}$$

### □ Small-Signal Equivalent Circuit Models for the BJT


- Small-Signal Model Parameters in terms of DC Bias Currents:

$$g_m = \frac{I_C}{V_T} \quad r_\pi = \frac{V_T}{I_B} \quad r_e = \frac{V_T}{I_E} \quad r_o = \frac{V_A}{I_C}$$

- Relationships between the Small-Signal Model Parameters of the BJT:

$$g_m = \frac{\alpha}{r_e} = \frac{\beta}{r_\pi} \quad r_\pi = (\beta + 1) r_e \quad \frac{1}{r_e} = g_m + \frac{1}{r_\pi}$$


#### Common-Base Configuration:

 


$$R_{in} \cong r_e \left[ \frac{r_o + R_L}{r_o + R_L / (\beta + 1)} \right]$$

$$R_{out} \cong r_o [1 + g_m (R_E \parallel r_\pi)]$$

 - Simplified Low-Frequency Equivalent-Circuit Models for the Small-Signal Operation of the BJT:




Hybrid- $\pi$  Model

 

T Model

 - High-Frequency Small-Signal Model of the BJT:



## SUMMARY OF MOSFET CHARACTERISTICS

### Current-Voltage Relationships (Square-Law MOSFET Model)

□ **NMOS Transistor**

- Overdrive (Effective) Voltage:  $v_{OV} = v_{GS} - V_t$
- Triode Region:  $[v_{GS} \geq V_t \Leftrightarrow v_{OV} \geq 0]$  and  $[v_{GD} \geq V_t \Leftrightarrow v_{DS} \leq v_{OV}]$

$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [2(v_{GS} - V_t)v_{DS} - v_{DS}^2]$$

For  $v_{DS} \ll 2v_{OV}$ :  $r_{DS} \equiv \frac{v_{DS}}{i_D} = 1 / \left[ \mu_n C_{ox} \frac{W}{L} (v_{GS} - V_t) \right]$

- Saturation Region:  $[v_{GS} \geq V_t \Leftrightarrow v_{OV} \geq 0]$  and  $[v_{GD} \leq V_t \Leftrightarrow v_{DS} \geq v_{OV}]$

$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - V_t)^2 (1 + \lambda v_{DS})$$

- Threshold Voltage:  $V_t = V_{t0} + \gamma(\sqrt{2\phi_f + |V_{SB}|} - \sqrt{2\phi_f})$



- Process Parameters:  $C_{ox} = \epsilon_{ox} / t_{ox}$  (F/ $\mu\text{m}^2$ )

$$k'_n = \mu_n C_{ox} \quad (\text{A/V}^2)$$

$$\lambda = \frac{1}{V_A} = \frac{1}{L \cdot V'_A} \quad (\text{V}^{-1})$$

□ **PMOS Transistor:** ( $V_{t0}$ ,  $\gamma$ , and  $\lambda$  are negative)

- Reverse the polarity of all terminal voltages and
- Exchange  $V_t$ ,  $\mu_n$ ,  $\lambda$ , and  $k'_n$  with  $|V_t|$ ,  $|\lambda|$ ,  $\mu_p$ , and  $k'_p$ , respectively.

  


### Approximation of the MOSFET Gate Capacitances (for Long-Channel MOSFETs)

Mode of Operation	$C_{gb}$	$C_{gs}$	$C_{gd}$
Cutoff	$WLC_{ox}$	0	0
Triode	0	$\frac{1}{2}WLC_{ox} + WL_{ov}C_{ox}$	$\frac{1}{2}WLC_{ox} + WL_{ov}C_{ox}$
Saturation	0	$\frac{2}{3}WLC_{ox} + WL_{ov}C_{ox}$	$WL_{ov}C_{ox}$

**Small-Signal Equivalent Circuit Models for the MOSFET: Common-Gate Configuration:**


- $g_m = \mu_n C_{ox} \frac{W}{L} V_{OV} = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} = \frac{2I_D}{V_{OV}}$
- $g_{mb} = \frac{\gamma}{2\sqrt{2\phi_F + |V_{SB}|}} g_m$
- $r_o = 1 / |\lambda I_D|$
- $C_{gs} = \frac{2}{3} W L C_{ox} + W L_{ov} C_{ox}$  and  $C_{gd} = W L_{ov} C_{ox}$
- $C_{db} = \frac{C_{db0}}{\left(1 + \frac{|V_{DB}|}{V_0}\right)^m}$

 


$$R_{in} \cong \frac{1}{g_m + g_{mb}} \left(1 + \frac{R_L}{r_o}\right)$$

$$R_{out} \cong R_S + r_o [1 + (g_m + g_{mb}) R_S]$$

 **Low-Frequency Small-Signal Models for the MOSFET:**



Hybrid- $\pi$  Model

 

T model when  $|V_{SB}| = 0$

**High-Frequency Small-Signal Model for the MOSFET with no body effect ( $|V_{SB}| = 0$ ):**

