

# Introduction to Microelectronics

## Final Examination - Fall 2004


Course no.: ECSE 334 A

Friday December 10<sup>th</sup>, 2003

14:00 - 17:00 (3 Hours)

Examiner: Prof. Mourad El-Gamal

Co-Examiner: Prof. Anas Hamoui

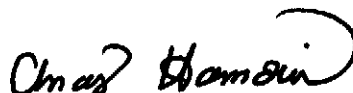

Student Last Name: \_\_\_\_\_

Student First Name: \_\_\_\_\_

McGill ID Number: \_\_\_\_\_

- Answer **ALL QUESTIONS on the exam booklet** provided.
- Please make sure to **fill and hand in back** with your exam booklet the **summary table of answers** sheet attached at the end of this exam. **Points will be deducted for every missing entry in this table.**
- Points distribution is indicated between brackets, when applicable.
- Do not forget to write your name and student ID number on the top of this sheet.
- This is a closed-book exam.
- Only the faculty supported calculators are permitted.
- Make sure you have a **total of 9 pages** (including this one) **BEFORE** you start.
- State any assumptions you find *necessary* to complete your answer.

*Good Luck !*

Question #	1	2	3	4	TOTAL
Mark					/ 100
Total Points	30	20	30	20	100

According to McGill's Code of Student Conduct and Disciplinary Procedures, plagiarism is an academic offence. Appropriate actions will be taken to deal with students who are found violating the Code, and they will be reported to the Associate Dean.

# Introduction to Microelectronics

## Final Examination - Fall 2004

Course no.: ECSE 334 A

Friday December 10<sup>th</sup>, 2003

14:00 - 17:00 (3 Hours)

**Examiner:** Prof. Mourad El-Gamal

**Co-Examiner:** Prof. Anas Hamoui

Student Last Name: \_\_\_\_\_

Student First Name: \_\_\_\_\_

McGill ID Number: \_\_\_\_\_

- Answer **ALL QUESTIONS** on the exam booklet provided.
- Please make sure to **fill and hand in back** with your exam booklet the **summary table of answers** sheet attached at the end of this exam. Points will be deducted for every missing entry in this table.
- Points distribution is indicated between brackets, when applicable.
- Do not forget to write your name and student ID number on the top of this sheet.
- This is a closed-book exam.
- Only the faculty supported calculators are permitted.
- Make sure you have a **total of 9 pages** (including this one) **BEFORE** you start.
- State any assumptions you find *necessary* to complete your answer.

*Good Luck !*


Question #	1	2	3	4	TOTAL
Mark					/ 100
Total Points	30	20	30	20	100

**According to McGill's Code of Student Conduct and Disciplinary Procedures, plagiarism is an academic offence. Appropriate actions will be taken to deal with students who are found violating the Code, and they will be reported to the Associate Dean.**

**QUESTION 1 - MULTI-STAGE AMPLIFIERS: [Total points 30]**

Figure 1 shows the circuit of a CMOS operational amplifier. All MOS devices have  $|V_{t1}| = 1 \text{ V}$ ,  $\mu_n C_{ox} = 2\mu_p C_{ox} = 40 \mu\text{A}/\text{V}^2$ ,  $|V_A| = 50 \text{ V}$ , and  $L = 5 \mu\text{m}$ . Device widths are indicated on the diagram as multiples of  $W$ , where  $W = 5 \mu\text{m}$ .

- 1.1- [2 points] Design  $R$  to provide a  $10\text{-}\mu\text{A}$  reference current  $I_{\text{REF}}$ .
- 1.2- [4 points] Assuming  $v_o = 0 \text{ V}$ , as established by external feedback, perform a bias analysis, finding all the labeled node voltages.
- 1.3- [5.2 points] Provide in table format  $I_D$ ,  $V_{GS}$ ,  $g_m$ , and  $r_o$  for all devices.
- 1.4- [6.8 points] Calculate the voltage gain  $A_v = v_o / (v_+ - v_-)$ , the differential input resistance  $R_{\text{indiff}}$ , and the output resistance  $R_{\text{out}}$ .
- 1.5- [3 points] What is the input common-mode range (ICMR) ?
- 1.6- [3 points] What is the output signal range for no load ?
- 1.7- [3 points] For what load resistance  $R_{\text{load}}$  connected to ground is the minimum output voltage limited to  $-1 \text{ V}$  before  $Q_7$  begins to conduct ?
- 1.8- [3 points] For a load resistance one-tenth of that found in part 1.7, what is the output signal swing ?

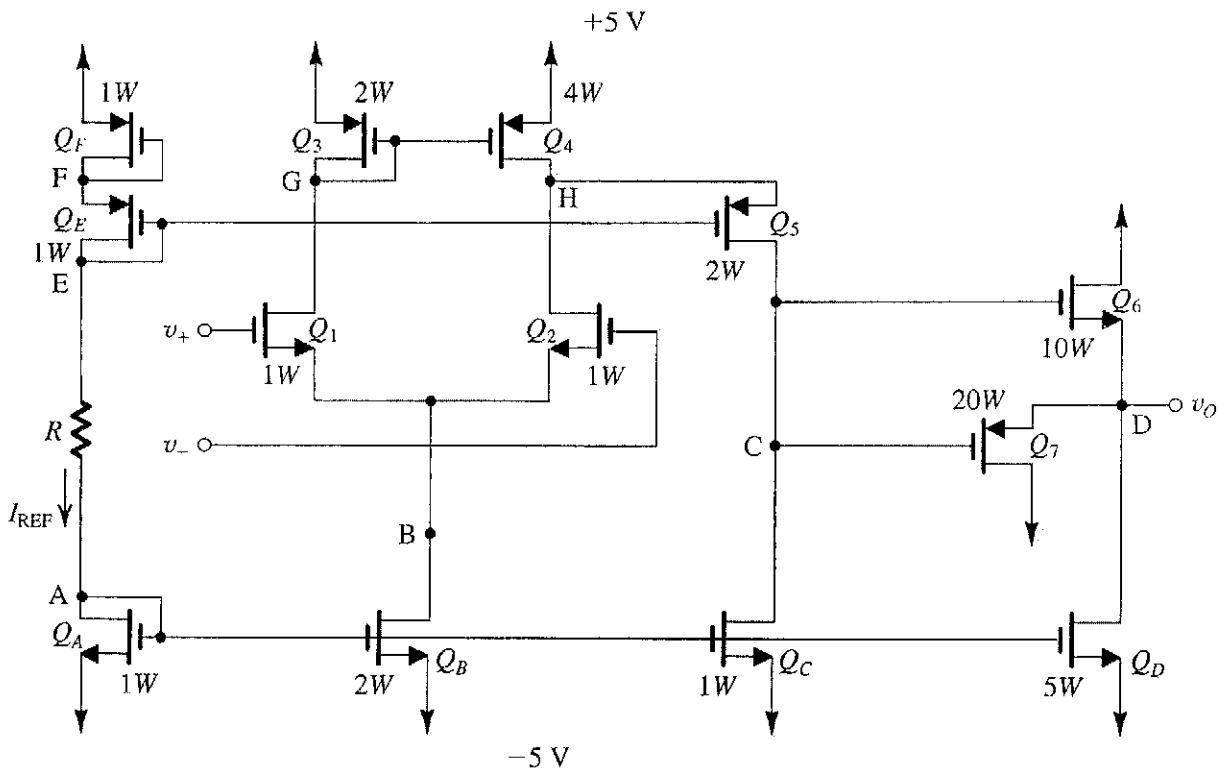


**Figure 1.**

**QUESTION 2 - OUTPUT STAGES:** [Total points 20]

The BiCMOS follower shown in Figure 2 uses devices for which  $V_{BE} = 0.7$  V,  $V_{CEsat} = 0.3$  V,  $\mu_n C_{ox} W/L = 20$  mA/V<sup>2</sup>, and  $V_t = -2$  V.


- 2.1- [5 points] For linear operation, what is the range of output voltages obtained with  $R_L = \text{infinity}$  ?
- 2.2- [5 points] For linear operation, what is the range of output voltages obtained with  $R_L = 100 \Omega$  ?
- 2.3- [5 points] What is the smallest load resistor allowed for which a 1-V peak sine-wave output is available ?
- 2.4- [5 points] What is the corresponding power conversion efficiency ?

 

**Figure 2.**


**QUESTION 4 - STABILITY: [Total points 20]**

Consider an op amp with an open-loop voltage gain of 80 dB and poles at  $10^5$  Hz,  $10^6$  Hz, and  $2 \times 10^6$  Hz is to be compensated to be stable for unity gain feedback (i.e.  $\beta=1$ ). Assume that the op-amp incorporates an amplifier equivalent to that in Figure 4, with  $C_1 = 150$  pF,  $C_2 = 5$  pF, and  $g_m = 40$  mA/V, and that the pole at  $f_{P1}$  is caused by the input circuit, and that the pole at  $f_{P2}$  is introduced by the output circuit of this amplifier. Find the value of the required compensating Miller capacitance  $C_f$  and the new frequency of the output pole.

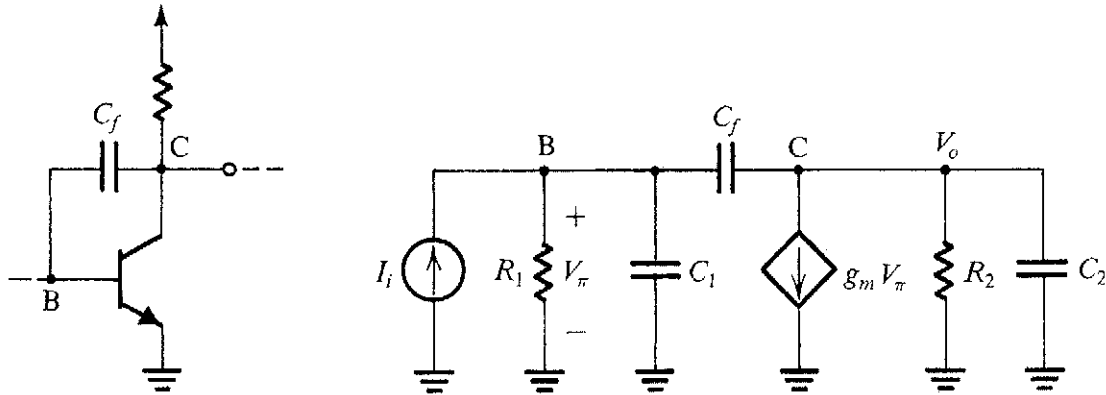

**Figure 4.**

**QUESTION 3 - FEEDBACK:** [Total points 30]

 

**Figure 3.**

Figure 3 shows a series-shunt feedback amplifier without the details of the bias circuit.

**3.1. [9 points]** Find expressions for the open-loop gain  $A$ , the feedback factor  $\beta$ , and the preprocessing stage  $\alpha$ . Draw the resulting Signal Flow Graph (SFG).

**3.2. [3 points]** Show that if  $A\beta$  is large, then the closed-loop voltage gain is given approximately by

$$A_f \equiv \frac{V_o}{V_S} \equiv \frac{R_F + R_E}{R_E}$$

**3.3. [3 points]** If  $R_E$  is selected equal to 50  $\Omega$ , find  $R_F$  that will result in a closed-loop gain of approximately 25 V/V.

**3.4. [6 points]** If Q1 is biased at 1 mA, Q2 at 2 mA, and Q3 at 5 mA, and assuming the transistors have  $h_{fe} = 100$ , find approximate values for  $R_{C1}$  and  $R_{C2}$  to obtain gains from the stages of the A-circuit as follows: a voltage gain from Q1 of about -10 V/V and a voltage gain from Q2 of about -50 V/V.

**3.5. [3 point]** For your design, what is the closed-loop voltage gain realized ?

**3.6. [6 points]** Calculate the input and output resistances of the closed-loop amplifier designed.

**Table 4.2** SUMMARY OF THE BJT CURRENT-VOLTAGE RELATIONSHIPS IN THE ACTIVE MODE

$$i_C = I_S e^{v_{BE}/V_T}$$

$$i_B = \frac{i_C}{\beta} = \left(\frac{I_S}{\beta}\right) e^{v_{BE}/V_T}$$

$$i_E = \frac{i_C}{\alpha} = \left(\frac{I_S}{\alpha}\right) e^{v_{BE}/V_T}$$

Note: For the *pnp* transistor, replace  $v_{BE}$  with  $v_{EB}$ .

$$i_C = \alpha i_E \quad i_B = (1 - \alpha)i_E = \frac{i_E}{\beta + 1}$$

$$i_C = \beta i_B \quad i_E = (\beta + 1)i_B$$

$$\beta = \frac{\alpha}{1 - \alpha} \quad \alpha = \frac{\beta}{\beta + 1}$$

$$V_T = \text{thermal voltage} = \frac{kT}{q} \cong 25 \text{ mV at room temperature}$$

**Table 4.3** RELATIONSHIPS BETWEEN THE SMALL-SIGNAL MODEL PARAMETERS OF THE BJT

Model Parameters in Terms of DC Bias Currents:

$$g_m = \frac{I_C}{V_T} \quad r_e = \frac{V_T}{I_E} = \alpha \left(\frac{V_T}{I_C}\right)$$

$$r_\pi = \frac{V_T}{I_B} = \beta \left(\frac{V_T}{I_C}\right) \quad r_o = \frac{V_A}{I_C}$$

In terms of  $g_m$ :

$$r_e = \frac{\alpha}{g_m} \quad r_\pi = \frac{\beta}{g_m}$$

In terms of  $r_e$ :

$$g_m = \frac{\alpha}{r_e} \quad r_\pi = (\beta + 1)r_e \quad g_m + \frac{1}{r_\pi} = \frac{1}{r_e}$$

Relationships between  $\alpha$  and  $\beta$ :

$$\beta = \frac{\alpha}{1 - \alpha} \quad \alpha = \frac{\beta}{\beta + 1} \quad \beta + 1 = \frac{1}{1 - \alpha}$$

---

### Current-Voltage Relationships

---

■ For NMOS Devices:

- Triode region ( $v_{GS} \geq V_t$ ,  $v_{DS} \leq v_{GS} - V_t$ )

$$i_D = k'_n \left( \frac{W}{L} \right) \left[ (v_{GS} - V_t)v_{DS} - \frac{1}{2} v_{DS}^2 \right]$$

$$\text{For small } v_{DS}: r_{DS} \equiv \frac{v_{DS}}{i_D} = \left[ k'_n \left( \frac{W}{L} \right) (v_{GS} - V_t) \right]^{-1}$$

- Saturation region ( $v_{GS} \geq V_t$ ,  $v_{DS} \geq v_{GS} - V_t$ )

$$i_D = \frac{1}{2} k'_n \left( \frac{W}{L} \right) (v_{GS} - V_t)^2 (1 + \lambda v_{DS})$$

- $k'_n = \mu_n C_{ox}$  (see Table 5.1)

$$V_t = V_{t0} + \gamma [\sqrt{2\phi_f + |V_{SB}|} - \sqrt{2\phi_f}]$$

$$\gamma = \frac{\sqrt{2qN_A\epsilon_s}}{C_{ox}}, \quad q = 1.6 \times 10^{-19} \text{ coulomb}, \quad \epsilon_s = 1.04 \times 10^{-12} \text{ F/cm}$$

$$\lambda = 1/V_A, \quad V_A \propto L$$


---

■ For PMOS Devices:  $V_t$ ,  $\gamma$ ,  $\lambda$  and  $V_A$  are negative

- For triode region,  $v_{GS} \leq V_t$  and  $v_{DS} \geq v_{GS} - V_t$
  - For saturation region,  $v_{GS} \leq V_t$  and  $v_{DS} \leq v_{GS} - V_t$
- 

■ For Depletion Devices (refer to Fig. 5.23):

- $n$  channel:  $V_t$  is negative
- $p$  channel:  $V_t$  is positive

$$i_{DSS} = \frac{1}{2} k' \left( \frac{W}{L} \right) V_t^2$$


---

### Small-Signal Model (Fig. 5.67)

---

$$g_m = \sqrt{2k'(W/L)} \sqrt{I_D} \quad r_o = \frac{|V_A|}{I_D}$$

$$g_m = k'(W/L)(V_{GS} - V_t)$$

$$g_m = \frac{2I_D}{V_{GS} - V_t} \quad V_{GS} - V_t \equiv V_{eff}$$

$$g_{mb} = \chi g_m, \quad \chi = \gamma/[2\sqrt{2\phi_f + |V_{SB}|}]$$

$$C_{gs} = \frac{2}{3} WLC_{ox} + WL_{ov}C_{ox} \quad C_{gd} = WL_{uv}C_{ox}$$

$$C_{sb} = \frac{C_{sb0}}{\sqrt{1 + \frac{|V_{SB}|}{V_0}}} \quad C_{db} = \frac{C_{db0}}{\sqrt{1 + \frac{|V_{DB}|}{V_0}}}$$

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$


---



Last Name:

ID Number:

First name:

Question Number		Value
1.1	<i>Biassing R</i>	
1.2	$V_A$	
	$V_B$	
	$V_C$	
	$V_D$	
	$V_E$	
	$V_F$	
	$V_G$	
	$V_H$	

Question Number		$I_D$ ( $\mu A$ )	$V_{GS}$ (V)	$g_m$ ( $\mu A/V$ )	$r_o$ (M $\Omega$ )
1.3	$Q_1$				
	$Q_2$				
	$Q_3$				
	$Q_4$				
	$Q_5$				
	$Q_6$				
	$Q_7$				
	$Q_A$				
	$Q_B$				
	$Q_C$				
	$Q_D$				
	$Q_E$				
	$Q_F$				

Question Number		Value
1.4	$A_v = v_o / (v_+ - v_-)$	
	$R_{indiff}$	
	$R_{out}$	
1.5	ICMR	$V_{ICM-max} =$ ; $V_{ICM-min} =$
1.6	Output range for no load	$V_{out-max} =$ ; $V_{out-min} =$
1.7	$R_{load}$	
1.8	Output signal swing	$V_{out-max} =$ ; $V_{out-min} =$

Last Name:

ID Number:

First name:

Question Number		Value
2.1	Output range ( $R_L = \text{infinity}$ )	$V_{\text{out-max}} =$ ; $V_{\text{out-min}} =$
2.2	Output range ( $R_L = 100 \Omega$ )	$V_{\text{out-max}} =$ ; $V_{\text{out-min}} =$
2.3	Smallest $R_L$ for a 1-V peak output	
2.4	Power efficiency	

Question Number		Value
3.1		Answer in booklet only
3.2		Answer in booklet only
3.3	$R_F$ for 25 V/V loop gain	
3.4	$R_{C1}$	
	$R_{C2}$	
3.5	Closed loop voltage gain	
3.6	Input resistance of closed loop	
	Output resistance of closed loop	

Question Number		Value
4.1	Miller compensating capacitance	
4.2	New frequency of the output pole	