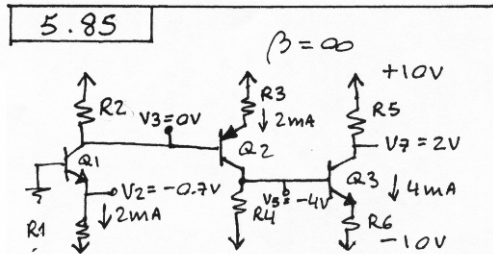


Solutions to Selected Problems (Problem Set 1)

Chapter 5: 5.85, 5.122, 5.136, 5.143

Chapter 6: 6.29, 6.30, 6.34

Microelectronic Circuits – 5th Edition – Sedra/Smith
 Copyright © 2004 by Oxford University Press, Inc.
DO NOT DUPLICATE



$\beta = \infty$

$$R_1 = \frac{9.3}{2} = \underline{4.7\text{ k}\Omega}$$


$$R_2 = \frac{10}{2} = 5 \rightarrow \underline{5.1\text{ k}\Omega}$$

$$R_3 = \frac{9.3}{2} = \underline{4.7\text{ k}\Omega}$$

$$R_4 = \frac{6}{2} = \underline{3\text{ k}\Omega}$$

$$R_5 = \frac{8}{4} = \underline{2\text{ k}\Omega}$$
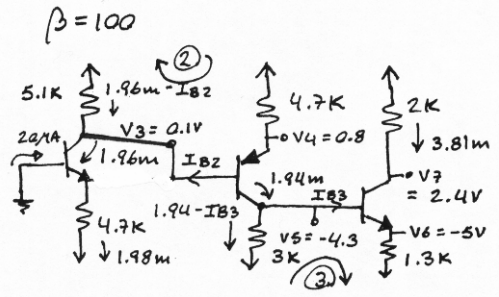
$$R_6 = \frac{10 - 4.7}{4} = \underline{1.3\text{ k}\Omega}$$




② $(1.96 - I_{B2}) \times 5.1$
 $= (\beta + 1) I_{B2} \times 4.7 + 0.7$
 $I_{B2} = 0.0194\text{ mA}$
 $I_{E2} = 1.96\text{ mA}$
 $V_3 = \underline{0.1\text{ V}}$ $V_4 = \underline{0.8\text{ V}}$

③ $(1.94 - I_{B3}) \times 3$
 $= 0.7 + 1.3 \times (\beta + 1) \cdot I_{B3}$
 $I_{B3} = 0.038\text{ mA}$
 $I_{E3} = 3.85\text{ mA}$
 $V_5 = \underline{-4.3\text{ V}}$ $V_6 = \underline{-5\text{ V}}$

$V_7 = \underline{2.4\text{ V}}$

5.122

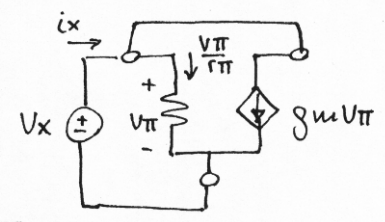

$$i_x = \frac{V_{\pi}}{r_{\pi}} + g_m V_{\pi}$$

$$= \frac{V_{\pi}}{r_{\pi}} (1 + g_m r_{\pi})$$

$$= \frac{V_{\pi}}{r_{\pi}} (1 + \beta)$$

But $V_{\pi} = V_x$

$$\rightarrow R_{in} = \frac{V_x}{i_x} = \frac{V_{\pi}}{i_x} = \frac{r_{\pi}}{\beta + 1}$$

$R_{in} = \underline{r_e}$

5.130

Refer to Fig. P5.130


$$I_E = \frac{V_{BB} - V_{BE}}{R_E + R_B / (\beta + 1)}$$

where, $V_{BB} = V_{cc} \cdot \frac{R_2}{R_1 + R_2}$

$$= 9 \cdot \frac{15}{27 + 15} = 3.21 \text{ V}$$

$$R_B = R_1 \parallel R_2 = 15 \parallel 27 = 9.64 \text{ k}\Omega$$

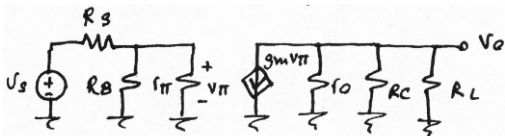Thus, $I_E = \frac{3.21 - 0.7}{1.2 + \frac{9.64}{101}} = \underline{\underline{1.94 \text{ mA}}}$



$$g_m = \frac{I_C}{V_T} = \frac{0.99 \times 1.94}{0.025} = 76.8 \frac{\text{mA}}{\text{V}}$$


$$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{76.8} = 1.3 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_C} = \frac{100}{0.99 \times 1.94} = 52.1 \text{ k}\Omega$$

$$R_i = R_B \parallel r_{\pi} = 9.64 \parallel 1.3 = \underline{\underline{1.15 \text{ k}\Omega}}$$

$$G_m = -g_m = -\underline{\underline{76.8 \frac{\text{mA}}{\text{V}}}}$$
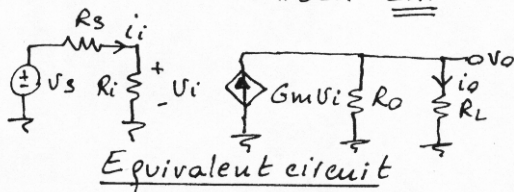
$$R_o = R_C \parallel r_o = 2.2 \parallel 52.1 = \underline{\underline{2.11 \text{ k}\Omega}}$$



$$\begin{aligned} A_V &= \frac{V_o}{V_s} = \frac{V_i}{V_s} \cdot \frac{V_o}{V_i} \\ &= \frac{R_i}{R_s + R_i} \cdot \frac{G_m (R_o \parallel R_L) V_i}{V_i} \\ &= \frac{-1.15}{10 + 1.15} \times 76.8 \times (2.11 \parallel 2) \\ &= \underline{\underline{-8.13 \text{ V/V}}} \end{aligned}$$

$$A_i = \frac{i_o}{i_i} = \frac{V_o \cdot R_L}{V_s / (R_s + R_i)}$$

$$\begin{aligned} \rightarrow A_i &= \frac{V_o}{V_s} \cdot \frac{R_s + R_i}{R_L} \\ &= -8.13 \times \frac{(10 + 1.15)}{2} \\ &= \underline{\underline{-45.3 \text{ A/A}}} \end{aligned}$$

5.136

Refer to the circuit in Fig. P5.136

$$R_{in} = (\beta + 1)(r_e + 250) \parallel 1M$$

$$\beta = 100 \quad r_e = \frac{V_T}{I_E} = \frac{0.025}{0.1} = 250\Omega$$

$$R_{in} = 101 \times (250 + 250) \parallel 1M$$

$$= \underline{50.5K\Omega}$$

$$\frac{U_6}{U_s} = \frac{R_{in}}{R_s + R_{in}} = \frac{50.5}{20 + 50.5}$$

$$= 0.72 \text{ V/V}$$

$$\frac{U_0}{U_6} = -\alpha \frac{(20 \parallel 20)}{(r_e + R_E)}$$

$$= -\frac{0.99 \times 10}{0.250 + 0.250} = \underline{-19.8 \text{ V/V}}$$

Thus, $\frac{U_0}{U_s} = 0.72 \times 19.8 = \underline{-14.2 \text{ V/V}}$

For $U_{be} = 5\text{mV}$, $I_E = 5\text{mA}$ also (since $r_e = r_e = 250\Omega$)

Thus,

$$U_6 = 5 + 5 = 10\text{mV}$$

$$U_s = \frac{10\text{mV}}{0.72} = \underline{13.88\text{mV}}$$

$$U_0 = 13.88 \times 14.2 = \underline{197.2\text{mV}}$$

5.143 Refer to Fig. P5.143

(a) $I_E = \frac{9 - 0.7}{1 + 100 \parallel (\beta + 1)}$

for $\beta = 40$, $I_E = \frac{8.3}{1 + \frac{100}{41}} = \underline{2.41\text{mA}}$

$$V_E = 1 \times 2.41 = \underline{2.41\text{V}}$$

$$V_B = 2.41 + 0.7 = \underline{3.11\text{V}}$$

for $\beta = 200$, $I_E = \frac{8.3}{1 + \frac{100}{201}} = \underline{5.54\text{mA}}$

$$V_E = + \underline{5.54\text{V}}$$

$$V_B = + \underline{6.24\text{V}}$$

(b) $R_i = 100K\Omega \parallel (\beta + 1)[r_e + (1 \parallel 1)]$

$$= 100 \parallel (\beta + 1)[r_e + 0.5]$$

For $\beta = 40$, $I_E = 2.41\text{mA}$

$$\rightarrow r_e = 10.37\Omega$$

thus $R_i = 100 \parallel 41 \times (0.01037 + 0.5)$

$$= 100 \parallel 21$$

$$= \underline{17.30\Omega}$$

For $\beta = 200$, $I_E = 5.54\text{mA}$

$$\rightarrow r_e = 4.51\Omega$$

thus $R_i = 100 \parallel 201(0.0045 + 0.5)$

$$= 100 \parallel 101.4$$

$$= \underline{50.3K\Omega}$$

(c) $\frac{U_0}{U_s} = \frac{U_6}{U_s} \cdot \frac{U_0}{U_6}$

$$= \frac{R_i}{R_s + R_i} \cdot \frac{(1 \parallel 1)}{(1 \parallel 1) + r_e}$$

For $\beta = 40$,

$$\frac{U_0}{U_s} = \frac{17.3}{10 + 17.3} \times \frac{0.5}{0.5 + 0.01037}$$

$$= \underline{0.621 \text{ V/V}}$$

For $\beta = 200$,

$$\frac{U_0}{U_s} = \frac{50.3}{10 + 50.3} \cdot \frac{0.5}{0.5 + 0.0045}$$

$$= \underline{0.827 \text{ V/V}}$$

6.29

$$I_s = 10^{-15}\text{A}$$

a) $I_{REF} = I_s e^{V_{BE}/V_T} \Rightarrow V_{BE} = V_T \ln \frac{I_{REF}}{I_s}$

$$I_{REF} = 10\mu\text{A} \Rightarrow V_{BE} = 0.025 \ln \frac{10 \times 10^{-6}}{10^{-15}} = 0.576\text{V}$$

$$I_{REF} = 1\text{mA} \Rightarrow V_{BE} = 0.025 \ln \frac{10 \times 10^{-3}}{10^{-15}} = 0.748\text{V}$$

Therefore: $10\mu\text{A} \leq I_{REF} \leq 1\text{mA} \Rightarrow 0.576\text{V} \leq V_{BE} \leq 0.748\text{V}$

Since β is very high, I_B is negligible and hence

$$I_0 \approx I_{REF} : 10\mu\text{A} \leq I_0 \leq 1\text{mA}$$

b) $I_0 = I_{REF} \frac{1}{1 + 2/\beta}$ (Eq. 6.21)

For $0.1 \leq I_C \leq 5\text{mA}$, β remains constant at 100.

$$I_{REF} = 10\text{mA} \Rightarrow I_0 = \frac{10}{1 + \frac{2}{100}} = 9.72\text{mA}$$

$$I_{REF} = 0.1\text{mA} \Rightarrow I_0 = \frac{0.1}{1 + \frac{2}{100}} = 0.098\text{mA}$$

$$I_{REF} = 1\text{mA} \Rightarrow I_0 = \frac{1}{1 + \frac{2}{100}} = 0.98\text{mA}$$

$$I_{REF} = 10\mu\text{A} \Rightarrow$$

6.30

$$I_{S2} = I_{S1} \times m, \quad I_{C1} = I_C$$

$$I_{REF} = I_C + \frac{I_C}{\beta} + \frac{I_0}{\beta} \quad (1)$$

$$V_{BE1} = V_{BE2} \Rightarrow$$

$$V_T \ln \frac{I_C}{I_{S1}} = V_T \ln \frac{I_0}{I_{S2}}$$

$$\Rightarrow \frac{I_0}{I_C} = \frac{I_{S2}}{I_{S1}} = m \Rightarrow I_C = I_0/m$$


by substituting for I_C in (1):

$$I_{REF} = \frac{I_0}{m} + \frac{I_0}{m\beta} + \frac{I_0}{\beta} \Rightarrow \frac{I_0}{I_{REF}} = \frac{m}{1 + \frac{1}{\beta} + \frac{m}{\beta}}$$

$$\frac{I_0}{I_{REF}} = \frac{m}{1 + \frac{1+m}{\beta}}$$

This result is the same as Eq. 6.22.

For large β , $I_0/I_{REF} = m$, with finite β this ratio drops to $I_0/I_{REF} = \frac{m}{1 + \frac{1+m}{\beta}}$. To keep the introduced error within 5%: $0.95m = \frac{m}{1 + \frac{1+m}{\beta}}$
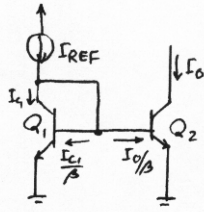
$$A_{min} = 80 \Rightarrow 0.95 = \frac{1}{1 + \frac{1+m}{80}} \Rightarrow m = 3.21$$


6.34

$$I_{C1} = I_{C2} = I_{R1}$$


$$V_{B1} = 10 - 0.7 = 9.3V, \quad V_{B2} = -10 + 0.7 = -9.3V, \quad I_{R1} = \frac{9.3 + 9.3}{10}$$

$$\Rightarrow I_{R1} = 1.86mA = I_{C1} = I_{C2} = I_{C3} = I_{C4} = I_{C5} = I_{C6}$$

$$V_{C3} = 1.86 \times 2k = 3.72V, \quad V_{C5} = 0.7V$$

$$V_{C6} = 5 - 1.86 \times 1 = 3.14V, \quad I_{C9} = I_{C8} = I_{C7} = I_{C2} = 1.86mA$$
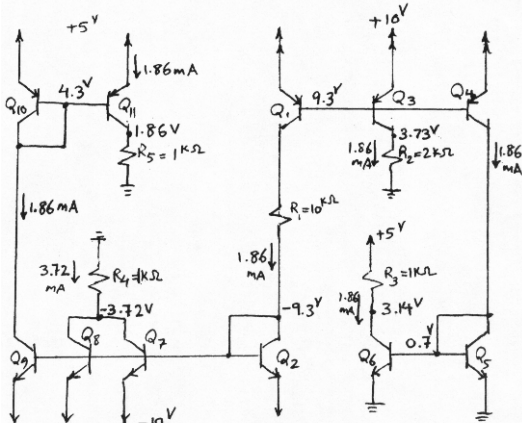
$$I_{R4} = 2 \times 1.86 = 3.72mA \Rightarrow V_{C7} = -3.72 \times 1 = -3.72V$$



$$I_{C10} = I_{C9} = 1.86mA$$

$$V_{C9} = V_{C10} = V_{B10} = 5 - 0.7 = 4.3V$$

$$I_{C11} = I_{C10} = 1.86mA$$

$$V_{C11} = 1.86 \times 1 = 1.86V$$