

Solutions to Selected Problems (Problem Set 2)

Chapter 7: 7.30, 7.32, 7.34, 7.35, 7.44

Microelectronic Circuits – 5th Edition – Sedra/Smith
 Copyright© 2004 by Oxford University Press, Inc.
DO NOT DUPLICATE


7.30

Refer to Fig. P7.30
 (a) For V_I sufficiently low so that Q_1 is cut off:

$$V_{BE}|_{Q_3} = 0.7 + V_T \ln \frac{10}{1} = 0.76V$$

$$V_{OH} = V_O = 5 - \frac{10}{101} \times 1 - V_{BE}|_{Q_3}$$

$$= 5 - \frac{10}{101} - 0.76 = 4.14V$$

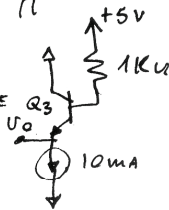


(b) For V_I sufficiently high so that Q_1 is conducting all the current I :

$$V_{BE}|_{Q_3} = 0.76V$$

$$V_{OL} = V_O = 5 - \left(\frac{10}{101} + 0.99 \right) \times 1 - 0.76$$

$$= 3.15V$$

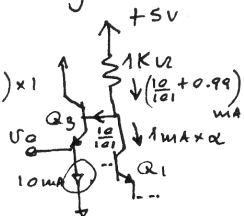

(c) $i_{E1} = I / (1 + e^{(V_{B2} - V_{B1})/V_T}) = I / 100$


$$e^{(3.64 - V_I)/V_T} = 99$$

$$V_I = 3.64 - V_T \ln 99 = 3.525V = V_{IL}$$

(d) $i_{E1} = 0.99I = \frac{I}{1 + e^{(3.64 - V_{IH})/V_T}}$

$$1 + e^{(3.64 - V_{IH})/V_T} = 1.01$$

$$V_{IH} = 3.64 + V_T \ln 100 = 3.755V$$

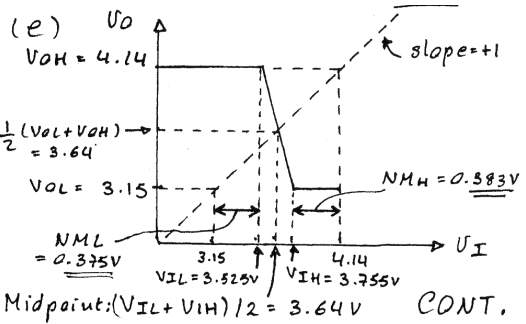

Since the mid-point of the output voltage swing is equal to 3.64V, the output voltage swing is centred on the mid-point of the input range; an ideal choice for it equalizes the noise margins.


7.32

$R_{id} > 10k\Omega$; $A_d = 200V/V$;
 $\beta > 100$; $V_{cc} = 10V$
 $R_{id} = 10^4 = 25\pi = 2 \times \frac{100}{g_m}$

$\Rightarrow g_m = 20mA/V$
 Thus each device is operating at 0.5mA and $I = 1mA$

Voltage gain = $g_m R_c$
 $200 = 20 R_c$
 $\Rightarrow R_c = 10k\Omega$

7.34

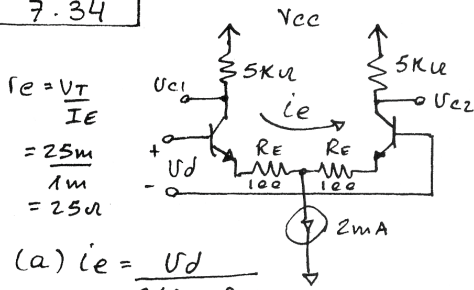

$$r_e = \frac{V_T}{I_E} = \frac{25mV}{1\mu A} = 25\Omega$$

$$(a) i_e = \frac{V_D}{2(r_e + R_E)} = \frac{0.1V}{2(25 + 100)\Omega} = 0.4\mu A$$

$$(b) i_{E1} = 1 + 0.4 = 1.4\mu A$$

$$i_{E2} = 1 - 0.4 = 0.6\mu A$$


$$(c) V_{C1} = -i_e R_c \approx -0.4 \times 5 = -2V$$

$$V_{C2} = +2V$$

$$(d) U_{od} = 4V$$

$$A_d = U_{od} / U_{id} = \frac{4}{0.1} = 40V/V$$

7.35

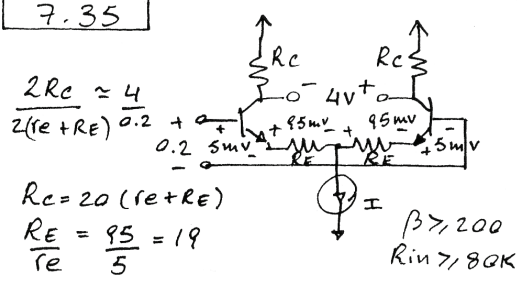

$$\frac{2R_c}{2(r_e + R_E)} \approx \frac{4}{0.2} + 0.2$$

$$R_c = 20(r_e + R_E)$$

$$\frac{R_E}{r_e} = \frac{95}{5} = 19$$

$$R_{in} > 80k$$

$$\beta > 200$$

$$R_{in} = 2(\beta + 1)(r_e + R_E) = 2 \times 201 \times 20r_e = 80k\Omega$$

$$\Rightarrow r_e = \frac{80000}{8000} = 10\Omega$$


Thus each device is operating at a current of $\frac{25mV}{10\Omega} = 2.5\mu A$

$$\Rightarrow I = 5\mu A$$

$$R_E = 19 \times 10 = 190\Omega$$


$$R_c = 20 \times 200 = 4k\Omega$$

7.44

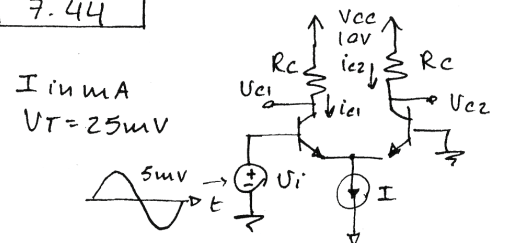

$$I \text{ in } \mu A$$

$$V_T = 25mV$$

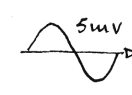

$$i_{e1} = \frac{I}{2} + \left(\frac{I/2}{V_T}\right)\left(\frac{5}{2}\right) \sin \omega t$$

$$i_{e2} = \frac{I}{2} - \left(\frac{I/2}{V_T}\right)\left(\frac{5}{2}\right) \sin \omega t$$


$$V_{C1} = V_{CC} - \frac{I}{2} R_c - \frac{I/2}{V_T} R_c \frac{5}{2} \sin \omega t$$

$$V_{C2} = V_{CC} - \frac{I}{2} R_c + \frac{I/2}{V_T} R_c \frac{5}{2} \sin \omega t$$

$$V_{C1}, V_{C2} \geq 0$$

$$\Rightarrow 10 - 5I - 0.5I = 0$$

$$I = 1.8\mu A$$

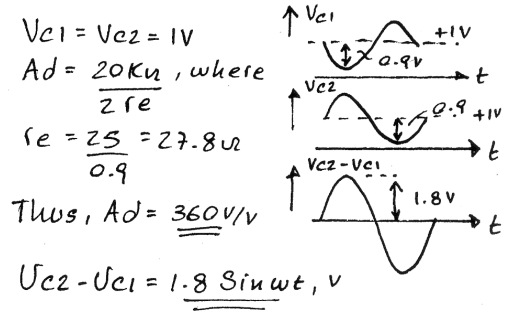

$$V_{C1} = V_{C2} = 1V$$

$$A_d = \frac{20k\Omega}{2r_e}, \text{ where } r_e = \frac{25}{0.9} = 27.8\Omega$$

$$\text{Thus, } A_d = 360V/V$$

$$V_{C2} - V_{C1} = 1.8 \sin \omega t, V$$