

Solutions to Selected Problems (Problem Set 3)

Chapter 7: 7.37, 7.38, 7.39, 7.40, 7.42, 7.46, 7.57, 7.67, 7.68

Microelectronic Circuits – 5th Edition – Sedra/Smith
 Copyright© 2004 by Oxford University Press, Inc.
DO NOT DUPLICATE

7.37

Refer to Fig. P7.37

$$\frac{V_o}{V_i} = \frac{\alpha \times 20 \text{ k}\Omega}{(2r_e + 2 \times 200) \Omega}$$

Where $r_e = \frac{V_T}{I_E} = \frac{0.025 \text{ V}}{0.5 \text{ mA}} = 50 \Omega$

$$\frac{V_o}{V_i} \approx \frac{20000}{500} = 33.3 \text{ V/V}$$

$$R_i = (\beta + 1)(2r_e + 2 \times 200) = 101 \times 2 \times 300 \approx 60 \text{ k}\Omega$$

7.38

Refer to Fig P.7.38

Each transistor is operating at $I_E = 1 \text{ mA}$, thus
 $r_e = 25 \Omega$ and $r_{\pi} = 101 \times 25 = 2525 \Omega$

$$\frac{V_o}{V_i} = \frac{\alpha \times 7.5 \text{ k}\Omega}{(2r_e + 200) \Omega} \approx \frac{7500}{250} = 30 \text{ V/V}$$

$$R_i = (\beta + 1)(r_e + 200 + r_e) \approx 25 \text{ k}\Omega$$


7.39

Refer to Fig P.7.39
 (a) As a differential amplifier, the gain is given by

$$\frac{V_o}{V_i} = \frac{\alpha R_c}{2r_e} \quad (1)$$

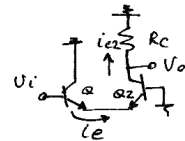(b) Transistor Q_1 can be considered as a common-collector stage. It is biased at I_{E2} and has a resistance r_{e2} in its emitter, thus.

$$i_e = \frac{v_i}{r_{e1} + r_{e2}} = \frac{v_i}{2r_e} \quad (2)$$



Now, Q_2 is connected in the common-base configuration. It has an input signal current i_e . Thus its collector signal current (in the direction indicated) will be $i_{c2} = \alpha i_e$ (3)

The output voltage will be $V_o = i_{c2} R_c$ (4)

Combining equations (2), (3) and (4) provides:

CONT.

$\frac{V_o}{V_i} = \frac{\alpha R_c}{2r_e}$, which is identical to the result found above in part (a)


7.40

(a) $V_E = -0.7V$

Thus, $I = \frac{-0.7 - (-5)}{4.3} = 1mA$ $r_e = 50\Omega$

$A_d = \frac{V_o}{V_d} = \frac{\alpha \times 2}{2r_e} \approx \frac{2000}{2 \times 50} = 20 V/V$

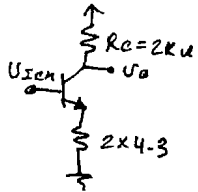(b) $A_{cm} = \frac{\alpha R_c}{8.6 + r_e} = \frac{2}{8.65} = 0.23 V/V$



(c) CMRR = $20 \log \left| \frac{A_d}{A_{cm}} \right| = 20 \log \frac{20}{0.23} = 38.8 \text{ dB}$

(d) $V_d = 2 \times 0.005 \sin(2\pi \times 1000t)$
 $V_{icm} = 0.1 \sin(2\pi \times 60t)$
 Thus, $V_o = A_d \cdot V_d + A_{cm} \cdot V_{icm}$
 $= 20 \times 0.01 \sin 2\pi \times 1000t + 0.23 \times 0.1 \sin(2\pi \times 60t)$
 $= 0.2 \sin 2\pi \times 1000t + 0.023 \sin 2\pi \times 60t$

7.42

Assume $\alpha = 1$ in small-signal calculations

(a) $A_d \Big|_{\text{single-ended output}} = \frac{R_c || r_o}{2r_e}$

where $r_e = \frac{0.025V}{0.25mA} = 100\Omega$

$r_o = \frac{200V}{0.25mA} = 800k\Omega$

$A_d \Big|_{\text{single-ended}} \approx \frac{20}{2 \times 0.1} = 100 V/V$

(b) $A_d \Big|_{\text{diff output}} = 2 \times A_d \Big|_{\text{single-ended}} = 200 V/V$

(c) $R_{id} = 2r_{\pi} = 2 \times 20k \times 100 = 40.2k\Omega$

CONT.

(d) $A_{cm} \Big|_{\text{single-ended output}} = \frac{R_c}{2R} = \frac{20}{2000} = 0.01 V/V$

(e) $A_{cm} \Big|_{\text{diff out}} = 0$

7.46

Taken single-endedly

$$A_{em_s} = \frac{\alpha R_c}{2R_o}$$

Let collector resistors be R_c & $R_c + \Delta R_c$, then

$$A_{em} = \frac{\alpha}{2R_o} (R_c + \Delta R_c - R_c)$$

$$= \alpha \frac{\Delta R_c}{2R_o}$$

Which can be written as

$$A_{em_s} = \frac{\alpha R_c}{2R_o} \cdot \frac{\Delta R_c}{R_c} = A_{em_s} \frac{\Delta R_c}{R_c}$$

$$CMRR = \frac{A_d}{A_{em_s}} = \frac{2A_s}{A_{em_s} \frac{\Delta R_c}{R_c}}$$

$$= \frac{A_s}{A_{em_s}} \cdot \frac{2}{\frac{\Delta R_c}{R_c}}$$

$$\text{Thus, } 20 \log \frac{2}{\frac{\Delta R_c}{R_c}} = 40 \text{ dB}$$

$$\rightarrow \frac{\Delta R_c}{R_c} = \underline{\underline{2\%}}$$

7.57

Refer to Fig. P7.57.

$$(a) R_{c1} = 5 \times 1.05 = 5.25 \text{ k}\Omega$$

$$R_{c2} = 5 \times 0.95 = 4.75 \text{ k}\Omega$$

Perfect offset nulling will be achieved when x is such that

$$R_{c1} + (x \times 1 \text{ k}\Omega) = R_{c2} + (1-x) \times 1 \text{ k}\Omega$$

$$\Rightarrow 5.25 + x = 4.75 + 1 - x$$

$$\Rightarrow x = \underline{\underline{0.25}}$$

$$(b) I_{c1} = 1.05 \text{ mA}$$

$$I_{c2} = 0.95 \text{ mA}$$

Offset nulling is achieved when x is such that

$$1.05(x + 5) = 0.95((1-x) + 5)$$

$$x = \underline{\underline{0.225}}$$

7.67

$$R_{id} = (\beta + 1) 2r_e ; r_e = \frac{25 \text{ mV}}{50 \mu\text{A}} = 500 \Omega$$

$$\rightarrow R_{id} = 101 \times 1000 = 101 \text{ k}\Omega$$

$$R_o = r_{o1} || r_{o2} = \frac{r_o}{2} ; r_o = \frac{V_A}{I_C}$$

$$\rightarrow r_o = \frac{160 \text{ V}}{50 \mu\text{A}} = 3.2 \text{ M}\Omega$$

$$\text{Thus, } R_o = \underline{\underline{1.6 \text{ M}\Omega}}$$

$$G_m = g_{m1} = g_{m2} = \frac{50 \mu\text{A}}{25 \text{ mV}} = \underline{\underline{2 \text{ mA/V}}}$$

$$A_d = G_m R_o = 2 \times 1600 = \underline{3200 \text{ V/V}}$$

With a subsequent stage having a 100kΩ input resistance,

$$A_d = G_m (R_o \parallel 100k\Omega) = \underline{188.2 \text{ V/V}}$$

even through its base-collector junction is forward biased by 0.4V)

$$R_{icm} \approx (\beta + 1) [r_{os} \parallel r_{oi} \parallel r_{oz}] = 151 \times (400 \parallel 800 \parallel 800) = \underline{30M\Omega}$$

7.68

$$G_m = \frac{I/2}{V_T} = \frac{5\text{mA}}{V}$$

$$I = \underline{250\mu\text{A}}$$

$$R = \frac{5 - (-5) - V_{BE}}{I} = \frac{9.3}{0.25} = \underline{37.2k\Omega}$$

$R_{id} = (\beta + 1) 2r_e$ where,

$$r_e = \frac{V_T}{I/2} = \frac{25\text{mV}}{0.125\text{mA}} = 200\Omega$$

$$\rightarrow R_{id} = 151 \times 2 \times 0.2 = \underline{60.4k\Omega}$$

$$r_o = \frac{V_A}{I_c} = \frac{100}{0.125} = 800k\Omega$$

$$R_o = \frac{r_o}{2} = \underline{400k\Omega}$$

$$A_d = g_m R_o = 5 \times 400 = \underline{2000 \text{ V/V}}$$

$$I_B = \frac{I/2}{\beta + 1} = \frac{125}{151} = \underline{0.83\mu\text{A}}$$

$$V_{icm}|_{\max} \approx V_{C1} + 0.4\text{V} = 5 - 0.7 + 0.4 = \underline{4.7\text{V}}$$

$$V_{icm}|_{\min} = V_{B5} - 0.4 + 0.7 = -4.3 - 0.4 + 0.7 = \underline{-4\text{V}}$$

Thus, the input common-mode range is -4V to +4.7V (where we have assumed that a transistor remains active

CONT.

For $R_E = 100\Omega$

$$G_m = \frac{\alpha}{V_T (I/2 + R_E)} = 5\text{mA/V}$$

$$I = \underline{500\mu\text{A}}$$

$$R = \frac{5 - (-5) - V_{BE}}{I} = \frac{9.3}{0.5} = \underline{18.6k\Omega}$$

$R_{id} = (\beta + 1)(2r_e + 2R_E)$ where

$$r_e = \frac{V_T}{I/2} = \frac{25\text{mV}}{0.25\text{mA}} = 100\Omega$$

$$\rightarrow R_{id} = 151 \times (2 \times 100 + 2 \times 100) = \underline{60.4k\Omega}$$

$$r_o = \frac{V_A}{I_c} = \frac{100}{0.25} = 400k\Omega$$

$$R_o = \frac{r_o}{2} = \underline{200k\Omega}$$

$$A_d = G_m R_o = 5 \times 200 = \underline{1000 \text{ V/V}}$$

$$I_B = \frac{I/2}{\beta + 1} = \frac{250}{151} = \underline{1.66\mu\text{A}}$$

$$V_{icm}|_{\max} = V_{C1} + 0.4\text{V} = 5 - 0.7 + 0.4 = \underline{4.7\text{V}}$$

$$V_{icm}|_{\min} = V_{B5} - 0.4 + (I/2)R_E + 0.7 = -4.3 - 0.4 + 0.05 + 0.7 = \underline{-3.95\text{V}}$$