

Solutions to Selected Problems (Problem Set 5)


Chapter 7: 7.1, 7.2, 7.8, 7.9, 7.11, 7.13, 7.16, 7.17, 7.62, 7.63

Microelectronic Circuits – 5th Edition – Sedra/Smith
 Copyright© 2004 by Oxford University Press, Inc.
DO NOT DUPLICATE

7.1

$V_{DD} = V_{SS} = 2.5V$
 $K_n' \frac{W}{L} = 3 \frac{mA}{V^2}$; $V_{tn} = 0.7V$
 $I = 0.2mA$; $R_D = 5k\Omega$

(a) $V_{ov} = \sqrt{I / K_n' W/L}$
 $= \sqrt{0.2/3} = \underline{0.26V}$
 $V_{GS} = V_{ov} + V_{t} = 0.26 + 0.7 = \underline{0.96V}$

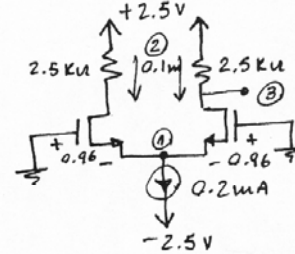(b) 

① $V_{S1} = V_{S2} = V_{cm} - V_{GS}$
 $= 0 - 0.96 = \underline{-0.96V}$

② $I_{D1} = I_{D2} = \frac{I}{2} = 0.1mA$

③ $V_{D1} = V_{D2} = V_{DD} - \frac{I}{2} \times R_D$
 $= +2.5 - 0.1 \times 2.5 = \underline{2.25V}$

(c) If $V_{cm} = +1V$
 $V_{S1} = V_{S2} = +1 - 0.96 = \underline{0.04V}$
 $I_{D1} = I_{D2} = 0.1mA$
 $V_{D1} = V_{D2} = \underline{2.25V}$

(d) If $V_{cm} = -1V$
 $V_{S1} = V_{S2} = -1 - 0.96 = \underline{-1.96V}$
 $I_{D1} = I_{D2} = 0.1mA$
 $V_{D1} = V_{D2} = \underline{2.25V}$

(e) $V_{CMmax} = V_t + V_{DD} - \frac{I}{2} R_D$
 $= 0.7 + 2.5 - 0.1 \times 2.5 = \underline{+2.95V}$

(f) $V_{CMmin} = -V_{SS} + V_{CS} + V_t + V_{ov}$
 $= -2.5 + 0.3 + 0.7 + 0.26 = \underline{-1.24V}$

$V_{Smin} = V_{CMmin} - V_{GS}$
 $= -1.24 - 0.96 = \underline{-2.2V}$

7.2

(a) $V_{ov} = -\sqrt{I / K_p' (W/L)}$
 $= -\sqrt{0.7/3.5} = \underline{-0.45V}$
 $V_{GS} = V_{ov} + V_t = -0.45 - 0.8 = \underline{-1.25V}$
 $V_{S1} = V_{S2} = V_G - V_{GS}$
 $= 0 + 1.25 = \underline{+1.25V}$
 $V_{D1} = V_{D2} = \frac{I}{2} \times R_D - V_{DD}$
 $= \frac{0.7 \times 2}{2} - 2.5 = \underline{-1.8V}$

(b) For Q_1 and Q_2 to remain in saturation:
 $V_{DS} \leq V_{GS} - V_t$
 $\rightarrow V_{CM} \geq \left(\frac{I}{2} R_D - V_{DD}\right) + V_t$
 $V_{CMmin} = \frac{0.7 \times 2}{2} - 2.5 - 0.8 = \underline{-2.6V}$

To allow sufficient voltage for the current source to operate properly:
 $V_{cm} \leq V_{SS} - V_{CS} + (V_t + V_{ov})$
 $\rightarrow V_{CMmax} = 2.5 - 0.5 - 1.25 = \underline{0.75V}$

7.8

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$

$$\frac{200}{2} = \frac{1}{2} \times 90 \times \frac{100}{1.6} (V_{GS} - 0.8)^2$$

$$\Rightarrow V_{GS} = \underline{1.19V}$$

$$g_m = \frac{2I_D}{V_{GS} - V_t} = \frac{2 \times 100}{(1.19 - 1)} = \underline{1.06 \frac{mA}{V}}$$

$$|v_{id}|_{\text{full current switching}} = \sqrt{2} (V_{GS} - V_t)$$

$$= \underline{0.27V}$$

To double this value, $V_{GS} - V_t$ must be doubled which means that I_D should be quadrupled. i.e. I changed to: 800 μ A

7.9

$$g_m = \frac{2I_D}{V_{ov}} \rightarrow 1m = \frac{I}{0.2}$$

$$\rightarrow I = \underline{0.2mA}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{ov}^2$$

$$100 = \frac{1}{2} \times 90 \times \frac{W}{L} \times (0.2)^2$$

$$\Rightarrow \frac{W}{L} = \underline{55.6}$$

7.11

$$V_{ov} = \sqrt{\frac{I}{K_n' \frac{W}{L}}} = \sqrt{\frac{0.5}{0.25 \times 50}} = \underline{0.2V}$$

$$g_m = \frac{I}{V_{ov}} = \frac{0.5mA}{0.2V} = \underline{2.5 \frac{mA}{V}}$$


$$r_o = \frac{V_A}{I_D} = \frac{10}{(0.5m/2)} = \underline{40k\Omega}$$

$$A_d = g_m \times (R_D \parallel r_o)$$

$$= 2.5 \frac{mA}{V} (4k\Omega \parallel 40k\Omega)$$

$$= \underline{9.09 V/V}$$

7.13

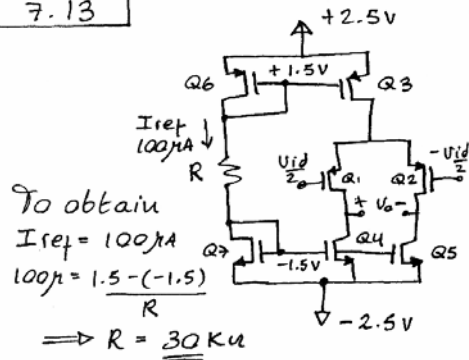

$$V_{GS_{7,4,5}} = -1.5 + 2.5 = \underline{1V}$$

$$V_{ov_{7,4,5}} = V_{GS} - V_{tn} = 1 - 0.7 = \underline{0.3V}$$

$$V_{GS_{6,3}} = 1.5 - 2.5 = \underline{-1V}$$

$$V_{ov_{6,3}} = -1 - (-0.7) = \underline{-0.3V}$$

The differential half circuit is an active-loaded common-source amplifier.

thus, for Q_1, Q_4 :

$$v_{o+} = \frac{v_{id}}{2} \times g_{m_1} (r_{o1} \parallel r_{o4})$$

For Q_2, Q_5 :

$$v_{o-} = -\frac{v_{id}}{2} \times g_{m_2} (r_{o2} \parallel r_{o5})$$

Since $r_{o1} = r_{o2} = r_{o4} = r_{o5} \equiv r_o$

$$v_{o+} - v_{o-} = v_{id} \times g_{m_{1,2}} \times \frac{r_o}{2}$$

$$\Rightarrow \frac{v_{o+} - v_{o-}}{v_{id}} = A_d = g_{m_{1,2}} \times \frac{r_o}{2}$$

$$= \frac{g_{m_{1,2}}}{2} \times \frac{V_{An}}{I_{D_{1,2}}}$$

$$= \frac{1}{2} \times 2 \frac{I_{D_{1,2}}}{V_{ov}} \times \frac{V_{An}}{I_{D_{1,2}}} = \frac{V_{An}}{V_{ov_{1,2}}}$$

thus:

$$80 = \frac{20}{|V_{ov_{1,2}}|} \rightarrow V_{ov_{1,2}} = \underline{0.25 \text{ V}}$$

phas.

Then $V_{GS1,2} = -0.25 - 0.7$
 $= -0.95V$

We have: $I_{D7} = I_{D6} = 100\mu A$

If we choose:

$I_{D3} = I_{D6} = 100\mu A //$

then $I_{D1} = I_{D2} = I_{D4} = I_{D5} = 50\mu A$

To obtain w/L ratios:

$I_D = \frac{1}{2} \mu_{Cox} (w/L) V_{ov}^2$

$\Rightarrow \frac{w}{L} = \frac{2I_D}{\mu_{Cox} V_{ov}^2}$

where:

$\mu_{nCox} = 90\mu A/V^2$

$\mu_{pCox} = 30\mu A/V^2$

For Q_7 :

$\left(\frac{w}{L}\right)_7 = \frac{2 \times 100\mu}{90\mu \times (0.3)^2} = 24.7$

For Q_4 and Q_5 :

$\left(\frac{w}{L}\right)_{4,5} = \frac{2 \times (100\mu/2)}{90\mu \times (0.3)^2} = 12.3$

For Q_1 and Q_2 :

$\left(\frac{w}{L}\right)_{1,2} = \frac{2 \times (100\mu/2)}{30\mu \times (0.25)^2} = 53.3$

For Q_6 and Q_3 :

$\left(\frac{w}{L}\right)_{6,3} = \frac{2 \times 100\mu}{30\mu \times (0.3)^2} = 74.1$

In summary, the results are:

	Q_1	Q_2	Q_3	Q_4	Q_5	Q_6	Q_7	
μ_{nCox}	30	30	30	90	90	30	90	$\mu A/V^2$
I_D	50	50	100	50	50	100	100	μA
V_{ov}	-0.25	-0.25	-0.3	0.3	0.3	-0.3	0.3	V
w/L	53.3	53.3	74.1	12.3	12.3	74.1	24.7	
V_{GS}	-0.95	-0.95	-1	1	1	-1	1	

7.16

$V_{ov} = -\sqrt{\frac{I}{K_p' w/L}} = -\sqrt{\frac{0.7mA}{3.5mA/V^2}}$
 $= -0.45V$

$g_m = \frac{I}{V_{ov}} = \frac{0.7mA}{0.45V} = 1.56 \frac{mA}{V}$

$|A_d| = g_m R_D = 1.56 \times 2 = 3.12 V/V$

$|A_{cm}| = \frac{R_D}{2R_{SS}} \left(\frac{\Delta R_D}{R_D}\right) = \frac{2}{2 \times 30} \times 0.02$
 $= 6.7 \times 10^{-4}$

$CMRR = \frac{3.12}{6.7 \times 10^{-4}} = 4680 \rightarrow 73.4 dB$

7.17

(a) $I_{D1} = I_{D2} = 1mA = 0.5mA$

$I_D = \frac{1}{2} K_n' \frac{w}{L} \cdot V_{ov}^2$

$\Rightarrow 0.5mA = \frac{1}{2} \times 2.5mA \times V_{ov}^2$

$\rightarrow V_{ov} = 0.632V$

$V_{ov} = V_{GS} - V_t = V_{GS} - 0.7$

$\rightarrow V_{GS} = 0.632 + 0.7$
 $= 1.332V$

To obtain $1mA$ over $R_{SS} = 1K\Omega$

$V_S = 1mA \times 1K = 1V$

$\rightarrow V_{cm} = V_S + V_{GS} = 1 + 1.332$
 $= 2.332V$

(b) $g_m = \frac{I}{V_{ov}} = \frac{1mA}{0.632V} = 1.6 \frac{mA}{V}$

Eqn. (7.45): $A_d = g_m \cdot R_D$

for $A_d = 8V/V$ $R_D = \frac{8}{1.6mA} = 5K\Omega$

(c) At the drains:


$$V_{D1} = V_{D2} = 5V - \frac{1\text{mA} \times 5\text{K}\Omega}{2} = \underline{\underline{2.5V}}$$

(d) Eqn. (7.39):

$$\frac{V_{o1}}{V_{i\text{cm}}} = \frac{-R_D}{\frac{1}{g_m} + 2R_{SS}}$$

$$\Rightarrow |A_{\text{cm}}| = \left| \frac{\Delta V_{D1}}{\Delta V_{\text{cm}}} \right| = \frac{5\text{K}}{\frac{1}{1.6\text{m}} + 2 \times 1\text{K}} = \underline{\underline{1.9 \text{ V/V}}}$$

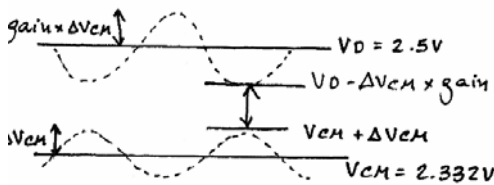(e) On the edge of the triode region:
 $V_G - V_D = V_t$



$$f: V_G - V_D = V_t$$

$$\Rightarrow V_{\text{cm}} + \Delta V_{\text{cm}} - V_D + \Delta V_{\text{cm}} |A_{\text{cm}}| = V_t$$

$$\Rightarrow 2.332 + \Delta V_{\text{cm}} - 2.5 + \Delta V_{\text{cm}} \cdot 1.9 = 0.7$$

$$2.9 \Delta V_{\text{cm}} = 0.868$$

$$\Delta V_{\text{cm}} = \underline{\underline{0.3V}}$$

7.62

For each transistor $I_D = I/2$.

From Eqn. (7.147): $f_{o2} = f_{o4} = f_o$
 $A_d = \frac{1}{2} g_m f_o$

but $g_m = \frac{2I_D}{V_{ov}}$ and $f_o = \frac{V_A}{I_D}$

$$\Rightarrow A_d = \frac{1}{2} \left(\frac{2I_D}{V_{ov}} \right) \frac{V_A}{I_D} = \frac{V_A}{V_{ov}}$$

$$\rightarrow 80 \text{ V/V} = 20 \text{ V} / V_{ov}$$

$$\rightarrow V_{ov} = 20/80 = 0.25 \text{ V}$$

Finally,

$$I = 2I_D = \frac{K'_W}{L} V_{ov}^2 = 3.2 \frac{\text{mA}}{\text{V}^2} (0.25 \text{ V})^2 = \underline{\underline{0.2 \text{ mA}}}$$

7.63

For all transistors $I_D = I/2$ and all r_o 's are equal.


$$V_{ov100} = \sqrt{\frac{2I_D}{K'_W/L}} = \sqrt{\frac{100\mu\text{A}}{0.2\text{mA/V}^2}} = 0.707 \text{ V}$$

$$V_{ov200} = \sqrt{\frac{400\mu\text{A}}{0.2\text{mA/V}^2}} = 1.414 \text{ V}$$

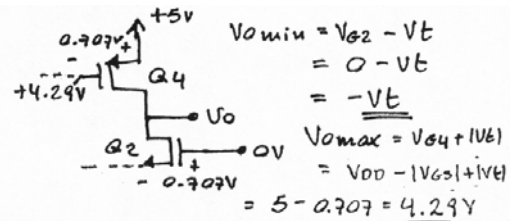(a) For $I = 100\mu\text{A}$:

Range of the differential mode is $-\sqrt{2} V_{ov} \leq V_{id} \leq \sqrt{2} V_{ov}$ (as in Eqn. (7.10))

But the range of V_o is limited by the requirement of keeping the transistors in saturation mode.



$$V_{o\text{min}} = V_{G2} - V_t = 0 - V_t = -V_t$$

$$V_{o\text{max}} = V_{G4} + |V_t| = V_{DD} - |V_{GS1}| + |V_t| = 5 - 0.707 = 4.29 \text{ V}$$

$$g_m = \frac{2I_D}{V_{ov}} \rightarrow g_{m1} = g_{m2} = \frac{100\mu\text{A}}{0.707} = 0.1414 \text{ mA/V}$$

$$f_o = \frac{V_A}{I_D} \Rightarrow f_{o2} = f_{o4} = f_o = \frac{20}{50\mu\text{A}} = 400 \text{ kHz}$$

$$R_o = f_{o2} || f_{o4} = \frac{1}{2} \times 400 \text{ kHz} = 200 \text{ kHz}$$

$$A_d = \frac{1}{2} g_m f_o = \frac{1}{2} \times (0.1414 \text{ mA/V}) (400 \text{ kHz})$$

$$A_d = \underline{\underline{28.28 \text{ V/V}}}$$

(b) For $I = 400 \mu\text{A}$:
Linear range of V_o

$$V_{o \min} = -V_{E1}$$

$$V_{o \max} = (5\text{V} - V_{GS}) + |V_{E1}| \\ = \underline{\underline{5 - 1 = 4\text{V}}}$$

$$g_m = \frac{2 \times 200 \mu\text{A}}{1.414} = \underline{\underline{0.28 \text{ mA/V}}}$$

$$r_o = 20 / (400 / 2) = \underline{\underline{100 \text{ k}\Omega}}$$

$$R_o = \frac{1}{2} 100 \text{ k}\Omega = \underline{\underline{50 \text{ k}\Omega}}$$

$$A_d = \frac{1}{2} (0.28 \text{ mA} \times 100 \text{ k}\Omega) = \underline{\underline{14 \text{ V/V}}}$$