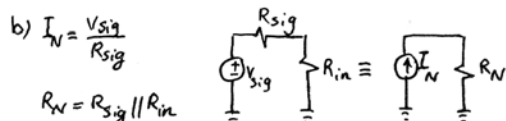


PROBLEM SET 6 - SOLUTION

Problem 1

6.54

$$a) R_{in} = \frac{R}{1-A} = \frac{R}{1-2} = -R \quad (\text{Miller's theorem})$$




$$R_N = R_{sig} \parallel R_{in}$$

IF $R_{sig} = R$ then:

$$R_N = R \parallel (-R) = \infty \Rightarrow I_L = I_N = \frac{V_{sig}}{R_{sig}} = \frac{V_{sig}}{R} \quad \text{Cont.}$$

KCL at A:

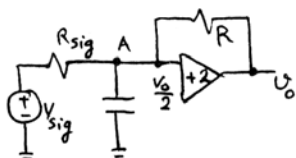

$$\frac{V_o - V_{sig}}{R_{sig}} + \frac{V_o}{2} \times CS + \frac{-V_o}{2R} = 0$$

$$\text{IF } R_{sig} = R \Rightarrow \frac{V_{sig}}{R} = \frac{V_o}{2} CS \Rightarrow \frac{V_o}{V_{sig}} = \frac{2}{RC S}$$

Problem 2

6.99

a) $I = \frac{1}{2} K_n' \frac{W}{L} V_{ov}^2 \Rightarrow \text{For same } I: \frac{V_{ov}^2}{V_{ov}^2} = \frac{(W/L)_a}{(W/L)_b}$
 For same I , if $\frac{W}{L}$ is divided by 4, $\frac{V_{ov}^2}{V_{ov}^2}$ is multiplied by 4, or equivalently
 then V_{ov}^2 is multiplied by 4, or equivalently
 Cont.

V_{ov} is doubled.

$g_m = \mu_n C_{ox} \frac{W}{L} V_{ov}$. Thus g_m for circuit (b) is half of the one for circuit (a).

$A_o = g_m r_o = \frac{2I_D}{V_{ov}} \times \frac{VA}{I_D} = \frac{2VA}{V_{ov}}$. Thus if L is multiplied by 4 and V_{ov} is halved, then A_o is doubled for circuit (b).

In summary, for circuit (b), V_{ov} is doubled, g_m is halved, A_o is doubled.

b) Each transistor in circuit (c) has the same overdrive voltage as the one in circuit (a). Referring to Eq. 6.129 and 6.30:

$$A_{vo} = -A_o^2 = -(g_m r_o)^2$$

$$G_m \approx g_{m1} = g_m \quad (\text{same as circuit (a)})$$

Note that for the transistors in circuit (c) the g_m and r_o are the same as the ones in circuit (a). Thus the intrinsic gain for circuit (c), $A_{vo} = -A_o^2$ where A_o is the intrinsic gain for circuit (a).

In general, circuit (c) has a higher output resistance and for the same V_{ov} of transistors it has lower output swing. The output swing is limited to $2V_{ov}$ on the low side for circuit (b) and (c) while it is only limited to V_{ov} for circuit (a).

PROBLEM 3

MOS Amplifiers

(a) MOS Common-Source Amplifier:


i) Midband voltage gain:

$$v_i = \frac{R_{in1}}{R_s + R_{in1}} v_s \approx v_s \quad (\text{since } R_{in1} \rightarrow \infty)$$

$$i_{d1} = g_{m1} v_i = g_{m1} v_s$$

$$v_o = -i_{d1} (R_{out1} \parallel R_L) = -g_{m1} (r_{o1} \parallel R_L) v_s$$

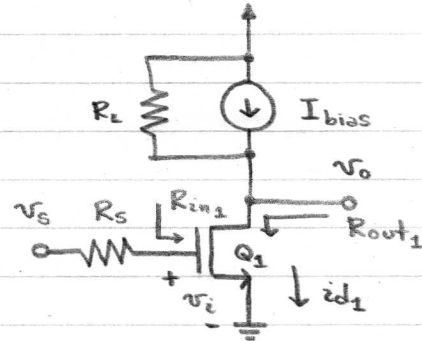
$$A_{m1} = \frac{v_o}{v_s} = -g_{m1} (r_{o1} \parallel R_L)$$



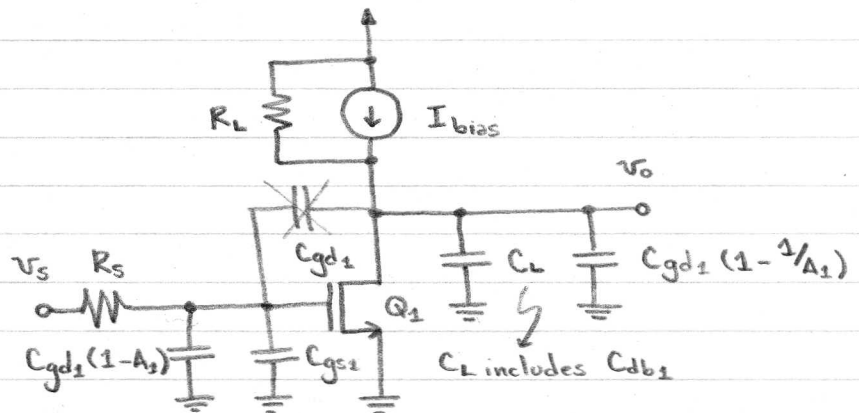ii) 3dB frequency:

Use Miller's theorem to split C_{gd1} into two caps. to ground ...

$$A_1 = A_{m1} \quad (\text{derived above})$$



@ the gate of Q_1

$$C_{g1} = C_{gs1} + C_{gd1} (1 - A_1)$$

$$R_{g1} = R_s$$

$$\tau_{g1} = R_{g1} C_{g1}$$

@ the drain of Q_1

$$C_{d1} = C_L + C_{gd1} (1 - 1/A_1)$$

$$R_{d1} = R_{out1} \parallel R_L = r_{o1} \parallel R_L$$

$$\tau_{d1} = R_{d1} C_{d1}$$

Using the open circuit time constants τ_{g1} & τ_{d1} , and assuming a dominant pole exists, the 3dB frequency can be derived as:

$$\omega_H = \frac{1}{\tau_{g1} + \tau_{d1}}$$


(b) MOS Common-Source Amplifier with Active Load:

i) Midband voltage gain:

$$i_{d1} = g_{m1} v_i = g_{m1} v_s \quad (R_{in1} \rightarrow \infty)$$

$$v_o = -i_{d1} (R_{out1} \parallel R_{out2}) = -g_{m1} (r_{o1} \parallel r_{o2}) v_s$$
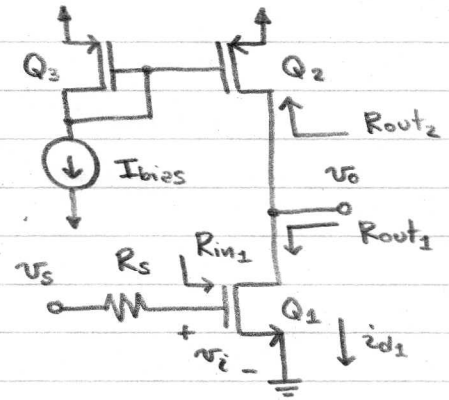
$$A_M = \frac{v_o}{v_s} = -g_{m1} (r_{o1} \parallel r_{o2})$$




ii) 3dB frequency:

Use Miller's theorem to split C_{gd1} into two caps. to ground...

$$A_1 = A_M \text{ (derived above)}$$

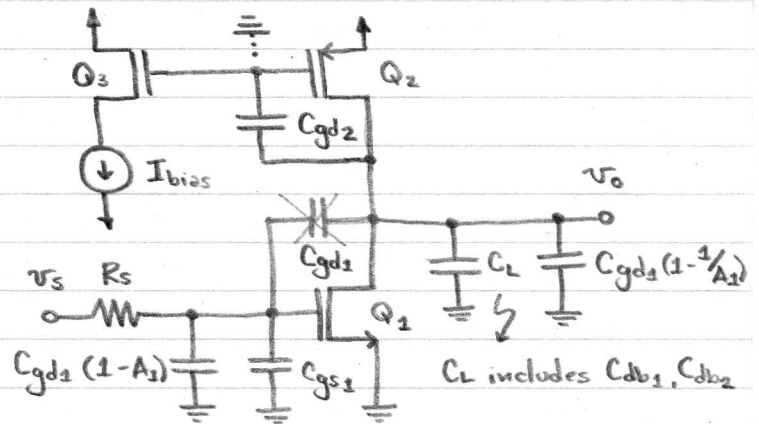Since V_{d2} is signal ground, C_{gd2} is connected between v_o and ground.



All remaining capacitances ($C_{gs3}, C_{gd3}, C_{db3}, C_{gs2}$) are outside the signal path and do not affect the response.

@ the gate of Q1

$$C_{g1} = C_{gs1} + C_{gd1}(1 - A_1)$$

$$R_{g1} = R_s$$

$$\tau_{g1} = R_{g1} C_{g1}$$

@ the drain of Q1

$$C_{d1} = C_L + C_{gd2} + C_{gd1}(1 - 1/A_1)$$

$$R_{d1} = R_{out1} \parallel R_{out2} = r_{o1} \parallel r_{o2}$$

$$\tau_{d1} = R_{d1} C_{d1}$$

Assuming a dominant pole exists, the 3dB frequency can be derived as:

$$\omega_H = \frac{1}{\tau_{g1} + \tau_{d1}}$$


(c) MOS Cascode Amplifier :

i) Midband voltage gain :

$$i_{d1} = g_{m1} v_i = g_{m1} v_s \quad (R_{in1} \rightarrow \infty)$$

$$v_o = -i_{d1} (R_{out2} \parallel R_L) \quad R_{out2} \approx g_{m2} v_{o2} r_{o2}$$
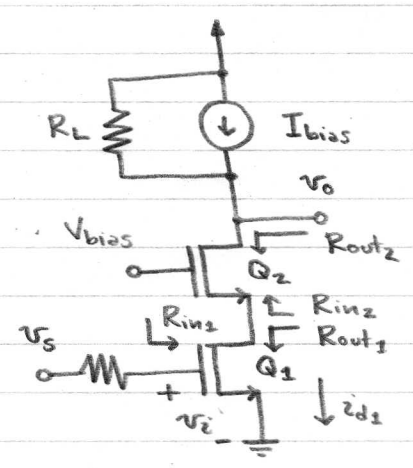
$$A_M = \frac{v_o}{v_s} = -g_{m1} (R_{out2} \parallel R_L)$$




ii) 3dB frequency :

Use Miller's theorem to split C_{gd1} into two caps. to ground...

$$A_1 = -g_{m1} (R_{out2} \parallel R_{in2})$$

$$R_{out1} = r_{o1}$$
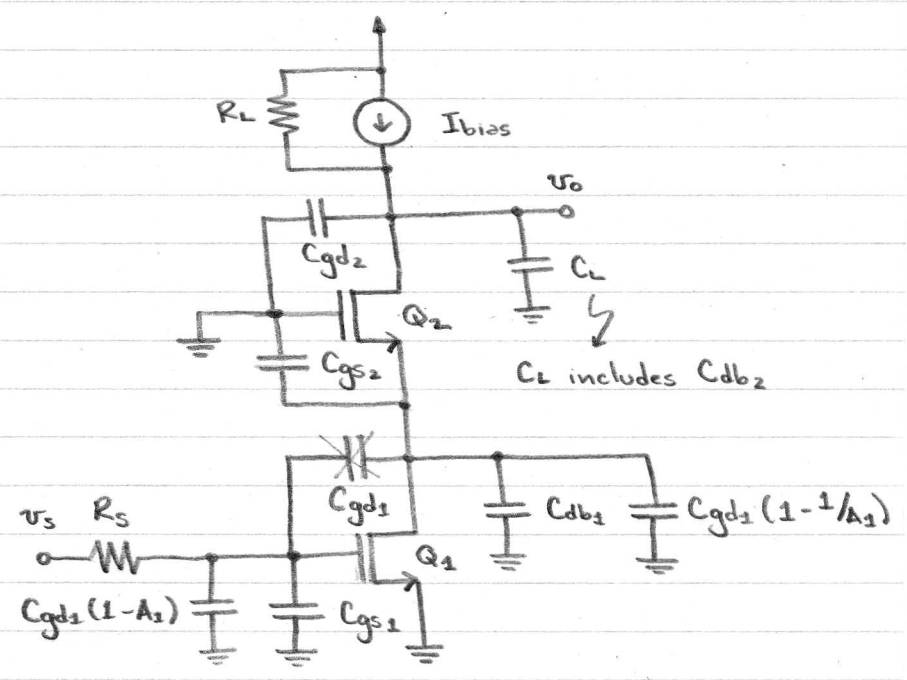
$$R_{in2} \approx \frac{1}{g_{m2}} \left(1 + \frac{R_L}{r_{o2}} \right)$$



@ the gate of Q_1
 $C_{g1} = C_{gs1} + C_{gd1}(1-A_1)$
 $R_{g1} = R_s$
 $\tau_{g1} = R_{g1} C_{g1}$

@ the drain of Q_1
 $C_{d1} = C_{db1} + C_{gd1}(1-1/A_1) + C_{gs2}$
 $R_{d1} = R_{in2} \parallel r_{o1}$
 $\tau_{d1} = R_{d1} C_{d1}$

@ the drain of Q_2
 $C_{d2} = C_L + C_{gd2}$
 $R_{d2} = R_{out2} \parallel R_L$
 $\tau_{d2} = R_{d2} C_{d2}$

Assuming a dominant pole exists, the 3dB frequency can be derived as :

$$\omega_H = \frac{1}{\tau_{g1} + \tau_{d1} + \tau_{d2}}$$


BJT Amplifiers

(a) BJT Common-Emitter Amplifier

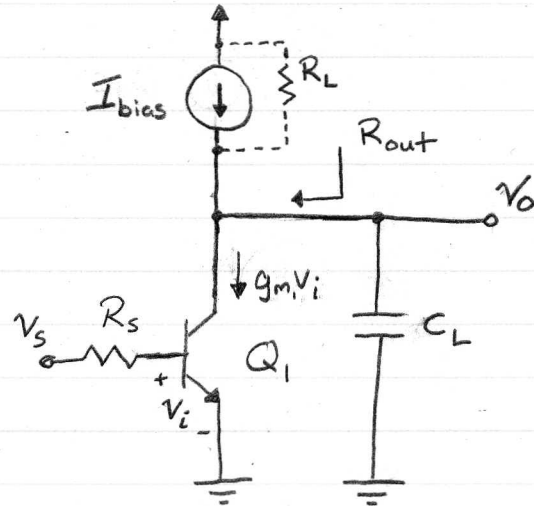i) Midband Voltage Gain

$$\bullet v_i = \frac{r_{\pi_1}}{R_s + r_{\pi_1}} v_s$$

$$\text{where } r_{\pi_1} = (\beta + 1)r_{e_1}$$




- Short-Circuit Transconductance:

$$G_m \triangleq \left. \frac{i_o}{v_s} \right|_{v_o=0} = \frac{-g_m v_i}{\frac{R_s + r_{\pi_1}}{r_{\pi_1}} v_i} = \frac{-g_m}{1 + R_s/r_{\pi_1}}$$

- $R_{out} = R_L \parallel r_{o_1}$

- Midband Voltage Gain:

$$A_M \triangleq \frac{v_o}{v_s} = G_m R_{out} = \frac{-g_m}{1 + R_s/r_{\pi_1}} R_L \parallel r_{o_1}$$

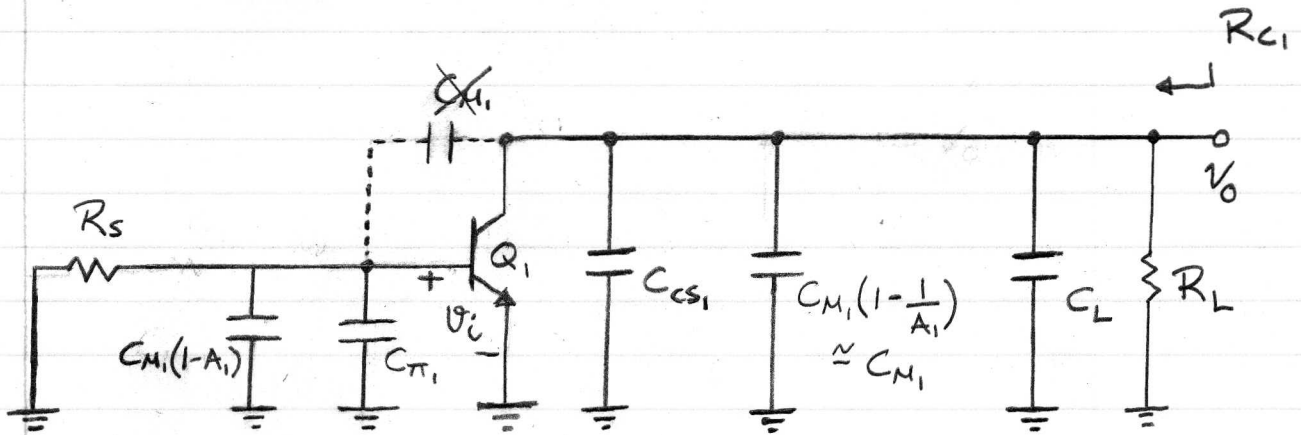ii) 3 dB Frequency

where $A_1 \triangleq \frac{v_{c1}}{v_{b1}} = \frac{v_o}{v_i} = -g_{m_1}(r_{o1} \parallel R_L)$

1) Apply Miller's theorem

⇒ All capacitors are now connected between a node and GND (shown on diagram)

2) Find Open-Circuit Time Constants associated with each node:

• C_1 (output) node

$$C_{c_1} = C_{c_1} + C_{M_1}\left(1 - \frac{1}{A_1}\right) + C_L$$

Resistance seen: $R_{c_1} = r_{o1} \parallel R_L$

$$\omega_{c_1} = 1/\tau_{c_1} = 1/(C_{c_1}R_{c_1})$$

• B1 node

$$C_{B1} = C_{M1}(1 - A_1) + C_{\pi_1}$$

$$\text{Resistance seen: } R_{B1} = r_{\pi_1} \parallel R_S$$

$$\Rightarrow \omega_{B1} = \frac{1}{\tau_{B1}} = \frac{1}{(C_{B1} R_{B1})}$$

3) Find ω_H

Assuming a Dominant Pole exists:

$$\omega_H = \frac{1}{\tau_{C1} + \tau_{B1}}$$


(b) BJT Common-Emitter Amplifier with Active Load

i) Midband Voltage Gain

$$\bullet v_i = \frac{r_{\pi_1}}{R_s + r_{\pi_1}} v_s$$

where

$$r_{\pi_1} = (\beta + 1)r_{e_1}$$

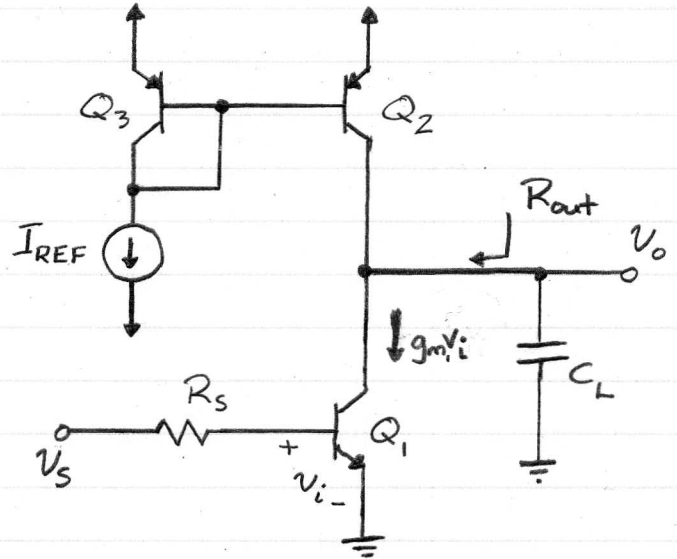

• Short-Circuit Transconductance


$$G_m \triangleq \left. \frac{i_o}{v_s} \right|_{v_o=0} = \frac{-g_{m_1} v_i}{\frac{R_s + r_{\pi_1}}{r_{\pi_1}} v_i} = \frac{-g_{m_1}}{1 + R_s / r_{\pi_1}}$$

$$\bullet R_{out} = r_{o_2} \parallel r_{o_1}$$

• Midband Voltage Gain

$$A_M \triangleq \frac{v_o}{v_s} = G_m R_{out} = \frac{-g_{m_1} r_{o_2} \parallel r_{o_1}}{1 + R_s / r_{\pi_1}}$$

ii) 3dB Frequency

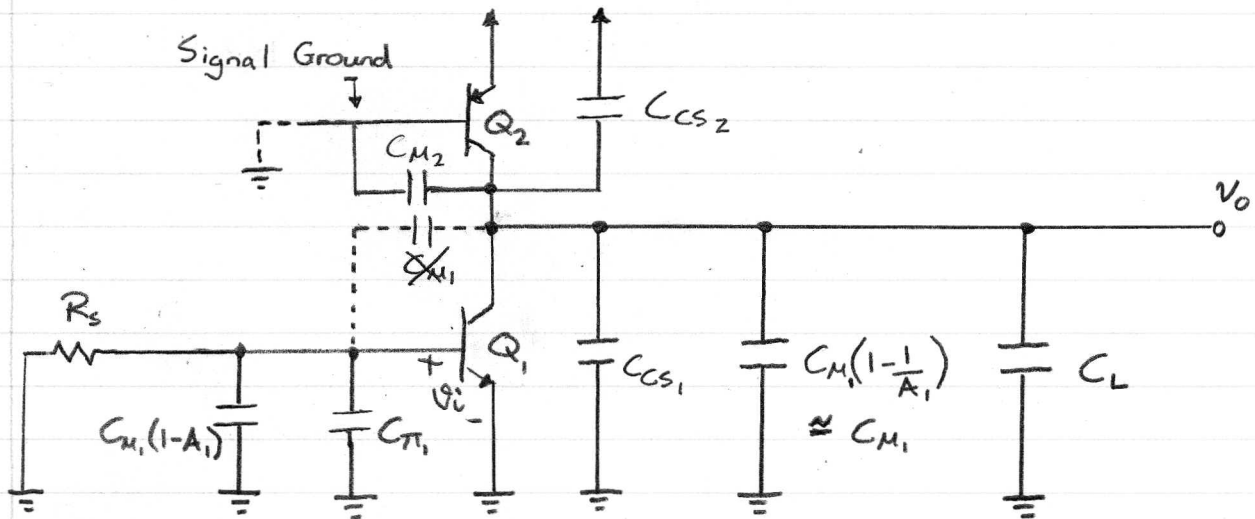

where $A_1 \triangleq \frac{v_{C1}}{v_{B1}} = \frac{v_0}{v_i} = -g_{m1} (r_{o1} \parallel r_{o2})$

1) Apply Miller's theorem

\Rightarrow All capacitors are now connected between a node and GND (shown on diagram)

2) Find Open-Circuit Time Constants associated with each node:

- C_1 (output) node

$$C_{C1} = C_{CS1} + C_{M1}(1 - \frac{1}{A_1}) + C_L + C_{CS2} + C_{M2}$$

Resistance seen: $R_{C1} = r_{o1} \parallel r_{o2}$

$$\Rightarrow \omega_{C1} = \frac{1}{\tau_{C1}} = \frac{1}{(C_{C1} R_{C1})}$$

• B1 node

$$C_{B1} = C_{\mu_1}(1 - A_1) + C_{\pi_1}$$

Resistance seen: $R_{B1} = r_{\pi_1} \parallel R_S$

$$\Rightarrow \omega_{C2} = \frac{1}{\tau_{C2}} = \frac{1}{(C_{B1} R_{B1})}$$

3) Find ω_H

Assuming a Dominant Pole exists:


$$\omega_H = \frac{1}{\tau_{C1} + \tau_{C2}}$$

(c) BJT Cascode Amplifier

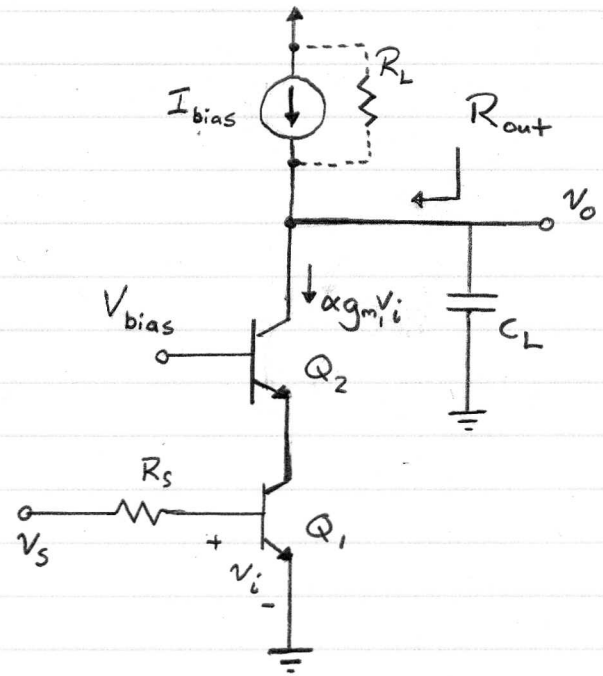i) Midband Voltage Gain

$$\bullet v_i = \frac{r_{\pi_1}}{R_s + r_{\pi_1}} v_s$$

$$\text{where } r_{\pi_1} = (\beta + 1)r_{e1}$$




• Short-Circuit Transconductance

$$G_m \triangleq \left. \frac{i_o}{v_s} \right|_{v_o=0} = \frac{-\alpha g_{m1} v_i}{\frac{R_s + r_{\pi_1}}{r_{\pi_1}} v_i} = \frac{-\alpha g_{m1}}{1 + R_s / r_{\pi_1}}$$

$$\bullet R_{out} = R_L \parallel \beta_2 r_{o2}$$

• Midband Voltage Gain

$$A_M \triangleq \frac{v_o}{v_s} = G_m R_{out} = \frac{-\alpha g_{m1}}{1 + R_s / r_{\pi_1}} R_L \parallel \beta_2 r_{o2}$$

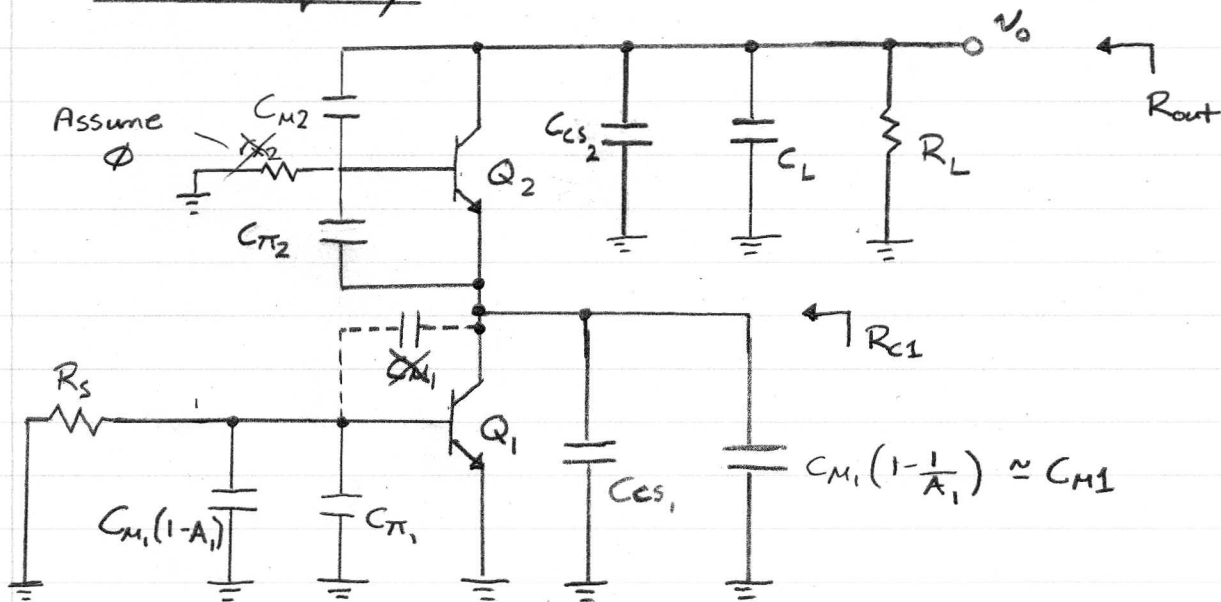ii) 3 dB Frequency

$$\text{where } A_1 \triangleq \frac{V_{C1}}{V_{B1}} = \frac{v_{o1}}{v_i} = -g_{m1} \left(r_{o1} \parallel r_{e2} \left[\frac{r_{o2} + R_L}{r_{o2} + R_L / (\beta_2 + 1)} \right] \right)$$

1) Apply Miller's theorem

⇒ All capacitors now connected between a node and GND (shown on diagram)

2) Find Open-Circuit Time Constants associated with each node:-

• C_2 (output) node

$$C_{c2} = C_{cs2} + C_{M2} + C_L$$

$$\text{Resistance seen: } R_{c2} = R_L \parallel \beta_2 r_{o2}$$

$$\Rightarrow \omega_{c2} = \frac{1}{\tau_{c2}} = \frac{1}{(C_{c2} R_{c2})}$$

• C1 node

$$C_{c1} = C_{\pi 2} + C_{cs1} + C_{M1} \left(1 - \frac{1}{A_1}\right)$$

Resistance seen:

$$R_{c1} = r_{o1} \parallel r_{e2} \left[\frac{r_{o2} + R_L}{r_{o2} + R_L / (\beta_2 + 1)} \right]$$

$$\Rightarrow \omega_{c1} = \frac{1}{\tau_{c1}} = \frac{1}{(C_{c1} R_{c1})}$$

• B1 node

$$C_{B1} = C_{M1} (1 - A_1) + C_{\pi 1}$$

Resistance seen: $R_{B1} = r_{\pi 1} \parallel R_S$

$$\Rightarrow \omega_{B1} = \frac{1}{\tau_{B1}} = \frac{1}{(C_{B1} R_{B1})}$$

3) Find ω_H

Assuming a Dominant Pole exists

$$\omega_H = \frac{1}{\tau_{c2} + \tau_{c1} + \tau_{B1}}$$

PROBLEM 4

$$I_{c7} \approx 4 \cdot \frac{1}{1 + 2/\beta^2} \cdot I_{bias} = 4 \cdot \frac{1}{1 + 2/50^2} \cdot 0.5 \text{ mA} \approx 2 \text{ mA}$$

(6.191) → base-current compensation

$$I_{c10} \approx \frac{1}{1 + 2/\beta^2} \cdot I_{bias} \approx 0.5 \text{ mA}$$

i) Small-signal voltage gain:

$$I_{E2} = I_{E1} = I_{c7} / 2 \approx 1 \text{ mA}$$

$$I_{Eq} \approx I_{c10} \approx 0.5 \text{ mA}$$

$$i_{e1,2} = \frac{v_{id}}{2r_{e1}} \rightarrow i_{c2} = \alpha i_{e1,2}$$

$$v_{o1} = 2i_{c2}(r_{o2} \parallel r_{o4} \parallel R_{inq}) \rightarrow i_{c4} \approx i_{c2}$$

$$A_{v1} = \frac{v_{o1}}{v_{id}} \approx \frac{r_{o2} \parallel r_{o4} \parallel R_{inq}}{r_{e1}} \quad (\alpha \approx 1)$$

$$r_{e1} = \frac{V_T}{I_{E1}} = \frac{25 \text{ mV}}{1 \text{ mA}} = 25 \Omega$$

$$r_{o2} = \frac{|V_A|}{I_{c2}} \approx \frac{80}{1 \text{ mA}} = 80 \text{ k}\Omega$$

$$r_{eq} = \frac{V_T}{I_{Eq}} = \frac{25 \text{ mV}}{0.5 \text{ mA}} = 50 \Omega$$

$$r_{o4} = \frac{|V_A|}{I_{c4}} \approx \frac{125}{1 \text{ mA}} = 125 \text{ k}\Omega$$

$$R_{inq} = (\beta + 1)(r_{eq} + R_{Eq})$$


$$= 251 \cdot (50 + 1.4 \text{ k})$$

$$= 364 \text{ k}\Omega$$

$$A_{v1} \approx \frac{r_{o2} \parallel r_{o4} \parallel R_{inq}}{r_{e1}}$$

$$= \frac{80 \text{ k} \parallel 125 \text{ k} \parallel 364 \text{ k}}{25}$$


$$= 1.72 \text{ kV/V}$$

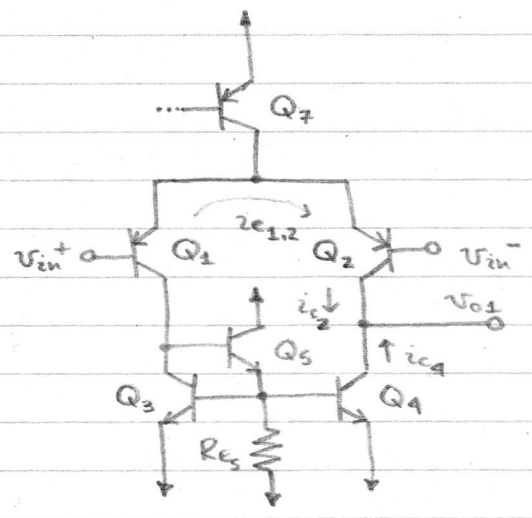

$$i_{eq} = \frac{v_{i2}}{r_{eq} + R_{Eq}} \rightarrow i_{c9} = \alpha i_{eq}$$

$$v_{out} = -i_{c9} (R_{o9} \parallel r_{o10}) \\ \approx -i_{c9} (r_{o9} \parallel r_{o10}) \quad (\text{according to prob. stmt.})$$
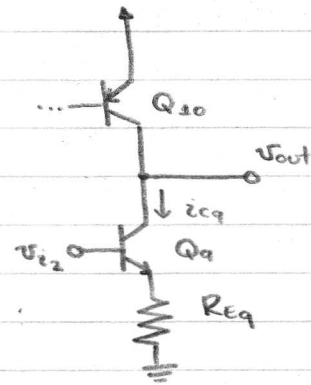
$$A_{v2} = \frac{v_{out}}{v_{i2}} \approx -\frac{r_{o9} \parallel r_{o10}}{r_{eq} + R_{Eq}} \quad (\alpha \approx 1)$$



$$r_{o9} = \frac{|V_A|}{I_{c9}} = \frac{125}{0.5\text{mA}} = 250 \text{ k}\Omega$$

$$r_{o10} = \frac{|V_A|}{I_{c10}} = \frac{80}{0.5\text{mA}} = 160 \text{ k}\Omega$$

$$A_{v2} \approx -\frac{(r_{o9} \parallel r_{o10})}{r_{eq} + R_{Eq}} \\ = -\frac{(250\text{k}\Omega \parallel 160\text{k}\Omega)}{50 + 1.4\text{k}} \\ = -67.3 \text{ V/V}$$

The voltage gain is then equal to:

$$\frac{v_{out}}{v_{in}} = A_{v1} \cdot A_{v2} = -1.72\text{k} \cdot 67.3 = 115.8 \text{ kV/V}$$

ii) Input common-mode range:

$$V_{CM,max} = V_{CC} - |V_{CEsat1}| - |V_{BEon1,2}| \\ = 3.3 - 0.3 - 0.7 \\ = 2.3 \text{ V}$$

$$V_{CM,min} = -V_{EE} + |V_{BEon3,4}| + |V_{BEon5}| + |V_{CEsat2}| - |V_{BEon1}| \\ = -3.3 + 0.7 + 0.7 + 0.3 - 0.7 \\ = -2.3 \text{ V}$$