

SOLUTION - Problem Set 7

6.105

Refer to Fig. 6.43.

$$I = \frac{1}{2} \mu_p C_o \frac{W}{L} V_{ov}^2 \Rightarrow 100 \mu A = \frac{1}{2} \times 60 \frac{W}{L} 0.2^2$$

$$\Rightarrow \frac{W}{L} = 83.3$$

$$V_{SG1} = V_{DD} - V_{BIAS1} = 3.3 - V_{BIAS1}$$

$$V_{ov} = V_{SG1} - |V_{tp}| = 0.2 \Rightarrow 0.2 = 3.3 - V_{BIAS1} - 0.8$$

$$\Rightarrow V_{BIAS1} = 2.3 V$$

For Maximum swing: $V_{SD1} = V_{ov} \Rightarrow V_{D1} = 3.3 - 0.2 = 3.1 V$
 $\Rightarrow V_{D1} = 3.1 V$

then: $V_{SG2} - |V_{tp}| = V_{ov} \Rightarrow 3.1 - V_{BIAS2} - 0.8 = 0.2$
 $V_{BIAS2} = 2.1 V$

The highest allowable voltage at the output
 is $V_{DD} - V_{ov} - V_{ov} = 3.3 - 0.2 - 0.2 = 2.9 V$

$$R_o \approx g_m r_o r_o \quad (\text{Eq. 6.141})$$

$$g_m = \frac{2I_o}{V_{ov}} = \frac{200 \mu}{0.2} = 1 m A/V \quad r_o = \frac{V_A}{I_D} = \frac{5}{100 \mu} = 50 k\Omega$$

$$R_o = 4 \times 50 \times 50 = 2.5 M\Omega$$

$$\underline{R_o = 2.5 M\Omega}$$

SOLUTION - PROBLEM SET 7 (contd.)

PROBLEM 1

Figure 1

A)

$$I_{E1,2} = \frac{I}{2}$$

$$I_{E3,4} = I_{E1,2} = \frac{I}{2}$$

B)

$$R_i = (\beta + 1) (2 r_{e1,2})$$

Assume $V_{A,npn} = V_{A,pnp} \Rightarrow r_{o,npn} = r_{o,pnp} \triangleq r_o$

$$R_o = R_{o4} \parallel R_{o7}$$

where

$$R_{o7} = \frac{\beta}{2} r_o \quad \text{Wilson current mirror}$$

$$R_{o4} \simeq r_o (1 + \beta) \simeq \beta r_o \quad \text{assuming } r_o \gg r_\pi$$

$$\Rightarrow R_o = \frac{\beta}{3} r_o$$

Figure 2

A)

$$I_{E1,2} = \frac{I}{2}$$

$$I_{E3,4} = \frac{3}{4} I - I_{E1,2} = \frac{1}{4} I$$

B)

- $R_i = (\beta + 1)(2r_{e1,2})$

- Assume $V_{A,npn} = V_{A,pnp} \Rightarrow r_{o,npn} = r_{o,pnp} \triangleq r_o$

$$R_o = R_{o4} \parallel R_{o5}$$

where

$$R_{o5} = \frac{\beta}{2} r_o \quad \text{Wilson current mirror}$$

$$R_{o4} = r_{o4} \left[1 + g_{m4} \left((r_{o2} \parallel R_L) \parallel r_{\pi4} \right) \right] \quad \begin{array}{l} \text{where } R_L \text{ is the output} \\ \text{resistance of source } \left(\frac{3}{4} I \right) \end{array}$$

$$\simeq r_o(1+\beta) \simeq \beta r_o \quad \text{assuming } R_L \gg r_o \text{ and } r_o \gg r_{\pi}$$

$$\Rightarrow R_o = \frac{\beta}{3} r_o$$

Figures 1 and 2


B) (contd.)

$$\cdot i_e = \frac{v_{in}}{2 r_{e1,2}} \Rightarrow i_c = \alpha i_e = \frac{1}{2} g_{m1,2} v_{in}$$

$$\Rightarrow i_{out} = 2 i_c = g_{m1,2} v_{in}$$

$$\Rightarrow G_m \triangleq \left. \frac{i_{out}}{v_{in}} \right|_{R_L=0} = g_{m1,2}$$

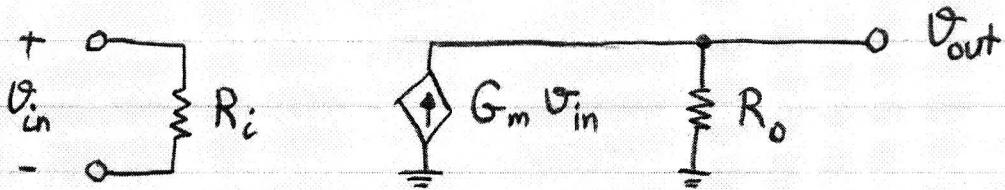Equivalent Transconductance Circuit Model:



$$\cdot A_v \triangleq \left. \frac{v_{out}}{v_{in}} \right|_{R_L=\infty} = G_m R_o = (g_{m1,2}) \left(\frac{1}{3} \beta R_o \right)$$

Figure 1

c)

$$\underline{V_{BIAS,min}} = \underline{V_{BEon}} + \underline{V_{CEsat}} + \underline{V_{CS}} - \underline{V_{EE}}$$

$$\underline{V_{BC1,2}} = \underline{V_{IN}} - (\underline{V_{BIAS}} - \underline{V_{BEon3,4}}) \leq \underline{V_{BCon1,2}}$$

$$\Rightarrow \underline{V_{INmax}} = \underline{V_{BIAS}} - \underline{V_{BEon}} + \underline{V_{BCon}} = \underline{V_{BIAS}} - \underline{V_{CEsat}}$$

$$\underline{V_{BE1,2}} = \underline{V_{IN}} - (-\underline{V_{EE}} + \underline{V_{CS}}) \geq \underline{V_{BEon}}$$

$$\Rightarrow \underline{V_{INmin}} = -\underline{V_{EE}} + \underline{V_{CS}} + \underline{V_{BEon}}$$

$$\underline{V_{CB7}} = \underline{V_o} - (\underline{V_{CC}} - |\underline{V_{EBon6}}| - |\underline{V_{EBon7}}|) \leq |\underline{V_{BCon7}}|$$

$$\Rightarrow \underline{V_{OUTmax}} = \underline{V_{CC}} - |\underline{V_{ECsat7}}| - |\underline{V_{EBon6}}| = \underline{V_{CC}} - (\underline{V_{BEon}} + \underline{V_{CEsat}})$$

$$\underline{V_{BC4}} = \underline{V_{BIAS}} - \underline{V_o} \leq \underline{V_{BCon4}}$$

$$\Rightarrow \underline{V_{OUTmin}} = \underline{V_{BIAS}} - \underline{V_{BCon}}$$

Figure 2

c)

$$\cdot V_{BIAS, \max} = V_{CC} - V_{CS} - V_{BEon}$$

$$\cdot V_{BC1,2} = V_{IN} - (V_{BIAS} + |V_{BEon3,4}|) \leq V_{BCon1,2}$$

$$\Rightarrow V_{IN\max} = V_{BIAS} + V_{BEon} + V_{BCon} = V_{BIAS} + 2V_{BEon} - V_{CEsat}$$

$$\cdot V_{BE1,2} = V_{IN} - (-V_{EE} + V_{CS}) \geq V_{BEon1,2}$$

$$\Rightarrow V_{IN\min} = -V_{EE} + V_{CS} + V_{BEon}$$

$$\cdot V_{CB4} = V_{OUT} - V_{BIAS} \leq |V_{CBon4}|$$

$$\Rightarrow V_{OUT\max} = V_{BIAS} + V_{BCon}$$

$$\cdot V_{BC5} = (V_{BEon5} + V_{BEon7} - V_{EE}) - V_{OUT} \leq V_{BCon5}$$

$$\Rightarrow V_{OUT\min} = -V_{EE} + V_{BEon} + V_{CEsat}$$

C) (contd.)

$\therefore \text{If } V_{CS} = |V_{CE\text{sat}} + V_{BE\text{on}}|$, then for proper operation:

Figure 1 : Cascade Amplifier

$$\begin{aligned} -V_{EE} + 2V_{BE\text{on}} + 2V_{CE\text{sat}} &\leq V_{BIAS} \\ -V_{EE} + 2V_{BE\text{on}} + V_{CE\text{sat}} &\leq V_{IN} \leq V_{BIAS} - V_{CE\text{sat}} \\ V_{BIAS} - V_{BE\text{on}} + V_{CE\text{sat}} &\leq V_{OUT} \leq V_{CC} - (V_{BE\text{on}} + V_{CE\text{sat}}) \end{aligned}$$

Figure 2 : Folded-Cascade Amplifier

$$\begin{aligned} V_{BIAS} &\leq V_{CC} - 2V_{BE\text{on}} - V_{CE\text{sat}} \\ -V_{EE} + 2V_{BE\text{on}} + V_{CE\text{sat}} &\leq V_{IN} \leq V_{BIAS} + 2V_{BE\text{on}} - V_{CE\text{sat}} \\ -V_{EE} + V_{BE\text{on}} + V_{CE\text{sat}} &\leq V_{OUT} \leq V_{BIAS} + V_{BE\text{on}} - V_{CE\text{sat}} \end{aligned}$$

Problem 2

$$\text{a) } V_{\text{OUTmax}} = V_{\text{CC}} - (V_{\text{BEon}} + V_{\text{CEsat}})$$

$$= 5 - (0.7 + 0.3) = \underline{\underline{4V}}$$

$$\text{b) } V_{\text{OUTbias}} = V_{\text{OUTmax}} - 1.5V = 4 - 1.5 = \underline{\underline{2.5V}}$$

$$\text{c) } V_{\text{OUTmin}} = V_{\text{OUTbias}} - 1.5V = \underline{\underline{1V}}$$

(Berechne)

$$V_{\text{BIAS}} \leq V_{\text{outmin}} + V_{\text{BCon}} = 1 + 0.4 = \underline{\underline{1.4V}}$$

$$\text{d) } V_{\text{INmax}} = V_{\text{BIAS}} - V_{\text{CEsat}} = V_{\text{BIAS}} - (V_{\text{BEon}} - V_{\text{BCon}})$$

$$= 1.4 - (0.7 - 0.4) = \underline{\underline{1.1V}}$$

PROBLEM 3

MOS Folded-Cascode Amplifier


i) Midband voltage gain:

$$i_{ds} = g_{m2} v_i = g_{m2} v_s \quad (R_{in2} \rightarrow \infty)$$

$$v_o = -i_{ds} (R_{out2} \parallel R_{L2})$$

$$\rightarrow R_{out2} \approx g_{m2} r_{o2} (v_{o2} \parallel R_{L2})$$
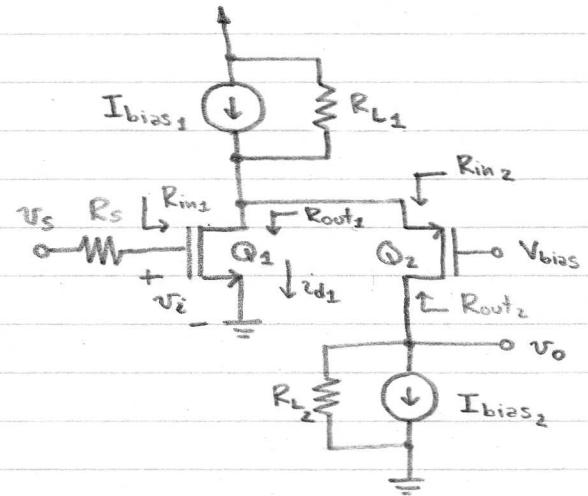
$$A_v = \frac{v_o}{v_s} = -g_{m2} (R_{out2} \parallel R_{L2})$$




ii) 3dB frequency:

Use Miller's theorem to split C_{gd2} into two caps. to ground...

$$A_1 = -g_{m1} (R_{out1} \parallel R_{in2} \parallel R_{L2})$$

$$R_{out1} = r_{o1}$$
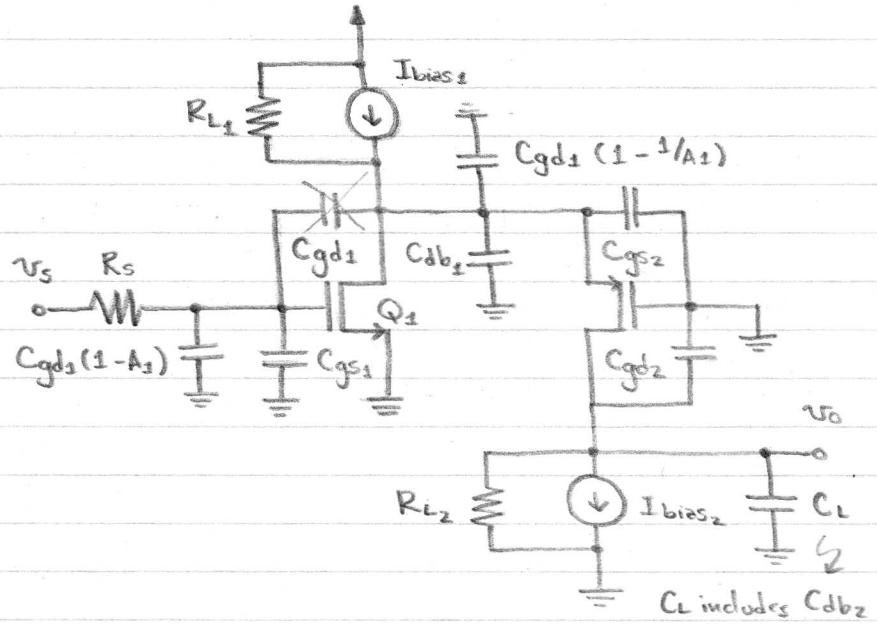
$$R_{in2} \approx \frac{1}{g_{m2}} \left(1 + \frac{R_{L2}}{r_{o2}} \right)$$



@ the gate of Q_1

$$C_{g1} = C_{gs1} + C_{gd1}(1-A_1)$$

$$R_{g1} = R_s$$

$$\tau_{g1} = R_{g1} C_{g1}$$

@ the drain of Q_1

$$C_{d1} = C_{db1} + C_{gd1}(1-A_1) + C_{gs1}$$

$$R_{d1} = R_{in2} \parallel r_{o1} \parallel R_{L2}$$

$$\tau_{d1} = R_{d1} C_{d1}$$

@ the drain of Q_2

$$C_{d2} = C_L + C_{gd2}$$

$$R_{d2} = R_{out2} \parallel R_{L2}$$

$$\tau_{d2} = R_{d2} C_{d2}$$

Assuming a dominant pole exists, the 3dB frequency can be derived as:


$$\omega_H = \frac{1}{\tau_{g1} + \tau_{d1} + \tau_{d2}}$$

Bjt Folded-Cascode Amplifier

i) Midband Voltage Gain

$$\cdot V_i = \frac{r_{\pi_1}}{R_s + r_{\pi_1}} V_s$$

where $r_{\pi_1} = (\beta+1)r_{e_1}$

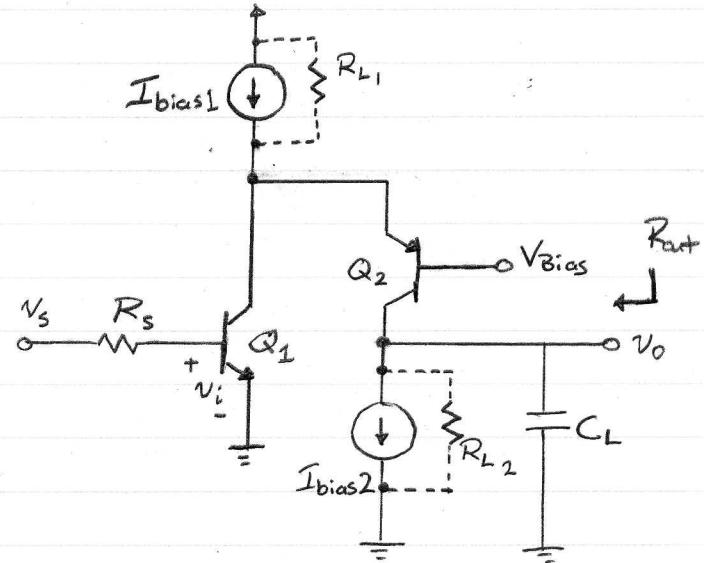

- Short-Circuit Transconductance


$$G_m \triangleq \left. \frac{i_o}{V_s} \right|_{V_o=0} = \frac{-\alpha g_m V_i}{\frac{R_s + r_{\pi_1}}{r_{\pi_1}} V_i} = \frac{-\alpha g_m}{1 + R_s / r_{\pi_1}}$$

$$\bullet R_{out} = R_{L_2} \parallel r_{o_2} [1 + g_{m_2} (R_{L_1} \parallel r_{o_1} \parallel r_{\pi_2})]$$

- Midband Voltage Gain

$$A_M \triangleq \frac{V_o}{V_s} = G_m R_{out}$$

$$= \frac{-\alpha g_m}{1 + R_s / r_{\pi_1}} R_{L_2} \parallel r_{o_2} [1 + g_{m_2} (R_{L_1} \parallel r_{o_1} \parallel r_{\pi_2})]$$

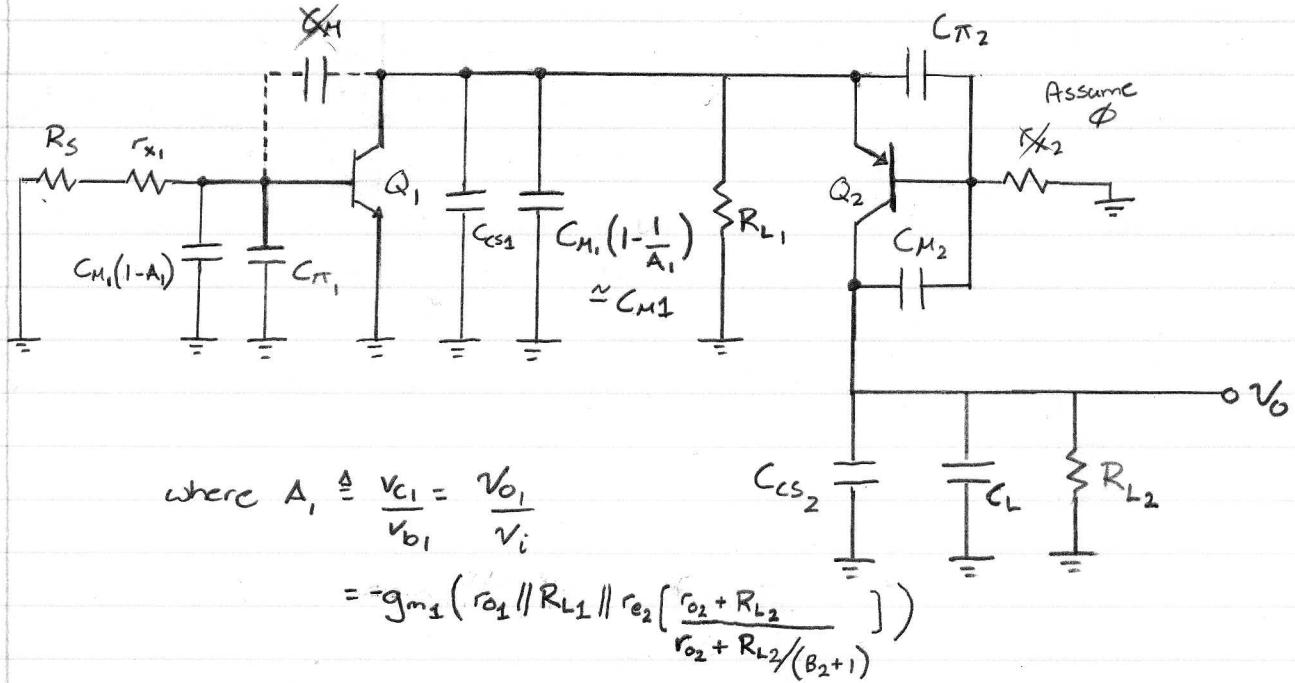ii) 3 dB Frequency

i) Apply Miller's theorem

\Rightarrow All capacitors now connected between
a node and GND (shown on diagram)

2) Find Open-Circuited Time Constants associated with
each node :• C_2 (output) node

$$C_{C2} = C_{CS2} + C_L + C_{M2}$$

$$\text{Resistance seen: } R_{C2} = R_{L2} \parallel r_{o2} [1 + g_{m2} (R_L \parallel r_{o1} \parallel r_{n2})]$$

$$\Rightarrow \omega_{C2} = \frac{1}{\tau_{C2}} = \frac{1}{(C_{C2} R_{C2})}$$

- C₁ node

$$C_{C1} = C_{\pi_2} + C_{CS1} + C_{M1}(1 - \frac{1}{A_1})$$

Resistance seen:

$$R_{C1} = r_{o1} \parallel R_{L2} \parallel r_{e2} \left[\frac{r_{o2} + R_{L2}}{r_{o2} + R_{L2}/(B_2+1)} \right]$$

$$\Rightarrow \omega_{C1} = \frac{1}{\tau_{C1}} = \frac{1}{(C_{C1} R_{C1})}$$

- B₁ node

$$C_{B1} = C_{M1}(1 - A_1) + C_{\pi_1}$$

$$\text{Resistance seen: } R_{B1} = r_{\pi_1} \parallel (r_x + R_s)$$

$$\Rightarrow \omega_{B1} = \frac{1}{\tau_{B1}} = \frac{1}{(C_{B1} R_{B1})}$$

- 3) Find ω_H

Assuming a Dominant Pole exists

$$\omega_H = \frac{1}{\tau_{C2} + \tau_{C1} + \tau_{B1}}$$