

Solutions to Selected Problems (Problem Set 8)

Chapter 8: 8.4, 8.10, 8.28, 8.34, 8.35, Ex. 8.5 (with $R_2=0$), 8.39, 8.50, 8.55, 8.61, 8.64, 8.70

Microelectronic Circuits – 5th Edition – Sedra/Smith
 Copyright© 2004 by Oxford University Press, Inc.
DO NOT DUPLICATE

8.4

All output voltage is fed back $\therefore \beta = 1$

$$A_f = \frac{100}{1+100 \times 1} = 0.99$$

$$1+A\beta = 1+100 \times 1 = 101 \approx 40.1 \text{ dB}$$

$$V_o = 0.99 V_s = 0.99 \text{ V}$$

$$V_i = V_s - V_o \beta = 1 - 0.99 = 10 \text{ mV}$$

$$A = 90 \Rightarrow A_f = \frac{90}{1+90 \times 1} \approx 0.989$$

$$\frac{\Delta A_f}{A_f} = \frac{0.989 - 0.99}{0.99} \approx -0.1\%$$

8.10

$A_o \approx 1000 \pm 30\%$ want $A_f = 100 \pm 1\%$

To reduce % change in A_o we need

$$\frac{1}{1+A\beta} \approx \frac{1}{30} \Rightarrow A_f = \frac{1000}{30} < 100$$

For single stage $A_f = \frac{A}{1+A\beta} \Rightarrow \frac{1}{1+A\beta} = \frac{100}{1000} = \frac{1}{10}$

For two stages $A_2 = \frac{A}{1+A\beta_2} \approx 10$
 (identical)

$$\Rightarrow (1+A\beta_2) = 1000/10 = 100$$

Thus each stage has $\pm 30/100\% = \pm 0.3\%$

But two such stages may give $\pm 0.6\%$ OK

[3 stages $A_3 = A_2^3 = 100^3$
 $(1+A\beta_3) = 1000/100^3 \approx 215$

Now each stage has $\pm 0.14\%$]

8.28

Here R_o is lowered by amount of feedback

i.e. $(1+A\beta) = 80$

$$\Rightarrow A\beta = 79$$

$$R_o = R_{of} (1+A\beta) = 100 \times 80 = 8 \text{ k}\Omega$$

8.34

Since $V_{G1} = 0 = V_{G2}$


$$\Rightarrow V_{E3} = V_o = 0 \text{ and } V_{B3} = +0.7 \text{ V}$$

$$q_{m1} = q_{m2} = 2 \sqrt{\frac{1}{2} K' (W/L) I} \\ = 2 \sqrt{\frac{1}{2} (1) (0.5)} = 1 \text{ mA/V}$$

$$r_{e3} = V_T / I_{SMA} = 5 \Omega$$

$$r_o = V_A / I = 100 / 0.5 = 200 \text{ k}\Omega$$

A-circuit

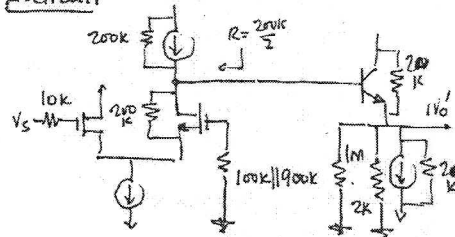

$$R_1 = \infty$$

$$R_o = 1 \text{ m}\Omega \parallel 2 \text{ k}\Omega \parallel \frac{20 \text{ k}\Omega}{2} \parallel \left(r_{e3} + \frac{200 \text{ k}\Omega}{\beta + 1} \right) = 622.2 \Omega$$

$$A = \frac{100 \parallel (\beta + 1) (r_{e3} + 1 \text{ m}\Omega \parallel 10 \text{ k}\Omega \parallel 2 \text{ k}\Omega)}{2 / q_m} \\ \times \frac{1.66 \text{ k}\Omega}{r_{e3} + 1.66 \text{ k}\Omega} = 31.3 \text{ V/V}$$

$$\beta = \frac{100}{100 + 900} = 0.1 \text{ V/V}$$

$$A_f = \frac{A}{1+A\beta} = \frac{31.3}{1+31.3 \times 0.1} = 7.58 \text{ V/V}$$

$$R_{if} = \infty \quad \therefore R_{1N} = \infty$$


$$R_{of} = \frac{R_o}{1+A\beta} = \frac{622.2}{1+31.3} = 150.6 \Omega$$

$$R_{of} = R_{out} \parallel R_L \Rightarrow R_{out} = 163 \Omega$$


Copyright © 2004 Oxford University Press, Inc.
DO NOT DUPLICATE

8.35

(a) A-circuit

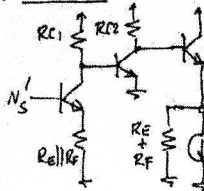

B-circuit

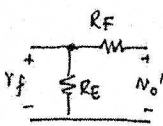

(b) For $A\beta \gg 1$: $A_f = \frac{A}{1+A\beta} \Rightarrow \frac{1}{\beta}$

$$\beta = \frac{R_E}{R_E + R_F} \Rightarrow A_f \approx \frac{R_E + R_F}{R_E} = 1 + \frac{R_F}{R_E}$$

(c) $R_E = 50 \Omega$

$$\Rightarrow A_f = 1 + \frac{R_F}{R_E} = 25 \text{ V/V}$$

$$\Rightarrow \frac{R_F}{R_E} = 24 \text{ and } R_F = 24 R_E = 1.2 \text{ k}\Omega$$

(d) $I_{Q1} = 1 \text{ mA}$, $I_{Q2} = 2 \text{ mA}$, $I_{B3} = 5 \text{ mA}$

$$\beta = 100$$

$$r_{e1} = \frac{25 \text{ mV}}{1 \text{ mA}} = 25 \Omega, r_{e2} = 12.5 \Omega, r_{e3} = 5 \Omega$$

$$A_1 = \frac{-R_{C1} \parallel r_{\pi 2}}{r_{e1} + R_E \parallel R_F} = -10$$

$$\Rightarrow R_{C1} \parallel r_{\pi 2} = 10(25 + 50 \parallel 1.2 \text{ k}) = 730 \Omega$$

$$\Rightarrow R_{C1} = 1.75 \text{ k}\Omega$$

$$A_2 = \frac{-R_{C2} \parallel [(\beta + 1)(r_{e1} + R_E + R_F)]}{r_{e2}} = -5$$

$$\Rightarrow R_{C2} \parallel 125.5 \text{ k} = 5 \times 12.5 = 625 \Omega$$

$$\Rightarrow R_{C2} = 628.1 \Omega$$

$$A_3 = \frac{R_E + R_F}{r_{e3} + R_E + R_F} = \frac{1.25}{1.255} = 0.996 \text{ V/V}$$

(e) $\therefore A_1 A_2 A_3 = 10 \times 50 \times 0.996 = 498 \text{ V/V}$

$$A\beta = 498(50/1250) = 19.92$$

$$A_f = \frac{A}{1+A\beta} = 23.8 \text{ V/V}$$


(f) $R_i = (\beta + 1)(r_{e1} + R_E \parallel R_F)$

$$\therefore R_i = 101(25 + 4.8) = 7.37 \text{ k}\Omega$$

$$R_f = R_1(1 + 19.92) = 154 \text{ k}\Omega$$

$$R_o = 1.25 \text{ k} \parallel (r_{e3} + R_{C2} \parallel 101) = 11.12 \Omega$$

$$R_{of} = \frac{R_o}{1 + 19.92} = 0.53 \Omega$$

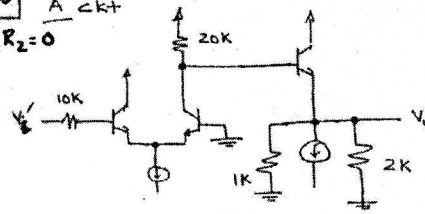Ex. 8.5 $A < k+$ with $R_2 = 0$ 

$$r_{e1} = r_{e2} = 50 \Omega, r_{e3} = 5 \Omega$$

$$R_i = (\beta + 1)20 \text{ k} + 10 \text{ k} = 20.1 \text{ k}\Omega$$

$$R_o = 1 \text{ k} \parallel 2 \text{ k} \parallel (r_{e3} + \frac{20 \text{ k}}{\beta + 1}) = 156.8 \Omega$$

$$A = A_1 A_2$$

$$= \frac{20 \text{ k} \parallel [(\beta + 1)(r_{e3} + 1 \text{ k} \parallel 2 \text{ k})]}{2 r_{e1} + \frac{10 \text{ k}}{\beta + 1}} \cdot \frac{1 \text{ k} \parallel 2 \text{ k}}{1 \text{ k} \parallel 2 \text{ k} + r_{e3}}$$

$$= 77(0.993) = \underline{76.5 \text{ V/V}}$$

$$\underline{\underline{\beta = 1}}$$

$$A_f = \frac{76.5}{1 + 76.5} = \underline{0.987 \text{ V/V}}$$

$$R_{if} = (1 + A\beta)R_i = (1 + 76.5)R_i$$

$$= (1 + 76.5)20.1 \text{ k}\Omega = 1.56 \text{ M}\Omega$$

$$R_{in} = R_{if} - R_1 = \underline{1.55 \text{ M}\Omega}$$

$$R_{of} = \frac{R_o}{1 + A} = \frac{156.8}{1 + 76.5} = 2.02 \Omega$$

$$R_{of} = R_{out} \parallel R_L$$

$$\Rightarrow R_{out} = \underline{2.03 \Omega}$$

8

Prob. 8.39

Series - Series feedback amplifier
input: VOLTAGE output: CURRENT

⇒ Transconductance amplifier
(i.e., a voltage-to-current converter)


• DC analysis:

$$I_{D1} = I_{D2} = I_{D3} = I_{D4} = 0.1 \text{ mA}$$

$$I_{D5} = 0.8 \text{ mA}$$



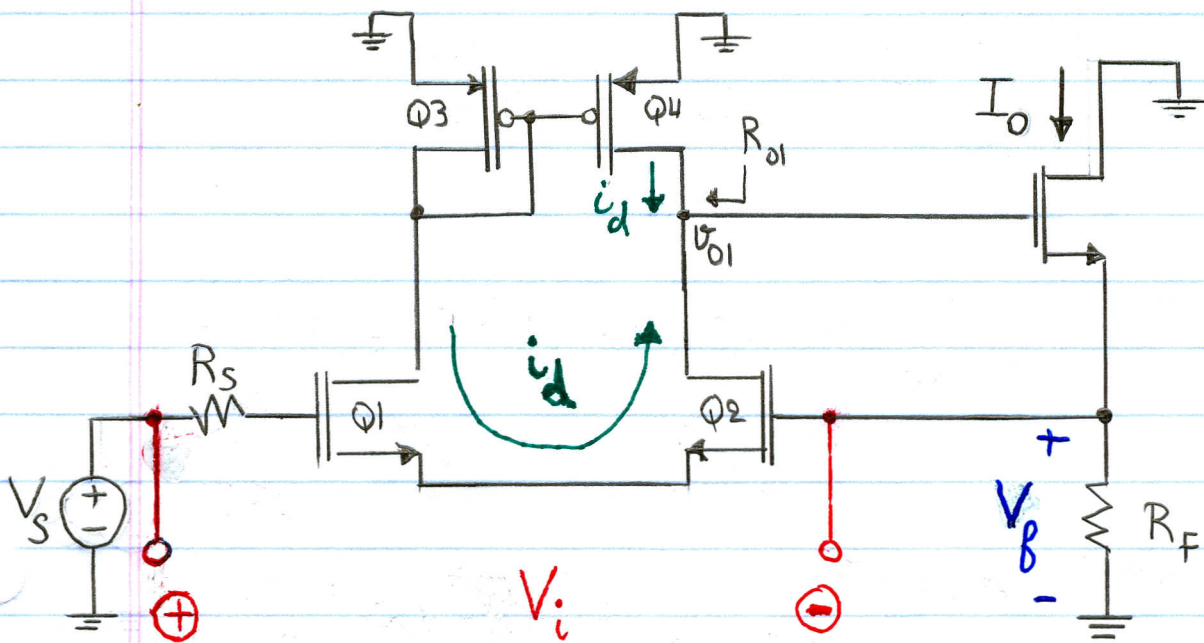- AC analysis : \Rightarrow open-circuit the ideal current sources
short-circuit the ideal voltage sources



Define : $V_b = V_{g2}$

$$V_i = V_s - V_b$$

Then : @ Input : KVL $\Rightarrow V_i = V_s - V_b \Rightarrow$ SERIES mixing

@ Output : sample $I_o \Rightarrow$ SERIES sampling



$$a) \quad V_{\beta} = I_o R_F \Rightarrow B \triangleq \frac{V_{\beta}}{I_o} = R_{\beta} = \underline{\underline{10k\Omega}}$$

For large loop gain ($AB \gg 1$):

$$A_{\beta} \triangleq \frac{I_o}{V_s} = \frac{A}{1+AB} \approx \frac{1}{B} = \frac{1}{R_{\beta}} = \underline{\underline{0.1 \text{ mA/V}}}$$

$$b) \quad i_d = \frac{V_i}{2/g_{m1}} \quad (\text{see circuit diagram})$$

$$R_{o1} = r_{o2} \parallel r_{o4}$$

$$\Rightarrow V_{o1} = 2 i_d R_{o1} = g_{m1} (r_{o2} \parallel r_{o4}) V_i$$

Assume $r_{o5} = \infty$:

$$I_o = \frac{V_{o1}}{\frac{1}{g_{m5}} + R_F}$$

$$\therefore A \triangleq \frac{I_o}{V_i} = g_{m1} \frac{(r_{o2} \parallel r_{o4})}{\frac{1}{g_{m5}} + R_F} \rightarrow \rightarrow$$

$$r_{o2} = r_{o4} = \frac{V_A}{I_{D2}} = 1 \text{ M}\Omega$$

$$g_{m1} = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_1 I_{D1}} = 0.12 \text{ mA/V}$$

$$g_{m5} = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_5 I_{D5}} = 0.8 \text{ mA/V}$$

$$\Rightarrow A = 5.33 \text{ mA/V}$$

$$\Rightarrow AB = (5.33 \text{ mA/V})(10 \text{ k}\Omega) = 53.3$$

$$\Rightarrow A_f \triangleq \frac{I_o}{V_s} = \frac{A}{1+AB} = \underline{\underline{0.0982 \text{ mA/V}}}$$

c) Assume $r_{o5} = \infty$:

at source of Q_5 : $V_o = I_o R_F$

$$\Rightarrow \frac{V_o}{V_s} = \frac{I_o}{V_s} R_F = A_f R_F = \underline{\underline{0.982 \text{ V/V}}}$$

8.50

$I_0/I_S = 100 \text{ A/A}$, $R_{in} = 1 \text{ k}$, $R_{out} = 10 \text{ k}$
 $\beta = 0.1$ shunt-series topology

$$A_p = \frac{I_0'}{I_S'} = 100$$

$$A_F = \frac{A_v}{1 + A_v \beta} = \frac{100}{1 + 100(0.1)} = 9.09 \text{ A/A}$$


$$R_i = 1 \text{ k}\Omega$$

$$\Rightarrow R_{if} = R_i(1 + A\beta) = 90.9 \text{ k}\Omega$$

$$R_o = 10 \text{ k}\Omega$$

$$\Rightarrow R_{of} = R_o(1 + A\beta) = 110 \text{ k}\Omega$$

8.55

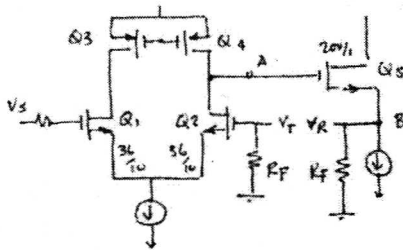

$$V_f = V_{GS} \text{ and } V_S \rightarrow 0$$

$$V_A = -g_{m2}(r_{o2} \parallel r_{o4})$$

$$V_B = V_A \frac{(R_F \parallel r_{o5})}{(R_F \parallel r_{o5}) + 1/g_{m5}}$$

$$AB = \frac{-V_f}{V_R} = +g_{m2} \frac{(r_{o2} \parallel r_{o4})(R_F \parallel r_{o5})}{(R_F \parallel r_{o5}) + 1/g_{m5}} \quad \text{QED}$$

8.61

$$A(s) = \frac{10^5}{1 + s/100}$$

$$\text{Ang}(A) = -\tan^{-1} \frac{\omega}{100} - 2 \tan^{-1} \frac{\omega}{10^4}$$

at ω_{180} : $\text{Ang}(A) = -180^\circ$ for $\omega_{180} \gg 100$
 $\Rightarrow 180^\circ = 90^\circ + 2 \tan^{-1} \left[\frac{\omega_{180}}{10^4} \right]$

hence $\tan^{-1} \frac{\omega_{180}}{10^4} = \frac{90^\circ}{2}$

i.e. $\frac{\omega_{180}}{10^4} = \tan(45^\circ) = 1$

$\therefore \omega_{180} = 10^4 \text{ rad/s}$

$$|AB| = \frac{10^5 \beta}{\sqrt{1 + (\omega_{180}/100)^2} \sqrt{1 + 1}^2} = 1$$

$$\Rightarrow \beta = 0.002$$

$$A_f(0) = \frac{10^5}{1 + 10^5(0.002)} \approx 500 \text{ V/V}$$

8.64

$$A(s) = \frac{1000}{(1 + s/10^4)(1 + s/10^5)^2}$$

and β is independent of frequency

$$\text{Ang}(A) = -\tan^{-1} \frac{\omega}{10^4} - 2 \tan^{-1} \frac{\omega}{10^5}$$

try $\omega = 10^4$: $\theta = 45^\circ + 2 \times 5.7 = 56.4^\circ$

try $\omega = 10^5$: $\theta = 84.2^\circ + 2 \times 45 = 174.2^\circ$

Iteration yields $\omega \approx 1.1 \times 10^5 \text{ rad/s}$

For oscillations: $|AB(\omega_{180})| \geq 1$

$$\frac{\beta 10^3}{(\sqrt{1 + 11^2})(\sqrt{1 + 11^2})^2} \geq 1$$

$$\Rightarrow \beta \geq 0.0244$$

8.70

$$A(f) = \frac{10^5}{1 + jf/10}$$

for $\beta = 1$: $A(f)B = \frac{10^5}{1 + jf/10}$

for $f \gg 10$: $|AB| \approx 10^5 \frac{10}{f}$

$$\Rightarrow f_1 = 1 \text{ MHz}$$

at f_1 : phase margin = $180^\circ - \tan^{-1} \frac{10^6}{10}$
 $= 90^\circ$